

RECEIVERS FOR SATELLITES

DECEMBER 1957

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

Multi-Way
Electronic
Crossovers

•

Servicing
Auxiliary
TV Circuits

•

Maintaining
The VTVM

•

Phonograph
Pickup Arms

•

Relay Averts
a Toyland
Tragedy ▶

(See page 102)

35c

U.S. and Canada



1,000,000,000

proofs a day...


and triplett model
630 leads all vom's

that a VOM is electronics' most basic Test Instrument
Yes, over 1,000,000,000 measurements are made
every day with Volt-Ohm-Milliammeters

in design, quality, performance, operating simplicity,
and value per dollar. The leader at only \$44.50


At leading electronic parts distributors everywhere.

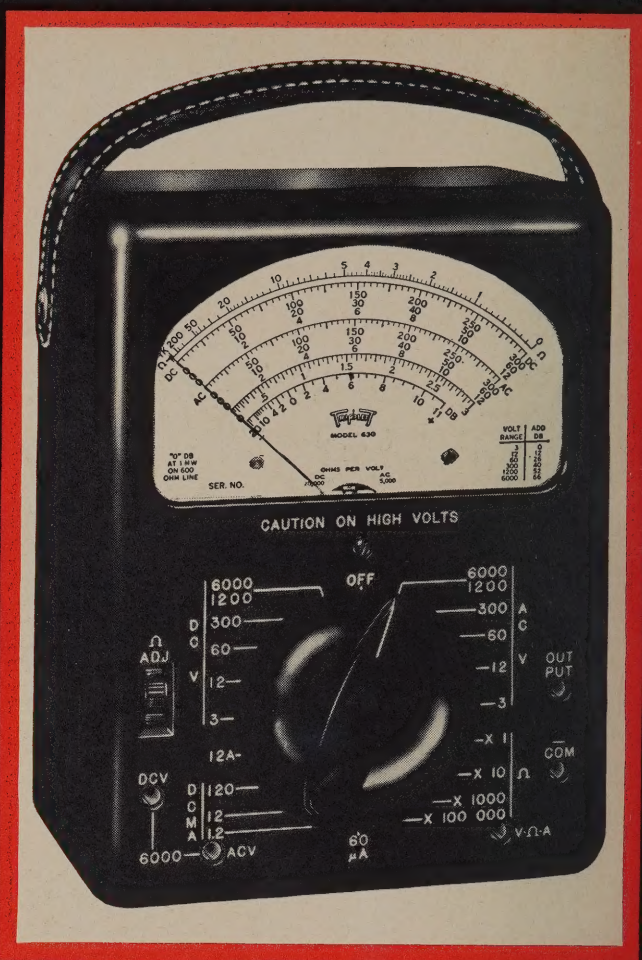TRIPLETT Model 630 VOM—the proof of 53
years' experience in test instruments.



TRIPLET

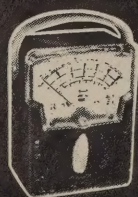Triplet Electrical
Instrument Company
Bluffton, Ohio



631




630-NA



630-A




310

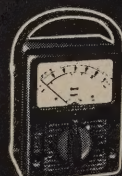

630-T



666-HH

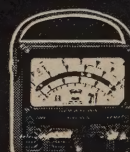


625-NA



666-R

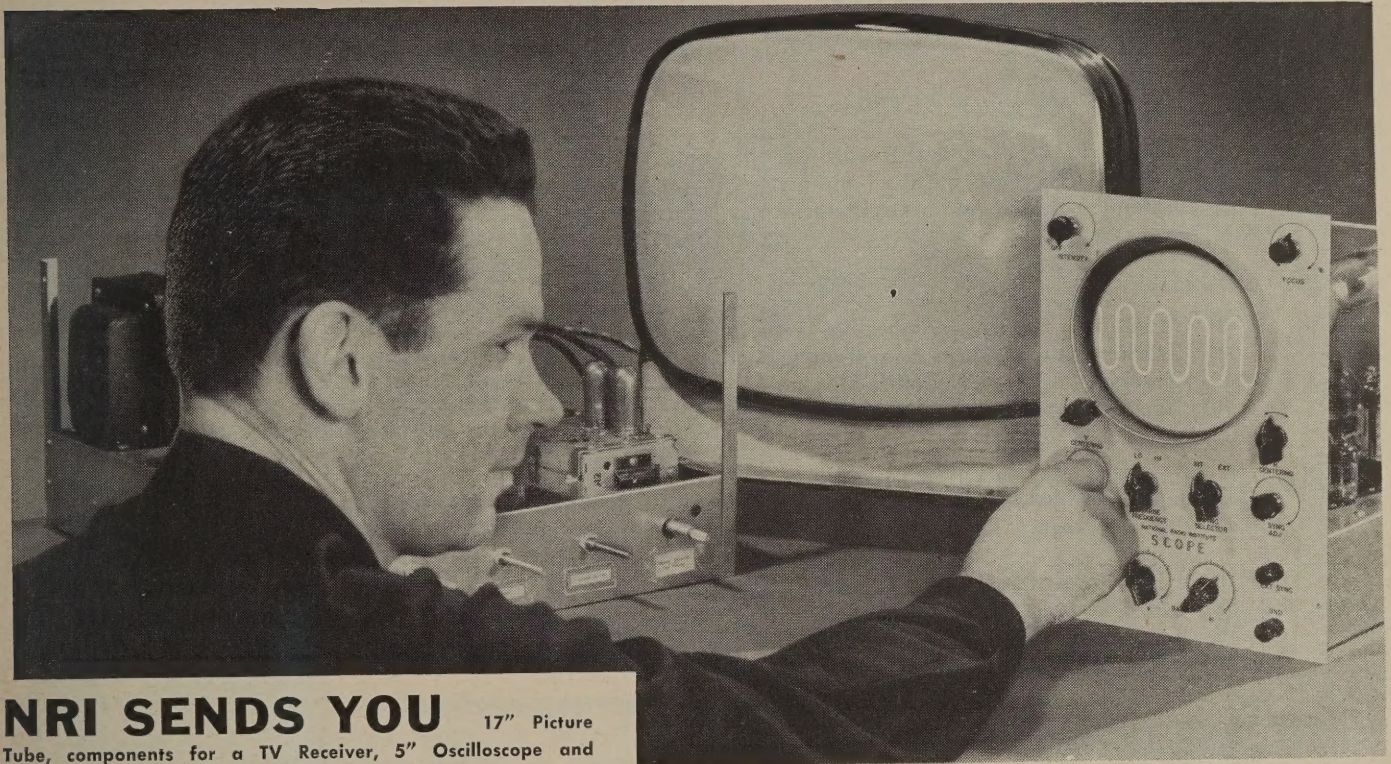NOW—A Faster Way to Reach the Top in TV SERVICING



NRI SENDS YOU 17" Picture Tube, components for a TV Receiver, 5" Oscilloscope and Signal Generator . . . All parts for these 4 complete units.

N. R. I. All-Practice Method Trains You at Home in Spare Time to Fix TV Sets, Quickly, with Confidence

The man who knows the answers—the Professional TV Technician enjoys the prestige, gets the better jobs, the higher pay. Here is the learn-by-practice training to be a Professional TV Technician. It shows you the way to be the boss, to earn top pay. Television Servicing needs more than well trained men. If you have a basic knowledge of radio and electronics you can make some Television repairs simply by trial and error. But sooner or later you will face TV Service problems you can not solve. And you can't get the training you need while customers wait.

N. R. I. Is Oldest and Largest Home Study Radio-TV School

Over forty years experience and the record and reputation of NRI back up this learn-by-doing Professional TV Servicing Course. Instead of just reading about TV problems, you build and conduct experiments on circuits in a TV receiver. You learn methods, "Tricks of the trade" proved by top TV Servicemen. You learn to fix any set, any model with confidence.

You Get COLOR TV Textbooks Early

The day you enroll, N.R.I. sends you special Color-TV books to speed your knowledge and understanding of this vast, growing phase of Television.

Many full color pictures and diagrams help you recognize defects and help you learn how to correct them quickly and properly. To cash in on the coming Color TV boom, you'll need the kind of knowledge and experience this NRI training gives.

This is 100% learn-by-doing, practical training. Here is a course for men who know basic theory, either from Radio or TV Servicing experience or planned training but realize the need for more knowledge to forge ahead. Here is what one graduate, G. G. Stethem of Belpre, Ohio, says, "I can not praise N.R.I.'s Professional TV Course highly enough. I have my own spare time

shop and all the Radio-TV work I can handle."

Another graduate, Edward Ravitsky of Northumberland, Pa., says, "I have taken your course in Professional TV Servicing. It takes the kind of experience you offer to really learn." If you want to go places faster in TV Servicing, make your future more secure as the industry develops, we invite you to find out what you get, what you practice, what you learn from NRI's Course in Professional TV Servicing. Mail the coupon now. There is no obligation. NATIONAL RADIO INSTITUTE, Dept. 7NFT, Washington 16, D. C.



**Send for
FREE
BOOK**

NATIONAL RADIO INSTITUTE

Dept. 7NFT, Washington 16, D. C.

Please send FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name.....Age.....

Address.....

City.....Zone.....State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

EDITORIAL

- 31 The U. S. A. at Bay—Hugo Gernsback

TEST INSTRUMENTS

- ✓32 The Vtvm—Its Care and Repair—Rhys Samuel
35 Add a Tuner Test to Your Field-Strength Meter—R. M. Centerville
36 Extended-Range Audio Oscillator—L. B. Hedge

RADIO

- ✓40 Monitoring the Russian Satellite—Robert F. Scott
42 Transistor and Hybrid Auto Radios, Part II—Jack Darr
✓44 Tracking the U. S. Satellite—Jordan McQuay
46 Ac-Dc Power Supply—George P. Pearce

AUDIO—HIGH FIDELITY

- 47 Phono Preamp Compensates for Cable Capacitance—G. Franklin Montgomery
✓49 Hi-Fi Pickup Arms, Part I—Julian D. Hirsch
52 Multi-Channel Electronic Crossovers—Norman H. Crowhurst
56 Tube Data and Amplifier Design, Part II—Herbert Ravenswood
130 New Records—Monitor

TELEVISION

- 58 Color Installation Problems—Robert G. Middleton
78 Television Hearing Aid—Joseph Cozzo
80 Understanding Auxiliary TV Circuits, Part I—Charles J. Garrett
82 Two-in-One Proposition—H. J. Miller
84 TV Service Clinic—Conducted by Robert G. Middleton
98 Do You Do a Maximum or Minimum Job—Art Margolis

ELECTRONICS

- 102 Relay Averts Toyland Tragedy (Cover Feature)—James A. McRoberts
✓106 Binary Photographic Timer—Alvin F. Rymsha
108 More About Transistor Types, Part II—Paul Penfield, Jr.
112 Using Neon Lamps—A. R. Clawson

- ANNUAL INDEX
150 Vol. XXVIII, January
through December, 1957
148 Books
142 Business and People
147 Corrections
16 Correspondence
136 New Devices
6 News Briefs

- 122 New Tubes and
Semiconductors
128 Patents
118 Radio-Electronic Circuits
145 Technical Literature
126 Technicians' News
133 Technotes
116 Try This One
127 35 Years Ago

NEXT MONTH: SERVICING TRANSISTOR AUTO RADIOS • NEW
AMPLIFIER USES KT88'S • ALL-TRANSISTOR DIRECT-READING AF METER

ON THE COVER

(Story on page 102)

This is one collision that won't take place. The gadget on the right is an electronic light-triggered relay that stops the train whenever the intersection is blocked.

Color original by James A. McRoberts

Hugo Gernsback
.....Editor and Publisher
M. Harvey Gernsback
.....Editorial Director
Fred Shunaman
.....Managing Editor
Robert F. Scott
.....W2PWG, Technical Editor
Larry Steckler
.....Assistant Editor
I. Queen
.....Editorial Associate
Robert G. Middleton
.....Television Consultant
Elizabeth Stalcup
.....Production Manager
Cathy Cocozza
.....Advertising Production
Wm. Lyon McLaughlin
.....Tech. Illustration Director
Sol Ehrlich
.....Art Director
Fred Neinast
.....Staff Artist
Lee Robinson
.....General Manager
John J. Lamson
.....Sales Manager
G. Aliquo
.....Circulation Manager
Adam J. Smith
.....Director, Newsstand Sales
Robert Fallath
.....Promotion Manager



Average Paid Circulation
Over 195,000

Associate Member Institute of High Fidelity Mfrs., Inc.

RADIO-ELECTRONICS, December, 1957, Vol. XXVIII, No. 12. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1957 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$9.00 for three years; single copies 35c, Pan-American countries \$4.50 for one year; \$8.00 for two years; \$10.50 for three years. All other countries \$5.00 a year; \$9.00 for two years; \$12.00 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 163.
POSTMASTER: If undeliverable, send Form 3578 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

**GREATEST
ADVANCE IN
SHOP-METHOD
HOME TRAINING**

EARN MORE MONEY...GET INTO

TELEVISION ELECTRONICS - RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE

At Home - In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester



**19 BIG KITS
YOURS TO KEEP**

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

- | | |
|------------------------------------|--------------------------------|
| 1. TELEVISION, INCLUDING COLOR TV | 5. PREPARATION FOR FCC LICENSE |
| 2. RADIO, FM AND AM | 6. AUTOMATION |
| 3. INDUSTRIAL ELECTRONICS | 7. RADAR AND MICRO WAVES |
| 4. SOUND RECORDING AND HI FIDELITY | 8. COMMUNICATIONS |

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY!

You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits - even prepare for FCC License without taking a special

course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!


EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED - Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects - all the valuable equipment shown above

- many other materials and services - consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics.

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment - professionally installed - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - and part time job while you learn. Check box in coupon for full information.

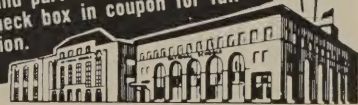

FREE! Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson - yours at no cost, no obligation. CLIP COUPON NOW... MAIL IT TODAY!

APPROVED FOR G.I. TRAINING

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.

NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE - MAIL NOW TO

NATIONAL SCHOOLS, DEPT. RG-127

4000 S. FIGUEROA ST.
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.


NAME _____ AGE _____

ADDRESS _____


CITY _____ ZONE _____ STATE _____

☐ Check if interested ONLY in Resident School training at Los Angeles.
VETERANS: Give date of Discharge _____

FOR
A **brighter**
TV picture

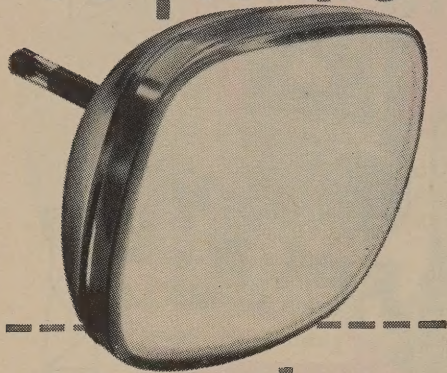


FOR
A **brighter**
profit.
picture

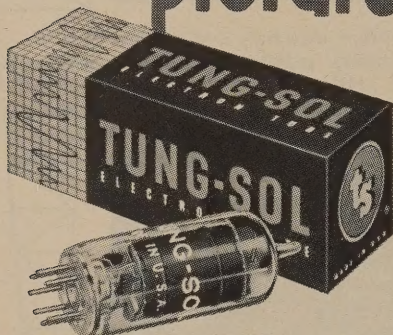

Keep your customers sold on you! Use the exact same tubes leading independent set makers specify. Tell your supplier you'd rather have Tung-Sol Tubes.

Tung-Sol Electric Inc., Newark 4, N. J.

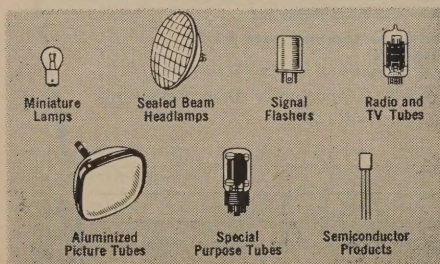TUNG-SOL®
MAGIC MIRROR ALUMINIZED
PICTURE TUBES
RECEIVING TUBES



News Briefs



STEREOPHONY as the dominant trend in the audio-radio field was evidenced at the Annual Audio Engineering Society Convention and High Fidelity Show held in New York City early in October. One complete session of the convention (Friday afternoon, Oct. 11) was devoted to stereophonic sound, highlighted by the demonstration of the Westrex discs. (See page 8.) Part of another session dealt with stereo FM transmission.

At the show, the dominance of stereo was even more pronounced. In addition to the manufacturers exhibiting stereo equipment, the majority of exhibitors demonstrating amplifiers, speakers or other apparatus used a stereophonic setup. Unfortunately the extremely high volume levels traditional at audio shows masked out the stereophonic effect in most cases, but could not conceal the conviction of the manufacturers that stereophony is the next big thing in the audio field. Some expressed the fear that the prospect of stereophonic discs might have a deterring effect on stereo tape similar to that color television is alleged to have had on the sale of black-and-white TV receivers but an equally large group insisted that disc and tape would help each other to promote stereo.

PHONE CABLE TO HAWAII, the worlds longest and deepest, provides 36 circuits between the United States mainland and the island of Oahu, where 80% of Hawaiian telephones are located. The distance between cable terminal points is 2,400 miles. At some places the cable is 3½ miles below the surface of the Pacific Ocean. The cable was built by American Telephone & Telegraph's Long Lines Department and the Hawaiian Telephone Co.

Amplifiers, needed to boost the strength of signals when they reach the fading point along the cable, were developed by Bell Telephone Laboratories. They are built into the cable at 44-mile intervals and are designed to withstand the pressures encountered on the ocean floor. They amplify voice currents 1 million times and are expected to operate without attention for at least 20 years.

It is now possible for operators on both the mainland and the island to dial directly, rapidly completing calls that span the Pacific.

TV SERVICING IN 1966 will be a vastly larger field than today, according to a recent survey made by Frank W. Mansfield, Sylvania's marketing research director. He shows a dollar volume of \$447 million in 1948, \$2.55

billion in 1957 and an expected \$3.97 billion by 1966.

An interesting sidelight is the predicted drop in number and total value of receiving tubes. This is due to the increased use of transistors and the expected reduced price of tubes because of competition from transistors.

Mansfield's survey is based on six service calls a year for color TV sets three a year for black-and-white sets, one a year for home radios and 0.5 a year for auto radios. Growth in the number of TV sets is also expected. Color sets from 160,000 now to 18,840,000 in 1966, and black-and-white sets from 42,580,000 now to 53,760,000. The number of service technicians for this year is listed as 132,970. Predicted growth at a rate of 5% per year should bring this to 206,640 by the beginning of 1966.

Calendar of Events

1957 Eastern Joint Computer Conference, Dec. 9-13, Sheraton-Park Hotel, Washington, D. C.

EIA Conference on Maintainability of Electronic Equipment, Dec. 18-19, University of Southern California, Los Angeles, Calif.

Fourth National Symposium on Reliability and Quality Control, Jan. 6-8, Statler Hotel, Washington, D. C.

Second EIA (RETMA) Conference on Automation, Jan. 22-24, Arizona State College, Tempe, Ariz.

THYRISTOR, a new high-frequency switching transistor, can switch substantial currents from one circuit to another in periods as short as 1/50,000-000 second. It is switched from on to off and vice versa by applying low energy pulses of the proper polarity to the base circuit. Announced by Dr. Irving Wolff, vice president of RCA's research department, it is described as a modified alloy-junction transistor. A novel feature is a new form of collector contact which makes the high-speed switching action possible. The Thyristor may be operated as either a bistable switching element or a more conventional high-frequency transistor, either in switching or amplifying circuits. The device is still under development and is not yet commercially available.

Similar units announced by Philco are a new class of field-accelerated transistors made possible by a Micro Alloy Diffused-Base Transistor (MADT) process. MADT's are available in various voltage and frequency specifications for use in transistorized equipment through the entire vhf and part of the uhf spectrum. These transistors feature a maximum frequency of 250 to 1,000 mc. Typical gain is 10 db

**LET DeVRY TECH PREPARE YOU IN
SPARE TIME AT HOME AS AN**

ELECTRONICS TECHNICIAN



**NO PREVIOUS TECHNICAL EXPERIENCE
OR ADVANCED EDUCATION NEEDED!**

Laborers and bookkeepers, store clerks, shop men, farmers, salesmen — men of nearly every calling — have taken the DeVry Tech program and today have good jobs or service shops of their own in Electronics. You don't have to quit your present job. If you are 17 to 55, see how you may get yourself ready for a future in the fast-growing Electronics field.

Whether you prepare at home or in our well-equipped Chicago or Toronto Laboratories, you get sound, basic training in both principles and practice. At home, you use educational movies. You build actual circuits and test equipment. You read simple directions, follow clear illustrations. When you finish, you are prepared to step into a good job in an excitingly different field. You may even start a service shop of your own. Mail coupon for free facts today.

Live-Wire Employment Service



Puts you in touch with job opportunities—or helps you toward a better position in the plant where you are now employed.



Draft Age?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

A SAMPLE LESSON

See for yourself how DeVry Tech trains you for real opportunities in Electronics. We'll also give you a free copy of an interesting booklet, "Electronics and YOU."

FREE

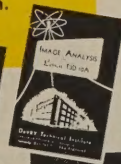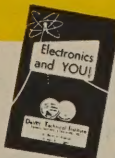

"One of North America's Foremost Electronics Training Centers"



Accredited Member
of National
Home Study Council

DEVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

FORMERLY

DEFOREST'S TRAINING, INC.



**AN INDEX
to a
BETTER JOB,
A BRIGHTER
FUTURE**

Electronics

Radar

Guided
Missiles

Television

Micro-Waves

Communications

Radio

Industrial
Electronics

Computers

Automation
Electronics

Remote Control
Systems

Broadcasting

Your Own
Service Shop

MAIL TODAY FOR FREE FACTS

DeVry Technical Institute

4141 Belmont Ave., Chicago 41, Ill., Dept. RE-12-N

Please give me a FREE Sample Lesson and your booklet, "Electronics and YOU."

NAME _____ AGE _____


STREET _____ APT. _____

CITY _____ ZONE _____ STATE _____

☐ Check here if subject to military training.
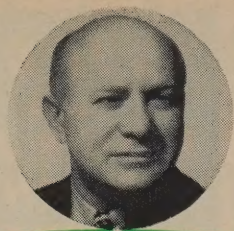
#1090

DeVry Tech's Canadian Training Center is located at
626 Roselawn Avenue, Toronto 12, Ontario



Mischa Elman
makes his home recordings on

irish
BRAND
ferro-sheen
recording
tape

That's not the reason
why you should use

irish
BRAND
ferro-sheen
recording
tape

Here's why you should use

irish
BRAND
ferro-sheen
recording
tape:

It's the best-engineered tape
in the world...

...gives you better highs...better lows...
better sound all around! Saves your tape
recorder, too—because the **irish** FERRO-
SHEEN process results in smoother tape
...tape that can't sand down your mag-
netic heads or shed oxide powder into your
machine. Price? Same as ordinary tape!



Available wherever quality tape is sold.
ORRadio Industries, Inc., Opelika, Alabama
Export: Morhan Exporting Corp., New York, N. Y.
Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

NEWS BRIEFS (Continued)

at 200 mc, more than 16 db at 100.

A logical outgrowth of MADT is the development of a super-high-speed switch. Engineers now discuss switching time in light feet instead of μ secs. Typically the MADT will switch on or off in 10 light feet. No type number was given for these transistors nor was unit price revealed. The unit is now in production.

STEREO DISC RECORDS were demonstrated by two companies during the recent Audio Engineering Society convention in New York City. Westrex, a subsidiary of Western Electric Co., demonstrated one system at the convention. The other, not shown at the convention itself, was demonstrated by London Records at an outside location. Opinion seemed to favor the London demonstration, though conditions surrounding the Westrex audition caused some to wonder if the records might not be somewhat better than circumstances permitted them to sound.

The London system—originated in England by London's parent company (British) Decca Records—combines vertical (hill-and-dale) and lateral recording. Vertical motion of the stylus produces one of the stereophonic channels, while lateral motion produces the other. The American system records the two channels on opposite sides of a 45° groove. Thus each of the two stereophonic signals is a combination of vertical and lateral movement of the stylus.

It was generally understood that manufacturers were ready to agree on a single standard before beginning to mass-produce records. Once agreement on the system to be used is reached, there need be little delay in putting stereophonic discs and cartridges on the market. The would-be stereophonic listener could use his own pickup arm and turntable, and his amplifier-speaker system would furnish the sound for one channel. It would then be necessary to obtain only one additional preamp, amplifier and speaker system, which many feel need not be of the extreme quality required in a single-channel true high-fidelity system.

5 NEW TV STATIONS since our last listing add to the bumper crop this fall:
KOAC-TV, Corvallis, Ore..... 7
WPTA, Roanoke, Ind.....21
WTIC-TV, Hartford, Conn..... 3
KETV, Omaha, Neb..... 7
WHYY-TV, Philadelphia, Pa.....35
New call letters were chosen by:
WLOF-TV, Orlando, Fla..... 9
(formerly WTLO)
KSOO-TV, Sioux Falls, S. D.....13
(formerly KSOO)

There are now 513 operating U.S. stations (422 vhf and 91 uhf), 27 of which are noncommercial (6 uhf).

Canada's list of TV stations has grown to 44 with:

CHAT-TV, Medicine Hat, Alta..... 6
CHBC-TV, Kelowna, B.C..... 3

Viewers should note that CHBC-TV

(Continued on page 12)

for

17 WATTS
PUSH-PULL POWER
at 300V. B+

with a pair of
MINIATURE tubes



the

Ampere[®]
EL84/6BQ5

LOW-DISTORTION,
HIGH-GAIN POWER PENTODE

- True pentode characteristics for low distortion and high peak power.
- High gain and sensitivity resulting in reduced driver stage distortion.
- 12 watts plate dissipation in a miniature envelope.
- At 300 volts, capable of 17 watts at 4% distortion (without feedback) in Class AB push-pull pairs.
- 5.7 watts output at 10% harmonic distortion (without feedback) as a single-ended output stage.

OTHER **Ampere** TUBES FOR
HIGH-FIDELITY AUDIO APPLICATIONS:

6CA7/EL34	High-power pentode; 100 W PP
EF86/6267	Low-noise high- μ pentode
ECC81/12AT7	Low-noise medium- μ dual triode
ECC82/12AU7	Low-noise low- μ dual triode
ECC83/12AX7	Low-noise high- μ dual triode
ECC85/6AQ8	High- μ dual triode for FM tuners
GZ34/5AR4	Cathode-type rectifier; 250 ma.
EZ80/6V4	9-pin rectifier; cathode; 90 ma.
EZ81/6CA4	9-pin rectifier; cathode; 150 ma.

At All Leading Electronic
Parts Distributors

Ampere
ELECTRONIC CORP.
230 Duffy Ave., Hicksville, Long Island, N.Y.



FREE!

ALLIED'S 1958 CATALOG

404 value-packed
PAGES

the only **COMPLETE** catalog
for everything in electronics

Get ALLIED's 1958 Catalog—it's *complete*, up-to-date—404 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

WORLD'S LARGEST STOCKS

- Latest Hi-Fi Systems and Components
- Money-Saving, Build-Your-Own KNIGHT-KITS
- Recorders and Supplies
- Public Address Systems and Accessories
- TV Tubes, Antennas and Accessories
- Amateur Receivers, Transmitters, Station Gear
- Test & Lab Instruments
- Specialized Industrial Electronic Equipment
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

EASY-PAY TERMS:

Only 10% down,
up to 18 months
to pay. Available
on orders over \$45.
Fast handling—
no red tape.


featuring:

ALLIED'S money-saving knight-kits:

Finest electronic equipment in money-saving kit form. Over 50 quality kits available—Hi-Fi amplifier, tuner and speaker kits, Hobby kits, Test Instruments, Ham kits (see our KNIGHT-KIT values elsewhere in this publication). ALLIED KNIGHT-KITS are easiest to build and they **SAVE YOU MORE.**

EVERYTHING IN HI-FI

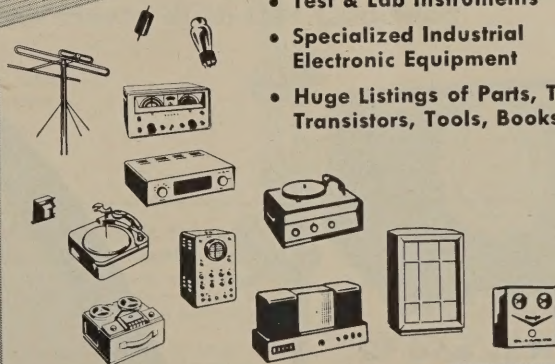World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Save on exclusive ALLIED-Recommended complete systems. Own the best in Hi-Fi for less!



send for the leading
electronic supply guide

FREE!

ALLIED RADIO CORP., Dept. 2-M7
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE 404-Page 1958 ALLIED Catalog

Name _____

Address _____


City _____ Zone _____ State _____




Our 37th Year

ALLIED RADIO


World's Largest Electronic Supply House

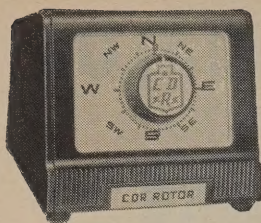


AR-22

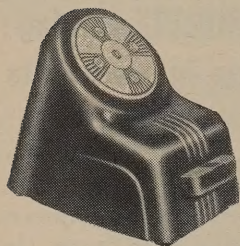

TR-2

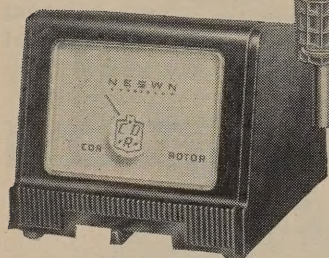

TR-4

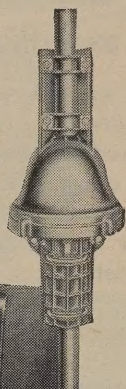

5-star feature...



1 the best color TV picture

the growth of color TV means an even greater demand for CDR Rotors for pin-point accuracy of antenna direction.




2 a better picture on more stations

CDR Rotors add to the pleasure of TV viewing because they line up the antenna perfectly with the transmitted TV signal giving a BETTER picture ... and making it possible to bring in MORE stations.



CDR ROTORS

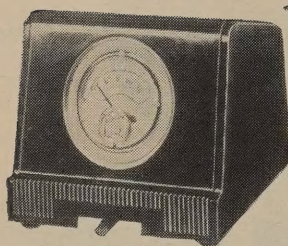

TR 11 and 12



3 tested and proven dependable

thousands and thousands of CDR Rotors have proven their dependability over years of unfailing performance in installations everywhere in the nation. Quality and engineering you know you can count on.




4 pre-sold to your customers

the greatest coverage and concentration of full minute spot announcements on leading TV stations is working for YOU ... pre-selling your customers.



5 the complete line

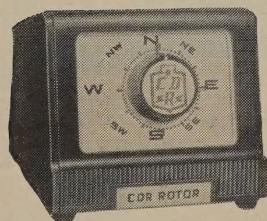a model for every need ... for every application. CDR Rotors make it possible for you to give your customer exactly what is needed ... the right CDR Rotor for the right job.



AR 1 and 2



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13 OHIO

How To
Increase your
Income
in
Electronics

FREE

tells
how

We Guarantee

To Train and Coach You At Home In
Spare Time Until You Get

Your FCC License

If you have had any practical experience—Amateur, Army, Navy, Radio repair, or experimenting.

Here Is Your Guarantee

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial License.

EFFECTIVE
JOB FINDING
SERVICE HELPS CIRE
TRAINEES GET
BETTER JOBS

Effective Job Finding Service Helps CIRE Trainees Get Better Jobs

Chief Engineer

"Since enrolling with Cleveland Institute I have received my 1st class license, served as a transmitter engineer and am now Chief Engineer of Station WAIN. I also have a Motorola 2-Way Service Station. Thanks to the Institute for making this possible!"
Lewis M. Owens, Columbia, Ky.

Test Engineer

"I am pleased to inform you that I recently secured a position as Test Engineer with Melpar, Inc. (Subsidiary of Westinghouse). A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."
Boyd Daugherty, Falls Church, Va.

Airlines

In a year and a half, he received his first class FCC License. He is continuing his training with Cleveland Institute. His goal is much higher than his present position with Eastern Airlines, so he is adding technical "know-how" to his practical experience.
Bob Thompson, Nashville 14, Tennessee

HERE'S PROOF
FCC LICENSES
ARE OFTEN SECURED
IN A FEW HOURS
WITH OUR
COACHING

Here's Proof FCC Licenses Are Often Secured In A Few Hours With Our Coaching

Name and Address	License	Time
John H. Johnson, Boise City, Okla.	1st	20 weeks
Prentice Harrison, Lewes, Delaware	1st	27 weeks
W. E. Evey, Ottawa, Kansas	2nd	24 weeks
J. A. Niedeck, Bethlehem, Pa.	2nd	8 weeks
Gerald J. Collier, Columbus, Ohio	2nd	16 weeks

EMPLOYERS
MAKE JOB OFFERS
LIKE THESE TO OUR
GRADUATES EVERY
MONTH

Employers Make Job Offers Like These To Our Graduates Every Month

Broadcast Station in Illinois: "We are in need of an engineer with a first class phone license, preferably a student of Cleveland Institute of Radio Electronics; 40 hour week plus 8 hours overtime."

West Coast Manufacturer: "We are currently in need of men with electronics training or experience in radar maintenance. We would appreciate your referral of interested persons to us."

Ours is the only home study course which supplies FCC-type examinations with all lessons and final tests.

Your FCC Ticket is recognized by employers as proof of your technical ability

Cleveland Institute of Radio Electronics

Desk RE-12, 4900 Euclid Bldg., Cleveland 3, Ohio

Accredited by the National Home Study Council

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | | |
|---|---|--|
| <input type="checkbox"/> Military | <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Broadcasting | <input type="checkbox"/> Other..... |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Home Experimenting | |

In what kind of work are you now engaged?.....


In what branch of Electronics are you interested?.....

Name..... Age..... Address.....

City..... Zone..... State.....

Special Tuition Rates to Members of Armed Forces


RE-12

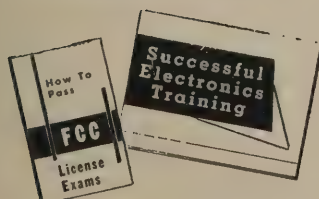

Act Now!

QUALITY REVOLVES AROUND

GI PHONOMOTORS

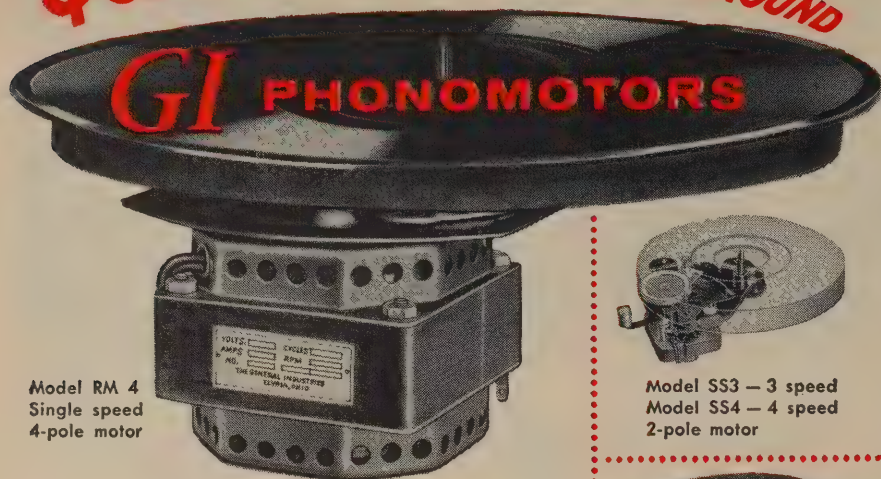


Model RM 4
Single speed
4-pole motor


• Why do America's leading O.E.M.'s specify GI phonomotors? Because they know that fine tone quality depends on a quiet, vibration-free power unit. No other line can match GI's record of dependability... and none can offer the convenience of a complete selection of models from a single source. When QUALITY counts, you can...

RELY on GI


"A Complete Line from a Single Source"

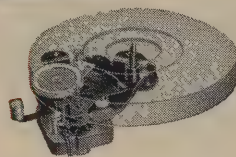

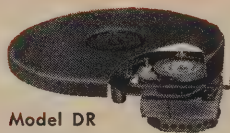
Model SS3 — 3 speed
Model SS4 — 4 speed
2-pole motor




Model DR
2-speed
4-pole motor

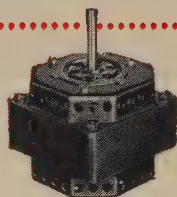

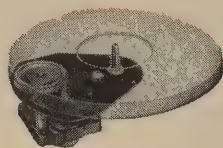Model D-10, 4-pole, shaded
pole A.C. induction type for
tape, wire, or disc recorders



Model AX
Single speed
2-pole motor

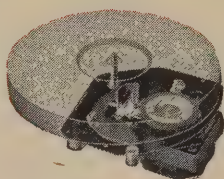

Model DSS
3-speed, 4-pole motor



Model BX
Battery Operated
3-speed motor
(45, 33 1/2, 16 1/2 R.P.M.)

Write for complete specifications and quantity
price quotations today!



THE GENERAL INDUSTRIES CO.

DEPT. GR • ELYRIA, OHIO

What the future holds for you in Radio-Electronics

- Direct-Reading Audio Frequency Meter
- New Amplifier with KT-88 Tubes
- Tricky Circuits in TV
- Common Fallacies in Color TV Servicing
- Tiny-Tran—A Real Pocket Radio
- Placing Speakers for Stereo Reproduction
- The Strange World of Color Vision

The JANUARY issue of RADIO-ELECTRONICS goes
on sale December 24 at all better parts distributors
and newsstands.

SUBSCRIPTION RATES

1 year \$4.00 2 years \$7.00 3 years \$9.00

RADIO-ELECTRONICS, 154 West 14th Street, New York 11, N. Y.

NEWS BRIEFS (Continued from page 8)

has two satellites, CHBC-TV-1 on channel 13 in Penticton, and CHBC-TV-2 on channel 7 in Vernon.

AIEE EDUCATION MEDAL has been awarded to Dr. William L. Everitt, dean of the College of Engineering at the University of Illinois, for outstanding service as a teacher in electrical engineering. He received the medal at the Fall General Meeting of the American Institute of Electrical Engineers in Chicago.

Dr. Everitt has devoted most of his life to education, except for two years as engineer in charge of PBX (Public Board Exchange) development for the North Electric Manufacturing Co. He is noted for inventions in the fields of automatic telephony, radio altimeters for aircraft, directional antenna systems, speech compression and radio tuning systems.

8-RPM RECORD PLAYS 10 HOURS. Speaking before the Audio Engineering Society at its convention at the Hotel New Yorker, New York City, Dr. Peter Goldmark, president of CBS laboratories, announced the new speed. He said that a 7-inch record plays for 4 hours while a 12-inch record would play for 10.

Dr. Golmark pointed out that reducing speed from 33 1/3 to 16 rpm reduced the average surface noise by 4 db. The speed reduction from 16 to 8 rpm cuts surface noise by another 3 db.

The 8-rpm record does lose some high-frequency response but, for speech, a 5,000-cycle maximum frequency gives adequate reproduction.


It was noted that research on the 8-rpm speed was performed with the cooperation of the American Foundation for the Blind and the Library of Congress.

RADIO LIBRARY FOR THE BLIND, sponsored by the South East Amateur Radio Club, Inc., 11519 Parkview Ave., Cleveland, Ohio, is now in operation. Among the library's services, mailed free to and from the borrower, are: electronics literature in manuscript form in braille; circulating copies of the *Braille Technical Press*; electronics literature recorded on tape; monthly tape featuring articles from major electronics magazines.

ULTRA-MAGNIFIER quadruples the enlarging power of RCA's model EMU-3 electron microscope. The new device enables the electron microscope to enlarge specimens as much as 200,000 times, compared to its present power of 50,000. This coupled with photographic enlargement permits magnifications as great as 1,000,000 times. The increased enlarging power is made possible primarily by a newly developed intermediate lens polepiece which focuses the microscope's electron beam. The ultra-magnifier kit is made up of the new lens polepiece and an electronic control unit which includes a nine-step switch to vary magnification over the new high range.

END

RADIO-ELECTRONICS

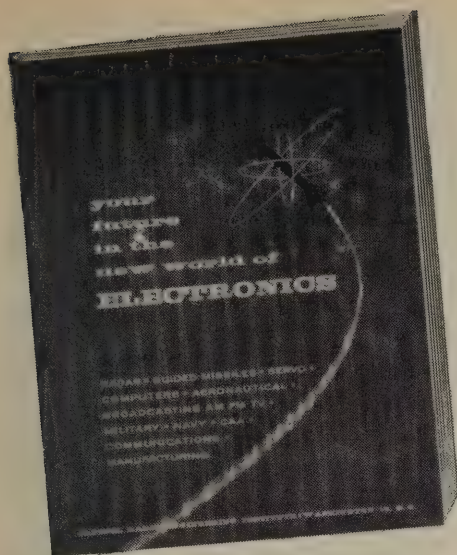

The data that Launched Thousands of Careers is yours **FREE**

Tells how you can be successful in **RADIO-TV-ELECTRONICS**

Send for Your Free Copy Today!

This is a brand new edition of the book which has launched thousands of men on good-paying careers in radio-tv-electronics.

It brings you completely up to date—answers important questions on newest career developments in electronics, including Radar, Guided Missiles, Servomechanisms, Computers, as well as Aeronautical Electronics, Broadcasting (AM, FM, TV), Military, Navy and CAA Electronics, Communications and Electronics Manufacturing.

This book, "Your Future in the New World of Electronics," also shows you how CREI Home Study leads the way to greater earnings in the booming electronics world.

However, CREI does not promise you a "snap." With an accredited technical school such as this you must study to convert your ambition into technical knowledge you can sell in the fabulous Electronics market.

Since its founding in 1927, CREI has provided thousands of professional electronics men with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics, at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Douglas Aircraft Co., Glenn L. Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair Ltd., Federal Electric Corp., and U. S. Information Agency. CREI courses are prepared by recognized experts, in a practical, easily understood manner. You get the benefit of time-tested study assignments under the personal supervision of a CREI staff instructor. This is accomplished on your own time, during hours selected by you, and controlled by your own will power. This com-

plete training is the reason that graduates find their CREI diplomas keys-to-success in radio, TV and Electronics. CREI alumni hold top positions in America's leading firms. At your service is the CREI Placement Bureau, which finds positions for advanced students and graduates. Although CREI does not guarantee jobs, requests for personnel far exceed current supply. Now is the time of decision for you. Luck will not

propel you forward unless it finds you trained. Contacts won't budge you an inch unless you have the skill to back them up. The answer is: Technical Training . . . and willingness to learn. Together they will bring you increased earnings in this new Age of Electronics. Fill out the coupon below and mail it now. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you!



CREI also offers Residence Training at same high technical level in Washington, D.C. Classes start at regular intervals. Qualified residence school graduates earn degree "Associate in Applied Science." Check coupon if you prefer residence study.

VETERANS: If eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

Industry Calls for CREI training By Name . . . SO SHOULD YOU!

← Here you see an actual help wanted ad from the *San Francisco Examiner*, one of many which specify "CREI or equal" training. This shows that industry approves CREI training, even insists on it.

FILL OUT AND MAIL TODAY—BEFORE YOU FORGET IT!

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 1412-D, 3224 16th St., N.W., Washington 10, D.C.

ECPD Accredited Technical Institute Curricula—Founded 1927

Please send me your course outline and **FREE** Illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology

CHECK FIELD OF GREATEST INTEREST

- ☐ Electronic Engineering Technology
- ☐ Broadcast (AM, FM, TV) Engineering Technology
- ☐ Aeronautical Electronic Engineering Technology
- ☐ Television Engineering Technology

Name..... Age.....

Street

City..... Zone..... State.....

CHECK: ☐ Home Study ☐ Residence School ☐ Veteran

To help us answer your request intelligently, please give the following information:


EMPLOYED BY.....

TYPE OF PRESENT WORK.....

SCHOOL BACKGROUND.....

ELECTRONICS EXPERIENCE.....

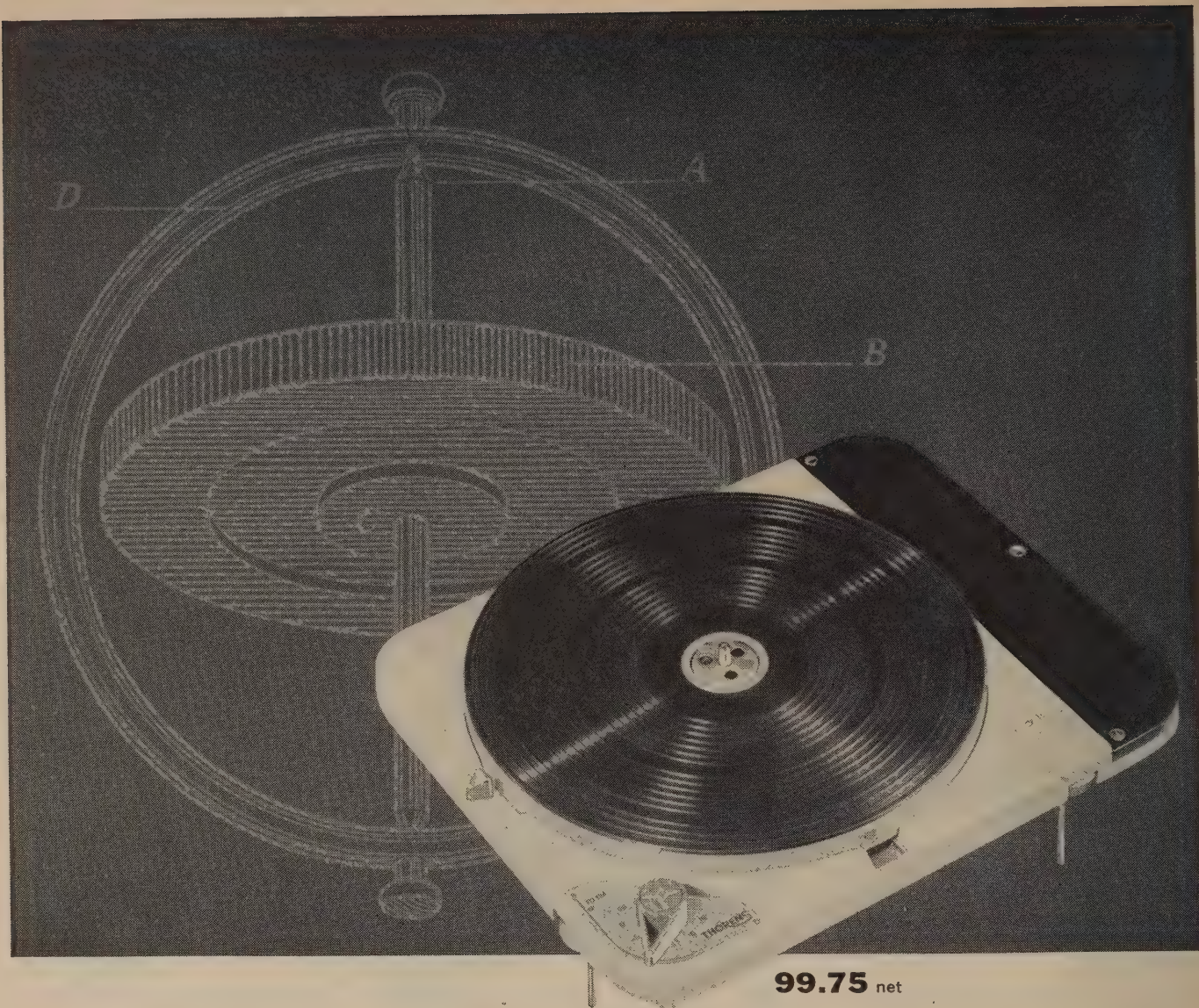IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED?



99.75 net

NEW 12" PRECISION TURNTABLE

OUTSTANDING FEATURES

Four speeds, each with $\pm 3\%$ speed adjustment. Built-in illuminated strobe disk for all speeds. Built-in level bubble and leveling screws. Precision 4-pole motor, extra-compliant belt-drive and idler system plus exclusive Thorens Roto-Drive principle, provide complete vibration isolation, absolutely constant speed. Provision for easily changing arms without leaving unsightly permanent marks—just replace low-cost arm mounting board, available for 12" or 16" arms in various finishes. Easy to mount, the TD-124 requires only $2\frac{3}{4}$ " clearance below mounting board. Furnished with attached line cord, shielded cable and solder plate.

Gyro-like Roto-Drive gives new Thorens TD-124 absolute speed uniformity. Heavier than 16-inch turntables, yet it starts, stops in less than $2/3$ turn!

How to get the heaviest possible turntable for smooth, absolutely quiet operation without sacrificing fast starts and stops.

That's the problem Thorens engineers faced when they set out to build the best four-speed, 12-inch, hi-fi turntable money can buy. You'll be amazed at the simplicity of their solution.

The new TD-124 really has two turntables in one: (1) a heavy 10-lb. rim-concentrated, cast-iron flywheel (outweighs 16" aluminum turntables) (2) a light aluminum cover, or turntable proper. An exclusive, Thorens-originated clutch couples or decouples the light aluminum table to the heavy flywheel for instant starts and stops. What's more, the Thorens double turntable system gives you the weight of a cast-iron table (3 times as heavy as aluminum) without danger of attracting any pickup magnet. And with this unique construction, your pickup gets magnetic shielding from motor or transformer hum fields by the iron turntable.

Ask your hi-fi dealer to show you the Thorens TD-124. Better yet, arrange to hear one of those critical, slow piano records on the TD-124. If you don't know who your dealer is, write Thorens Company, Dept. E12.7, New Hyde Park, N. Y. 79



THORENS

SWISS MADE PRODUCTS

HI-FI COMPONENTS • LIGHTERS • SPRING-POWERED SHAVERS • MUSIC BOXES

RADIO-ELECTRONICS

HOW WOULD YOU LIKE TO BREAK INTO ENGINEERING STARTING NEXT MONTH?

Your start in Engineering could mean higher pay, more interesting work, a real chance for advancement. Here's how to do it—fast!

A career in Engineering may be closer than you think, whatever your age or education or present job.

You know about the tremendous demand for engineers and technicians. But do you know how easy it is to get the training that will qualify you for this vital work, and how quickly you can advance?

First Step Wins Job Consideration

The moment you enroll for a course in Engineering you're in a position to change your job. I.C.S. Engineering Courses, for example, start you off with Basic Mathematics and Drafting. Most employers are quick to accept men who start technical training.

Your Advancement Is Rapid

Your interest, your determination, your willingness to spend free hours improving your-

self all work in your favor. But your mastery of engineering subjects is what wins you the biggest boosts.

The I. C. S. method makes it possible for you to learn while you earn, to qualify yourself for upgrading step by step—from Draftsman to Detail Designer to Engineering Technician to full-fledged Engineer. It's a plan fitted to your needs, with personalized instruction and guidance, and, if you like, regular progress reports to your employer.

Mail Coupon for Free Books

If you are seriously interested in a fresh start in an opportunity-packed field, then mark and mail the coupon today. We'll send you *three* free books—(1) the 36-page career guide "How to Succeed," (2) Opportunity outlooks in your field of interest, (3) sample lesson (Math) demonstrating I. C. S. method.

For Real Job Security—Get an I. C. S. Diploma!

I. C. S., Scranton 15, Penna.

Accredited Member,
National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 14910L, SCRANTON 15, PENNA.

(Partial list of 257 courses)

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

- | | | | | |
|--|--|---|--|--|
| ARCHITECTURE and BUILDING CONSTRUCTION
<input type="checkbox"/> Air Conditioning
<input type="checkbox"/> Architecture
<input type="checkbox"/> Arch. Drawing and Designing
<input type="checkbox"/> Building Contractor
<input type="checkbox"/> Building Estimator
<input type="checkbox"/> Carpentry and Millwork
<input type="checkbox"/> Carpenter Foreman
<input type="checkbox"/> Heating
<input type="checkbox"/> Interior Decoration
<input type="checkbox"/> Painting Contractor
<input type="checkbox"/> Plumbing
<input type="checkbox"/> Reading Arch. Blueprints
ART
<input type="checkbox"/> Commercial Art
<input type="checkbox"/> Magazine & Book Illus.
<input type="checkbox"/> Show Card and Sign Lettering
<input type="checkbox"/> Sketching and Painting
AUTOMOTIVE
<input type="checkbox"/> Automobiles
<input type="checkbox"/> Auto Body Rebuilding and Refinishing
<input type="checkbox"/> Auto Engine Tuneup
<input type="checkbox"/> Auto Technician | AVIATION
<input type="checkbox"/> Aero-Engineering Technology
<input type="checkbox"/> Aircraft & Engine Mechanic
BUSINESS
<input type="checkbox"/> Accounting
<input type="checkbox"/> Advertising
<input type="checkbox"/> Business Administration
<input type="checkbox"/> Business Management
<input type="checkbox"/> Cost Accounting
<input type="checkbox"/> Creative Salesmanship
<input type="checkbox"/> Managing a Small Business
<input type="checkbox"/> Professional Secretary
<input type="checkbox"/> Public Accounting
<input type="checkbox"/> Purchasing Agent
<input type="checkbox"/> Salesmanship
<input type="checkbox"/> Salesmanship and Management
<input type="checkbox"/> Traffic Management
CHEMICAL
<input type="checkbox"/> Analytical Chemistry
<input type="checkbox"/> Chemical Engineering
<input type="checkbox"/> Chem. Lab. Technician
<input type="checkbox"/> Elements of Nuclear Energy
<input type="checkbox"/> General Chemistry
<input type="checkbox"/> Natural Gas Prod. and Trans.
<input type="checkbox"/> Petroleum Prod. and Engr.
<input type="checkbox"/> Professional Engineer (Chem)
<input type="checkbox"/> Pulp and Paper Making | CIVIL ENGINEERING
<input type="checkbox"/> Civil Engineering
<input type="checkbox"/> Construction Engineering
<input type="checkbox"/> Highway Engineering
<input type="checkbox"/> Professional Engineer (Civil)
<input type="checkbox"/> Reading Struc. Blueprints
<input type="checkbox"/> Structural Engineering
<input type="checkbox"/> Surveying and Mapping
DRAFTING
<input type="checkbox"/> Aircraft Drafting
<input type="checkbox"/> Architectural Drafting
<input type="checkbox"/> Drafting Machine Design
<input type="checkbox"/> Electrical Drafting
<input type="checkbox"/> Mechanical Drafting
<input type="checkbox"/> Sheet Metal Drafting
<input type="checkbox"/> Structural Drafting
ELECTRICAL
<input type="checkbox"/> Electrical Engineering
<input type="checkbox"/> Elec. Engr. Technician
<input type="checkbox"/> Elec. Light and Power
<input type="checkbox"/> Practical Electrician
<input type="checkbox"/> Practical Lineman
<input type="checkbox"/> Professional Engineer (Elec)
HIGH SCHOOL
<input type="checkbox"/> High School Diploma | <input type="checkbox"/> Good English
<input type="checkbox"/> High School Mathematics
<input type="checkbox"/> Short Story Writing
LEADERSHIP
<input type="checkbox"/> Industrial Foremanship
<input type="checkbox"/> Industrial Supervision
<input type="checkbox"/> Personnel-Labor Relations
<input type="checkbox"/> Supervision
MECHANICAL and SHOP
<input type="checkbox"/> Diesel Engines
<input type="checkbox"/> Gas-Elec. Welding
<input type="checkbox"/> Industrial Engineering
<input type="checkbox"/> Industrial Instrumentation
<input type="checkbox"/> Industrial Metallurgy
<input type="checkbox"/> Industrial Safety
<input type="checkbox"/> Machine Design
<input type="checkbox"/> Machine Shop Practice
<input type="checkbox"/> Mechanical Engineering
<input type="checkbox"/> Professional Engineer (Mech)
<input type="checkbox"/> Quality Control
<input type="checkbox"/> Reading Shop Blueprints
<input type="checkbox"/> Refrigeration and Air Conditioning
<input type="checkbox"/> Tool Design <input type="checkbox"/> Tool Making
RADIO, TELEVISION
<input type="checkbox"/> General Electronics Tech. | <input type="checkbox"/> Industrial Electronics
<input type="checkbox"/> Practical Radio-TV Eng'g
<input type="checkbox"/> Practical Telephony
<input type="checkbox"/> Radio-TV Servicing
RAILROAD
<input type="checkbox"/> Car Inspector and Air Brake
<input type="checkbox"/> Diesel Electrician
<input type="checkbox"/> Diesel Engr. and Fireman
<input type="checkbox"/> Diesel Locomotive
STEAM and DIESEL POWER
<input type="checkbox"/> Combustion Engineering
<input type="checkbox"/> Power Plant Engineer
<input type="checkbox"/> Stationary Diesel Engr.
<input type="checkbox"/> Stationary Fireman
TEXTILE
<input type="checkbox"/> Carding and Spinning
<input type="checkbox"/> Cotton Manufacture
<input type="checkbox"/> Cotton Warping and Weaving
<input type="checkbox"/> Loom Fixing Technician
<input type="checkbox"/> Textile Designing
<input type="checkbox"/> Textile Finishing & Dyeing
<input type="checkbox"/> Throwing
<input type="checkbox"/> Warping and Weaving
<input type="checkbox"/> Worsted Manufacturing |
|--|--|---|--|--|

Name _____ Age _____ Home Address _____
 City _____ Zone _____ State _____ Working Hours _____ A.M. to P.M. _____
 Occupation _____

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

**Just what
the doctor ordered
for a "healthier"
service
reputation...**

Check these "undoctored" facts yourself to learn why CRL MD (molded disc) ceramic capacitors outlast and outperform conventional "mud" discs—yet cost the same. You'll find that CRL molded discs give you:

1. *Three times* the voltage breakdown — 3000 V.D.C. breakdown to ground.
2. *Eight times* the lead strength—greater than the breaking strength of the No. 22 tinned-copper wire itself.
3. *Ten times* the humidity resistance — .005% or less moisture absorption by the molded casing.
4. *Many times* the resistance of ordinary discs to physical shock and vibration.

The results: more satisfied customers . . . more business for you . . . and a self-assurance that you gave the best.

Pick them up at your CRL distributor who handles these and thousands of other quality components described in Centralab Catalog 30, which is available on request.

Centralab

© Centralab Trademark

A DIVISION OF GLOBE-UNION INC.
922L EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
IN CANADA: 804 MT. PLEASANT ROAD • TORONTO, ONTARIO



Correspondence



X-RAYS FROM TV SETS

Dear Editor:

"Hot Words on Boosters" (page 16, October issue) hit a point close to home. Therefore, I am writing this to correct what seems a gross misunderstanding of a rather vague subject.

Since I am a radiation physicist, one of the very first things I found myself doing was measuring the X-rays that emanate from picture tubes and other high-voltage tubes to find out if they would be strong enough to be harmful.

Using a Victoreen R-meter, which is commonly used in X-ray laboratories for measuring X-ray strength, I empirically determined that very little radiation emanated from the face of a TV picture tube. So little, in fact, that the readings were barely indicated on the R-meter. With the TV set in the cabinet, no reading was available, indicating that the strength of X-rays was way below the sensitivity of the meter.

Around the neck of the picture tube, where the glass is rather thin, a definite reading was indicated. However, this reading (at the usual voltages in black-and-white TV sets) was so low that a person would have to spend 6 or 8 months near the neck of the picture tube (or inches from it) to get enough radiation to pass the minimum safe requirements (100 milliroentgens per week) of the Radiological Safety Conference.

There is, however, a more serious danger point. That is at or near the 1B3, 1X2 and 1V2 tubes used as rectifiers. Here, X-ray dosages were such that a long exposure of perhaps an hour, at 6 inches from these tubes, could cause an overdose of these soft rays. Fortunately, these tubes are usually enclosed in a metal can or placed under the chassis in where the X-rays are heavily absorbed. No reading of any value was available from sets in their cabinet or from sets where all the hardware was in place. My measurements were made within 6 inches since, frankly, I cannot see anyone getting closer than this to a "hot" high-voltage rectifier.


My conclusions from this were very definite:

1. A properly manufactured TV set gives off no appreciable radiation to the user or his family.

2. A properly manufactured TV set has sufficient protection so the service technician need not be worried.

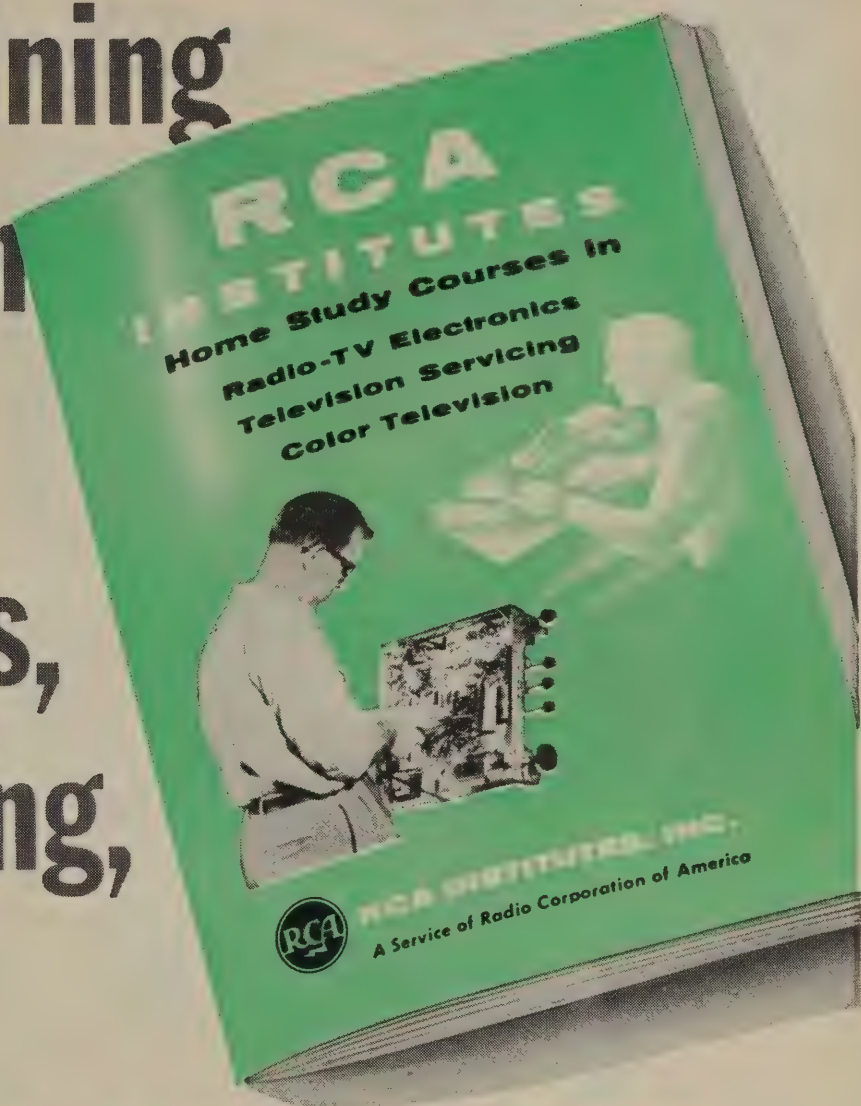3. A technician who has developed suitable methods of working so that

RCA offers you the finest training at home in Radio-TV electronics, TV servicing, Color TV



SEND FOR THIS FREE BOOK NOW!



RCA INSTITUTES, INC.

A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

In Canada—RCA Victor Company, Ltd.,
5001 Cote de Liesse Rd., Montreal 9, Que.

Pay-as-you-learn. You need pay for only one study group at a time. Practical work with very first lesson. All text material and equipment is yours to keep. Courses for the beginner and advanced student.

RCA Institutes, Inc., Home Study Dept. RE-127
350 West Fourth Street, New York 14, N. Y.

Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No Salesman will call.

Name.....
Please Print

Address.....



City..... Zone.... State.....

KOREAN VETS! Enter discharge date.....

To save time, paste coupon on postcard

MORE USES—MORE INCOME

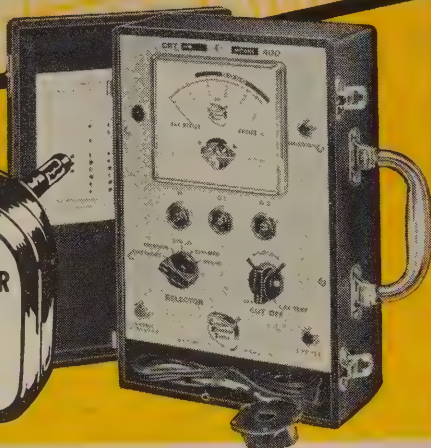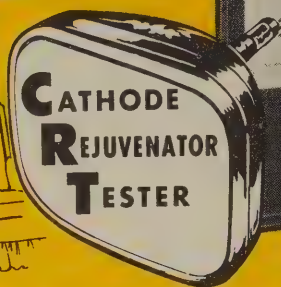With New Adapter, the famous B&K CRT Now Also Tests and Repairs Color and 110° Picture Tubes



CRT 400 PROVES REAL MONEY-MAKER

Thousands of servicemen today make money and keep customer good-will by checking and correcting b/w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!

Model 400 (without adapter) Net, **\$59.95**

NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT

Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.

Model C40 Adapter Net, **\$9.95**

See your B&K distributor, or write for Bulletin 400-C40-E

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR
B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



BUY AND USE CHRISTMAS SEALS

Christmas Seals make possible a year-round gift to every man, woman and child—help and protection against tuberculosis. From now 'til Christmas make every card, letter, and package a double gift—with Christmas Seals.

CORRESPONDENCE (Continued)

he does not allow himself to get close enough to high-voltage components to get sparkover to his body or hands does not have to worry about X-rays since he is usually far enough from their source or well enough protected from their source (by shields, etc.) that he is in no danger.

4. When replacing a TV set in a cabinet, technicians should at all times replace *all* hardware, especially high-voltage cans, and safety glass to insure his customers against *possible* low dosages of X-rays as well as to provide the security these devices offer from shock hazards.

The only tube (picture tube) that seemed a potential X-ray hazard other than the rectifiers was the 3-inch Philips projection tube *when used, and only when used outside its housing*. This tube, remember, has a rather thin glass window, uses some 30,000 volts (which is definitely in the X-ray range), and its cathode is rather close to the screen (it being a short-neck tube). Be careful when using this tube.

Unfortunately, I have not been able to obtain any X-ray measurements on color TV tubes at this time. However, I intend to do this as soon as possible.

CHARLES R. MADUELL, JR.

Consulting Physicist
New Orleans, La.

KLIPSCH VS. VILLCHUR

Dear Editor:

I read with extreme interest the two sides of the speaker-distortion argument presented by Messrs. Klipsch and Villchur in October. But it seems to me that the issue, an extremely important one, has not been joined. Mr. Villchur speaks of harmonic distortion and Mr. Klipsch of intermodulation distortion.

Mr. Villchur shows an oscilloscope trace of a sine wave reproduced by an acoustic suspension system at 30 cycles with a 39-watt input. The waveform is clean to the eye, and this is remarkable. But the eye cannot discern harmonic distortion much below 5%. If harmonic distortion were, say, 3 or 4%, the eye could not tell but this might conceivably imply quite a high order of intermodulation distortion, *perhaps* as high as Mr. Klipsch indicates with a ½-inch cone excursion. *I don't know, I can only guess at what is possible.* The possibilities include that the relationship between harmonic and intermodulation distortion in a speaker resembles that in a tape recorder where, for example, only 3% harmonic distortion may correspond to 20 or 30% intermodulation distortion.

HERMAN BURSTEIN

Wantage, N. Y.

A HI-FI PROBLEM



Dear Editor

An increasing number of customers are bringing back records with the

Learn TELEVISION-RADIO

Servicing or Communications by Practicing at Home in Spare Time

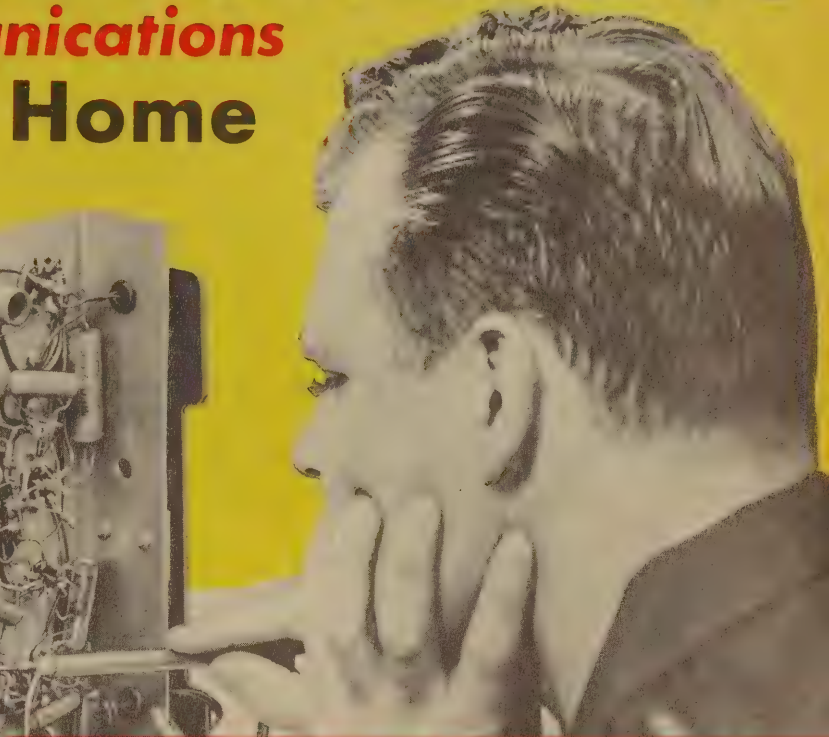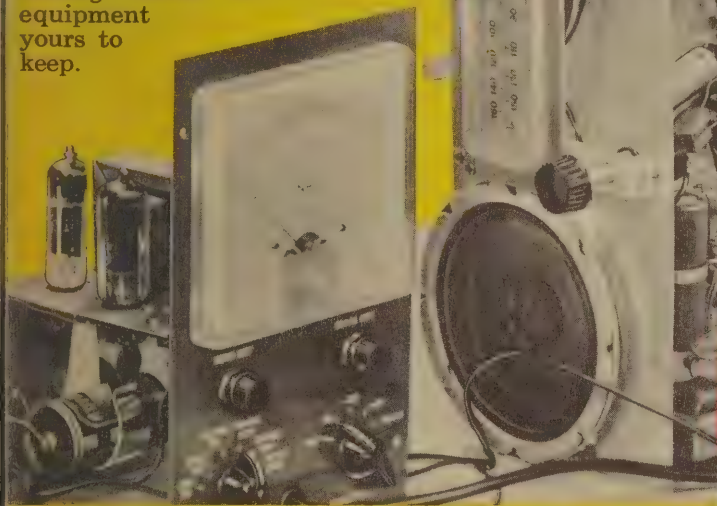WITHOUT EXTRA CHARGE you get special NRI kits developed to give actual experience with TV-Radio equipment. You build, test, experiment with receiver or broadcasting circuits. All equipment yours to keep.



**NRI Has Trained Thousands for
Successful Careers in TV-Radio**



Have the High Pay, Prestige, Good Future of a Skilled TV-Radio Technician

People look up to and depend on the Technician, more than ever before. Offices, plants, homes everywhere are obliged to buy his knowledge and services. His opportunities are great and are increasing. Become a TV-Radio Technician. At home, and in your spare time, you can learn to do this interesting, satisfying work—qualify for important pay. To ambitious men everywhere here in the fast growing Television-Radio field is rich promise of fascinating jobs, satisfaction and prestige as well as increasing personal prosperity.

Increased Opportunities in Growing Field

A steady stream of new Electronic products is increasing the job and promotion opportunities for Television-Radio Technicians. Right now, a solid, proven field of opportunity for good pay is servicing the tens of millions of Television and Radio sets now in use. The hundreds of TV and Radio Stations on the air offer interesting jobs for Operators and Technicians.

More Money Soon—Make \$10 to \$15 a Week Extra Fixing Sets in Spare Time

NRI students find it easy and profitable to start fixing sets for friends and neighbors a few months after enrolling. Picking up \$10, \$15 and more a week gives substantial extra spending money. Many who start in spare time soon build full time TV-Radio sales and service businesses.

Act Now—See What NRI Can Do for You

NRI has devoted over 40 years to developing simplified practical training methods. You train at home. Get practical experience, learn-by-doing. Address: **NATIONAL RADIO INSTITUTE, Washington 16, D. C.**

Studio Engr., Station KATV
"I am now Studio Engineer at Television Station KATV. Before enrolling for the NRI Course, I was held back by limitation of a sixth grade education." **BILLY SANCHEZ, Pine Bluff, Ark.**

Has All the Work He Can Do
"Since finishing NRI Course I have repaired more than 2,000 TV and Radio sets a year. NRI training certainly proved to be a good foundation." **H. R. GORDON, Milledgeville, Ga.**

Has Good Part Time Business
"Quite early in my training I started servicing sets. Now have completely equipped shop. My NRI training is the backbone of my progress." **E. A. BRED, Tacoma, Wash.**

The Tested Way To Better Pay

See Other Side

CUT OUT AND MAIL CARD NOW

**SAMPLE LESSON
AND CATALOG
BOTH FREE**

**NO STAMP NEEDED!
WE PAY POSTAGE**

This card entitles you to Actual Lesson on Servicing, shows how you learn Television-Radio at home. You'll also receive 64-Page Catalog.

**NATIONAL RADIO INSTITUTE, Dept. A
Washington 16, D. C.**

Please mail me the FREE sample lesson and 64-Page Catalog. (No Salesman will call.)

Name.....Age.....

Address.....

City.....Zone.....State.....


ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

**The ABC's of
SERVICING**

**Job and Career
Opportunities
for
RADIO-TV
TECHNICIANS**





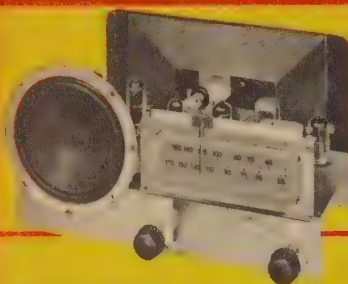**Technical "KNOW-HOW" Can Give You Interesting, Important Work
LEARN-BY-DOING with Kits NRI Sends at No Extra Charge**



YOU BUILD AC-DC Superhet Receiver

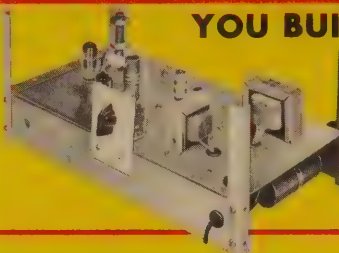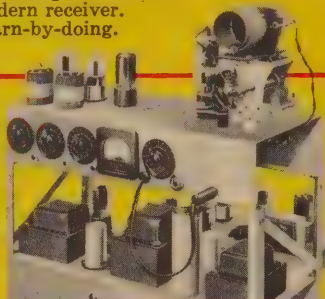NRI Servicing Course includes all needed parts. By introducing defects you get actual servicing experience practicing with this modern receiver. Learn-by-doing.



YOU BUILD Signal Generator

You build this Signal Generator. Learn how to compensate high frequency amplifiers, practice aligning typical I.F. amplifiers in receiver circuits. Make tests, conduct experiments.



YOU BUILD Vacuum Tube Voltmeter

Use it to earn extra cash fixing neighbors' sets; bring to life theory you learn from NRI's easy-to-understand texts.

YOU BUILD Broadcasting Transmitter

As part of NRI Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures. Train for your FCC Commercial Operator's License.



For Higher Pay, Better Jobs Be a Television-Radio Technician



Servicing Needs More Trained Men

Portable TV, Hi-Fi, Transistor Radios, Color TV are making new demands for trained Technicians. Good opportunities for spare time earnings or a business of your own.



**J. E. Smith,
Founder**


Train at Home the NRI Way Famous for Over 40 Years

NRI is America's oldest and largest home study Television-Radio school. The more than 40 years' experience training men for success, the outstanding record and reputation of this school—benefits you in many ways. NRI methods are tested, proven. Successful graduates are everywhere, from coast to coast, in small towns and big cities. You train in your own home, keep your present job while learning. Many successful NRI men did not finish high school. Let us send you an actual lesson, judge for yourself how easy it is to learn.

No Experience Necessary—NRI Sends Many Kits for Practical Experience

You don't have to know anything about electricity or Radio to understand and succeed with NRI Courses. Clearly written, well-illustrated NRI lessons teach TV-Radio-Electronic principles. You get NRI kits for actual experience. All equipment is yours to keep. You learn-by-doing. Mailing the postage-free card may be one of the most important acts of your life. Do it now. Reasonable tuition. Low monthly payments available. Address: **NATIONAL RADIO INSTITUTE, Washington 16, D. C.**

NRI Graduates Do Important Work

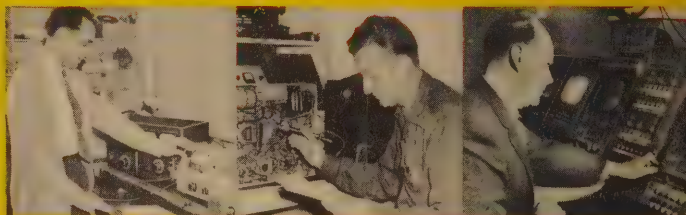

New Quality Control Chief
"Had no other training in Radio before enrolling, obtained job working on TV amplifiers before finishing course. Now Quality Control Chief." **T. R. FAVARLO, Norwich, N. Y.**

NRI Course Easy to Understand
"I opened my own shop before receiving my diploma. I have had to hire extra help. I am independent in my own business." **D. P. CRESSEY, Stockton, Cal.**

Works on Color-TV
"NRI changed my whole life. If I had not taken the course, probably would still be a fireman, struggling along. Now Control Supervisor at WRCA - TV." **J. F. MELINE, New York, N. Y.**

**SAMPLE LESSON
64-page CATALOG
both FREE**

**See Other Side
for more
information on
the Tested Way
to Better Pay**

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

Washington 16, D. C.

**FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.**

complaint that they are defective because "they skip" and are "scratched and keep repeating."

When this happens here, we immediately put the record on one of our players and it plays perfectly. Some people then realize that perhaps their own player can be corrected to play the record properly, too.

But the majority remain unconvinced because "the other side plays all right; all my *other* records play all right; it's a new *hi-fi* and I *know* that nothing could be wrong with it". The statements are stereotyped; the phrasing, the emphasis, the attitude.

These individuals want one action only. They want "a *fresh* record." We know from experience that giving one to them is no solution. It also repeats in exactly the same places. This exasperates them till they think that we gave them still another "wornout record." Worse, these potential purchasers may lose interest in buying records.

Who is responsible for the state of mind of these customers and the conditions which cause it? Is the record dealer, who sold only the record and not the player? (We do sell record-playing equipment, and we are careful to sell only those we know and can guarantee will not skip or repeat.) Is it the record manufacturer? Is it the tone-arm manufacturer? Is it the stylus manufacturer?

This needless situation comes from the sale of certain players and records that are incompatible.

As a retail record dealer, I resent and protest against being the scapegoat and taking the resulting blame, enmity and loss of patronage.

For the benefit of both the public and the industry, I ask that adequate standards of relationship between records and reproducers be established and thoroughly publicized.

The following statement is printed on our carry bags: *Farrington's Record Store guarantees that every record is fresh and undamaged when it leaves our store. Records are not allowed out for home trial.*

We are not responsible for records damaged by record-playing equipment which "keeps repeating," "sticks in the grooves," etc., regardless of whether "it's a new player," or "the other side plays all right."


The responsibility lies with those who sell such equipment.

We guarantee that any record player bought from us will not damage records by "sticking" or "repeating."

For the benefit of the public and industry, I ask that adequate standards or relationships between records and reproducers be established and publicized. The prevalent passive acceptance of normal merchandise as "defective" is not a solution. Thousands of customers are still sore.

CHARLES W. FARRINGTON
Farrington Record Store
Arlington, Mass.

LEARN BASIC ELECTRICITY *first!*

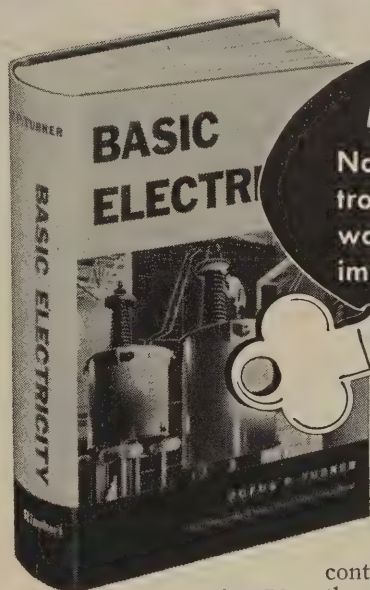

BRAND NEW!

No matter what kind of radio, electronic, communications or electrical work you plan to do, this is the most important training of all.

Your Key to Success in Radio-Electronics

Every piece of electrical equipment from giant industrial units to TV sets; from guided missile controls to hi-fi systems and all the rest are based on the same fundamental electrical principles.

That's why we say: **Learn your basic electricity first . . . learn it thoroughly! . . . then everything else comes 10 times as easy!**

You'll read advanced technical literature with new understanding. You'll have a firm grasp of ALL electrical-electronic matters that will amaze you. And you'll be far better fitted for interesting, good-paying jobs along almost any electrical line.

This new 396-page BASIC ELECTRICITY Manual by Rufus Turner brings you the kind of intensely practical, diversified training that can pay off in a dozen different ways!

From basic currents and circuits to electromagnetism . . . from polyphase systems to 'phone fundamentals . . . from ammeters to oscilloscopes . . . right down the line to transistors, tubes, sound reproduction, industrial applications and even telemetering, BASIC ELECTRICITY covers the entire field.

PRACTICAL TRAINING that shows you how!

300 pictures and charts make things doubly clear.

You get practical examples of such things as reactance, phase relations, impedance . . . even power factor.

You see how and why to make measurements by various methods. You learn about all instruments in common use.

"Set up" diagrams teach you to extend meter ranges or to measure temperature, speed, strain, thickness, etc. Essential elements such as motors, generators, batteries, polyphase, etc., often neglected by ordinary electronic books are fully covered. Complicated controls are explained . . . with no need for advanced mathematics to understand them.

BASIC ELECTRICITY is "must" training for beginners—and is equally ideal as a "brush up" course for experienced technicians. Send coupon today. You be the judge without risking a cent.

Only \$6.50
for the complete training . . .
NO LESSONS TO WAIT FOR

Includes BASIC ELECTRONICS . . .

both general and industrial
. . . even covers transistors
and their uses

BRINGS YOU THE COMPLETE "KNOW HOW" OF:

Circuits & Currents; Controls; Magnetism & Electromagnetism; Capacitance; Inductance; Resistance; Phase Relations; Generators; Motors; Transformers; Rectifiers; Wiring Illumination; Instruments and Measurements; PLUS Electronic Tubes; Amplifiers; Oscillators; Transistors; Industrial Electronics and Automation; X-Rays; Power Factor; Servos . . . and dozens of other subjects.

"MUST" TRAINING for beginners . . . ideal as a refresher course for experienced men.

10-Day Free Examination
Send coupon today

Dept. RE-127, Rinehart & Co., Inc.

232 Madison Ave., New York 36, N. Y.

Send Turner's 396-page BASIC ELECTRICITY for 10-day FREE EXAMINATION. If book is satisfactory, I will then send you \$6.50 (plus postage) promptly in full payment. If not, I will return book within 10 days and owe nothing. (Save! Send \$6.50 with order and we pay postage. Same 10-day return privilege with money refunded.)

Name

Address

City, Zone, State.....

OUTSIDE U.S.A.—Price \$7.00 cash with order. Money back if you return book within 10 days.




INDUCED WAVEFORM ANALYZER

MODEL 850

Top-O'-Chassis Troubleshooting... greatest servicing advance in years!

Perfect for Portable TV

Localizes defective stage in entire TV receiver in less than 5 minutes—without a direct circuit connection. Adapts any 'scope for spotting defects quickly by the modern, easy-to-use Induced Waveform Method. Unique, Phantom Detector Probe makes any tube a convenient test point. Just slip probe successively over each tube, then view and trace waveforms on scope from antenna thru RF, IF, audio, video & sync. Speeds servicing of TV, radios, amplifiers, instruments, industrial and laboratory equipment tool. Compatible for color. Phone jack for audio monitoring.

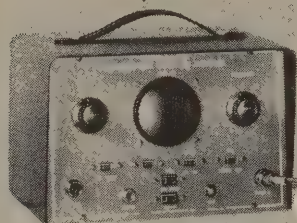

\$89.95 Net

INTERMITTENT CONDITION ANALYZER

MODEL 828

Pinpoints Intermittents without waiting...cooking...or freezing.

Exclusive new principle makes any TV or radio super-sensitive to intermittents and noisy components... without waiting for breakdowns. Saves time and bench space. Cuts callbacks by detecting borderline components before they fail. Special Wintronix Probe and capacity pickup attachments let you hear intermittents thru built-in speaker.



\$79.95 Net

AGC CIRCUIT ANALYZER

MODEL 825

AGC Troubles Won't Fool You Any More!

Saves hours by detecting hard-to-find AGC faults that may look like sync trouble, etc. Furnishes standard, adjustable r-f signal to antenna; monitors AGC action; checks AGC buss for opens and shorts; measures action of gated pulse systems; supplies AGC bias to restore operation by substitution.

Wintronix ANALYZERS

Electronic "Wonder Drugs" for Troubleshooting Pains



Here are the instruments you need to diagnose ailments fast and profitably in today's

complicated—often inaccessible—TV, radio & hi-fi sets.

These four Wintronix *Analyzers* swiftly turn wasted trouble-shooting time into profitable parts replacement time on more and more jobs. Obscure radio and TV faults get tracked down fast by Winston's specialized reference signals and measurements. Like X-rays, they quickly give a complete picture of circuit operation—at far lower cost, with fewer circuit connections, and with less set-up time than with separate conventional instruments.

Today, issue a prescription to yourself for a healthier servicing business—see and try these new Wintronix *Analyzers* at your local parts distributor or write for detailed literature.

SWEEP CIRCUIT ANALYZER

MODEL 820

Rapid, Dynamic Sweep Testing

\$69.95 Net



Completely troubleshoots entire sweep circuits and restores raster by substituting for defective stage. Tests all flybacks and yokes for continuity and shorts. Self-calibrating. Compatible for color.

Model 915/960 Adapter converts Model 820 to a Sync Circuit Analyzer for signal substitution of vertical and horizontal sync pulses.


\$14.95 Net

WINSTON ELECTRONICS INC.

4312 Main Street, Philadelphia 27, Pa.

Learn PRACTICAL RADIO-TV with 25 BIG KITS

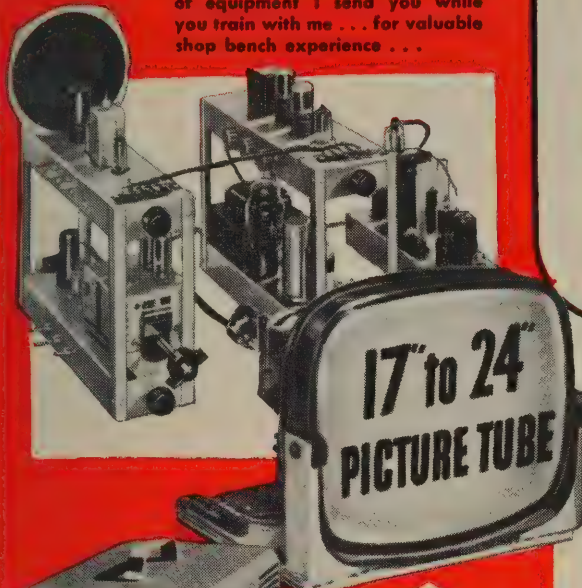
of equipment I send you while
you train with me . . . for valuable
shop bench experience . . .



This is the new Sprayberry Training
Television receiver, built and tested
in sections for greatest instruction
value.

I built every line from modern oscil-
loscope to help you learn practical
Television servicing.

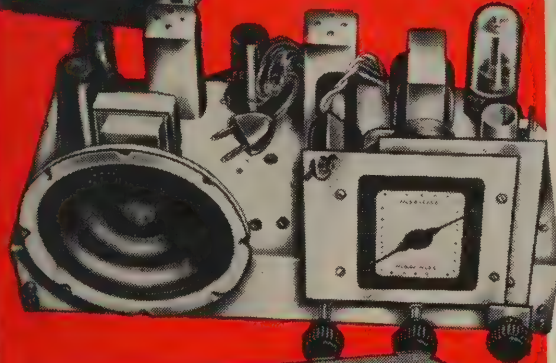You will build this powerful dual
wave and broadcast superhet radio
receiver for valuable shop instruc-
tion practice.



You build the new
Sprayberry Tester . . . 18-range
Volt-Ohm-Milliammeter readings
plus output meter and condenser
and resistor substitution switches.


Average cost per lesson
ONLY \$3.42
Including Kits and Equipment

Clip and Mail the Coupon Below—Now!

**Train in Spare Hours at Home
for the Best Jobs and Big Pay in
Radio-Television
—my new, faster way!**

**Want Proof? Send for my
big FREE CATALOG and
Sample Lesson. Let the facts
speak for themselves!**

Why wait—get into Radio-Television fast!
I will train you in as little as 10 months
to step into the top paying Radio-Tele-
vision field as a much-needed Service
Technician! You will train entirely at
home in your spare time . . . which means
you can train as fast or as slowly as you
like. You have a choice of THREE Sprayberry Training Plans . . .
one *exactly* suited to your needs. My easier-than-ever payment terms
make it possible for you to get set for the good jobs in Radio-Tele-
vision without the slightest strain on your budget! Get the true facts
. . . just mail the coupon for my big new 56 page fact-filled catalog
plus actual sample lesson—both FREE.

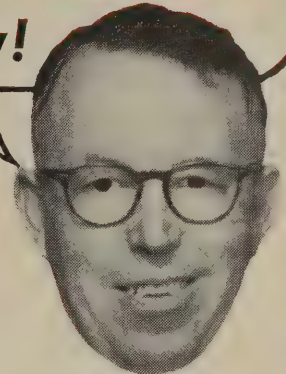

Frank L. Sprayberry
Educational Director

REALLY PRACTICAL TRAINING—NO PREVIOUS EXPERIENCE NEEDED

My students do better because I train both the mind and the hands.
Sprayberry Training is offered in 25 individual training units, each includes
a practice giving kit of parts and equipment . . . all yours to keep. You
will gain priceless practical experience building the specially engineered
Sprayberry Television Training Receiver, Two-Band Radio Set, Signal
Generator, Audio Tester and the new Sprayberry 18 range Multi-Tester,
plus other test units. You will have a complete set of Radio-TV test equip-
ment to start your own shop. My lessons are regularly revised and every
important new development is covered. My graduates are completely
trained Radio-Television Service Technicians.

NEWEST DEVELOPMENTS

Your training
covers U H F, Color
Television, F M,
Oscilloscope
Servicing, High
Fidelity Sound
and Transistors.

MAIL THE COUPON—See what's ahead in Radio-TV . . . No Salesman Will Call On You!

The coupon below brings you my big new catalog
plus an actual sample Sprayberry Lesson. I invite
you to read the facts . . . to see that I actually illus-
trate every item in my training. With the facts in
your hands, you will be able to decide. No salesman
will call on you. The coupon places you under no
obligation. Mail it now, today, and get ready for
your place in Radio-Television.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

1512 Jarvis Avenue, Dept. 20-W, Chicago 26, Illinois

Mail This Coupon For Free Facts and Sample Lesson



1512 Jarvis Ave., Dept 20-W, Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Tele-
vision Training Plan. I understand this does not obligate me
and that no salesman will call upon me. Include New Cata-
log and Sample Lesson FREE.

Name _____ Age _____



Address _____

City _____ Zone _____ State _____



Again!

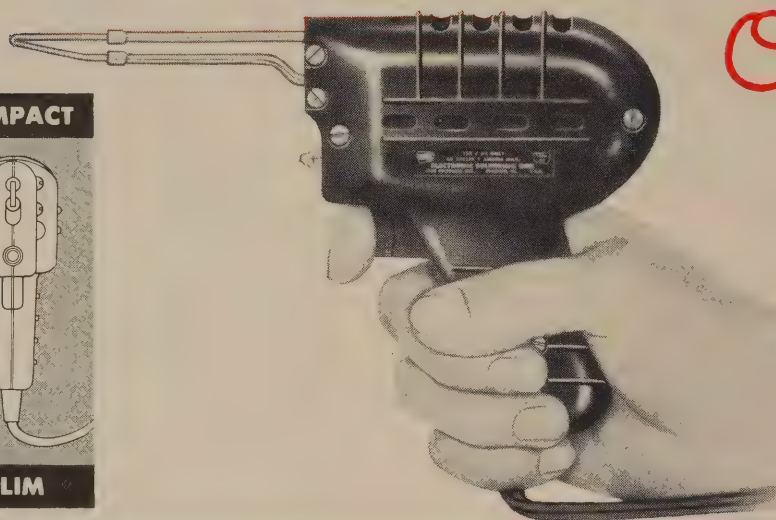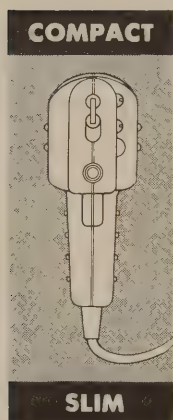
new feather-light 100 WATT ELECTRONIC SOLDERING GUN



Only
\$5⁹⁵
LIST

IT'S SMALLER, LIGHTER, HANDY AS YOUR HAND, IDEAL FOR THE WORK YOU DO

Weights only 19 oz. . . . Heats in 3 seconds on ordinary 110-120 V. A.C. 60 cycle . . . Cools quickly too . . . Automatic spotlight . . . Long reach, long life tips . . . Soldering tips interchangeable with hot-cutting or flat iron finish-repair tips . . . Ebony black plastic handle and housing are heat and impact resistant . . . Beautifully balanced—easy to use . . . Ideal for service calls, bench repairs, home work shops. Lowest priced soldering gun on record.

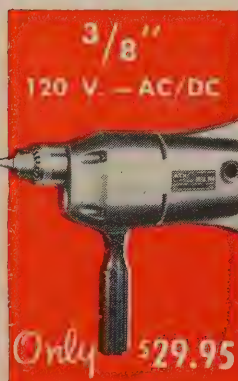

LIST

Also


2 SPEED POWER DRILL

1000 - 3000 RPM as needed. Speed change quick, positive. Provides just the right speeds for different jobs. Geared Jacobs chuck. All you need in an electric drill in this 1 tool. With attachments—it is a whole work shop.

And

ALL PURPOSE POWER SAW

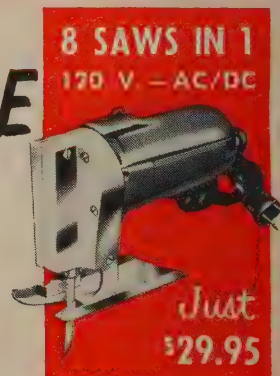Has no equal. Cuts anything smoothly, swiftly—2 x 4's in seconds, 1/2" steel, plastics, conduits. Cuts circles, scrolls, dovetails, straight lines or angles. Makes own starting holes. Blows off sawdust. 3 blades—coarse, medium, fine.



LIST

Also ask about other WEN "Quick-Hot" Soldering Guns & Kits from \$7.95 to \$12.95. Also fine finish and heavy duty Sander-Polishers and Kits from \$13.95 to \$19.95. They'd help in your work.



PRODUCTS, INC. 5808 NORTHWEST HIGHWAY, CHICAGO 31, ILL.
(Export sales, Scheel International, Inc., Chicago)

ALL WEN PRODUCTS ARE SUPERBLY MADE — U. I. APPROVED — FULLY GUARANTEED.

how long would it take you to solve this service problem?

PHOTOFACT

helps you lick problems

like this in just minutes

for only ***2½¢** per model!

SYMPTOM:

Horizontal Foldover affecting the right side of the screen, accompanied by an overall reduction in width




Let's look at this problem: When the fold-over occurs at the right side of the picture, the trouble usually originates in the horizontal discharge or output circuits. Look for the following possible causes:

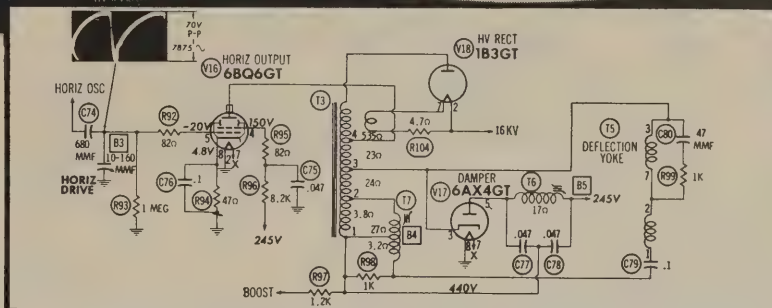1. Defective tube in the flyback circuit
2. Leaky coupling capacitor (C74)
3. Misadjusted or defective drive control
4. Open or leaky capacitor (C76) in the cathode of the output stage
5. Incorrect value of the grid resistor (R93) in the horizontal output stage
6. Open or leaky screen bypass capacitor (C75) in the output stage
7. Incorrect value of the cathode resistor (R94) in horizontal output stage
8. Incorrect value of the screen resistor (R96) in horizontal output stage
9. Defective yoke or flyback transformer

With the applicable PHOTOFACT Folder at your fingertips, you'll trouble-shoot and solve this problem in just seconds. Here's-how:

Using the Tube Placement Chart (you'll find it in every PHOTOFACT TV Folder) you'll quickly locate and check the tubes in the Flyback Circuit. Tubes okay?—then: A waveform analysis of the signal in the sweep section is perhaps



(Based on an actual case history taken from the Howard W. Sams book "TV Servicing Guide")

the quickest procedure you can use to localize the trouble. Check the waveform at the junction of the two capacitors, B3 and C74. The correct waveform and peak-to-peak voltages are shown right on the PHOTOFACT Standard Notation Schematic. Waveform incorrect?—Then, using the easy-to-read resistance chart and the correct voltages shown on the schematic, check for proper resistance and voltage values to determine which part is defective. The exclusive PHOTOFACT chassis photos with "call-outs" keyed to the schematic help you locate the faulty part quickly. Important! Horizontal Foldover may result from improperly matched components in this circuit. It is imperative that all parts replaced duplicate the originals. You'll find the proper replacement parts for all components listed in the complete PHOTOFACT parts list.

Remember, whatever the trouble may be, you'll locate it faster and solve it easier and more profitably with a PHOTOFACT Folder by your side.

Use the servicing method you prefer—checking of waveform, voltage or resistance—you'll find all the information you need at your finger-tips in PHOTOFACT.

For only *2½¢ per model, PHOTOFACT helps you solve your service problems in just minutes—helps you service more sets and earn more daily!

*Based on the average number of models covered in a single set of PHOTOFACT Folders.

MONEY BACK GUARANTEE!

Got a tough repair? Try this—at Howard W. Sams' own risk: see your Parts Distributor and buy the proper PHOTOFACT Folder Set covering the receiver. Then use it on the actual repair. If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly. GET THE PROOF FOR YOURSELF—TRY PHOTOFACT NOW!

FREE



FOR SERVICE TECHNICIANS ONLY

Fill out and mail coupon today for Free subscription to the Sams Photofact Index—your up-to-date guide to virtually any receiver model ever to come into your shop. Send coupon now.

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc.
2205 E. 46th St., Indianapolis 5, Ind.

☐ Put me on your mailing list to receive the Sams Photofact Index and Supplements. My (letterhead) (business card) is attached.

☐ I'm a Service Technician: ☐ full time; ☐ part time

My Distributor is: _____


Shop Name _____

Attn: _____

Address: _____

City _____ Zone _____ State _____

RAYTHEON

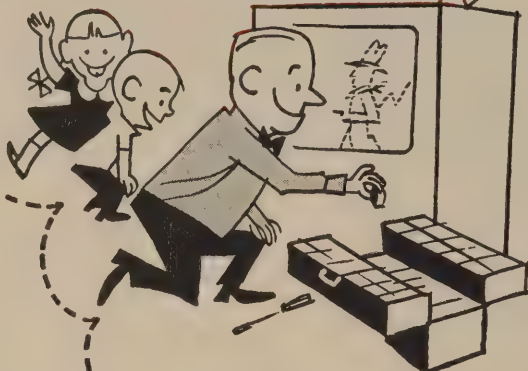

RAYTHEON

"ALL-SET" TUBES

designed with Independent
Service Dealers in mind

When Raytheon engineers design tubes, they are not restricted to engineering the tubes to the limited specifications of a specific TV or radio receiver. On the contrary, Raytheon engineers must design tubes that combine top quality with all-around performance in all makes and models of receivers. Proof of their success lies in the fact that Raytheon tubes are sold to virtually all TV and radio set manufacturers on a competitive technical basis.

This ability to perform in many circuits makes Raytheon "All-Set" Tubes ideal for service dealer replacement work. Fill your Tube Carrying Cases and tube shelves with Raytheon "All-Set" TV and Radio Tubes and you'll be able to meet tube replacement needs of all sets.

TV-Radio service is your business . . . serving you is ours



RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



COMMUNICATIONS ELECTRONICS



F.C.C. License—the Key to Better Jobs

An F.C.C. commercial (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire licensed technicians.

Learn by Mail or in Resident Classes

Grantham School and Electronics specializes in preparing students to pass F.C.C. examinations. Correspondence training is conducted from Washington and Hollywood; resident DAY and EVENING classes are held in both cities. Either way, we train you quickly and well—NO previous training required. A beginner may qualify for his first class F.C.C. license in as little as 12 weeks.

Here's Proof... that Grantham Students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Wks.
Leo Bishop, 37 Calle Contenta, Flagstaff, Ariz.	1st	12
Carl Deare, Jr., P.O. Box 467, Jeanerette, La.	1st	11
Robert Umthun, 1918 Eye St., NW, Washington, D.C.	1st	21
Tommy Lesley, 422 Wood St., Maysville, Ky.	1st	9
Dan Breece, Station KOVE, Lander, Wyo.	1st	12
Robert Todd, Station WWBG, Bowling Green, Ohio	1st	13
Jackson York, 1029 N. Quincy St., Arlington, Va.	1st	15
Paul Chuckray, 6874 Weber Rd., Afton, Mo.	1st	11

OUR GUARANTEE: If you should fail the F.C.C. exam after finishing our course, we guarantee to give you additional training at NO ADDITIONAL COST. Read details in our free booklet.

Two Complete Schools

To better serve our many students throughout the entire country, Grantham School of Electronics maintains two complete schools—one in Hollywood, California and one in Washington, D.C. Both schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.


821 - 19th Street, N. W. Washington 6, D. C.
Phone: ST 3-3614

Washington Division

GRANTHAM SCHOOL OF ELECTRONICS

Hollywood Division

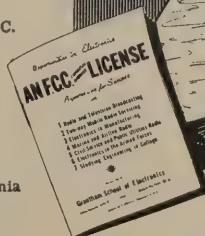1505 N. Western Avenue Hollywood 27, California
Phone: HO 2-1411



Get This
Booklet... **FREE!**

MAIL COUPON TO NEAREST OFFICE !!!

(mail in envelope or paste on postal card)

Grantham Schools Desk 74-T

1505 N. Western Ave. OR 821-19th Street, N. W.
Hollywood 27, Calif. OR Washington 6, D. C.

Please send me your booklet, telling how I can get my commercial FCC license quickly. I understand there is no obligation, and no salesman will call.


Name.....Age.....

Address.....


City.....State.....

I am interested in: ☐ home study ☐ residence classes.

Thermo-compression bonding—

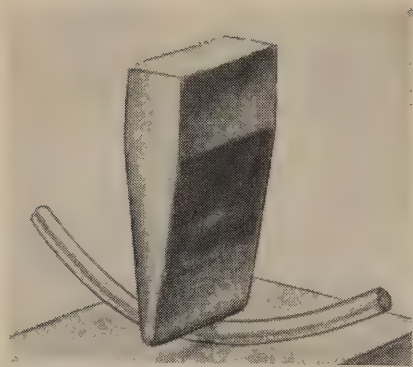

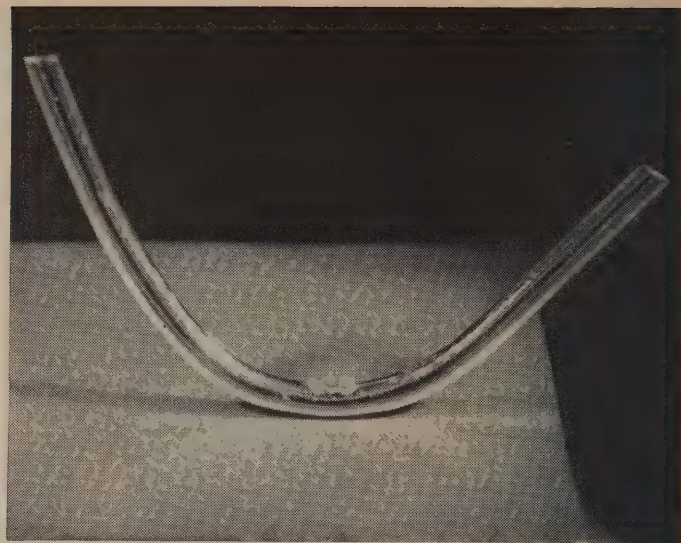One method of thermo-compression bonding. A heated wedge presses a wire against a heated semiconductor with enough force to deform the wire. Adhesion occurs in seconds.



Wire bonded to germanium by thermo-compression technique (enlarged). Wires only 1/10 the breadth of a human hair have been successfully anchored to germanium wafers only three hairs thick. The bond may be an ohmic contact or rectifying contact by adding suitable impurities to the wire and the semiconductor.

new way to join metal to semiconductors


Thermo-compression bonding provides a new way to attach a wire to a semiconductor. It calls for heat and pressure—nothing else. The wire and the semiconductor are moderately heated, then pressed together under moderate pressure. The resulting bond is very strong—stronger actually than the wire. No chemical flux or molten metal is required.

Eliminating molten metal provides an enormous advantage in fixing electrical connections to transistors. That's because molten metal tends to spatter and spread uncontrollably over the surface of

a semiconductor. And it may alloy with the semiconductor to alter its all-important crystalline structure and chemical purity. Thermo-compression bonding easily and quickly makes a strong permanent electrical connection without damaging the semiconductor. Furthermore, the lead may be attached to microscopic areas and precisely positioned, a most valuable aid in the construction of high-frequency transistors.

Thermo-compression bonding will speed the production of transistors . . . the transistors needed to fill all the new jobs Bell Lab-

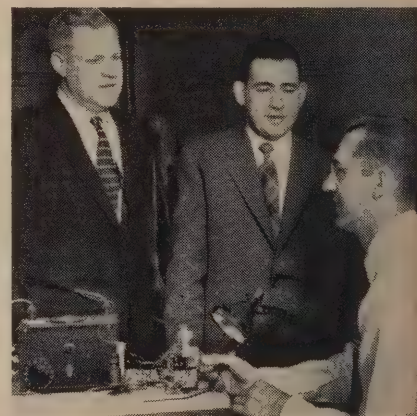oratories finds for them in the quest to provide still better telephone service to our growing country.



At Bell Labs Howard Christensen and Orson Anderson discuss their discovery of new bonding principle with Peter Andreach, Jr., who collaborated in the studies.

BELL TELEPHONE LABORATORIES


WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT



NEW! 12-WATT Williamson-type HIGH FIDELITY INTEGRATED AMPLIFIER HF12
with Preamplifier,
Equalizer &
Control Section
KIT \$34⁹⁵ WIRED \$57⁹⁵


Compact, beautifully packaged & styled. Provides complete "front-end" facilities and true high fidelity performance. Direct tape head & magnetic phono inputs with NARTB (tape) & RIAA (phono) feedback equalizations. 6-tube circuit, dual triode for variable turnover bass & treble feedback-type tone controls. **Output Power:** 12 w cont., 25 w pk. **IM Dist.** (60 & 6000 cps @ 4:1): 1.5% @ 12 w; 0.55% @ 6 w; 0.3% @ 4 w. **Freq. Resp.:** 1 w: ± 0.5 db 12 cps - 50 kc; 12 w: ± 0.5 db 25 cps - 20 kc. **Harmonic Dist:** 20 cps: 2% @ 4.2 w; $\frac{1}{2}$ % @ 2.5 w; 30 cps: 2% @ 11 w; $\frac{1}{2}$ % @ 6.3 w; 40 cps: 1% @ 12 w; $\frac{1}{2}$ % @ 9.3 w; 2000 cps: $\frac{1}{2}$ % @ 12 w; 10 kc: 1% @ 10 w; $\frac{1}{2}$ % @ 6 w. **Transient Resp:** excellent square wave reproduction (4 usec rise-time); negligible ringing, rapid settling on 10 kc square wave. **Inverse Feedback:** 20 db. **Stability Margin:** 12 db. **Damping Factor:** above 8, 20 cps - 15 kc. **Speaker Connections:** 4, 8, 16 ohms. **Tone Control Range:** @ 10 kc, ± 13 db; @ 50 cps, ± 16 db. **Tubes:** 2-ECC83/12AX7, 1-ECC82/12AU7, 2-EL84, 1-EZ81. **Size:** 5 $\frac{3}{4}$ " x 12" x 8 $\frac{1}{4}$ ". 13 lbs. Mounts in or out of cabinet.

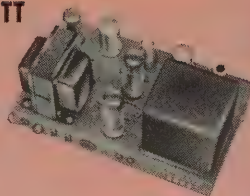NEW! 50-WATT Ultra-Linear HIGH FIDELITY POWER AMPLIFIER



HF50 KIT \$57⁹⁵ WIRED \$87⁹⁵

Like the HF60 shown below, the HF50 features virtually absolute stability, flawless transient response under either resistive or reactive (speaker) load, and no bounce or flutter under pulsed conditions. Extremely high quality output transformer with extensively interleaved windings, 4, 8, & 16 ohm speaker connections, grain-oriented steel, & fully potted in seamless steel case. Otherwise identical to HF60. **Output Power:** 50 w cont., 100 w pk. **IM Distortion** (60 & 6000 cps @ 4:1): below 1% at 50 w; 0.5% @ 45 w. **Harmonic Dist.:** below 0.5% between 20 cps & 20 kc within 1 db of rated power. **Freq. Resp.** at 1 w: ± 0.5 db 6 cps - 60 kc; ± 0.1 db 15 cps - 30 kc at any level from 1 mw to rated power; no peaking or raggedness outside audio range. All other specs identical to HF60 below. Matching cover Model E-2, \$4.50.

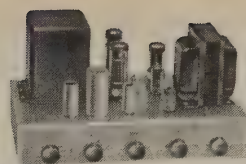

NEW! 50-WATT Ultra-Linear HIGH-FIDELITY INTEGRATED POWER AMPLIFIER HF52
with Preamplifier, Equalizer & Control
KIT \$69⁹⁵ WIRED \$109⁹⁵ Section

Combines a power amplifier section essentially identical to the HF50 power amplifier with a preamp-equalizer control section similar to HF20 below. Provision for use with electronic crossover network & additional amplifier(s). See HF50 for response & distortion specs; HF60 for square wave response, rise-time, inverse feedback, stability margin, damping factor, speaker connections; HF20 for preamplifier, equalizer & control section description. **Hum & noise** 60 db below rated output on magnetic phono input (8 mv input for rated output), & 75 db below rated output on high level inputs (0.6 v input for rated output). Matching cover Model E-1, \$4.50.

7 NEW BEST BUYS by



NEW




HIGH FIDELITY PREAMPLIFIER
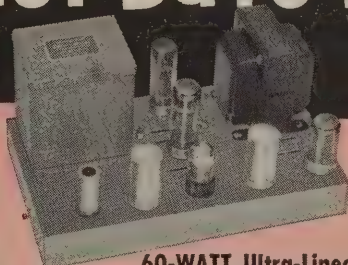
#HF61A KIT \$24⁹⁵, WIRED \$37⁹⁵

With Power Supply: **#HF61 KIT \$29⁹⁵, WIRED \$44⁹⁵**

Will not add distortion or detract from the wide-band or transient response of the finest power amplifiers at any control settings. High quality feedback circuitry throughout plus the most complete control & switching facilities. Heavy-gauge solid brushed brass panel, concentric controls, one-piece brown enamel steel cabinet for lasting attractive appearance. **Feedback-type, sharp cut-off (12 db/octave) scratch & rumble filters.** **Low-distortion feedback equalization:** 5 most common recording curves for LPs & 78s including RIAA. **Low-distortion feedback tone controls:** provide large boost or cut in bass or treble with mid-freqs & volume unaffected. **Centralab printed-circuit Senior "Compentrol" loudness control** with concentric level control, 4 hi-level switched inputs (tuner, tv, tape, aux.) & 3 low-level inputs (separate front panel low-level input selector permits concurrent use of changer & turntable). **Proper pick-up loading & attenuation** provided for all quality cartridges. **Hum bal. control.** **DC superimposed on filament supply.** 4 convenience outlets. **Extremely flat wideband freq. resp.** ± 1 db 8-100,000 cps; ± 0.3 db 12-50,000 cps. **Extremely sensitive.** Negligible hum, noise, harmonic or IM distortion. **Size:** 4-7/8" x 12-5/16" x 4-7/8". 8 lbs.




60-WATT Ultra-Linear

HIGH FIDELITY POWER AMPLIFIER #HF60
with ACRO TO-330 OUTPUT TRANSFORMER
KIT \$72⁹⁵ WIRED \$99⁹⁵

Superlative performance, obtained through finest components & circuitry. EF86 low-noise voltage amplifier direct-coupled to 6SN7GTB cathode coupled phase inverter driving a pair of Ultra-Linear connected push-pull EL34 output tubes operated with fixed bias. **Rated power output:** 60 w (130 w peak). **IM Distortion** (60 & 6000 cps at 4:1): less than 1% at 60 w; less than 0.5% at 50 w. **Harmonic Distortion:** less than 0.5% at any freq. between 20 cps & 20 kc within 1 db of 60 w. **Sinusoidal Freq. Resp.** at 1 w: 35 kc at any level from 1 mw to rated power; no peaking or raggedness outside audio range. **Square Wave Resp.:** excellent from 20 cps to 25 kc, 3 usec rise-time. **Sensitivity:** 0.55 v for 60 w. **Damping Factor:** 17. **Inverse Feedback:** 21 db. **Stability Margin:** 16 db. **Hum:** 90 db below rated output. **ACRO TO-330 Output Transformer** (fully potted). **Speaker Taps:** 4, 8, 16 ohms. **CZ34 extra-rugged rectifier** (indirectly-heated cathode eliminates high starting voltage on electrolytics & delays B+ until amplifier tubes warm up). **Input level control.** **Panel mount fuse holder.** Both bias and DC balance adjustments. Std octal socket provided for pre-amplifier power take-off. **Size:** 7" x 14" x 8". 30 lbs. Matching cover Model E-2 \$4.50.

NEW

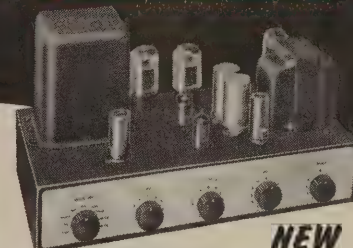

NEW

COMPLETE with Preamplifier, Equalizer & Control Section



20-WATT Ultra-Linear Williamson-Type HIGH FIDELITY AMPLIFIER #HF-20

KIT \$49⁹⁵ WIRED \$79⁹⁵

A low-cost, complete-facility amplifier of the highest quality that sets a new standard of performance at the price, kit or wired. **Rated Power Output:** 20 w (34 w peak). **IM Distortion** (60 & 6000 cps/4:1) at rated power: 1.3%. **Max. Harmonic Distortion** between 20 & 20,000 cps at 1 db under rated power: approx. 1%. **Mid-band Harmonic Distortion** at rated power: 0.3%. **Power Response** (20 w): ± 0.5 db 20-20,000 cps; ± 1.5 db 10-40,000 cps. **Freq. Resp.** (1/4 w): ± 0.5 db 13-35,000 cps; ± 1.5 db 7-50,000 cps. 5 feedback equalizations for LPs & 78s. **Low-distortion feedback tone controls:** large boosts or cuts in bass or treble with mid-freqs & volume unaffected. **Loudness control & separate level set control** on front panel. **Low Z output** to tape recorder. 4 hi-level switched inputs: tuner, tv, tape, aux; 2 low-level inputs for proper loading with all cartridges. **Hum bal. control.** **DC superimposed on filament supply.** **Extremely fine output transformer:** interleaved windings, tight coupling, careful balancing, grain-oriented steel. 8 $\frac{1}{2}$ " x 15" x 10". 24 lbs. Matching cover Model E-1, \$4.50.

NEW COMPLETE with FACTORY-BUILT CABINET— 2-WAY HI-FI SPEAKER SYSTEM #HFS1 \$39⁹⁵

Genuine 2-way book-shelf size speaker system. Jensen heavy duty 8" woofer (6.8 oz. magnet) & matching Jensen compression-driver exponential horn tweeter with level control. Smooth clean bass & crisp extended highs free of coloration or artificial brilliance. **Factory-built tuned bass reflex birch hardwood cabinet** (not a kit) constructed to high quality standards. **Neutral acoustical grille cloth** framed by a smooth-sanded solid birch molding. **Freq. Resp.** measured 2 ft. away on principal axis in anechoic chamber with 1 watt input - **Woofer:** ± 4 db 80-1800 cps; **Tweeter:** ± 2 db 2800-10,000 cps; **Crossover Region:** 1800-2800 cps, shift in level over this region depends on tweeter level control setting. **Power-handling capacity:** 25 watts. **Size:** 23"x11"x9". 25 lbs. **Wiring Time:** 15 min.

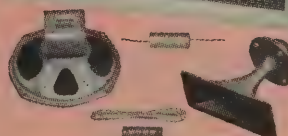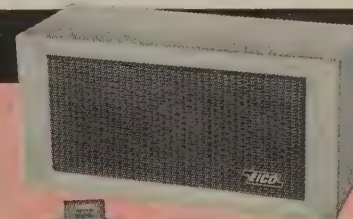

See the "BEST BUYS" NOW IN STOCK at your nearest distributor. Fill out coupon on other side for FREE CATALOG.

Prices 3% higher on West Coast.



33-00 Northern Blvd., L.I.C. 1, N.Y.

Turn page for other EICO ad.

the specs prove it...
your BEST BUY is

EICO®

for COLOR & Monochrome TV servicing

FREE CATALOG

shows you HOW TO SAVE 50%
on 50 models of top quality
professional test equipment.
MAIL COUPON NOW!




NEW!
**TV-FM SWEEP
GENERATOR &
MARKER #368**

KIT \$69⁹⁵
WIRED \$119⁹⁵


Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional tuning accuracy; edge-lit hairlines eliminate parallax. Sweep Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 80-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, scope horiz., scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

**NEW! RF
SIGNAL GENERATOR
#324**

KIT \$26⁹⁵
WIRED \$39⁹⁵

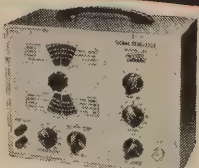

150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to $\pm 1.5\%$; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexiglass windows, edge-lit hairlines. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. amplifier: only 3.0 v needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

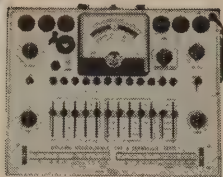


**NEW! DYNAMIC
CONDUCTANCE
TUBE & TRANSISTOR
TESTER #666**

KIT \$69⁹⁵
WIRED \$109⁹⁵

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy & thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. CRA Adapter \$4.50

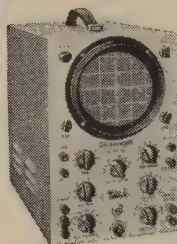


NEW!

**COLOR
and Monochrome
DC to 5 MC LAB & TV
5" OSCILLOSCOPE
#460**

KIT \$79⁹⁵
WIRED \$129⁹⁵

• **Features DC Amplifiers!**

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); preset TV V & H positions; auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equip. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.

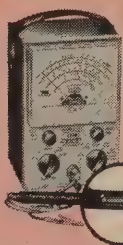


**NEW! PEAK-to-PEAK
VTVM #232 & UNI-
PROBE (pat. pend.)**

KIT \$29⁹⁵
WIRED \$49⁹⁵


Half-turn of probe tip selects DC or AC-Ohms.

Uni-Probe — exclusive with EICO — only 1 probe performs all functions!

Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/2" meter, can't burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms. Uniform 5 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.

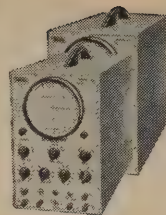


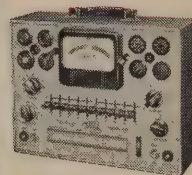**5" PUSH-PULL
OSCILLOSCOPE
#425**
KIT \$44.95
Wired \$79.95



**TUBE TESTER
#625**
KIT \$34.95
Wired \$49.95
• tests 600 mil series string type tubes
• illuminated roll-chart


Pix Tube Test Adapter\$4.50

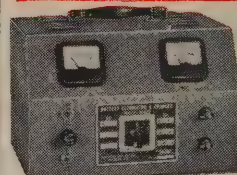

Sep. volt-meter & ammeter

KIT \$29.95
Wired \$38.95

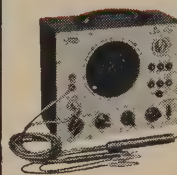6V & 12V BATTERY ELIMINATOR & CHARGER #1050



Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.

KIT \$24.95
Wired \$39.95

DELUXE MULTI-SIGNAL TRACER #147



**20,000 Ohms/Volt
MULTIMETER #565**
KIT 24.95
Wired \$29.95




**1000 Ohms/Volt
MULTIMETER
#536**
KIT \$12.90
Wired \$14.90



Reads 0.5 ohms — 500 megs, 10 mmfd — 5000 mfd, power factor.

KIT \$19.95
Wired \$29.95

R-C BRIDGE & R-C-L COMPARATOR #950B

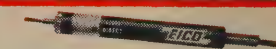

VTVM PROBES	KIT	Wired
Peak-to-Peak	\$4.95	\$6.95
RF	\$3.75	\$4.95
High Voltage Probe-1	\$8.95	
High Voltage Probe-2	\$4.95	

SCOPE PROBES	KIT	Wired
Demodulator	\$3.75	\$5.75
Direct	\$2.75	\$3.95
Low Capacity	\$3.75	\$5.75

TURN PAGE
FOR MORE
EICO VALUES

EICO®

Send for
FREE CATALOG
now

Prices 5% higher on West Coast.

33-00 Northern Blvd., Long Island City 1, N.Y.

EICO, 33-00 Northern Blvd., Long Island City 1, N.Y. C-12
Show me HOW TO SAVE 50% on Test Equipment and Hi-Fi. Send me FREE Catalog and name of neighborhood distributor.

Name.....
Address.....
City.....Zone.....State.....

THE U.S.A. AT BAY

... Teleducation Can Safeguard Your Future ...

THE greatest accomplishment of the Russians was not their famed earth satellite, great as that feat was, but a deadly aroused United States, now awakening to its shocking peril.

For make no mistake, the Russian *Sputnik* is only a moving finger in the sky, writing out plainly Nikita Krushchev's recent threat to us: "*We will bury you!*" That threat is not an idle boast in Russia, a country that glorifies its men of science, technicians and inventors, while in the U. S. many politicians and others delight in ridiculing them. In Soviet Russia, boys with a scientific or technical bent crowd the large number of technical schools to such extent that there is no room for all who wish to attend. Why? In Russia, a scientist is a near-hero. In the United States, there is—and has been—a serious shortage of technical pupils—on which our very future life depends. The result: the United States is now a very bad second runner in a world where science and technology are replacing the soldier, the regiments and the military divisions of former days.

What is the remedy in our perilous dilemma? It is far too late now for a crash program in technical education using our antique teaching methods. There are not enough good teachers to supply such a demand. And good teachers are not made overnight—it takes many years. What then is the answer? **MASS NATION-WIDE TELEDUCATION.**

In 1945, we were the first to broach the subject in a short article entitled "*Television Teaching.*" We said: "Outstanding educators . . . lecture via (closed circuit) televue from central *Teletoriums.* . . . Thus one teacher can lecture and instruct hundreds of classes."

Since that time we have published a number of articles on this subject.*

A condensed version of this far-reaching plan is summarized thus:

1. The United States government to set up a nation-wide closed circuit educational television network, tying together all schools and colleges. The Government to finance and build the network, but to have no voice in the teaching. Schools, however, would have to agree to a specified amount of *technical* teaching hours per week.

2. We have a sufficient number of *good* teachers right now to teach 50,000 or 5,000,000 pupils or students. These teachers now are wasted, literally.

3. *To be effective, science and technology must start with the 6-year-old child, in easy stages, to awaken his interest.* Television has shown that simple science things fascinate youngsters and, *if presented right, hold his interest.* The marvels of science and the wonders still to come would always have to be emphasized, with the result that a large

percentage of youngsters 10 years hence would be well on the way to fill our sadly lagging ranks of scientists and technologists.

4. So as not to confuse, we repeat that the proposed *Nation-Wide Teleducation Network* is to be strictly **CLOSED-CIRCUIT**—not broadcast. We have all the necessary technical means now to build it. On a crash basis, it could be working in a year or less.

5. Who will do the science teaching? This will be left to a National Science Instruction Board. For details, see "*The Elements of Teleducation,*" in our May, 1956, issue.

Since we first broached the idea of teleducation in 1945, teaching via television has become a rather well established method of teaching. Old-fashioned orthodox pedagogues, skeptic at first, have now become enthusiastic supporters of the idea. Many schools and colleges now have become *TV-integrated*, and wherever funds are available, more schools are coming into the fold.

One of the most recent successful experiments was inaugurated in September, 1956, in Hagerstown, Md., where

6,000 children, in 6 elementary and 2 high schools, are now being educated experimentally via a local *TV school closed-circuit network.* The pupils receive televised lessons in English, geometry, art, music, history and social studies. It has been termed by a very prominent educator, Dr. Alexander Stoddard, who for 10 years was chairman of the Educational Policies Commission of the National Education Association, as "*the most significant thing going on in America today.*"

The schoolrooms in Hagerstown today have an average of four 21- or 24-inch regulation TV receivers spotted around the class in strategic positions, so most of the students can get a good view of the proceedings.

We can foresee the day when a single large theater type wall-projection televisior will prevail instead of the box type receiver. The wall-projection type, when mass produced and consequently much cheaper than the comparatively few in use today, will give a better view for the entire class, particularly when the picture is in color, as it surely will be. Much later, it will also be a three-dimensional picture, rather than a flat one. This is most important for science teaching when during televised experiments instruments, apparatus and machines must be viewed from several angles by the student for better understanding.

In the meanwhile, it is understood that the many schools and colleges that are TV-equipped now can readily be integrated into a nation-wide closed-circuit network without difficulty.

Yes, as in all revolutionary new undertakings, there will be many squabbles by the various boards of education in cities and states as to methodology in teaching, procedure, curriculum and many other details. These we feel certain will and must be resolved speedily.

They are not serious *vis-à-vis* the life of our nation, which depends on a successful outcome of this plan.—H. G.

IF YOU are convinced of the feasibility of MASS NATION-WIDE TELEDUCATION and its urgency, in view of the serious danger your country now faces, write or wire your Senators and Congressman calling their attention to this article. They have received copies.

* *Time*, December, 1945; *Newsweek*, December, 1950; RADIO-ELECTRONICS, September, 1951. Also Tec-Teleducation, *Forecast*, December, 1954, RADIO-ELECTRONICS, February, 1955, and May, 1956.

Send for free reprints of all RADIO-ELECTRONICS articles on Teleducation.

The VTVM...its care and repair

By RHYS SAMUEL*

How to keep your vtvm at top efficiency

THE vtvm is such a reliable device that the technician gives it little thought until that inopportune moment when it breaks down.

A defective vtvm should offer no special problems because it is basically a simple instrument. It uses two or three tubes, conventional parts and straightforward circuitry. For the experienced tech especially, troubleshooting should be a snap.

The best way to minimize vtvm down time is to prevent trouble in the first place by following the simple precautions and periodically making the brief checks described in this article. Although many of these points may seem academic, they are often overlooked by techs who should know better. Hundreds of defective vtvm's are returned to manufacturers and instrument repair shops yearly because of user carelessness or neglect.

Preventive maintenance

Probes and cables are a frequent source of trouble because they are subject to constant handling. Internal connections break or become intermittent. Detachable probes are often dropped. Check the condition of ohms probes and cables by shorting them together and flexing the leads while watching the meter pointer. Erratic changes of the meter reading indicate loose or broken connections. Voltage leads should be checked in a similar manner while connected to a test-voltage source.

When a vtvm is used in the shop, mount it securely so that an accidental tug on the test leads will not pull it off the bench or shelf and break the meter movement. Keep detachable probes in an out-of-the-way place or clamp them in fuse type clips on the vtvm case.

To check the condition of the ohms battery:

1. Set the FUNCTION SELECTOR to ohms.
2. Set the RANGE CONTROL to $R \times 1$.
3. Rotate the OHMS ADJUST control to bring the pointer to full-scale deflection. If it is impossible to adjust the pointer to full scale, replace the battery.
4. If OK as checked for full-scale deflection, short the ohms cable to ground for about 10 seconds.
5. Open the short circuit and observe

*RCA Commercial Engineering Electron-Tube Division, Harrison, N. J. Author, *The VTVM—How It Works, How To Use It*, Gernsback Library, Inc. Some of the information in this article has been abstracted from the book.

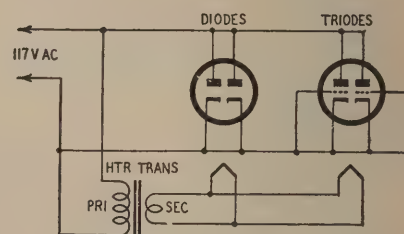


Fig. 1—Recommended test setup for aging tubes for vtvm's.

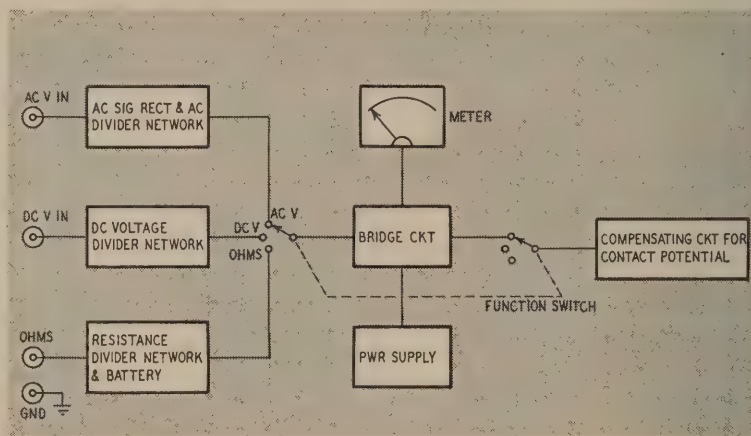


Fig. 2—Block diagram of typical vtvm.

the scale indication. Any appreciable deviation of the pointer from full-scale deflection indicates a weak battery.

If it is impossible at any time for the meter pointer to deflect to the full-scale point on ohms, it is advisable to replace the battery. *Never leave exhausted batteries in the instrument.* If any inspection reveals a battery that is leaking or corroded, replace it immediately and thoroughly clean out all chemical deposits inside the case and on the battery contacts. Before a new battery is installed in a holder with spring contacts, clean the contacts thoroughly and adjust the springs to insure a solid contact with low contact resistance. Be sure to observe correct polarity during battery installation.

Like the switches in TV tuners, vtvm switches should be checked and attended to periodically. Keep panel nuts tightened to prevent movement of the switch assembly, broken leads and shorted components. Take care during soldering to prevent overheating or scraping the resistors mounted on the switches. Excessive heat can permanently change the value of precision resistors and result in inaccurate meter readings. Avoid twisting or loosening the switch contacts.

Improper use of a vtvm is a major

cause of failure and expensive repairs. While its design makes it almost impossible to burn out the meter movement, excessive and repeated overloads can cause other types of damage. Excessive inputs, which result from improper settings of the FUNCTION and RANGE switches, may change the value of the precision resistors in the divider networks or burn out the low-value resistors. Many vtvm's returned to manufacturers have damaged resistors in the ohms-divider network because the operator attempted to measure voltage with the FUNCTION selector set to ohms.

Replacement parts

Whenever possible, exact replacement parts should be used. Most divider-network resistors have a $\pm 1\%$ tolerance, and many have special values obtainable only from the instrument manufacturer.

Individual replacement parts for meter movements generally are not stocked by the manufacturer. Defective meters are best returned to a repair shop which specializes in this work. Never attempt to check the continuity of a meter movement with an ohmmeter or general-purpose continuity checker. The battery voltage in the ohmmeter may be high enough to burn

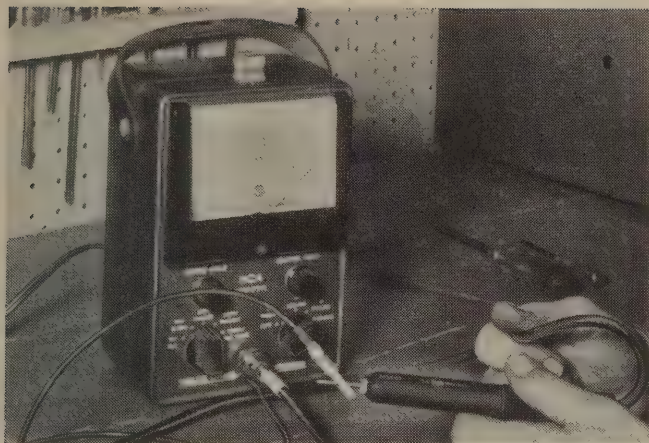


Photo at left shows condition of probe and cables being checked by setting vtvm to ohms, connecting cables together and flexing. Action of meter pointer indicates possible defects. At right, replacing an exhausted ohms battery.

out the meter movement under test.

Tube replacement

Most vtvm's use tubes specially aged or selected to insure a low amount of gas and contact-potential current. Although tube-replacement requirements differ among instrument models, it is usually desirable to age replacement tubes intended for installation in bridge circuits and ac signal rectifiers.

Unless a bridge-circuit tube has suitable operating characteristics and a low value of gas current, it may cause off-zero deflection of the meter pointer when the RANGE switch is changed from the lowest dc-voltage range to the higher ones. This condition requires that the operator re-zero the meter pointer whenever ranges are changed. Often a tube will prove unsuitable for installation, even after a lengthy aging period.

The acceptability of a tube for bridge-circuit use will depend upon the vtvm's design and the manufacturer's recommendations. Usually, a change of one or more divisions in the meter-zero setting as the RANGE switch is changed indicates that the tube requires more aging or is unacceptable for use in a vtvm. If several tubes are available, install them in the instrument one at a time, before aging, to determine which has the lowest value of gas. The tube which produces the least amount of off-zero deflection as the range is changed is the best tube to select for aging.

Single or twin diodes used in the ac signal-rectifying section may or may not require selection or aging, depending upon manufacturer's recommendations. The diode selected should provide a minimum amount of off-zero deflection of the meter pointer when the FUNCTION switch is changed from dc volts or ohms to ac volts, as well as the minimum amount of deflection when the RANGE switch is rotated. Many vtvm's have internal adjustments for differences between signal-rectifier tubes. Hence, tube selection and aging may not be critical.

A new tube may be aged by installing it in the vtvm and running the instrument for a number of hours or days. An alternate and sometimes quicker method of aging diodes or triodes is to use the simple setup shown in Fig. 1. The grids and cathodes of triodes are tied to one side of the ac line and the plates to the other side. Heaters are operated at a normal voltage supplied by a transformer. Diodes are aged in the same manner except that no grid connections are required.

The aging period is from 24 to 100 hours. Aging by this method usually requires less time than aging in the instrument. Whenever a new tube is installed, the vtvm should be checked for calibration and accuracy. Recalibration may be needed to insure accurate ac and dc voltage measurements.

Zero setting, accuracy

When the vtvm is switched off, the meter pointer should rest at the left-hand zero mark. If the pointer comes to rest above or below this mark, the mechanical zero requires adjustment. This adjustment is accessible from the front of the meter case and may be a small setscrew or lever. On some vtvm's the adjustment screw is accessible through a hole in the front of the meter case. The hole may be covered with a small cap or screw plug.

With the power off, remove the cap or plug and adjust the setscrew to bring the pointer into line. On vtvm's with a lever adjustment, insert a small scriber or similar tool into the hole and move the lever right or left, as required. Take extreme care to avoid inserting the scriber into the movement. Always replace the screw plug or cap to seal the movement against dust and moisture.

The inside of plastic meter faceplates of vtvm's is often coated with a special antistatic solution to eliminate effects of static charges on the meter pointer. If this coating is removed, the meter pointer action may be erratic.

On plastic meter cases, therefore, do not rub the inside of the faceplate.

If the antistatic coating is ineffective, apply additional antistatic solution to eliminate the trouble. A detergent soap, such as Gleem, is a substitute for the solution. Use a medium amount in water, fill the inside of the case and pour out. Shake off any remaining solution and allow the meter case to dry.

When you suspect that changed-value divider resistors are responsible for faulty readings, check the resistor values on a resistance bridge, if possible. Because many resistors used in commercial vtvm's are accurate to 1%, conventional ohmmeters cannot be used to measure their values accurately.

Factory-fresh flashlight cells are a fair substitute for a dc voltage standard. When new, one of these cells should provide 1.55 volts under the high-resistance load of a vtvm.

Analyzing the trouble


Like a television receiver, a vtvm has a number of individual sections and circuits which perform specific functions. In a vtvm, some circuits, such as the ac signal rectifier and the ohms-divider network, are inoperative (disconnected) for all other functions. Others, like the power supply, bridge circuit and meter movement, are used for all operations of the vtvm.

A block diagram of a typical vtvm is shown in Fig. 2.

The vtvm is built around a vacuum-tube bridge circuit and indicating meter. The function of the ac signal rectifier and the divider networks for ac and dc volts and ohms is to supply a fixed proportion of the input test voltage to the bridge circuit. During operation, a dc voltage is fed to the bridge from one of these three sections.

On resistance measurements, a resistance-divider network in series with an internal battery furnishes a value of dc voltage in proportion to the value of the unknown resistance placed across the ohms network through the ohms probe and ground cable. On dc voltage checks, the voltage being measured is applied across the dc voltage-divider network which, in turn, applies a pro-

TEST INSTRUMENTS

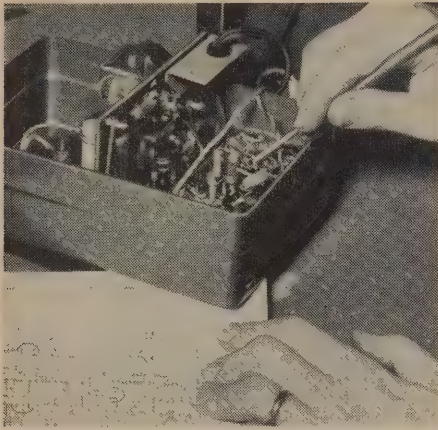

Intermittent troubles can often be found by probing parts and wiring with an insulated tool.

portionate part of the test voltage to the bridge circuit.

In ac voltage tests, the signal is rectified and the resultant dc voltage is applied to the bridge circuit. The input-divider networks for all three measurement functions are designed so that only a small part of the input voltage (1.5 to 3 volts) reaches the bridge circuit.

Voltage for ohms measurements is obtained from an internal battery; all other voltages are obtained from a built-in power supply. The compensating circuit for contact potential is used when the vtvm is switched to ac.

The first step to be taken in localizing trouble consists of inspecting the instrument's performance on all ranges and functions. Set the FUNCTION switch to the first position (—DC VOLTS, for example), and rotate the RANGE switch through each of its range settings. Turn the FUNCTION switch to its next position and again rotate the RANGE switch through all its positions. Repeat this procedure for all remaining settings of the FUNCTION and RANGE switches and note the vtvm's performance at each new step.

Check probes and cables in some routine application while these checks are made. When a complete check has been made, you should have a complete picture of over-all performance. If the vtvm is inoperative on all functions, look for trouble in sections or circuits common to all functions. If the defect occurs only on one or two functions or ranges, look for trouble in the corresponding sections of the instrument.

With some vtvm's, a single probe and cable are used for all voltage and resistance measurements. On other instruments, separate probes and cables are provided. Some common troubles and probable causes are given below.

General troubles

Instrument fails to operate on all functions; pilot light does not light.

Check the line cord and switch wafer section of the FUNCTION switch for defects. Fuse may be open (if used) or perhaps primary winding of power transformer has opened. Check con-

tinuity with another ohmmeter.

Instrument fails to operate on all functions; tubes light.

Lead may be broken in ground cable or at ground connection inside case. There may be faulty tube in the bridge circuit, open or short circuit in bridge circuit, or faulty tube or component in the power supply. There may be an open or short in probe or cable, if the vtvm uses multipurpose probe and cable. Meter movement may be defective.

Meter pointer sticks.

Jewel bearing in meter may be cracked or broken. Return meter to meter manufacturer or meter repair shop. Scale plate of meter may be loose and striking meter pointer. Remove meter from case and tighten faceplate screws.

Meter pointer bangs hard left or right, depending upon setting of FUNCTION switch.

There may be open or short circuit in bridge network. Check parts mounted on switch wafers. Take continuity readings with another ohmmeter. Bridge tube may be defective.

Intermittent operation on all functions.

Connection may be loose or broken in ground cable or in probe if multipurpose probe is used. Check as described under preventive maintenance. There may be a faulty wiper or contact in the switching section, or loose or broken connection in bridge-circuit wiring. With power applied, check wiring, connections and components with an insulated probe. There may be a defective tube or component in bridge circuit or power supply.

Ohms-function troubles

Instrument fails to operate on OHMS; works normally on ac and dc voltage measurements.

Battery may be dead or not making contact. There may be a loose or broken connection in ohms cable if separate cable is used. Contact on FUNCTION switch may be defective. There may be open circuit in resistance-divider network. (NOTE: In some vtvm's this network is made up of series-added resistors. An open circuit can affect operation on two or more ranges. On other vtvm's, separate resistors are switched in when the RANGE is changed. In these instruments, a defective resistor will cause inaccurate readings on only one range.)

OHMS ADJUST control fails to give infinity setting on resistance scale.

Ohms battery may be dead. OHMS ADJUST potentiometer may be defective. Bridge tube may be defective.

Ohms readings inaccurate on some or all resistance ranges.

(NOTE: Manufacturers usually do not publish accuracy figures for ohms measurements. Generally, the vtvm should provide readings within 10% of the actual value. If readings of greater precision are required, use a calibrated resistance bridge.) One or more resistors in the ohms-divider network may have changed value. Excessive leakage

in this network can also cause trouble. Check OHMS RANGE switch for dirt or damage. High humidity may cause leakage and inaccurate readings on high ohms scales. Bake inside of instrument with low-wattage light bulb. Check ground jack and cable for poor connection. Check for shorted wiring in ohms-divider network.

Meter pointer moves off infinity mark when RANGE SWITCH is changed.

Replace bridge tube with new tube having a low value of gas current. (NOTE: A small deviation should be considered acceptable.) There may be excessive leakage in ohms circuit. Check by baking for several hours with light bulb. Do not overheat and damage components.

Ac voltage measurement troubles

Instrument fails to operate on any ac voltage range; works normally on ohms and dc voltage measurements.

Ac signal-rectifier tube may be defective. Ac volts contacts on FUNCTION switch may be defective. There may be open or short circuit in ac signal-rectifier circuitry. Check wiring and components with another ohmmeter.

Meter pointer moves off zero when ranges are changed.

Ac zero potentiometer may be out of adjustment. Adjust according to manufacturer's instructions. If this adjustment fails to correct trouble, replace the ac signal rectifier or bridge tube or both. Check resistance values in network around contact-potential bucking tube, if one is used.

Ac voltage inaccurate on some or all ac ranges; performance on ohms and dc voltage ranges normal.

Resistor network around ac voltage divider may be defective. There may be defective contacts or excessive leakage in switches. Ac signal-rectifier tube may be defective. Check for leaky capacitors or changed-value resistors in ac signal-rectifier circuits or in ac voltage-divider network.

Dc voltage measurement troubles

Instrument fails to operate on any range of +volts or -volts; works normally on ohms and ac volts.

Dc (isolating) probe may be defective. Check isolating resistor. Check all switch contacts used on dc voltage function.

Instrument fails to operate on any range of +volts but normal on -volts, or vice versa; works normally on ohms and ac volts.

Check calibrating potentiometer in series with meter movement. Check for defective switch contacts or wipers in polarity-reversing circuit.

Voltage readings inaccurate on +volts, -volts, or both; ac voltage and resistance readings correct.

Dc calibrating potentiometers may be out of adjustment. Isolating resistor in dc probe may have changed value. Check cable and connectors. Check out resistors in the dc voltage divider network for changed values.

END

the manufacturer for \$4. Orders are usually shipped within 24 hours of receipt.)

The grid resistor in the oscillator may be any value between 22,000 and 220,000 ohms. I'll start with around 56,000 ohms and experiment to find the optimum value. If the oscillator provides too much signal, I'll lower it by inserting a dropping resistor between the B-plus line and the bottom of L4. The oscillator coil (L5) may be a CTC (Cambridge Thermionic Corp.) type LS-3 30-mc type or any coil and capacitor combination that will tune to 32 mc.

The antenna coil L1 and mixer coil L2 may be approximately 15 turns of No. 20 wire, $\frac{3}{4}$ inch in diameter and 1 inch long. This may be cut from B & W type 3011 Miniductors. The tap on L1 is made at the fourth turn from the ground end. The mixer plate coil L3 may consist of a 1-inch-long close-wound coil of No. 28 enameled wire on the upper part of a National XR-91 form. L4 is a 10-turn coil of No. 28 wire over the cold end of L3.

Other frequencies between 20 and 40 mc can be used for the oscillator. The point where either channel comes in on the receiver will be the difference between the oscillator and signal frequencies.

Circuit alignment is comparatively simple. Pretune L1, L2, L3 and L5 with a grid-dip meter. Then, use a signal generator to align the if amplifier, mixer and rf circuits in that order. If you don't have a signal generator, you may be able to align the circuits on WWV transmissions on 20 mc. Vary the values of resistance across the if transformer for relatively even response between 8 and 12 mc. Rig up a simple noise generator and use it to set the taps on L1 and L2 for minimum noise.

In bringing you details of this converter we could not wait until the crystal arrived, and therefore had no opportunity to try it, before press deadline. So minor modifications may be needed when the converter is put on the air. For example, you may have to keep all leads as short as practical and use good vhf wiring and layout techniques.

Gonna try 108 mc?

The selection of a 32-mc crystal is a good idea if you plan a 108-mc converter for monitoring our satellite. You will probably be able to use the same oscillator circuit and components as in the 20-40-mc converter. The third-harmonic (96-mc) output of the 32-mc oscillator will probably be strong enough for good conversion to 12 mc.

If the 96-mc signal is too weak, try a small coupling capacitor between mixer grid and oscillator plate. If this fails, insert a 35-40-mc tuned circuit in the oscillator's cathode return and connect the crystal directly between the grid and cathode. Tune the plate circuit to 96 mc.

END



all good wishes for a

**MERRY
CHRISTMAS**
and

HAPPY NEW YEAR

from everyone at
Radio-Electronics

TRANSISTOR & HYBRID AUTO RADIOS

By JACK DARR

Part II—Printed-circuit boards, and some special circuitry found in auto radios today

LAST month we had a rundown of the new look in auto radios. These transistorized (in places) receivers have some interesting special features we will now examine.


As in many other types of electronic equipment, printed circuits have appeared in auto radios. Motorola uses Pla-Cir plated-wiring boards in several of the new sets, as does Philco. Delco is also using printed-wiring boards in quite a few sets. In the signal-seeking tuners, switch panels and station-selector tab boards are small plated circuits. Quite a bit of printed wiring is used in the Chevrolet, especially in the rf, oscillator and if stages (see Fig. 6).

Motorola's Res-Caps are actually small printed-circuit combinations of resistors and capacitors, similar to the Couplates and vertical integrators familiar to the TV technician. They are used, in various combinations of capacitance and resistance, in many parts of the sets. If one of the parts fails, it may be replaced individually, or the whole unit may be replaced.

Special circuits

A novel circuit is found in the Motorola 79MS, the set designed for Ford Thunderbirds. Fundamentally, the purpose of the circuit is to increase the

Fig. 6—Printed-circuitry used in the Chevrolet 987575.

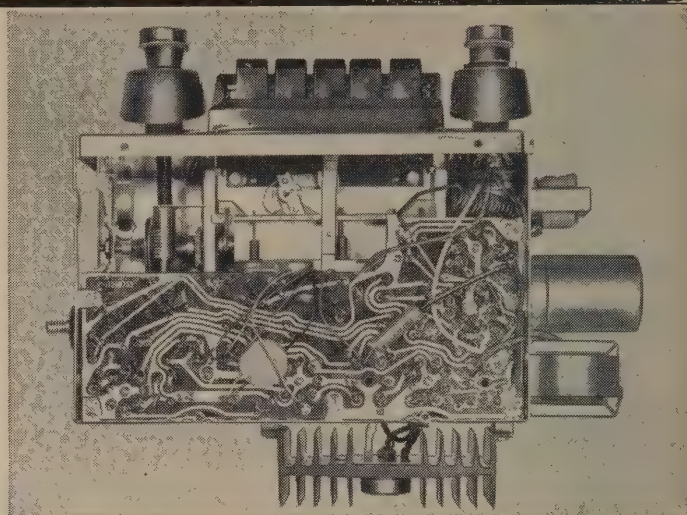

radio's volume as the speed of the engine increases. With an increase in speed, wind and road noises get louder and the volume of the radio is automatically increased to compensate for this.

Specifically, volume is increased as the car's engine is speeded up. This is done by the circuit shown in Fig. 7. A special cable connected to the high side of the breaker points feeds noise pulses from the distributor to a 12AL5 dual-diode, through a .005- μ f blocking capacitor C1. Negative pulses are shunted to ground by diode 1, as is any charge that may be built up in the blocking capacitor. Positive pulses are rectified and cause a voltage drop across cathode resistor R1. This positive voltage is coupled to the grid of the 12CR6 audio amplifier, through a filter consisting of R2, R3, R4 and C2. The amount of this voltage determines the gain of the pentode section of the 12CR6, directly controlling the receiver's volume.

The time constants of the circuit are such that the action will not be affected by normal rapid increases and decreases in engine rpm, which might occur when shifting gears, but will follow a gradual increase in speed. As the pulses become more frequent, the charge on C2 builds up and the added positive voltage on the grid causes an increase in the stage's gain. As the engine gradually slows down, the voltage across C2 discharges, allowing the volume to drop. These variations, of course, take place around the operating point of the tube, as selected by the position of the manual volume control R5.

Motorola also is continuing the use of their Volumatic age control circuit in their present line of auto radios.

Replacing the conventional avc circuit, which is actually an age circuit as it has no effect on the audio section of the set, this circuit not only controls rf gain but directly controls the audio volume as well. The circuit uses a 6CR6 or 12CR6 diode-pentode tube and is shown in Fig. 8. Grid resistor R1 returns to the age bus instead of ground. This provides a variable bias that is in direct proportion to the amplitude of the signal picked up by the set. The bias controls the gain of the pentode section of the tube, the audio stage. Conventional age is also used, in a standard circuit, from the diode section. This added degree of control has proved successful in eliminating fading from changes in signal levels, due to movement of the car, that is so prevalent in auto radios. It also aids in the operation of automatic tuning devices. The output level variations between the various stations are smoothed out to the point where it is not necessary to adjust the manual volume control

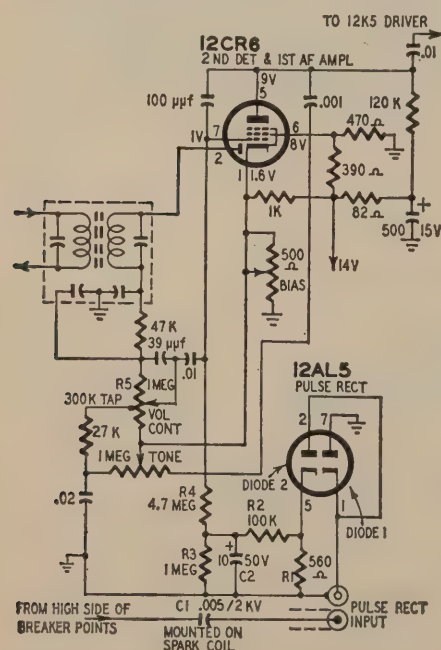


Fig. 7—Circuit increases radio's volume as car speeds up.

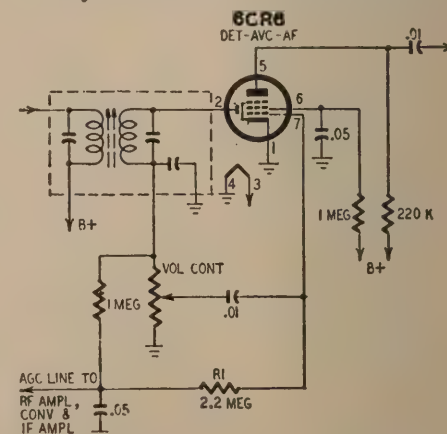


Fig. 8—Volumatic circuit controls rf gain and audio volume.

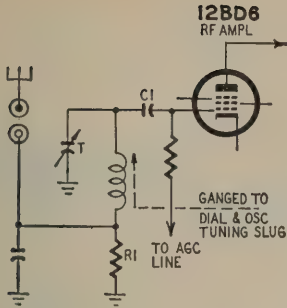


Fig. 9—Differentiating filter, called an *Eliminoise* circuit, is found in new Motorola auto radios.

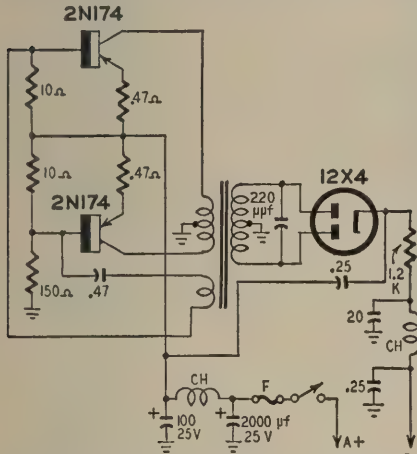


Fig. 10—Transistorized power supply replaces familiar vibrator.

while using the automatic tuner, search tuner or other forms of automatic tuning.

A differentiating filter, of the high-pass variety, is used in the antenna input circuit to help eliminate high-line noise and other electrical interference (see Fig. 9). R1 and C1 values are chosen to eliminate reception of the low or prevalent noise frequencies. This reduces the amplitude of 60-cycle pickup from power lines and helps reduce the ill effects of standing waves on the antenna, resulting in a much cleaner signal.

The transistor power supply

The versatile transistor, not only replaces tubes, but has even been used to replace the vibrator itself. This is found in the Chevrolet Corvette radio, Delco model 3725156. Conventional tubes are used in all but the output stage where a pair of 2N173 transistors supply audio output. Power requirements are about 200 volts. This is supplied by transistors.

A pair of 2N174 p-n-p power transistors are hooked up in an oscillator circuit (see Fig. 10). This is a relaxation or blocking oscillator, very familiar to all TV technicians. A frequency of around 20,000 cycles is used, to eliminate hum and buzz and simplify filtering problems. The frequency of oscillation is determined mainly by the inductance of the power transformer primary. This is a special unit with a primary, high-voltage secondary and a tertiary feedback winding.

As the first transistor conducts,

Fig. 11—Heavy aluminum fins keep power transistor cool during operation.



through the center-tapped primary, the other is cut off. When the first transistor reaches saturation, the field collapses, inducing a voltage in the opposite direction in the tertiary winding. This voltage drives the second transistor into conduction, then into saturation, and the first transistor into cutoff. Since the second transistor conducts in the opposite direction, a square wave is produced. Through the stepup action of the secondary winding, the voltage is raised to 200–250 ac. This is rectified by the 12X4, filtered and applied to the set. Filter components are not nearly as large as in the older sets. The input filter is a 20-μf unit, while the output filter is only 0.25 μf!

The ac voltage may be measured across the secondary; if it is not present the transistor may not be oscillating. This could be caused by a defective transistor, power transformer or by excessive loading of the B-plus line to the receiver. Tests for oscillation may easily be made with a scope or by pulling the 12X4 from the socket, removing the load and measuring the ac voltage.

The heat sink

Another new feature will be the heat sink necessary for proper operation of the power transistors. The technician will be able to spot transistor sets by the appearance of a set of fins on the end of the set, on either side of the small round object which is the power transistor. Power type transistors, such as the 2N173, 2N278, Philco's AR-5 and AR-6, etc., are all basically alike in structure, although their individual characteristics differ somewhat. All require some means of radiating the heat generated during normal operation (see Fig. 11).

Transistors of this type draw up to 900 ma during operation and generate quite a bit of heat. The transistor must not be allowed to get too hot, otherwise a condition known as thermal runaway may occur and the transistor will be ruined. Therefore, the transistors are mounted solidly to the end of the chassis, on a special plate which is insulated from the chassis on many sets. In others, the transistors themselves are insulated with thin mica spacers which allow heat transfer to the chassis but prevent grounding the collector which is connected to the case in most of the common power types. Some use a central stud and two flexible leads or lugs; the stud is the collector connection while base and emitter are connected to the leads. Others use three flexible

leads, mounting the transistor by means of small bolts through the ears of the case.

When testing power transistors in actual operation, they must be firmly clamped to their heat sinks. Otherwise, they may get too hot and become defective. Insulation must be perfect to prevent grounding of the collector to the chassis. Almost all circuits up to this time use the common-emitter configuration, which uses the collector as the output element. While the collector returns to ground through the primary of the output transformer, grounding it would cause trouble.

Control of the normal thermal increase in collector current is accomplished in the design of the circuit. Delco uses a small resistor (0.47 ohm) in the emitter circuit. If the transistor overheats, this resistor increases the bias voltage, opposing the current increase. Thermistors are also used in the larger sets with push-pull output (see Fig. 12) for the same purpose. In addition to the 0.3-ohm emitter resistor, a thermistor is connected across the 4.7- and 39-ohm base voltage-divider resistors. It changes the base-emitter voltage to compensate for temperature increases which would otherwise cause much increased collector current and possible thermal runaway.

This completes a full look at the new line of transistor radios and their special features. I'm sure you'll feel as I do—there have been some changes made. Next, we are going to discuss servicing these sets. END


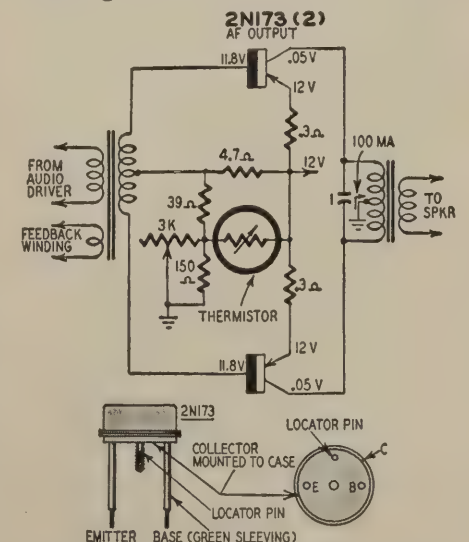


Fig. 12—Delco output stages use thermistor to protect transistors against overheating.

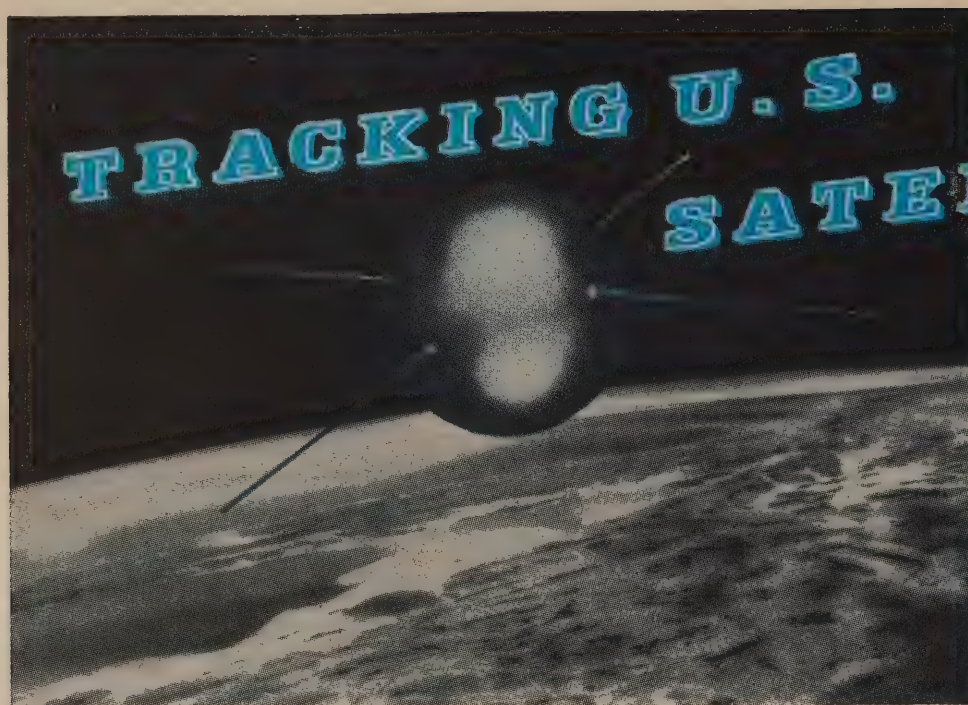

*Want to track our
space satellite?
Here's how to go about it*

By JORDAN McQUAY

DURING the winter and spring of 1957-58, the United States will launch a number of earth satellites into interplanetary space as part of our participation in the International Geophysical Year.

After launching via a multistage rocket, each satellite will circle the earth in an elliptical orbit at altitudes above 500 miles and at speeds of nearly 20,000 miles an hour. Purpose of the space voyage is to collect scientific data about the earth and the upper atmosphere.

In addition to special instruments, the metal sphere of each satellite contains a tiny radio transmitter weighing about 12 ounces. Various atmospheric data collected by the satellite are transmitted on a frequency of 108 mc, but with an extremely low power of less than 50 mw.

With appropriate ground-based receivers, this radio signal permits tracking of the satellite through most of its flight. Large and elaborate installations—known as Minitrack stations—have been installed by the Government to track and receive data from the satellites.

With a receiving system that's sufficiently sensitive, however, anyone can pick up the coded signals from a U.S. satellite. And with slightly more elaborate equipment, you can help directly in locating and tracking the satellites as they pass over or near your area of the country.

If you're a radio ham or dx fan with a yearning to contact stations in outer space, here's your chance!

A receiving system, based on the interferometer principle and similar to that used by the Minitrack stations, has been developed by the Naval Research

Laboratory in Washington for tracking U.S. satellites.

In its simplest form (Fig. 1), the system requires (1) a set of two identical Yagi antennas on a single base line from 20 to 500 feet long, (2) a coaxial T junction centrally located on the antenna base line, (3) a frequency converter to shift the incoming 108-mc signal to a lower frequency acceptable to a standard type of communications receiver, and (4) an S-meter or visual recording device connected to the output of the standard receiver. The two Yagi antennas should have the same shape and spacing of elements, and should be mounted parallel to each other. The antenna base line should be as long as possible—preferably running in a somewhat east-west direction. A number of economical, commercial frequency converters will probably be on the market soon. But a conventional overtone crystal oscillator with a buffer amplifier can be used to convert the satellite signal to a clear frequency acceptable to the range of your communications receiver. Amateur receivers and converters intended for the 144-mc band may also be modified for the lower frequency. The really ambitious constructor may wish to try the preamp-converter shown in Fig. 2. It was designed especially for the purpose of satellite tracking by the Naval Research Laboratory. The tubes are expensive—the GL-6299 lists at \$56—and the layout and construction requires considerable experience with vhf circuitry. (Construction details and design data on the equipment may be found in the article "A Low-Noise Preamplifier for Satellite Tracking" in the December, 1956, issue of *QST* magazine.)


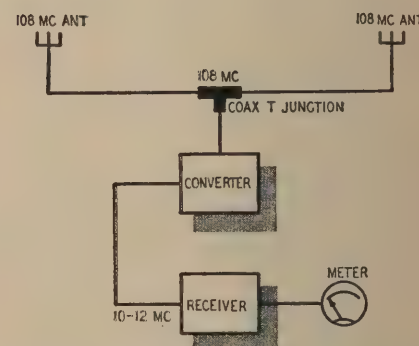


Fig. 1—Simple system for tracking satellite launched by United States.

Experimenters wishing to try a less expensive version of the circuit might substitute a 6Q4/EF80 in place of the expensive 6299. It is a low-noise tube whose characteristics are somewhat similar. The 5842/417A or a triode-connected E180F/6688 could also be tried, although they do not closely approximate the original tube.

Another approach would be to substitute the cascode rf amplifier described in the "Low-Noise TV Booster" (*RADIO-ELECTRONICS*, November, 1957) for the portion of the circuit between the antenna terminal and the input to the mixer. Coils would have to be adjusted for the spectrum, of course. Further savings might be realized by using a 12AT7 for the 12AT7-WA and a 6AQ5 for the buffer.

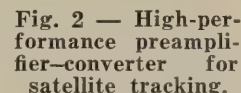
When a U.S. satellite is expected over or near your area, you'll know about it from your local newspaper or radio or TV station. Then, at an appropriate time, fire up your converter and receiver, and tune carefully for a weak pulsed signal at or near 108 mc. It may be difficult to detect at first. If you fail



12 tpi. Must resonate with capacitance of crystal holder
L21, 24—5.6- μ h rf choke, Jeffers 101
L22, 23—0.15- μ h, Jeffers 101 pruned for required value
L25—0.33- μ h, Jeffers 101 pruned for required value
*Jeffers Electronics Division of Speer Carbon Co.,
Dubois, Pa.

tracking systems will result in improved reception and more accurate recording of satellite signals, and can be made by introducing additional sets of antennas, use of large broadside arrays and more precise recording devices.

By designing and building your own system for receiving and recording radio signals from the U.S. satellites, you'll get personal satisfaction from contacting and tracking stations in interplanetary space and you'll be making a direct contribution to this important phase of the International Geophysical Year. END

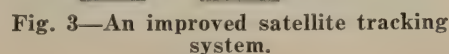Geophysical Year. END

AC DC POWER SUPPLY

By **GEORGE P. PEARCE**

IN hobby and experimental work there is frequently a need for a small ac or dc power supply—for example, in electroplating, generation of small quantities of oxygen and hydrogen, running miniature electric motors and models, charging storage batteries, rejuvenating dry cells, operating electromagnets, low-voltage lamps and innumerable experiments and tests where a low voltage is required.

To meet my own needs along this line and to avoid the annoyance of finding that my batteries are dead just when I want to use them, I set to work and built a compact electric power supply that provides trouble-free, reliable dc at 9 or 18 volts and ac at 3.15 or 6.3 volts with current up to 1 ampere.



The unit is built around a small filament transformer with 117-volt primary and a 6.3-volt secondary with center tap rated at 1.2 amperes. This transformer is a standard type and can be obtained from most radio supply houses. The outside terminals give 6.3 volts and either outside terminal to the center tap gives 3.15 volts ac. For dc I use a voltage-doubler circuit which gives me 9 and 18 volts.

The voltage doubler may be a pair of 1-ampere 26-volt (maximum ac input) half-wave selenium rectifiers or a 26-volt 500-ma full-wave bridge with the normal ac terminals strapped to provide two series-connected 1-amp half-wave rectifiers. Suitable 1-amp half-wave units are not readily available so you can use a full-wave bridge such as the Sarkes Tarzian A-2, Radio Receptor P1B1S1G and International JD507G.

Note that this voltage doubler actually produces 2.82 times the rms voltage on open circuit. The voltage drops as the current demand is increased. The amount of drop or the voltage regulation depends greatly on the size of the capacitors used. The larger the capacitors, the better the voltage regulation.

The circuit shown in the diagram was designed to use odds and ends I had in my junkbox except for the small steel cabinet which I bought for around \$1.75. The photos show the completed unit ready to deliver dc or ac power up to 1 ampere.

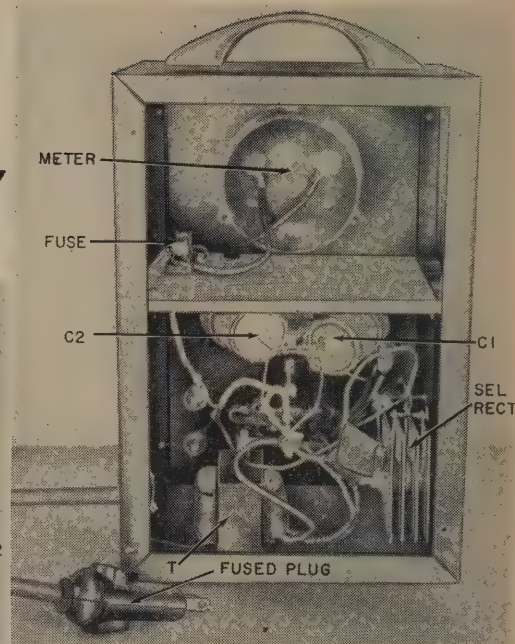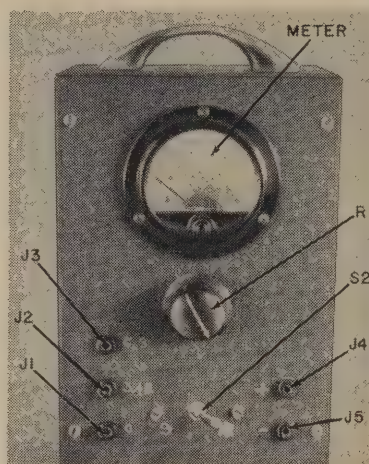Before attempting the design of the final assembly, I made a temporary hookup on a breadboard to test all components and be sure they were in proper working order. I then made the final design and arranged everything



Above—Inside view shows simple construction.

Left—Completed power supply in handy carrying case.

to fit into the 9 x 6 x 5-inch steel cabinet so they would be in good balance when carrying the unit.

In planning the design, these steps were taken to obtain the highest efficiency out of the materials on hand: The 1-ampere voltage-doubler rectifier was placed in an open space near the bottom of the cabinet where it would be surrounded with the coolest air available. The transformer was also located on the bottom and as far away from the rectifier as possible without getting the cabinet out of balance.


To get everything into the cabinet I had to make a double decker, but I was careful to cut vent slots in the shelf to permit free circulation of air. This has proven very effective and, since the entire steel cabinet acts as a radiating surface of approximately 250 square inches, there was no need to drill a grid of ventilating holes which let in dust and insects to cause trouble. It can be seen from the photos that nothing whatever is attached to the back panel, which is easily removed by taking out four screws. This provides quick access to the works for replacing a blown fuse or for repairs. The view also shows the inside arrange-

ment. The front panel can be removed by taking off one nut on the back of the meter and unclipping four wires.


The fuse is placed in a convenient spot in the assembly and a spare is clipped close by so I need not hunt for a new fuse in an emergency. Since the 1-ampere meter is the most expensive item in the assembly the fuse is placed next to it to protect the meter no matter where an overload or internal short may develop. You may prefer to use a 0-25-volt dc voltmeter. In this case, wire as indicated by the dotted lines in the diagram.

The 3.15-volt ac circuit is taken off one side of the transformer center tap. The other side goes to the dc rectifier so that both supplies can operate at the same time. It was not thought necessary to protect the ac output side of the supply, since there are two fuses in the power-cord plug, which protect the input side of the transformer.

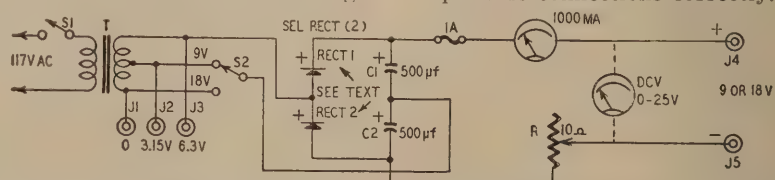The banana plug receptacles for the output are color-coded—red for positive and black for negative. The banana plugs have similar color-coded bodies as well as the alligator clips at the power delivery end which make it easy to polarize connections correctly. END



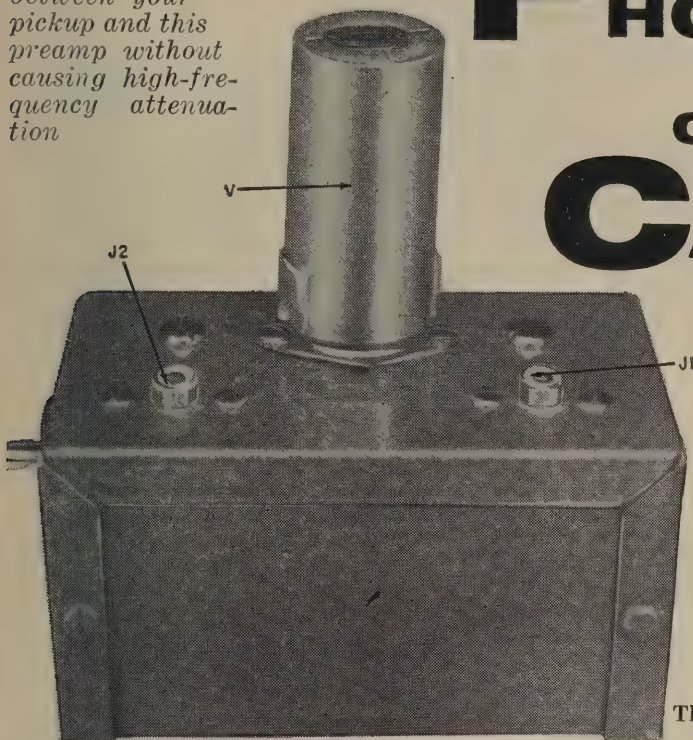Up to 400 feet of cable can be run between your pickup and this preamp without causing high-frequency attenuation




PHONO-PREAMP

COMPENSATES FOR CABLE CAPACITANCE

By G. FRANKLIN MONTGOMERY

The completed preamp.

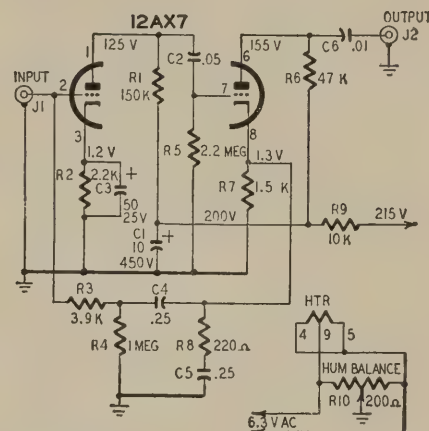

R1—150,000 ohms
R2—2,200 ohms
R3—3,900 ohms
R4—1 megohm
R5—2.2 megohms
R6—47,000 ohms
R7—1,500 ohms
R8—220 ohms
R9—10,000 ohms
R10—pot, 200 ohms
C1—10 μf, 450 volts, electrolytic
C2—.05 μf

C3—50 μf, 25 volts, electrolytic
C4, 5—.025 μf
C6—.01 μf
J1, 2—phono jacks
V—12AX7
Case, 4 x 2 1/4 x 2 1/4 inches
Socket, 9-pin miniature, shielded
Shield for 12AX7
Miscellaneous hardware
All resistors 1/2 watt

other high-impedance pickups.

Circuit action

The circuit design is based on the following reasoning. Suppose the con-

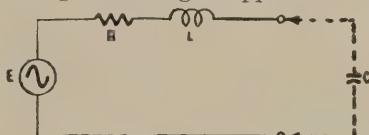


Fig. 1—Equivalent circuit of a magnetic cartridge.

Fig. 2—Circuit of one-tube preamp.

THERE are times when you might like to operate a phonograph turntable and pickup at distances of more than a few feet from the nearest electronic equipment. With a high-impedance magnetic pickup, such operation is usually impractical as the pickup's high-frequency output is attenuated by the capacitance of a long connecting cable. The preamp described in this article can be used with over a hundred feet of cable between it and the terminals of a G-E cartridge, without high-frequency loss and without requiring additional equipment.

The reason for phonograph cable loss is apparent from the equivalent circuit of a magnetic pickup (see Fig. 1). The voltage developed by the pickup is represented by E, the inductance of the pickup coil by L and the effective coil resistance by R. If the pickup is terminated in a capacitance C (the cable capacitance, for instance), L and C form a low-pass filter section. With practical values of L and C, the cutoff frequency of this filter can easily fall within the audio-frequency range and the pickup's output will become negligible at frequencies above this point.^{1,2}

One solution to the problem is to provide a cathode-follower amplifier between the pickup and the cable.² The drawback of this arrangement is the extra equipment and the need to supply power for it. The unit described here simply replaces the usual phonograph preamp so that no extra equipment is necessary and permits using a long cable. It has been designed particularly for the G-E series of magnetic cartridges RPX-050, 052, etc., although the amplifier's circuit constants can be worked out for use with a number of

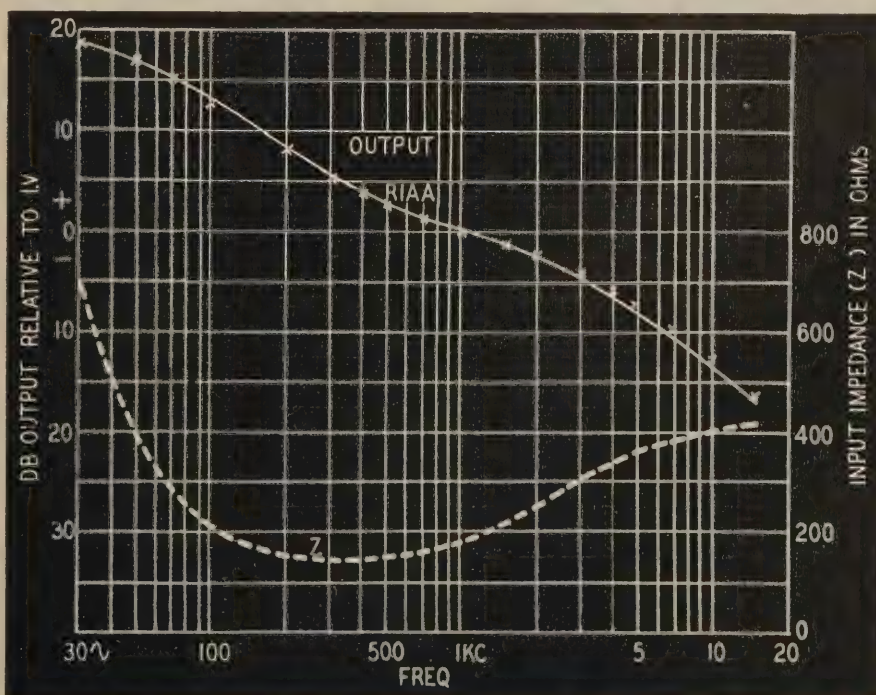


Fig. 3—Solid line: RIAA characteristic, X indicates actual preamp frequency response; dashed line: preamp input impedance.

AUDIO—HIGH FIDELITY

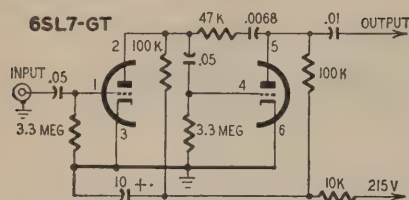


Fig. 4—Standard preamp circuit.

necting cable were terminated in a low resistance R_0 . If R_0 were equal to the characteristic impedance of the cable, then the pickup would always be terminated in R_0 and its performance would be independent of cable length no matter how long the cable might be. Even if R_0 were made several times the characteristic cable impedance, it would still be possible to use a considerable length of cable before its capacitive reactance became equal to R_0 at the upper limit of the af range.


Terminating the pickup in a low resistance produces high-frequency attenuation by itself, of course, but it is an attenuation that is predictable and controllable. In addition, its slope with frequency is such that with minor modifications it can be used to compensate the pickup response for modern recording characteristics.

A simple resistive termination of this sort is impractical due to the low developed voltage of the usual magnetic pickup. To overcome tube noise and hum in the preamp, the amplifier input must be kept as large as possible and little or no attenuation of the pickup's output can be permitted.

We now recall two facts concerning feedback amplifiers: First, an amplifier's input impedance can be modified by feedback. Second, the application of feedback does not change the signal-to-noise ratio of an amplifier. These facts suggest that a phonograph preamp can be made that will load the cartridge cable with a low impedance and at the same time maintain the signal-to-noise ratio that exists when a short cable and no feedback are used.

Fig. 2 is a circuit for such an amplifier. The two sections of the 12AX7 are connected in cascade. Negative feedback is taken from the cathode of the second section and is applied through the network consisting of C4, C5, R3, R8 and R4 to the amplifier's input. If the network consisted only of R3, the amplifier's input impedance would be a constant resistance throughout the audio range. The purpose of the additional elements is to vary the input impedance with frequency and correct the output of the G-E cartridge in accordance with the RIAA playback characteristic. The RIAA characteristic is plotted in Fig. 3. The crosses on this curve indicate the measured amplifier response, obtained by driving the unit from a signal source of 10 mv in series with a 330-ohm 500-mh impedance, which simulates the G-E cartridge.

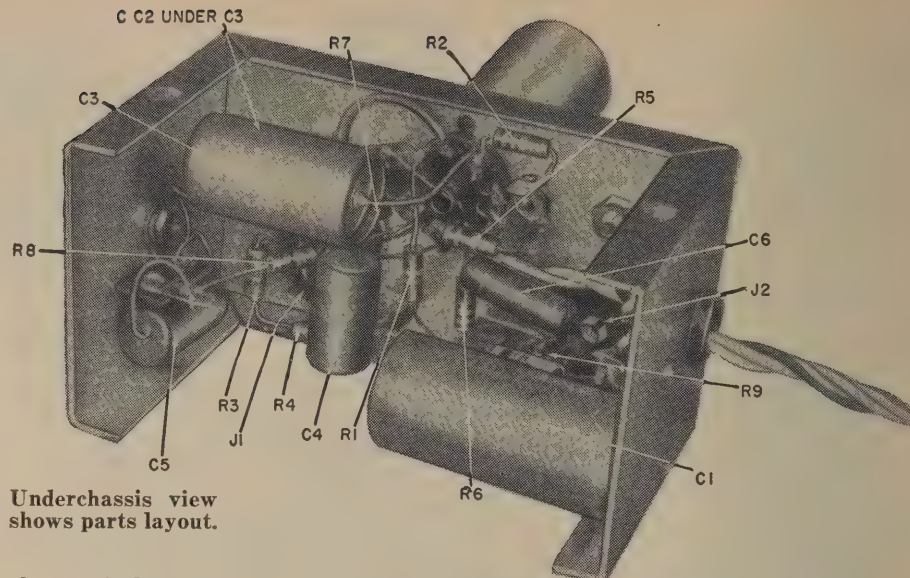Also shown in Fig. 3 is the magnitude of the preamp's input impedance. Note that at the high-frequency limit of the range, the impedance is a resistance of



Underchassis view shows parts layout.

about 400 ohms. If an ordinary preamp were used with the G-E cartridge, a terminating capacitance of 200 μ f would place the cutoff frequency at about 16,000 cycles. With a cable capacitance of 50 μ f per foot, the cable should be no longer than about 4 feet. Using the feedback preamp, a capacitance of .02 μ f is permissible for the same cutoff frequency and the cable may be up to 400 feet long.

Reducing input impedance by using negative feedback may seem curious, because we are accustomed to amplifiers in which the input impedance is raised by this means. The reduction will be less strange to readers who follow design advances in audio power amplifiers; it is now common practice to modify amplifier output impedance by a combination of positive and negative feedback. The output impedance is reduced by either negative voltage or positive current feedback, and increased by either positive voltage or negative current feedback.

In the preamplifier, the input impedance is similarly affected. The voltage fed back to the input is negative with respect to the source voltage, but it is applied in *shunt* with the source, thereby increasing the source loading, which is the same as reducing the amplifier input impedance. Had the feedback voltage been applied in *series* with the source, the source loading would have been reduced and the effective input impedance increased.

Low distortion level

The negative feedback used in the preamp helps reduce amplifier distortion. The circuit shown in Fig. 4, which corresponds to one used in many installations, was set up with a 1,000-cycle source in series with 3,300 ohms. With an amplifier output of 1 volt, the total harmonic distortion was 0.5%. The same test on the feedback preamp gave 0.1% distortion. Since the audio generator used in the measurements had inherent distortion of the same order, the actual preamp distortion may be less than 0.1%.

Total hum and noise in the preamp's

output is over 60 db below 1 volt. This hum level was obtained only with selected 12AX7 tubes and with the usual arrangement of a hum-balancing potentiometer connected across the heater supply, as shown in Fig. 2.

The feedback network C4, C5, R3, R8 and R4 has been determined only for the G-E series of cartridges. Other pickups, having different values of resistance and inductance, will require a different set of feedback circuit constants. The easiest way to determine

TABLE OF PHONOGRAPH CARTRIDGE CHARACTERISTICS

Manufacturer and type	R (ohms)	L (mh)	E (rated mv)
Audax HiQ7	575	700	20
Clarkstan 204	1,300	350	30
G-E RPX-050, 052, etc.	340	520	10
Pickering 120, 140	600	165	30
Pickering 260	750	130	30
Recoton-Goldring 500	1,500	550	30

these is by experiment. The procedure is to connect a low-impedance audio signal source (10 ohms or less) of rated pickup output voltage in series with the cartridge and amplifier input. An ac vtm is connected to the amplifier's output. Curves of output voltage vs. frequency are then run for different feedback circuit values until the set is found that matches the RIAA characteristic or whatever characteristic is desired. Alternatively, a dummy network may be used in series with the generator instead of the pickup itself. The resistance and inductance of the dummy should duplicate the actual pickup constants. The accompanying table lists these constants for most high-impedance cartridges.

This preamp—with only slight modifications—was used in the "Bookshelf Audio Amplifier" (RADIO-ELECTRONICS, April, 1957, page 32) and has turned in an excellent job.

END

References

- 1 Norman Pickering, "Effect of Load Impedance on Magnetic Pickup Response," *Audio Engineering*, March, 1953.
- 2 W. A. Fitzmaurice and W. Joseph, "Pickup Loading and its Effect on Frequency Response," *Audio*, July, 1954.

HI-FI

PICKUP ARMS

By JULIAN D. HIRSCH

THE vital role of the pickup arm in audio reproduction is not as widely understood as it should be.

The arm bears the same relationship to the cartridge as the speaker enclosure does to the speaker it houses. Most, if not all, of the extreme low-frequency reproduction of a phono system is dependent on the properties of the arm. Because its contributions are largely confined to frequencies below 40 cycles, they are not as audibly striking as those of a speaker enclosure which may influence the response for several octaves higher.

Apart from frequency-response considerations, pickup arms have a considerable effect on playback distortion. A poor arm may introduce large amounts of distortion or may even cause the pickup to fail to stay in the groove. Operating convenience must also be considered since, unlike the speaker enclosure, a phono arm is handled frequently and contains a rather delicate mechanism—the phono cartridge. An arm which is awkward to handle or is easily dropped may prove unsatisfactory even though its acoustical design be excellent.

A surprisingly large number of phono arms are offered for home use. In this series of articles I will describe most of the approximately 20 high-quality types, pointing out their unique features and essential design principles.

The arms may be classified according to several of their design characteristics. For example, some arms do not employ damping means, while others use various forms of viscous damping to eliminate or minimize the major resonance. From the standpoint of the user, perhaps the most obvious difference between various makes is the manner of pivoting the arm in the vertical and horizontal planes. (We will consider the vertical pivot as that which allows the arm to move vertically, although the pivot axis is horizontal. Similarly, the horizontal pivot is the one that allows the arm to traverse the record.)

In some designs, both pivots are located essentially at the same point, usually near the rear of the arm. In handling this type, the entire arm

swings upward when it is lifted to or from the record. Other arms have the vertical pivot located well forward of the horizontal pivot. A large portion of the arm does not move vertically when the cartridge is lifted from the record. This type of construction allows a fairly large counterweight to be used. This gives the arm considerable lateral mass and a low resonant frequency, while the vertical mass is kept low for reduced record wear. A third type is actually the ultimate refinement of the second, in which the vertical pivot is at the front of the arm, immediately behind the cartridge. Such arms have little or no up and down movement in handling, and require the user to develop a special technique if he is accustomed to the more conventional designs.

Several unconventional arms have been designed to reduce or eliminate entirely the tracking error which is the inevitable result of playing a record made with a cutter which travels on a radius with an arm that rotates on a single pivot point outside the record diameter.

Other distinctions between arms include the degree of lateral balance, various types of leveling and height adjusting mechanisms, use of springs or counterweights for stylus-force adjustment and others too minor to consider. Obviously, to categorize the large number of arms for comparison purposes, it is necessary to make certain arbitrary decisions as to the basic

design differences. Since the relative location of vertical and horizontal pivots directly affects the feel of the arm more than any other factor (except the presence of viscous damping, which is used on only a few types), we will use this as our basis for grouping the arms.

Separated pivots

The first two arms in this category are the Fairchild 280A/281A and the Audax KT-12/KT-16. Each has its vertical pivot located several inches forward of the horizontal one. Apart from this, they have little in common in the way of appearance or handling feel.

The Fairchild 280A (Fig. 1) and 281A are of similar design, and are intended for playing 12- and 16-inch records, respectively. They are laterally balanced by the counterweight at their rear. Because of this, leveling is not critical and they are relatively insensitive to the effects of jarring. The vertical pivots are located about 40% of the way from the rear of the arm to its front.

The arm is constructed of extruded aluminum, of about 1-inch-square cross-section. This provides rigidity and minimizes torsional resonances which can occur in an arm. The weight of the forward portion of the arm and the

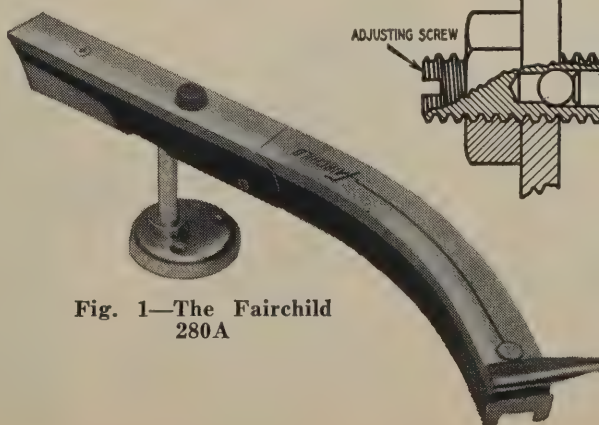


Fig. 1—The Fairchild 280A


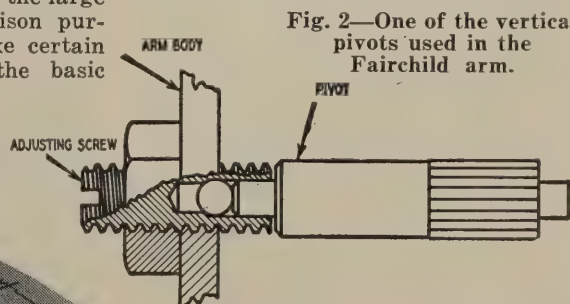


Fig. 2—One of the vertical pivots used in the Fairchild arm.

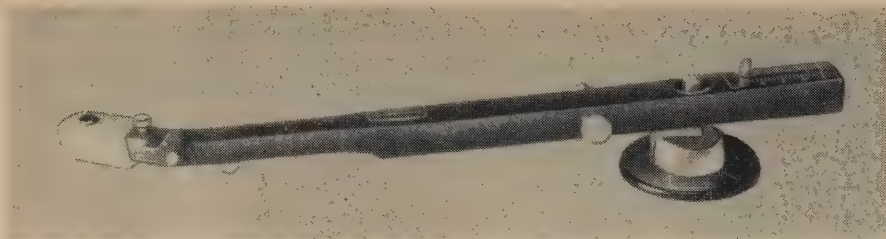

cartridge is counterbalanced by a long spring which is adjusted with a thumb-screw under the arm.

The pivot bearings are simple yet effective. Fig. 2 shows their construction. They are individually adjusted at the factory for optimum performance. The base of the Fairchild arm is fastened to the motor board by three screws and rests on rubber grommets. The screws may be tightened against these grommets to level the arm relative to the motor board. A single screw may be loosened to permit vertical adjustment of arm height to accommodate any turntable. Another adjusting screw enables the arm to be set so the stylus cannot strike the turntable if no record is on it.

Two unique features of the Fairchild arms are the absence of an arm rest and the plug-in drawers (or heads) for cartridges. A detent built into the base holds the arm in rest position without the need of mounting the usual separate arm rest on the motor board. The cartridge is mounted in a separate metal drawer which slides into the open front of the arm. It will accommodate practically any cartridge which mounts on standard 1/2-inch centers.

In the arm are a pair of springs which make solderless connections to the cartridge pins, for a wide range of lengths and spacings of these pins. When the drawer is removed, the springs short-circuit, preventing loud hum or noise when changing cartridges (and also safeguarding the speaker cone).

Audax KT-12/KT-16

The basic Audax arm has been on the hi-fi scene for many years and has enjoyed an excellent reputation. In the past, its usefulness has been limited by the fact that it would accept only Audax cartridges. But the new KT series has a removable shell which accommodates any standard magnetic cartridge as well. Fig. 3 shows the Audax KT-16 arm.

Perhaps the most novel feature of these arms is that they are sold in kit form at a saving of nearly 50% over their assembled prices. The arms can be assembled in less than 15 minutes, using only a screwdriver.

Unlike the Fairchild arm, the entire body of the Audax arm moves in the vertical plane. Only a small angular movement is possible vertically since the vertical pivots are 2 inches forward of the horizontal pivots and the rear of the arm strikes the base assembly

when the arm is raised more than a few degrees.

The arm is made of light aluminum with a U-shaped cross-section. A heavy brass counterweight in the rear is adjusted by loosening a knurled screw, permitting a wide range of stylus-force adjustment with any cartridge. The vertical pivots are simply screws with conical ends which are threaded through the sides of the arm and fit into small dimples in the pivot casting. The adjustment for low friction and low play is easily made, after which protective caps lock the pivot screws.

The horizontal pivot, described by Audax as "compass-point pivoting," can be seen in Fig. 4. The entire arm mass is supported on a needlepoint, which provides low friction and has no adjustments or wearing parts. The slot, which covers a 90° arc in the base, is engaged by a screw in the pivot casting and prevents the arm from being rotated more than 90°. This is to keep the pickup from being placed on the wrong side of the record, which could damage the record grooves. The screw visible at the front of the pivot casting provides a stop to prevent the stylus from striking the turntable in the absence of a record.

The outstanding feature of the Audax design is its simplicity, since it has a minimum number of moving or adjustable parts. One minor disadvantage of this emphasis on simplicity is the need for shims to adjust arm height. Cardboard shims are supplied with the arm and are placed under the base as needed to fit the turntable height.

Pickering 190D

For many years Pickering 190-


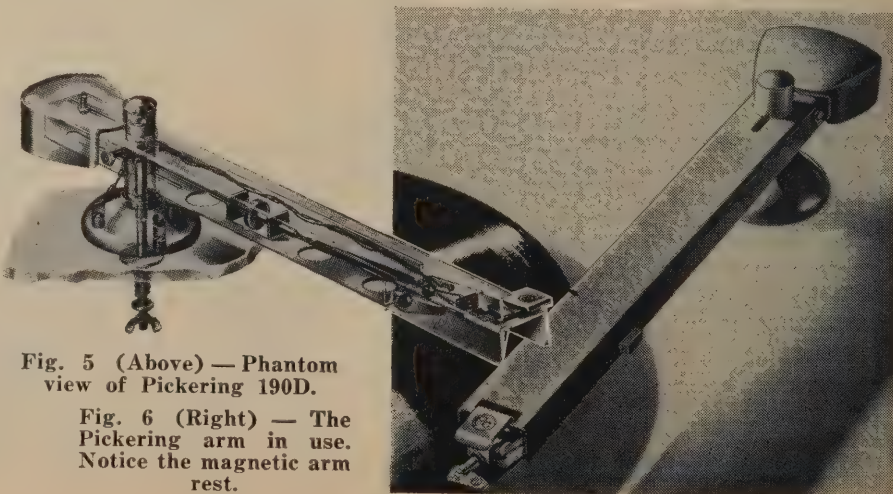


Fig. 5 (Above) — Phantom view of Pickering 190D.

Fig. 6 (Right) — The Pickering arm in use. Notice the magnetic arm rest.

Fig. 3 (Left) — Audax KT-16, sold in kits or fully assembled.

Fig. 4 (Below) — Closeup of Audax pivot assembly.

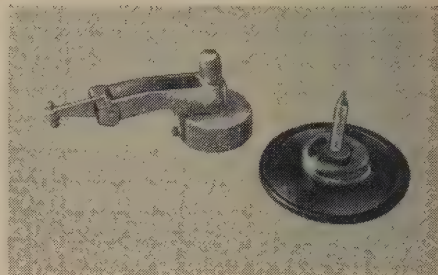

series arms have held a unique place in the field. The entire arm is constrained in the vertical plane, and only the cartridge pivots vertically. Fig. 5 is a phantom view of the Pickering arm. The arm body has a rectangular cross section and is extremely rigid. It is counterweighted and is balanced about the horizontal pivots. Leveling the arm is completely noncritical, as it will track records with the motor board inclined 45° or more to the horizontal.

The arm's height is adjusted by loosening a single screw and sliding the entire arm up or down on the upright rotating spindle which forms the horizontal pivot. This spindle contains two precision ball-bearing assemblies and has extremely low friction. The base mounts with a single screw passing through the motor board, and three adjusting screws permit the arm to be set parallel to the turntable surface. This is an important adjustment since the arm cannot move in the vertical plane.

At the extreme forward end of the arm is a small pivoted plate on which the cartridge is mounted. Needle bearings are used for the vertical pivots. A long stretched spring counterbalances the weight of the cartridge and its mounting plate, and a knurled wheel underneath the arm permits the stylus force to be adjusted conveniently.

Although the body of the Pickering 190D arm is straight, the necessary

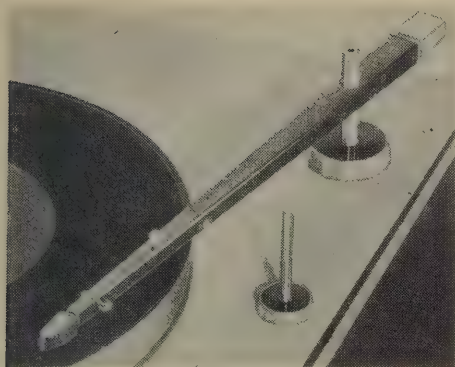


Fig. 7—Shure Studio Dynetic also has a magnetic rest.

offset angle is provided by the orientation of the cartridge mounting. The arm is supplied with a mounting clip for the Pickering 350 Fluxvalve cartridge, but this can be removed and any cartridges having standard $\frac{1}{2}$ -inch centers can be mounted. The finger lift at the end of the arm merely lifts the stylus clear of the groove, and the arm is swung to the desired position without any vertical motion. This requires a somewhat different technique than any other arm does.

This design has the advantage that the cartridge is protected and cannot strike the center spindle of the turntable. The design of the finger lift also prevents the stylus from striking the turntable in the absence of a record, if properly adjusted.

The salient feature of the Pickering design is the reduction of vertical mass to a practical minimum, using conventional cartridges. Not only is the cartridge mounting plate as small and light as possible, but a spring counterbalance is used instead of a counterweight which would add to the vertical mass. The heavy counterweight at the end of the arm serves the dual function of balancing the arm laterally and providing a high lateral mass, resulting in an arm resonance well below the audio range.

Another novel feature of the Pickering 190D is the magnetic arm rest (Fig. 6). The arm is shown installed on a motor board and the magnet can be seen on the side of the arm. The arm rest (not shown) is an upright piece of steel to which the arm is held by the magnet.

The Pickering 190D is available only in a 16-inch model, but the stubby counterweight gives little overhang and it can frequently be installed in locations too cramped for other 16-inch arms.

Shure Studio Dynetic

The basic philosophy behind the design of the Shure Studio Dynetic arm is similar to that of the Pickering 190D, although there does not appear to be any physical resemblance between them.

Fig. 7 shows the Shure arm in playing position. It comes in 12- and 16-inch models. Notice the magnetic

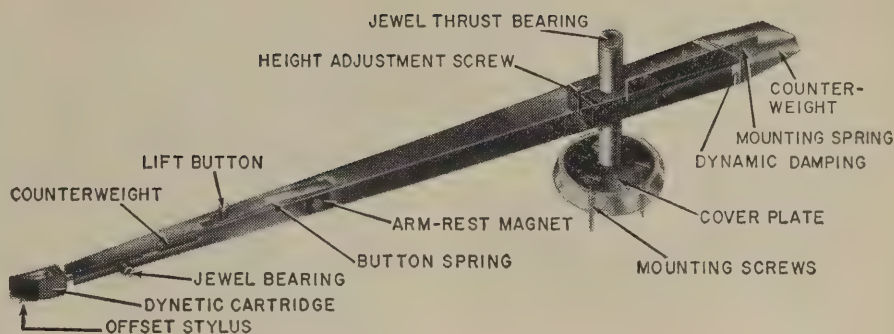


Fig. 8—Phantom look at the Shure arm.

arm rest. Fig. 8 is a phantom view of the Shure pickup. The vertical pivot is located just behind the cartridge. Ruby jeweled bearings are used in both vertical and horizontal pivots. The arm is a slim streamlined device and can be adjusted vertically for turntable height by loosening a screw and sliding it up or down on the horizontal pivot spindle.

The cartridge mass is counterbalanced by a threaded weight, which is moved back and forth for stylus-force adjustment. The special Shure cartridge, an integral part of this arm¹, has a very low mass so the total vertical mass is still quite small. The arm itself is straight, with the offset angle built into the stylus assembly of the cartridge.

Like the Pickering 190D, the Shure arm does not move in the vertical plane. A unique system lifts the stylus from the record. A small plastic button on the top of the arm is pressed down to lift the cartridge and released to lower it to the record. Since the cartridge itself is never handled by the user, and the maximum downward force it can exert is only 2 grams, it is impossible to damage the record or stylus by accidentally knocking the arm across the record.

The Shure design incorporates a new and novel damping system, termed "dynamic damping." The weight at the rear of the arm balances it about the horizontal pivot's axis. It is connected to the body of the arm by a springlike suspension bar. The space between the weight and arm is filled with a plastic material. The physical and mechanical constants of the system are chosen so that at the arm's resonant frequency the plastic provides mechanical resistance which effectively damps the resonant peak. At other frequencies, the mechanical resistance has no effect

¹J. D. Hirsch, "Modern Phono Cartridges," Part IV, RADIO-ELECTRONICS, July, 1957.

so there is no possibility of a viscous drag which might introduce undesirable lateral or vertical forces when playing eccentric or warped records.

G-E A1-500/A1-501

Like the preceding two, General Electric arms (see Fig. 9) have a wide separation between vertical and horizontal pivots, with most of the arm constrained in the vertical plane.

The main body is a rigid tube, mounted on a very-low-friction, horizontal pivot spindle. Its height is adjusted by sliding the arm up or down the spindle. The cartridge shell is re-

The Rek-O-Kut A-120/A-160, Pickering 194D, Leak Dynamic and Weathers pickup arms will be described in the next installment.

movable for easy cartridge installation, though it is not a plug-in shell. The entire shell is offset for correct tracking.


The cartridge is counterbalanced by a sliding weight on a boom extending to the rear of the shell. This boom has a gram scale which reads the stylus force directly when using G-E cartridges or others of equal weight.

The cartridge shell may be tilted upward 90° to inspect, clean, or replace the stylus.

There is almost no overhang to the rear of the horizontal pivot, so the arm can be installed in limited space, especially in its 12-inch version (A1-500). However, it is not laterally balanced and must be carefully leveled for proper operation.

The next article in this series will describe the large group of arms with vertical and horizontal pivots located close to each other. TO BE CONTINUED

Fig. 9—A tubular arm is used in the G-E A1-500.

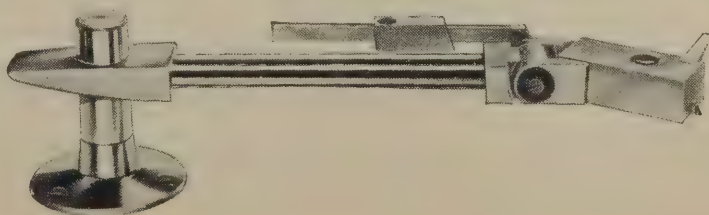

Multi-Channel

Two 3-channel units that can be used to provide any crossover frequencies between 100 and 10,000 cycles

electronic crossovers

By NORMAN H. CROWHURST

AN increasing number of readers have been writing me to ask about electronic channel separators. Circuits they have tried suffer from excessive noise, hum or distortion. Then, too, some want to adjust the crossover frequencies in different ways. To overcome all these problems I have developed a couple of universal channel-filter circuits, along with a design chart that indicates component values for any desired crossover frequencies.

The two circuits have been carefully designed so the amplification level does not run up into distortion or down into the noise region. Sometimes these problems occur because the channel separator provides extra gain and proper attenuation is not inserted at the right place. The circuits presented here have zero insertion loss—the input and output levels are the same. Also, considerable feedback minimizes distortion.

Both circuits can readily be added to existing equipment, an essential feature for our purpose, because the single tube for each channel filter requires less

than 1 ma at 250 volts for its plate-screen supply. If existing equipment does not have reserve heater supply (6.3 volts at 300 ma for each channel), it can be obtained cheaply from an additional filament transformer.

Both circuits use a single 6AU6 for each channel. The difference between them is that the simpler circuit gives a 12-db-per-octave transition rate, while the more complicated one steps up the transition to an ultimate slope of 24 db per octave. As previous articles have pointed out, the shallower transition is usually recommended. But some readers have asked, "How can I make the transition more sudden," so a circuit is included that gives the full 24 db per octave. However, circuit values are much more critical if the correct response is to be obtained. Various values around the circuit may have to be adjusted to get a smooth response, turning over at the correct frequency.

Simpler 12-db circuit

In the simpler circuit (Fig. 1), the effective dynamic range of the 6AU6


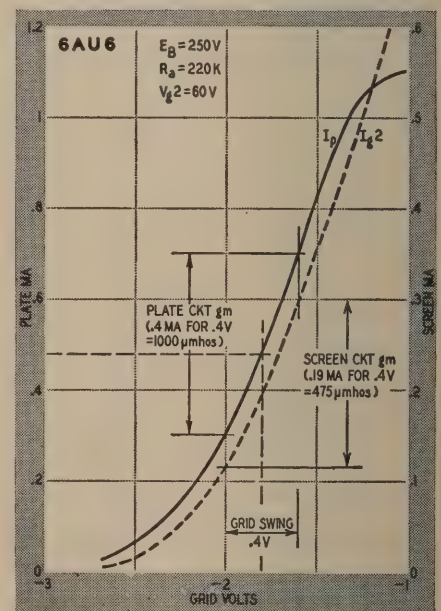


Fig. 2—Plate- and screen-current characteristics of the 6AU6, showing how values are chosen to give minimum distortion in the circuit of Fig. 1.

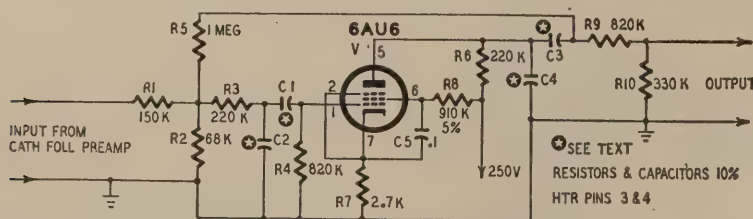

R1—150,000 ohms
R2—68,000 ohms
R3, 6—220,000 ohms
R4, 9—820,000 ohms
R5—1 megohm
R7—2,700 ohms
R8—910,000 ohms, 5%
R10—330,000 ohms

All resistors 1/2 watt, 10% unless noted
C1, 2, 3, 4—See text
C5—0.1 μf
All capacitors, ceramic, molded or high-quality paper; 10% tolerance
V—6AU6
HTR PINS 3 & 4

Fig. 1—Basic circuit of bandpass channel filter giving 12-db-per-octave rolloffs.


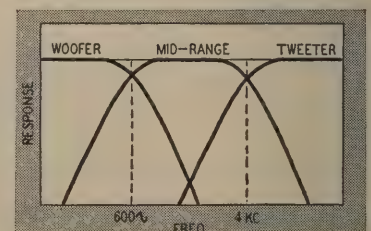



Fig. 3—The frequency distribution used for the sample calculations in the text.

-VALUES FOR CIRCUIT OF FIG. 1.

VALUES FOR CIRCUIT OF FIG. 5.

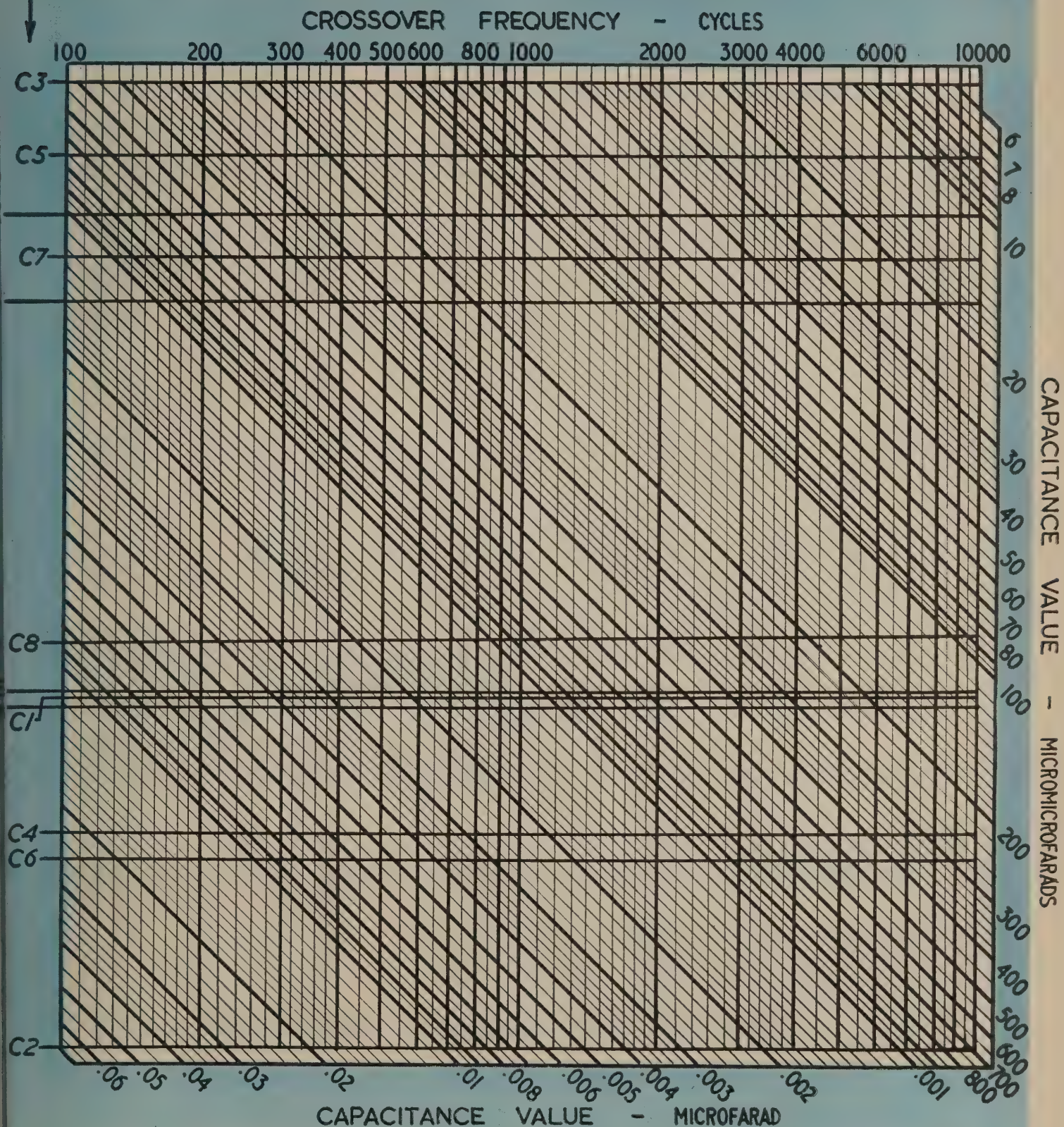

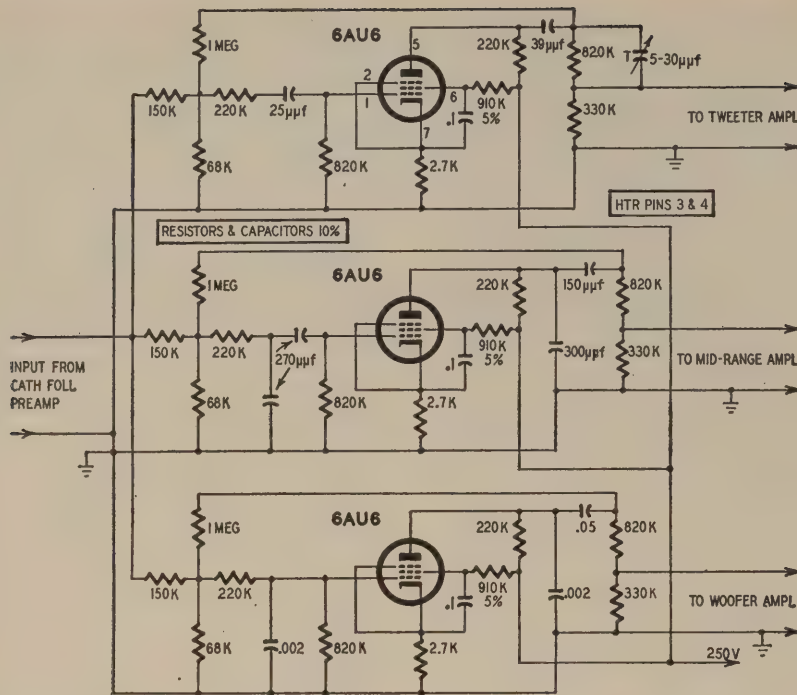CAPACITOR RATINGS FOR ELECTRONIC CROSSOVER CIRCUITS



NOTE: When purchasing parts for this circuit, use parts list for Fig. 1 and multiply the number of individual components by the number of channels in the system. Some capacitors are omitted in the tweeter and woofer channels. See text.

Fig. 4—Complete circuit of 3-way separator with 12-db-per-octave rolloffs.


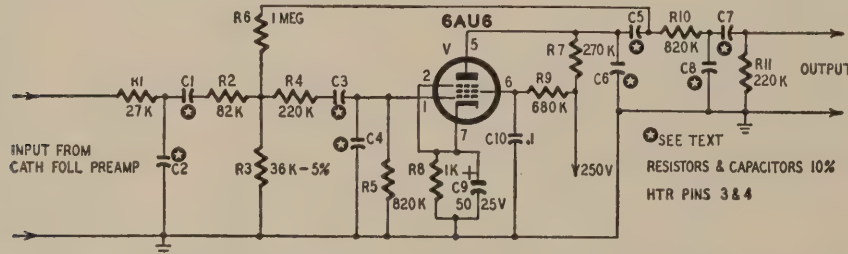


Fig. 5—Basic circuit of bandpass channel filter giving 24-db-per-octave rolloffs.

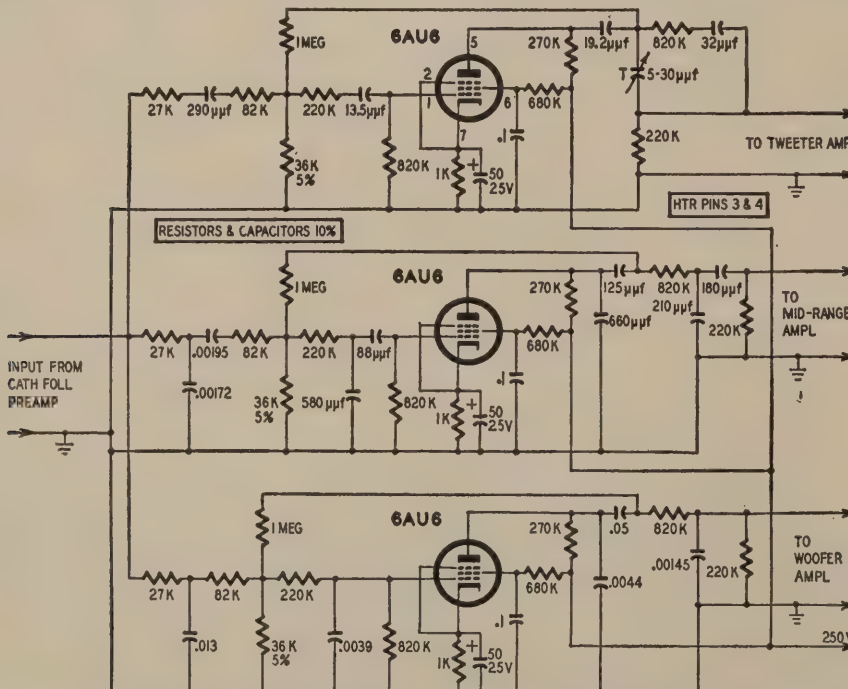

NOTE: When purchasing parts for this circuit, use parts list for Fig. 5 and multiply the number of individual components by the number of channels in the system. Some capacitors are omitted in the tweeter and woofer channels. See text.

Fig. 6—Complete circuit for 3-way separator with 24-db-per-octave rolloffs.

is increased by using about 14 db of degenerative feedback through the 2,700-ohm bias resistor in the cathode circuit. Values of plate and screen feed resistors are such that the operating condition works the tube around the point where the curvature of plate and screen current is very similar (Fig. 2). This is important because the cathode resistor linearizes the total signal current. If the curvatures of plate and screen current differ, the feedback may well produce more distortion rather than less.

The cathode feedback gain reduction is not frequency-discriminating and leaves a highly linear amplifier with a gain of 30. The 1-megohm resistor from output to input reduces the gain, this time including the rolloff components, by a further 6 db, leaving the tube with a working gain of 15. The 220,000- and 820,000-ohm resistors in the grid circuit reduce this to 12. Finally, input and output resistor networks dissipate the rest of the gain, so the output voltage is approximately equal to that of the input.

The 6-db controlling feedback is dependent on the circuit being fed from

Parts List for Fig. 5.

R1—27,000 ohms
R2—82,000 ohms
R3—36,000 ohms, 5%
R4, 11—220,000 ohms
R5, 10—820,000 ohms
R6—1 megohm
R7—270,000 ohms
R8—1,000 ohms
R9—680,000 ohms
All resistors 1/2 watt, 10% unless noted
C1—8—See text
C2—50 μf, 25 volts, electrolytic
C3—0.1 μf

All capacitors are ceramic, molded or high-quality paper, 10% tolerance unless noted
V—6AU6

a cathode follower with a source resistance of not more than about 5,000 ohms. If the filters are fed from the plate circuit of a preamplifier tube, subtract the tube's plate resistance from 150,000 ohms for the input feed resistor R1.

The capacitors responsible for low-frequency rolloff are C1 and C3, while those for high-frequency rolloff are C2 and C4. For a section to feed a mid-range speaker all these capacitors will be needed. For the woofer unit C1 is not needed, and C3 can be a convenient value, .05 μf. Capacitors C2 and C4 are selected (using the chart) according to the crossover frequency desired from woofer to mid-range unit.

For the mid-range, C1 and C3 are determined for the crossover frequency between woofer and mid-range, while C2 and C4 are determined for the crossover from mid-range to tweeter. For the feed to the amplifier supplying the tweeter C2 and C4 are omitted and the chart supplies values for C1 and C3 to get the right low-frequency rolloff to match the mid-range unit according to crossover frequency.

For example, assume the desired crossover frequencies are 600 and 4,000 cycles (Fig. 3). For the woofer unit, C2 is .00185 μf and C4 .002 μf. This circuit is not highly critical and if one capacitor is a little higher and one a

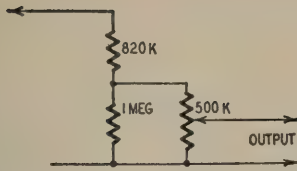


Fig. 7—How to combine the amplifier's gain control with outputs of Fig. 4 to provide a balance adjustment.

little lower than the indicated value the result will come out about right. Both capacitors could be .002 nominal, and response would probably come pretty close to the desired performance.

For the mid-range unit, C1 is 170 μf and C3 is 260 μf . These are calculated using the 600-cycle design frequency. One at 150 and one at 270 or 300 μf will probably be close enough. Alternatively, both at 220 would also come pretty close. Capacitors C2 and C4 are calculated with the 4,000-cycle design frequency and come out to 280 and 300 μf , respectively. Capacitors of 270 and 300 μf will do nicely.

For the tweeter unit C1 and C3 are 26 and 40 μf , respectively. Thus, we have all the values to build up a three-way filter which can conveniently be fed from a preamp's cathode-follower output. The complete three-channel circuit is shown in Fig. 4.

24-db-per-octave roll-off

The more complicated 24-db circuit (see Fig. 5) uses 18 db of feedback from plate to grid and consequently does not need the cathode degenerative feedback employed with the simpler cir-

cuit. Now, the circuit has to be arranged to get the maximum possible gain out of the 6AU6, if we are to adjust circuit values to get a reasonable degree of independence in action.

The working gain of the tube, with the values shown, is 250. The output provides a voltage stepdown of 5 to 1. Feedback reduces the working gain by an effective 8 to 1. The grid circuit drops it by 5 to 4 and the input attenuation arrangement gets rid of the rest.

Correct response is dependent on feeding from a cathode follower. It would be difficult to allow the kind of latitude needed for plate-coupled circuits, with a 24-db-per-octave type. Outside the passband the rate of rolloff approaches 24 db per octave at each end.

As before, for the woofer unit, the odd-numbered capacitors can be omitted where they are not required for dc blocking purposes—only C5 is required, which can be some convenient value, like .05 μf . The capacitors with even numbers are selected (use the chart) using the low-frequency crossover point.

With the same example of 600 cycles, the values required for the feed unit to the woofer amplifier are: C2, .0115 μf ; C4 .0039 μf ; C6, .0044 μf , and C8 .00145 μf .

For the mid-range feed, using the same frequency at 600 cycles to select the capacitors with odd numbers, we get: C1, .00195 μf ; C3, 88 μf ; C5, 125 μf , and C7, 210 μf . For the even-number capacitors in the mid-range feed the 4,000-cycle frequency is used, giving the following values: C2,

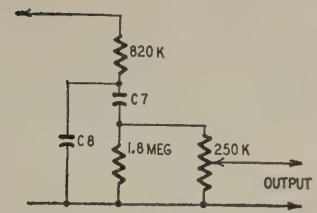


Fig. 8—How to combine the amplifier's gain control with outputs of Fig. 6 to provide a balance adjustment.

.00172 μf ; C4, 580 μf ; C6, 660 μf , and C8, 210 μf .

For the tweeter unit, the odd-numbered capacitors are again calculated with 4,000 cycles: C1, 290 μf ; C3, 13.5 μf ; C5, 19.2 μf , and C7, 32 μf . For the tweeter unit, C2, C4, C6 and C8 are omitted. The complete three-channel circuit is shown in Fig. 6.

If the power amplifier's input capacitance in conjunction with the output resistances of these circuits produces a high-frequency loss on the tweeter unit (above 10,000 cycles), compensation must be provided. Use a small trimmer, about 5 to 30 μf , across the upper resistor of the output voltage divider. As shown at Figs. 4 and 6, that can be used to adjust the frequency response obtained in the tweeter unit.

Most feedback amplifiers have their gain control right in the input circuit. This will shunt the output of the filters, altering both gain and response. Using a 500,000-ohm input potentiometer in the circuit of Fig. 1 and a 250,000-ohm input potentiometer for the circuit of Fig. 5, the output circuits will be as in Figs. 7 and 8.

END

NEXT MONTH

Servicing Transistor Auto Radios

Veteran service technician *Jack Darr* tells of some of the things the service tech will run into in the newer sets, and some of the differences between them and their older tube counterparts.

New Amplifier Uses KT88's

Dave Hafler, one of the originators of the Ultra-Linear circuit, tells how certain features of the new tubes are used to advantage in a 60-watt 20–20,000-cycle amplifier.

All-transistor Direct-reading AF Meter

The man who services high-quality audio equipment will find this a valuable instrument, as will the advanced hi-fi enthusiast.

Tube Data and Amplifier Design

Part II—Tube data for R-C-coupled triode circuits and swing to drive output tubes

By HERBERT RAVENSWOOD

LAST month we discussed the use of information presented in tube manuals for designing R-C-coupled pentode amplifiers. This month we shall cover triode circuits.

Let's use a 12AY7, a very good input stage for audio work. The RCA manual does not list this one. The Sylvania does; in fact it gives a table for it. But let's assume for the purpose of this article that we don't have the Sylvania book. It often happens that the tube we want is not in the book we have. But in one of those comprehensive tube data manuals that list every tube made, we find the following (ratings may differ in different manuals:

Type	Heater volts	Heater amps	Plate volts	Plate ma	Negative grid volts	Plate resistance	Trans-conductance	Ampl factor
12AY7	6.3	0.3	150	2.0	2.5	26,500	1550	40
	12.6	0.15	250	3.0	4.0	23,500	1700	40

For a low-level input stage, we shall probably decouple so that the plate supply point is about 150 volts. With a plate resistance of 26,500 ohms, the coupling resistor should be at least three times this and, allowing for the increase of plate resistance at lower currents, 100,000 ohms would seem a good value. Assuming that the biggest part of the supply voltage will drop across this, we should have about 1 ma of plate current, with a plate voltage in the region of 50. For 150 volts on the plate, a 2.5-volt bias gives a plate current of 2 ma. Reducing everything to one-third, 50 volts on the plate should give a plate current of 0.67 ma with a negative grid voltage of 1.67. So 1 milliamp would require rather lower grid voltage, say 1.5. This means the cathode resistor should be 1,500 ohms. For this kind of stage the following grid resistor could well be 470,000 ohms.

We will estimate the gain on this basis. As ratings are proportional to those listed we can assume that the amplification factor will still be about 40. But due to the drop in plate current, plate resistance will be higher. On the previous basis, as the current is halved, we would expect the g_m to be divided by about 1.6. The square of 1.6 is 2.56, and 2 is an approximate mean between 1.6 and 2.56. So the ac resistance will be multiplied by 1.6, to keep the same amplification factor, giving a value of $26.5 \times 1.6 = 42,500$. The 100,000-ohm plate resistor is parallel,

ac-wise, with the 470,000-ohm grid resistor following, giving a plate load of about 82,000 ohms. So the stage gain is likely to approximate

$$40 \times \frac{82}{42.5 + 82} = 26.$$

Taking a peep at the Sylvania table, we find values for a plate supply of 150 and of 250 volts. By averaging the gain figures and bias values, it would seem that we may be a little conservative on the gain, and the bias and operating condition we hit about right. Using the tube characteristic as a check—which we have to get from the Tung-Sol book (Fig. 1)—we will get a gain of 27 with these values (cathode properly bypassed) and the plate current will be 0.82 ma, the bias 1.23 volts and the plate voltage 68. On the whole as good a guess as can be expected from the information we used!

To complete the stage design, we want suitable coupling capacitors. With a following grid resistor of 470,000 ohms, the reactance of the coupling capacitor must be less than 470,000 ohms down to 20 cycles. A .02- μ f capacitor satisfies this with 400,000 ohms, or a .05- μ f capacitor will give a better margin, with 160,000 ohms.

For the cathode bypass, we first calculate the gain without it. With a 1,500-ohm cathode resistor and a gain of 26 (taking our own figure) into 82,000 ohms, the gain from grid to

cathode will be $26 \times \frac{1.5}{82} = 0.475$. This

means that we need 1.475 volts in to get 1 volt from grid to cathode, without the bypass. This represents a gain reduction of almost exactly 3 db due to the 1,500-ohm cathode resistor. This means there will be a loss of 1.5 db when the reactance of the bypass capacitor is 1,500 ohms. A value of 5.5 μ f gives a reactance of 1,500 ohms at 20 cycles. So anything above 10 μ f should be OK.

The circuit for a two-stage amplifier developing a gain of 675 to 730 (according to whether you take the guess figure of 26 or the one from the tube characteristic, 27), is shown in Fig. 2.

Other design problems

Another job in R-C-coupled amplifier design that often sets problems is providing sufficient swing to drive the output tubes. The more straightforward

circuits require only a relatively small swing but some need a very large one—for example, the cathode-follower output stage. None of the tabulated data gives a large enough swing for this purpose. How can we get more?

Increasing the B-supply voltage enables a stage to provide a larger output: the highest working voltage listed in the RCA manual is 300, and in some other manuals it is only 250, but supplies for output stages deliver as much as 450. Here's an example.

Looking through the RCA manual, the best triode tube for providing a large output swing is the 6SN7 group. If need be, we can work two in push-pull, which will help by cancelling the second harmonic which is bound to predominate in any tube operating at this large swing. Suppose we are limited on the output tube grid resistors to 500,000 ohms. The table lists two combinations at 300 volts using a 470,000-ohm grid resistor R_g : one with R_p of 100,000 ohms, giving a maximum E_o of 96, and the other with R_p of 220,000 ohms, giving an E_o of 85. Obviously the latter arrangement fails to improve the output because the high resistance values are starving the tube of current and working it too far round the bend.

Fig. 3 shows the tube characteristics for one half of a 6SN7-GT, with load lines drawn for 100,000- and 470,000-ohm conditions. First the 100,000-ohm line is drawn by aligning 300 volts with 3 ma, and the operating point found from the cathode resistor given in the manual, 3,900 ohms. The operating point is 1.55 ma, -6 volts bias, from which the plate voltage is seen to be about 137. Now draw a load line through this point to represent the ac resistance of 100,000 ohms in parallel with 470,000 or 82,000 ohms. This can be done by aligning 5 ma and 410 volts with a straightedge and then drawing a parallel line through the found operating point.

We now have the limits of voltage excursion for a 6-volt grid swing each way from the -6-volt bias point: 33 and 225. This is a peak-to-peak swing of 192 volts, or a peak output of 96 volts, which agrees with the manual. Next we can see how much second harmonic we have.

The midpoint between 33 and 225 is 129 volts. But the operating position is

137 volts. So the swing is 8 volts off center in a peak-to-peak of 192. This represents a second harmonic of just over 4% ($8/192$).

Now let's see what we can do with 450 volts of B plus: Drawing the 100,000-ohm line by aligning 450 volts with 4.5 ma, we select an operating point at about 200 volts. This would represent a bias of about 8.8 volts, so the total swing would go almost to -18 volts, which looks as if it is getting well into the curvature. Dropping a little, to 8.5 volts bias, the plate current is 2.5 ma so the bias resistor calculates to the convenient value of 3,300 ohms. Now we draw the 82,000-ohm load line through this point and note the voltages corresponding with 0 and -17 volts on the grid: 48 and 323. A peak-to-peak swing of 275, or $E_o = 137.5$.

To estimate distortion, the midpoint between 48 and 323 is 185.5, while the operating point is 196. This is a difference of 10.5 volts in a peak-to-peak of 275, representing about 3.8% second harmonic, which is a little lower than the previous figure. We could use a little more bias and get a little more swing. Say we use 3,600 ohms, giving 9 volts bias with 2.5 ma. The relevant voltages will then be 48, 202 and 380, which works out to an E_o of 166 volts with still less than 4% distortion.

The chart in Fig. 3 comes from the Tung-Sol manual. If you have been following along in another book, you may not read exactly the same voltages. These curves differ slightly from one source to another.

But even allowing for differences, investigation has shown the trend on which we can base our "inspired guesswork" when the only data available are not enough. Going back to the table, we find that, using the same values of R_p and R_g at the three voltages of 90, 180 and 300, E_o steps up by a slightly larger ratio than B plus each time. The first step is double, but E_o goes from 23 to 51, which is more than double—a ratio of 2.2. The second step, from 180 to 300, is a ratio of 1 to 1.67, but E_o jumps from 51 to 96, a ratio of 1 to 1.88. The third step, from 300 to 450, is a ratio of 1 to 1.5, but E_o jumps from 96 to 166, a ratio of 1 to 1.73. So the pattern is fairly consistent and should enable us to make a reasonable estimate. Notice what happens to the cathode resistor: In order, the values for 90, 180, 300 and 450 volts are: 4,800, 4,140, 3,900 and 3,600 ohms. Again a consistent trend.

There are some points that must be watched in pushing up the B plus. See that tube ratings—voltage or dissipation—are not exceeded. This is usually fairly safe, but a danger that may be overlooked is the condition during warmup. Single-ended tubes (plate connection at the base) have a maximum plate voltage rating that should be watched. If it is seriously exceeded during warmup, there is risk of internal flashover. Either get a special type in which allowance is made for this (such as the 6SN7-GTA, whose max-

imum plate voltage is extended from 300 to 450) or use a slow warmup rectifier to insure that the tube heater is "up" before B plus arrives.

Using a larger cathode bias resistor with the same plate circuit resistors will always increase the available swing before clipping occurs, but will also increase the curvature producing second harmonic. If you don't need the full swing, operation will be better with a somewhat lower cathode resistor. This will reduce second-harmonic curvature and the operating plate voltage and plate dissipation, when high-value plate resistors are used.

In general we use a certain amount of guesswork unless we can get the tube characteristics and use the full method, based on load-line technique, which has been discussed elsewhere (RADIO-ELECTRONICS, June, 1955; April, 1956). After a little practice, the guesswork becomes almost inspired!

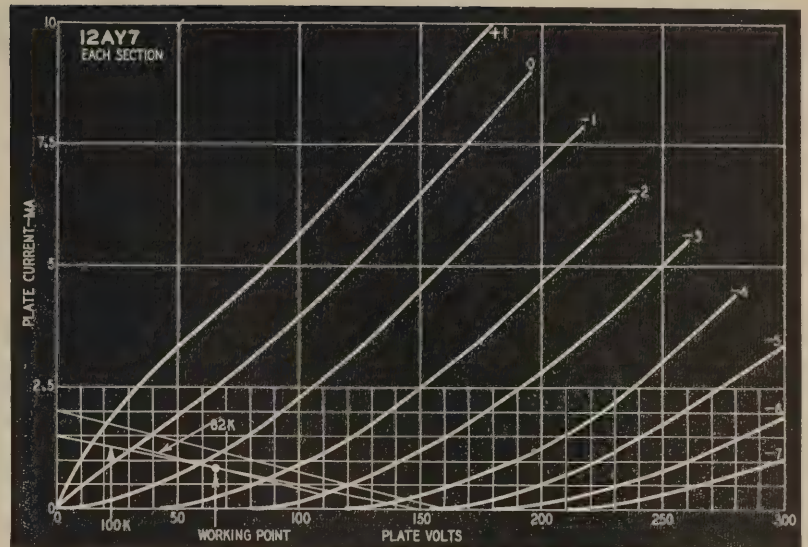


Fig. 1—Characteristic curves of a 12AY7.

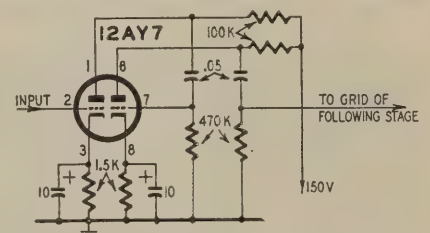


Fig. 2—Two-stage, R-C-coupled triode amplifier.

Even when we have access to tube characteristics and can draw load lines to our heart's content, some adjustment is sometimes necessary experimentally. So we are not much worse off without this advantage. The best data for R-C-coupled design is undoubtedly the kind given in the RCA manual and similar publications, *when the tube we want to use happens to be included*. Otherwise we have to resort to the kind of estimating outlined in this article. END


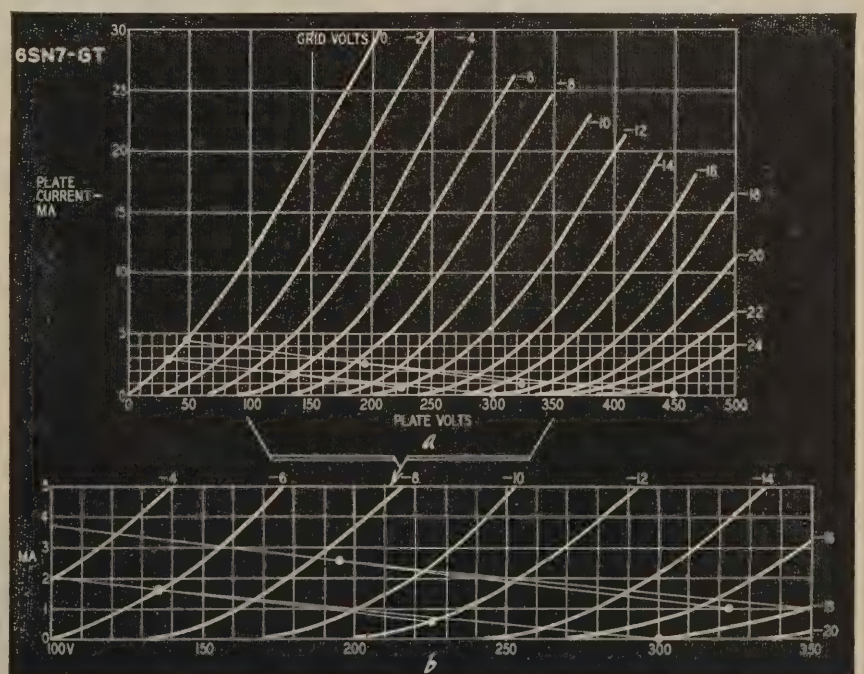


Fig. 3-a—Characteristics of a 6SN7-GT triode section; b—expanded section indicating load lines and operating points.

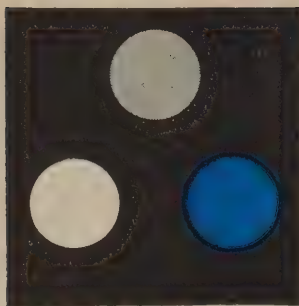

color installation problems

Fuzz tells Red of his problems during his latest color job—red and green dots are like horsefeathers; they're all over

By **BOB MIDDLETON***
TELEVISION CONSULTANT

// PULLED your egg and forgot to wreck it," Bess apologized.

"Skip it," Fuzzball replied. "At least you didn't forget it entirely."

Turning with a hurt look to Red, he said, "Did you do me dirty the other day?"

"Did I?" asked Red noncommittally.

"Yes, you dog, you did."

"What now?"

"You told me that the blue lateral corrector moves the blue beam left and right on the screen, didn't you?"

"Sure did," Red replied.

"Then why doesn't it do what you say?"

"Maybe the blue lateral corrector was mounted in the 2 o'clock position on the picture tube's neck."

"You mean that makes a difference?" asked Fuzzball in amazement.

"Looks like you found out the hard way," Red observed. "Reckon I ought to have told you. There are two ways to mount the corrector magnet."

"Now you tell me," Fuzzball protested. "Here I am slowly going crazy trying to remember everything you said, and you didn't even say it."

Bess dropped the corner of her mouth open. "You've gone, boy, if you ask me."

"Nobody . . ." Fuzz started to say, as Red reached for the sugar and stuck his elbow in Fuzzball's mouth.

"Yes," continued Red, "on some sets you'll find the corrector magnet is *not* mounted directly over the blue gun. Instead, it's turned to the 2 o'clock position, if you call the blue gun 12 o'clock."

"Why?" Fuzz asked.

"Gives a little better purity, that way," Red explained.

Where's 2 o'clock?

"I see," Fuzzball said, nodding his head slowly. Then a crafty look crossed

his face. "Do you mean 2 o'clock standing in front or behind the set?"

"Well, let's put it this way," Red replied, "just remember that the 2 o'clock position is between the blue and green guns."

"I guess that ties it down OK," admitted Fuzzball, "but will you or can you explain that crazy motion I was fighting on the blue dot?"

Red lit a fag thoughtfully, and then replied, "It is a little harder to get the color dots together, with a 2 o'clock corrector."

"You're the guy that's making it hard," Fuzzball protested. "Why don't you tell me these things before I go out on the job?"

"Look, Fuzz," Red replied evenly, "life is like that. Who do you suppose told *me*? Nobody, but nobody. It's lumps on the head."

"Excuse me for living," Fuzzball said resignedly, "but how *does* the blue dot move?"

"It moves in a sort of an ellipse. Here, Fuzz. Here is a drawing that I tore out of RADIO-ELECTRONICS. Glom on to that." (See Fig. 1.)

"Dig them crazy dots," Fuzzball remarked. "That's what makes it so rough—the red and green dots are like horse feathers—they're all over."

"But not so much," Red observed. "The blue dots move the most."

"It's a lot tougher to bring in a blue dot on an ellipse than on a straight line," Fuzzball bellyached.

Red exhaled a perfect smoke ring, making no comment.

"I'm just lucky I could stall on the job until tomorrow," Fuzzball continued.

"It is a little tougher to converge the blue dots with a 2 o'clock corrector," Red finally agreed. "But it's still a lot easier than making the dynamic convergence."

"Don't remind me," Fuzzball groaned.

"How did you make out on the purity?" Red asked.

"I fought it for a while, and finally ended up with the degaussing coil, and got it looking OK."

"Tell you what," Red remarked, "I was talking to Jack Darr, and he recommends that we should degauss picture tubes as a matter of course."

"Before we adjust the purity?"

"Yep. The way Jack puts it, you save time on the average. It makes a lot of sense."

"Are you going to follow Jack's advice?" asked Fuzz.

"Sure am," Red replied. "That's a shop rule from now on."

"How's Jack making out with this color racket?"

"Good enough, it seems," Red replied. "But he sure got hold of a weird dog last week, on black-and-white."

"What's the scoop?"

"Well, this was a Raytheon, last year's model—14AY21, or something like that. Had pix and no sound. On turning the *volume* control full up, it gave a fairly good picture. But, when the volume control was turned down, the picture quietly folded up in the middle, overlapped, pulled in from the sides, and the screen went black."

"What could cause that?" asked Fuzzball.

"Well, that's a good question," Red remarked. "I couldn't figure it, myself. He explained that a coupling capacitor had shorted from the plate line to the audio grid, so that it was grounded at one end by action of the volume control."

"Why did the screen go black?" asked Fuzzball with a puzzled look.


"Well," Red explained, "he pointed out that this grounded the 150-volt line which supplies plate voltage to the horizontal oscillator."

"That's the d.....t symptom I ever heard of," Fuzzball said, shaking his head.

"Worse than the 2 o'clock lateral corrector?" asked Red with a grin.

"I hate to admit it, but the lateral

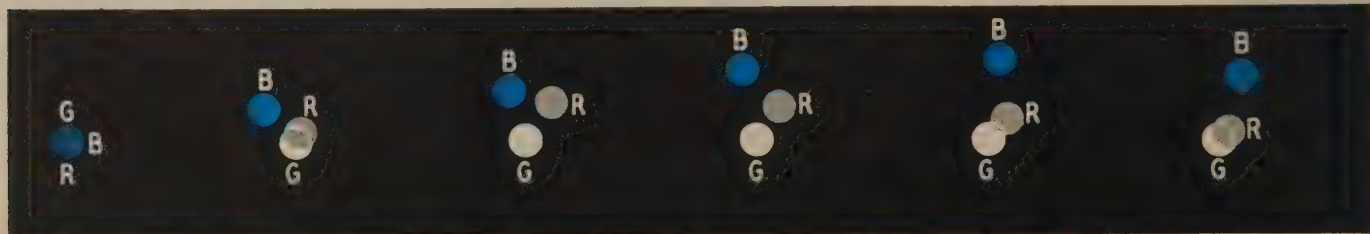* Author, *Servicing Color TV and Sweep and Marker Generators for Television and Radio* (Gernsback Library).



deal is a breeze compared to something like that," Fuzzball said meekly.

"How did you make out on dynamic convergence?" Red asked.

"Tell you the truth . . ." Fuzzball started.

"Do so, by all means," Red encouraged him.

"I got so fouled up on the 2 o'clock corrector that I never got that far."

"We all go through the same mill," Red advised him. "Dame History is a very old lady and likes to repeat herself."

Dynamic-convergence tips

"Can you give me some handy-dandy tips to save headaches on the dynamic convergence?" Fuzzball asked.

"I wouldn't be splashed," agreed Red. "Just remember, No. 1, that you bear down on the vertical dynamic convergence before going to the horizontal."

"I won't forget," Fuzz promised.

"And No. 2, it helps to start the job with crosshatch, instead of white dots."

"Why?" asked Fuzzball.

"Simply because we start the dynamic job by lining up the red and green columns to make them straight and parallel. Look, here's a photo." (See Fig. 2.)

"You say it's easier to start with lines than with dots?" Fuzz persisted.

"My opinion is yes," Red asserted. "Maybe you wouldn't agree, but take a look at this other photo showing the dot deal. See the difference?" (See Fig. 3.)

Fuzzball compared the photos carefully. "I would go along," he announced. "It's quite a bit easier to size up the columns on the crosshatch pattern."

"Thank you, Mr. F." Red returned humbly. "I am greatly honored to have my own judgment confirmed by no less an authority than yourself."

"Cut the sarcasm," Fuzz said, "anyone would think I was a Ph.D. or something, trying to fix his own TV set."

"What's a Ph.D.?" asked Red innocently.

Fuzzball looked sharply at Red, to see if he was joking. His face was blank.

"For your information," said Fuzzball, "a Ph.D. is a degree from an institution—it means piled high and deep, or something like that."

"Do you notice anything about this photo (Fig. 2)?" Red asked.

"The blue line is out," Fuzzball suggested.

"Right," Red agreed. "You don't have to cut off the blue gun, but lot's of guys figure it makes things less confusing to start."

"Tell me something, now," Fuzzball blurted.

"OK."

"On this interaction business that drives me nuts, what effect do the blue vertical amplitude and blue vertical tilt have on red and green lines?"

"There's some interaction," Red advised him.

"So, even after I get the red and green lines straightened up, I can't forget about them until after the blue has been brought in?"

"They'll be giving you a gold star on your report card," Red remarked. "Just remember one thing, now. Set up the red and green lines with the crosshatch, like we've been saying. But bring in the blue gun on the dots."

"Any fool can see that," agreed Fuzzball. "I can see it."

"You might remember it," suggested Red, "by making it a rule to always start a job with crosshatch and always end with dots."

"By a job I guess you mean static convergence, vertical dynamic and horizontal dynamic—that would make three jobs."

"You're right in the groove, Buddy," Red agreed.

Horizontal yoke balancer?

"There's just one thing that's got me in the dark," Fuzzball recalled, "and that's a little coil on top of the deflection yoke. Motorola I worked on yesterday had it. There's a slug can be slid up and down in the coil."

"Old Eagle-Eye Fuzzball," Red exclaimed, patting him on the back. "Yep, that's part of the convergence line-up on that model. That, Fuzz, is a horizontal yoke balancer."

"OK, you joker," Fuzzball replied, "What's a yoke balancer?"

"Well, on a color set, the yoke is very critical. If there's a little more inductance in one coil than the other, edge convergence won't come in right. The nearer the edge you get, the more serious it becomes. So, the yoke balancer is a gismo which lets you add or subtract a little inductance on one coil and throw it over to the other."

"What's that got to do with the price of peas?"

"Well, you don't worry about the yoke balancer until you get near the end of the horizontal convergence. Then, when you have the dots pretty well in, except for the ends of the pattern, you diddle with the yoke balancer."

"So I suppose I have interaction between the horizontal controls and the yoke balancer, already."

"A little," Red agreed. "But it's a small price to pay for the improvement in edge convergence."

"Next thing you know," Fuzzball predicted, "we'll be having vertical yoke

balancers too."

"We already have," Red advised him. "The 21-inch model has both horizontal and vertical balancers."

"Great gosh and little goldfish," Fuzzball exclaimed.

"Relax, man," Red suggested. "I realize that the yoke balancers and the dynamic controls make 14 adjustments to fiddle with. But it's like learning to play horsetail poker—you got kings and queens and aces and deuces and four colors instead of three. But I never saw you in no bind in horsetail poker."

"That's different," Fuzzball protested. "But tell me, how long should I take to tame them little color dots?"

"The boss gives you three days on your first job," Red advised, "but he charges the set owner for a half hour of convergence time."

"You mean the shop's losing money on me?" asked Fuzzball in an unbelieving tone.

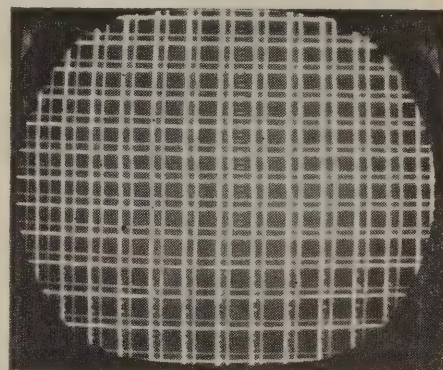


Fig. 2—The red and green columns must be lined up straight and parallel with each other.

"No," said Red, "at least I don't figure it is. The boss is investing money in you—leastways, he's taking a calculated risk as he says, and hopes that it's an investment."

"I never thought of it quite like that," Fuzzball remarked.

"Them's the conditions that prevail," Red advised.

A grin crossed Fuzzball's face. "Suppose I throw in the sponge?" he asked.

"You'll get stomped," Red promised.

"Can I make a suggestion?" Bess asked, and without waiting for a reply, said, "Don't just sit there, boys—buy something."

"OK. Couple cups of mud and sinkers, Bess. How was the egg, Fuzzball?" Red asked.

Fuzzball cast a wary eye in Bess' direction and lowered his voice. "I was

(Continued on page 76)

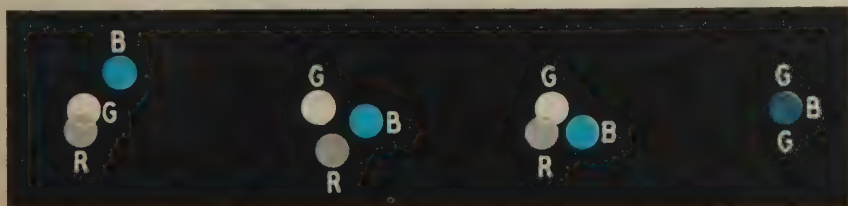


Fig. 1—Motions of the blue, red and green dots when a 2 o'clock lateral corrector is adjusted.



Mail Early and Avoid Christmas RUSH

FIRST CLASS
PERMIT 3062
New York, N. Y.

BUSINESS REPLY ENVELOPE

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY

Radio-Electronics

154 WEST 14TH STREET

NEW YORK 11, N. Y.



You'll get plenty of these detailed pictorial diagrams in your Heathkit construction manual to show where each and every wire and part is to be placed. Everything you do is spelled out in pictures so you can't go wrong.

That's what makes it such fun!

and here's why...

1. You get higher quality at lower cost by dealing direct, and by doing your own assembly.
2. You receive personal, friendly, service (before and after sale) for complete satisfaction.
3. You benefit from the latest in engineering designs because of our concentration on kit-form equipment only.
4. You may depend on performance as advertised—backed by Heath's world-wide reputation for quality.
5. You can take a full year to pay with the HEATH EASY TIME PAYMENT PLAN.

and a thrill to own!

- (✓) Connect a 22 K Ω resistor (red-red-orange) from socket C1 (NS) to ground lug C9 (NS). See Figure 8.
- (✓) Connect a .005 μ f disc capacitor from socket C4 (NS) to IF transformer Q4 (NS).
- () Bend socket lug C5 and IF transformer lug Q3 toward each other until they make contact and overlap slightly. Solder the connection securely. (1).
- () Install a .005 μ f capacitor from socket C4 (NS) to ground lug C9 (NS). Dress the capacitor close to chassis, under the capacitor previously installed.

Read the step . . . perform the operation . . . and check it off—it's just that simple. These plainly-worded, easy-to-follow, steps are combined with pictorial diagrams to take you through every phase of assembly. Let our experience be your teacher!

TIME PAYMENTS . . .

The Heath Time Payment Plan was designed for your convenience. Now, you can order the kits of your choice, and pay for them in small monthly installments. Write for full details.

HEATHKIT EXTRA PERFORMANCE 70-WATT AMPLIFIER KIT

For really high performance, with plenty of reserve power, the W-6M is a natural. The full 70-watts output will seldom, if ever, be required. However, this reserve insures distortion-less sound on power peaks. The W-6M will loaf along at normal listening levels and yet is always ready to extend itself when program material demands it, without the least amount of strain. The output circuit employs 6550 tubes with a special-design Peerless output transformer for maximum stability at all power levels. A quick-change plug selects 4, 8 and 16 ohms or 70-volt output and the correct feedback resistance. A variable damping control is also provided for optimum performance with any speaker system. Extremely good power supply regulation is possible through the use of a heavy-duty transformer along with silicon-diode rectifiers, which are noted for their very long life, and yet are smaller than a house fuse. Frequency response at 1 watt is ± 1 db from 5 cps to 80 kc with controlled hf rolloff above 100 kc. At 70 watts output harmonic distortion is below 2%, 20 to 20,000 cps and IM distortion below 1%, 60 and 6,000 cps. Hum and noise 88 db below full output. In addition to high performance, its fine appearance makes it a pleasure to display in your living room. Proper layout of chassis insures ease of assembly by eliminating those cramped and difficult places to get at. Clear instructions—and top-quality components. Get started now and make this amplifier the heart of your hi-fi system. Shipped express only. Shpg. Wt. 50 lbs.

MODEL W-6M

\$109⁹⁵

MODEL W-6: Consists of W-6M kit, plus WA-P2 preamplifier. Express only. Shpg. Wt. 59 lbs. \$129.70

HEATHKIT HIGH FIDELITY FM TUNER KIT

This tuner can bring you a rich store of FM programming, your least expensive source of high fidelity material. It covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. Features broadbanded circuits for full fidelity, and better than 10 uv sensitivity for 20 db of quieting, to pull in stations with clarity and full volume. Employs a high gain, cascode RF amplifier, and has AGC. A ratio detector provides high-efficiency demodulation without sacrificing hi-fi performance. IF and ratio transformers are prealigned, as is the front end tuning unit. Special alignment equipment is not necessary. Edge-lighted glass dial for easy tuning. Here is FM for your home at a price you can afford. Shpg. Wt. 8 lbs.

MODEL FM-3A

\$25⁹⁵

(with cabinet)

HEATHKIT BROADBAND AM TUNER KIT

This AM tuner was designed especially for high fidelity applications. It incorporates a special detector using crystal diodes, and the IF circuits feature broad band-width, to insure low signal distortion. Audio response is ± 1 db from 20 cps to 9 kc, with 5 db of preemphasis at 10 kc to compensate for station rolloff. Sensitivity and selectivity are excellent, and tuner covers complete broadcast band from

550 to 1600 kc. Quiet performance is assured by 6 db signal-to-noise ratio at 2.5 UV. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs, and built-in power supply. Edge-lighted glass slide-rule dial for easy tuning. Your "best buy" in an AM tuner. Shpg. Wt. 8 lbs.

MODEL BC-1A

\$25⁹⁵

(with cabinet)

HEATHKIT MASTER CONTROL PREAMPLIFIER KIT


Designed for use with any of the Williamson-type amplifiers, the WA-P2 has five switch-selected inputs, each having its own level control to eliminate blasting or fading while switching through the various inputs, plus a tape recorder output. A hum control allows setting for minimum hum level. Frequency response is within $\pm 1\frac{1}{2}$ db from 15 to 35,000 cps. Equalization provided for LP, RIAA, AES, and early 78's. Separate bass and treble controls. Low impedance cathode follower output circuit. All components were specially selected for their high quality. Includes many features which will eventually be desired. Shpg. Wt. 7 lbs.

MODEL WA-P2


\$19⁷⁵

(with cabinet)

*An amplifier
you will be
proud to own*

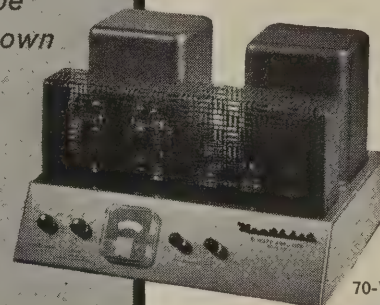

70-WATT
AMPLIFIER

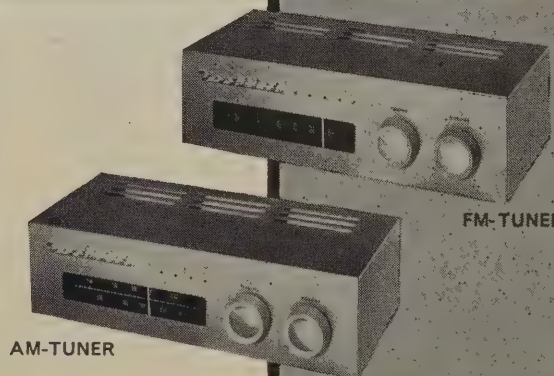

AM-TUNER

FM-TUNER

*Selects and
controls sound
to your taste*




PREAMPLIFIER




**ADVANCED-DESIGN
25-WATT AMPLIFIER**

*Top performance
in its
power class!*

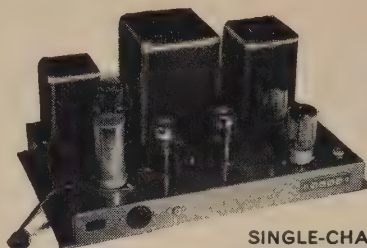

**SINGLE-CHASSIS
20-WATT AMPLIFIER**

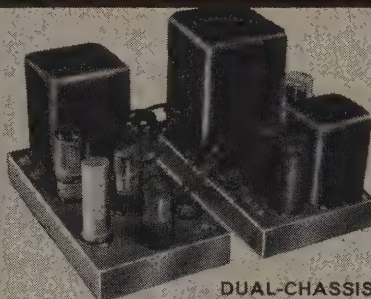*Hi-Fi equipment
for your listening
pleasure!*



**DUAL-CHASSIS
20-WATT AMPLIFIER**



**GENERAL-PURPOSE
20-WATT AMPLIFIER**

HEATHKIT ADVANCED-DESIGN 25-WATT HIGH FIDELITY AMPLIFIER KIT

Designed especially to satisfy critical audio requirements, the W-5M incorporates the extra features needed to complement the finest in program sources and speaker systems. Faithful sound reproduction is assured with a frequency response of ± 1 db from 5 to 160,000 cps at 1 watt, and harmonic distortion is less than 1% at 25 watts, with IM distortion less than 1% at 20 watts. Hum and noise are a full 99 db below rated output, assuring quiet, hum-free operation. Output taps are 4, 8 and 16 ohms. Exclusive Heathkit features include the "tweeter saver", and the "bas-bal" balancing circuit, requiring only a voltmeter for indication. Years of reliable service are guaranteed through the use of conservatively rated, high quality components. KT66 tubes and Peerless output transformer are typical. Shipped express only. Shpg. Wt. 31 lbs.

MODEL W-5: Consists of W-5M kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 38 lbs. \$79.50

MODEL W-5M
\$59⁷⁵

HEATHKIT DUAL-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W3-AM is a Williamson-type amplifier built on two separate chassis. The power supply is on one chassis, and the amplifier stages are on the other chassis. Using two separate chassis provides additional flexibility in installation. Features include the famous acrosound model TO-300 "ultralinear" output transformer and 5881 tubes for broad frequency response, low distortion, and low hum level. The result is exceptionally fine overall tone quality. Frequency response is ± 1 db from 6 cps to 150 kc at 1 watt. Harmonic distortion is less than 1% and IM distortion is less than 1.3% at 20 watts. Hum and noise are 88 db below 20 watts. Designed to match the speaker system of your choice, with taps for 4, 8 or 16 ohms impedance. A very popular high fidelity unit employing top quality components throughout. Shipped express only. Shpg. Wt. 29 lbs.

MODEL W-3A: Consists of W-3AM kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 37 lbs. \$69.50

MODEL W-3AM
\$49⁷⁵

HEATHKIT SINGLE-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W4-AM Williamson-type amplifier will amaze you with its outstanding performance. A true Williamson circuit, featuring extended frequency response, low distortion, and low hum levels, this amplifier can provide you with many hours of listening enjoyment with only a minimum investment compared to other units on the market. 5881 tubes and a special Chicago-standard output transformer are employed to give you full fidelity at minimum cost. Frequency response extending from 10 cps to 100 kc within ± 1 db at 1 watt assures you of full coverage of the audio range, and clean clear sound amplification takes place in circuits that hold harmonic distortion at 1.5% and IM distortion below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps on the output transformer are at 4, 8 or 16 ohms. Shipped express only. Shpg. Wt. 28 lbs.

MODEL W-4A: Consists of W-4AM kit above, plus model WA-P2 preamplifier. Express only. Shpg. Wt. 35 lbs. \$59.50.

MODEL W4-AM
\$39⁷⁵

Heathkits...

By DAYSTROM

*bring you the lasting satisfaction
of personal accomplishment*

HEATHKIT GENERAL-PURPOSE 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model A-9C will provide you with high quality sound at low cost. Features a built-in preamplifier with four separate inputs, and individual volume, bass and treble controls. Frequency response covers 20 to 20,000 cps within ± 1 db. Total harmonic distortion is less than 1% at 3 db below rated output. Push-pull 6L6 tubes are used, with output transformer tapped at 4, 8, 16 and 500 ohms. A true hi-fi unit using high-quality components throughout, including heavy-duty "potted" transformers. Shpg. Wt. 23 lbs.

MODEL A-9C
\$35⁵⁰

HEATHKIT "BASIC RANGE" HI-FI SPEAKER SYSTEM KIT

The extremely popular Heathkit model SS-1 Speaker System provides amazing high fidelity performance for its size. Features two high-quality Jensen speakers, an 8" mid-range woofer and compression-type tweeter with flared horn. Covers from 50 to 12,000 CPS within ± 5 db, in a special-design ducted-port, bass reflex enclosure. Impedance is 16 ohms. Cabinet measures $11\frac{1}{2}$ " H x $23\frac{1}{2}$ " W x $11\frac{3}{4}$ " D. Constructed of veneer-surfaced plywood, $\frac{1}{2}$ " thick, suitable for light or dark finish. All wood parts are pre-cut and pre-drilled for easy, quick assembly. Shpg. Wt. 30 lbs.

MODEL SS-1

\$39⁹⁵

HEATHKIT "RANGE EXTENDING" HI-FI SPEAKER SYSTEM KIT

Extends the range of the SS-1 to ± 5 db from 35 to 16,000 CPS. Uses 15" woofer and super-tweeter both by Jensen. Kit includes crossover circuit. Impedance is 16 ohms and power rating is 35 watts. Measures 29" H x 23" W x $17\frac{1}{2}$ " D. Constructed of veneer-surfaced plywood $\frac{3}{4}$ " thick. Easy to build! Shpg. Wt. 80 lbs.

MODEL SS-1B

\$99⁹⁵

HEATHKIT "LEGATO" HIGH FIDELITY SPEAKER SYSTEM KIT

The quality of the Legato, in terms of the engineering that went into the initial design, and in terms of the materials used in its construction, is matched in only the most expensive speaker systems available today. The listening experience it provides approaches the ultimate in esthetic satisfaction. Two 15" theater-type Altec Lansing speakers cover 25 to 500 CPS, and an Altec Lansing high-frequency driver with sectoral horn covers 500 to 20,000 CPS. A precise amount of phase shift in the crossover network brings the high frequency channel into phase with the low frequency channel to eliminate peaks or valleys at the crossover point, by equalizing the acoustical centers of the speakers. The enclosure is a modified infinite baffle type, especially designed for these speakers. Cabinet is constructed of veneer-surfaced plywood, $\frac{3}{4}$ " thick, pre-cut and pre-drilled for easy assembly. Frequency response 25 to 20,000 CPS. Power rating, 50 watts program material. Impedance is 16 ohms. Cabinet dimensions 41" L x $22\frac{1}{4}$ " D x 34" H.

Choice of two beautiful cabinets. Model HH-1-C in imported white birch for light finishes, and HH-1-CM in African mahogany for dark finishes. Shpg. Wt. 195 lbs.

MODEL HH-1-C
MODEL HH-1-CM

\$325⁰⁰
EACH

Heathkits...

By DAYSTROM

*let you save up to $\frac{1}{2}$
or more on all types
of electronic equipment.*

HEATHKIT SINE-SQUARE GENERATOR

The new AG-10 provides high quality, sine and square waves over a wide range, for countless applications. Some of these are; radio and TV repair work, checking scope performance, as a variable trigger source for telemetering and pulse work, and checking audio, video and hi-fi amplifier response. Frequency response is ± 1.5 db from 20 CPS to 1 MC on both sine and square waves, with less than .25% sine wave distortion, 20 to 20,000 CPS. Sine wave output impedance 600 ohms, square wave output impedance 50 ohms, (except on 10v ranges). Square wave rise time less than .15 usec. Five-position band switch—continuously variable tuning—shielded oscillator circuit—separate step and variable output attenuators in ranges of 10, 1, and .1 volts for both sine and square wave, with extra range of .01 volt on sine wave. Both sine and square wave can be used at the same time without affecting either wave form. Power supply uses silicon-diode rectifiers. Shpg. Wt. 12 lbs.

MODEL AG-10


\$49⁹⁵

HEATHKIT AUDIO ANALYZER KIT


The AA-1 is actually three instruments in one compact package. It combines the functions of an AC VTVM, an audio wattmeter, and an intermodulation analyzer. Input and output terminals are combined, and high and low frequency oscillators are built in. VTVM ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts (RMS). Wattmeter ranges are .15 mw, 1.5 mw, 15 mw, 150 mw, 1.5 w, 15 w and 150 w. IM scales are 1%, 3%, 10%, 30% and 100%. Provides internal load resistors of 4, 8, 16 or 600 ohms. A tremendous dollar value. Shpg. Wt. 13 lbs.

MODEL AA-1

\$49⁹⁵

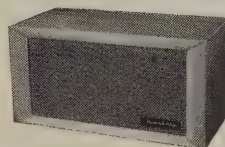


"BASIC RANGE" HI-FI
SPEAKER SYSTEM

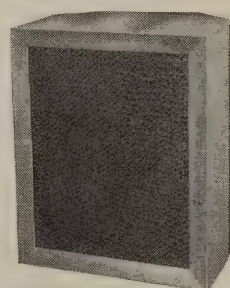


"RANGE EXTENDING"
HI-FI SPEAKER SYSTEM

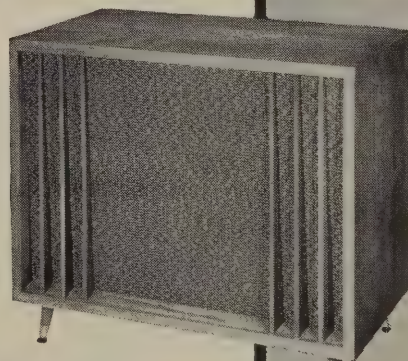
*Superlative
sound reproduction
through the speaker
system of your choice*



"LEGATO" HI-FI
SPEAKER SYSTEM

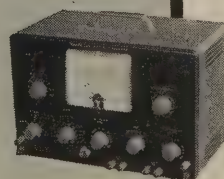


AUDIO
ANALYZER

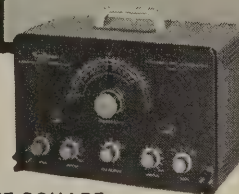

SINE-SQUARE
GENERATOR

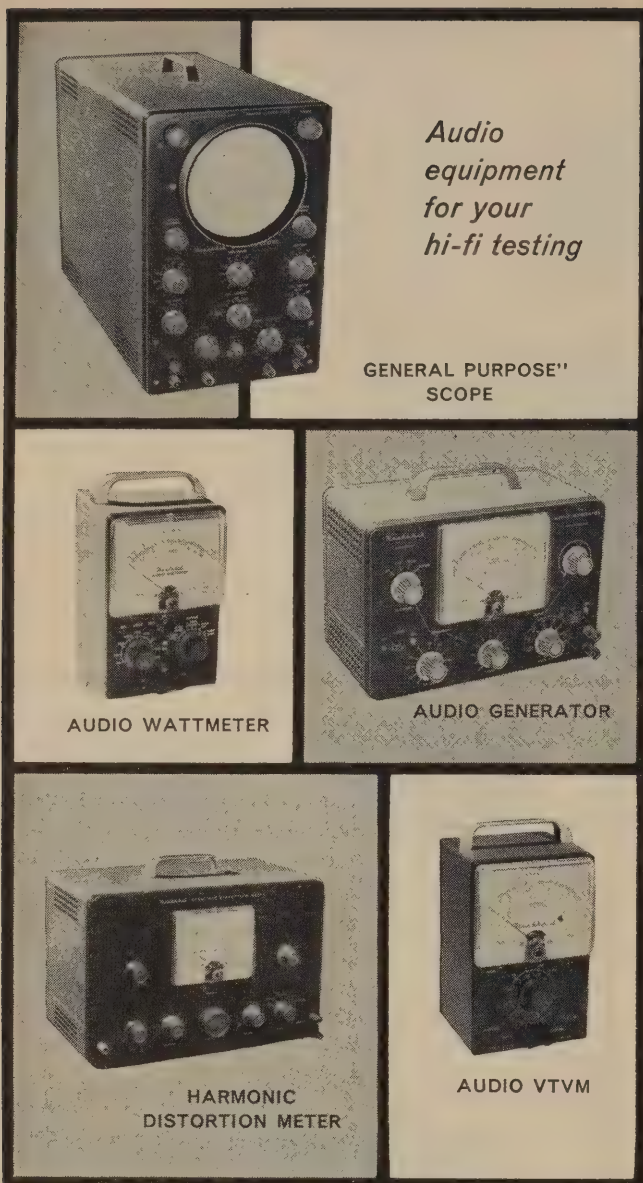*Sine and square
waves for countless
applications.*



*Audio
equipment
for your
hi-fi testing*

**GENERAL PURPOSE"
SCOPE**

AUDIO WATTMETER

AUDIO GENERATOR

**HARMONIC
DISTORTION METER**

AUDIO VTVM

HEATHKIT "GENERAL PURPOSE" 5" OSCILLOSCOPE KIT

The model OM-2 Oscilloscope is especially popular with part-time service technicians, students, and high fidelity enthusiasts. It features good vertical frequency response ± 3 db from 4 cps to over 1.2 mc. A full five-inch crt, and sweep generator operation from 20 cps to over 150 kc. Stability is excellent and calibrated grid screen allows precise signal observation. Extra features include external or internal sweep and sync, 1-volt peak-to-peak calibrating reference, 3-position step-attenuated input, adjustable spot shape control, push-pull horizontal and vertical amplifiers, and modern etched-metal circuits. Easy to build and a pleasure to use. Ideal for use with other audio equipment for checking amplifiers. Shpg. Wt. 21 lbs.

MODEL OM-2

\$42⁵⁰

HEATHKIT AUDIO WATTMETER KIT

The AW-1 Audio Wattmeter can be used in any application where audio power output is to be measured. Non-inductive LOAD resistors are built in for 4, 8, 16 or 600 ohms impedance. Five power ranges cover 0.5 mw, 50 mw, 500 mw, 5 w, and 50 w full scale. Five switch-selected db ranges cover -10 db to +30 db. All indications are read directly on a large $4\frac{1}{2}$ " 200 microampere meter. Frequency response is

± 1 db from 10 cps to 250 kc. Precision type multiplier resistors used for high accuracy, and crystal diode bridge for wide-range frequency response. This meter is used in many recording studios and broadcast stations as a monitor as well as servicing. A fine meter to help supply the answers to your audio operating or power output problems. Shpg. Wt. 6 lbs.

MODEL AW-1

\$29⁵⁰

HEATHKIT AUDIO SIGNAL GENERATOR KIT

The model AG-9A is "made to order" for high fidelity applications, and provides quick and accurate selection of low-distortion signals throughout the audio range. Three rotary switches select two significant figures and a multiplier to determine audio frequency. Incorporates step-type and a continuously variable output attenuator. Output indicated on large $4\frac{1}{2}$ " panel meter, calibrated in volts and db. Attenuator system operates in 10 db steps, corresponding to meter calibration, in ranges of 0.003, .01, .03, .1, .3, 1.3 and 10 volts RMS. "Load" switch permits use of built-in 600-ohm load, or external load of different impedance. Output and frequency indicators accurate to within $\pm 5\%$. Distortion less than .1 of 1% between 20 and 20,000 cps. Total range is 10 cps to 100 kc. Shpg. Wt. 8 lbs.

MODEL AG-9A

\$34⁵⁰

HEATHKIT HARMONIC DISTORTION METER KIT

All sounds consist of dominant tones plus harmonics (over-tones). These harmonics enrich the quality and brightness of the music. However, additional harmonics which originate in the audio equipment, represent distortion. Used with an audio signal generator, the HD-1 will accurately measure this harmonic distortion at any or all frequencies between 20 and 20,000 cps. Distortion is read directly on the panel meter in ranges of 0-1, 3, 10, 30 and 100% full scale. Voltage ranges of 0-1, 3, 10 and 30 volts are provided for the initial reference settings. Signal-to-noise ratio measurements are also permitted through the use of a separate meter scale calibrated in db. High quality components insure years of outstanding performance. Full instructions are provided. Shpg. Wt. 13 lbs.

MODEL HD-1

\$49⁵⁰

Heathkits...

By DAYSTROM

*are well known for
their high quality
and reliability.*

HEATHKIT AUDIO VTVM KIT

This new and improved AC Vacuum Tube Voltmeter is designed especially for audio measurements and low-level AC measurements in power supply filters, etc. Employs an entirely new circuit featuring a cascode amplifier with cathode-follower isolation between the input and the amplifier, and between the output stage and the preceding stages. It emphasizes stability, broad frequency response, and sensitivity. Frequency response is essentially flat from 10 cps to 200 kc. Input impedance is 1 megohm at 1000 cps. AC (RMS) voltage ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover -52 db to +52 db. Features large $4\frac{1}{2}$ " 200 microampere meter, with increased damping in meter circuit for stability in low frequency tests. 1% precision resistors employed for maximum accuracy. Stable, reliable performance in all applications. Shpg. Wt. 5 lbs.

MODEL AV-3

\$29⁵⁰

HEATHKIT COLOR BAR AND DOT GENERATOR

The CD-1 combines the two basic color service instruments, a Color Bar Generator and White Dot Generator in one versatile portable unit, which has crystal-controlled accuracy and stability (no external sync lead required). Produces white-dots, cross hatch, horizontal and vertical bars, 10 vertical color bars, and a new shading bar pattern for screen and background adjustments. Variable RF output on any channel from 2 to 6. Positive or negative video output, variable from 0 to 10 volts peak-to-peak. Crystal controlled sound carrier with off-on switch. Voltage regulated power supply using long-life silicon rectifiers. Gain knowledge of a new and profitable field by constructing this kit. Shpg. Wt. 12 lbs.

MODEL CD-1

\$59⁹⁵

Heathkits...

By DAYSTROM

*are guaranteed to
meet or exceed
advertised specifications*

HEATHKIT TV ALIGNMENT GENERATOR KIT

This fine TV alignment generator offers stability and flexibility difficult to obtain even in instruments costing several times this low Heathkit price. It covers 3.6 mc to 220 mc in four bands. Sweep deviation is controllable from 0 to 42 mc. The all-electronic sweep circuit insures stability. Crystal marker and variable marker oscillators are built in. Crystal (included with kit) provides output at 4.5 mc and multiples thereof. Variable marker provides output from 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking to eliminate return trace. Phasing control. Kit is complete, including three output cables. Shpg. Wt. 16 lbs.

MODEL TS-4A

\$49⁵⁰

HEATHKIT "EXTRA DUTY" 5" OSCILLOSCOPE KIT

This fine oscilloscope compares favorably to other scopes costing twice its price. It contains the extra performance so necessary for monochrome and color-TV servicing. Features push-pull horizontal and vertical output amplifiers, a 5UPI CRT, built in peak-to-peak calibration source, a fully compensated 3-position step-type input attenuator, retrace blanking, phasing control, and provision for Z-axis modulation. Vertical amplifier frequency response is within ± 1.5 and -5 db from 3 CPS to 5 MC. Response at 3.58 MC down only 2.2 db. Sensitivity is 0.025 volts RMS / inch at 1 kc. Sweep generator covers 20 CPS to 500 kc in five steps, five times the usual sweep obtained in other scopes through the use of the patented Heath sweep circuit. Etched-metal circuit boards reduce assembly time and minimize errors in assembly, and more importantly, permit a level of circuit stability never before achieved in an oscilloscope of this type. Shpg. Wt. 21 lbs.

MODEL O-11

\$69⁵⁰

HEATHKIT ELECTRONIC SWITCH KIT

A valuable accessory for any oscilloscope owner. It allows simultaneous oscilloscope observation of two signals by producing both signals, alternately, at its output. Four switching rates. Provides gain for input signals. Frequency response ± 1 db, 0 to 100 kc. A sync output is provided to control and stabilize scope sweep. Ideal for observing input and output of amplifiers simultaneously. Shpg. Wt. 8 lbs.

MODEL S-3

\$21⁹⁵

HEATHKIT VOLTAGE CALIBRATOR KIT

This unit is an excellent companion for your oscilloscope. Used as a source of calibrating voltage, it produces near-perfect square wave signals of known amplitude. Precision 1% attenuator resistors insure accurate output amplitude, and multivibrator circuit guarantees good sharp square waves. Output frequency is approximately 1000 CPS. Fixed outputs selected by panel switches are: .03, 0.1, 0.3, 1.0, 3.0, 10, 30 and 100 volts peak-to-peak. Allows measurement of unknown signal amplitude by comparing it to the known output of the VC-3 on oscilloscope. Shpg. Wt. 4 lbs.


MODEL VC-3

\$12⁵⁰

*Functional
styling with
clean uncluttered
look*



COLOR BAR AND
DOT GENERATOR

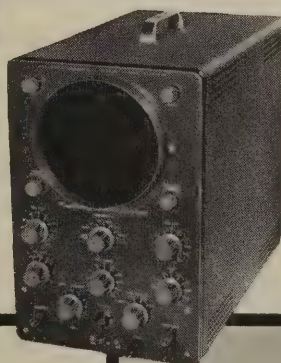


"EXTRA DUTY"
SCOPE



TV ALIGNMENT
GENERATOR



ELECTRONIC
SWITCH

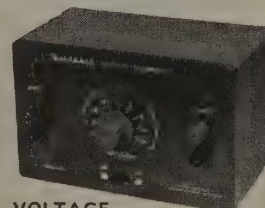

VOLTAGE
CALIBRATOR

HEATHKIT TUBE CHECKER KIT

Eliminate guesswork, and save time in servicing or experimenting. The TC-2 tests tubes for shorted elements, open elements, filament continuity, and operating quality on the basis of total emission. It tests all tube types encountered in radio and TV service work. Sockets are provided for 4, 5, 6 and 7-pin, octal, and loctal tubes, 7 and 9 pin miniature tubes, 5 pin hytron miniatures, and pilot lamps. Tube condition indicated on $4\frac{1}{2}$ " meter with multi-color "good-bad" scale. Illuminated roll chart with all test data built in. Switch selection of 14 different filament voltages from .75 to 117 volts. Color-coded cable harness allows neat professional wiring and simplifies construction. Very easy to build, even for a beginner. Shpg. Wt. 12 lbs.

MODEL TC-2

\$29⁵⁰

HEATHKIT HANDITESTER KIT

The small size and rugged construction of this tester makes it perfect for any portable application. The combination function-range switch simplifies operations. Measures AC or DC voltage at 0-10, 30, 300, 1000 and 5000 volts. Direct current ranges are 0-10 ma and 0-100 ma. Ohmmeter ranges are 0-3000 (30 ohm center scale) and 0-300,000 (3000 ohm center scale). Very popular with home experimenters, electricians, and appliance repairmen. Slips easily into your tool box, glove compartment, coat pocket, or desk drawer. Shpg. Wt. 3 lbs.

MODEL M-1

\$14⁵⁰

HEATHKIT PICTURE TUBE CHECKER KIT

The CC-1 can be taken with you on service calls so that you can clearly demonstrate the quality of a customer's picture tube in his own home. Tubes can be tested without removing them from the receiver or cartons if desired. Checks cathode emission, beam current, shorted elements, and leakage between elements in electromagnetic picture tube types. Self-contained power supply, and large $4\frac{1}{2}$ " meter. CRT condition indicated on "good-bad" scale. Relative condition of tubes fluorescent coating is shown in "shadow-graph" test. Permanent test cable with CRT socket and anode connector. No tubes to burn out, designed to last a lifetime. Luggage-type portable case. Shpg. Wt. 10 lbs.

MODEL CC-1

\$22⁵⁰

HEATHKIT ETCHED-CIRCUIT VTVM KIT

This multi-purpose VTVM is the world's largest selling instrument of its type—and is especially popular in laboratories, service shops, home workshops and schools. It employs a large $4\frac{1}{2}$ " panel meter, precision 1% resistors, etched metal circuit board, and many other "extras" to insure top quality and top performance. It's easy to build, and you may rely on its accuracy and dependability. The V7-A will measure AC (RMS) and DC voltages in ranges of 0-1.5, 5, 15, 50, 150, 500 and 1500. It measures peak-to-peak AC voltage in ranges of 0-4, 14, 40, 140, 400, 1400 and 4000. Resistance ranges provide multiplying factors of X 1, X 10, X 100, X 1000, X 10k, X 100k, and X 1 megohm. Center-scale resistance readings are 10, 100, 1000, 10k, 100k, 1 megohm and 10 megohms. A db scale is also provided. The precision and quality of this VTVM cannot be duplicated at this price. Shpg. Wt. 7-lbs.

MODEL V7-A

\$24⁵⁰

Heathkits...

By DAYSTROM


*let you fill your exact needs
from a wide variety
of instruments*

HEATHKIT 20,000 OHMS/VOLT VOM KIT


This fine instrument provides a total of 25 meter ranges on its two-color scale. It employs a 50 ua $4\frac{1}{2}$ " meter, and features 1% precision multiplier resistors. Requires no external power. Ideal for portable applications. Sensitivity is 20,000 ohms-per-volt DC and 5000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5000 volts, AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are X 1, X 100 and X 10,000, with center-scale readings of 15, 1500 and 150,000 ohms. Covers —10 db to +65 db. Easy to build and fun to use. Attractive bakelite case with plastic carrying handle. Shpg. Wt. 6 lbs.

MODEL MM-1

\$29⁵⁰

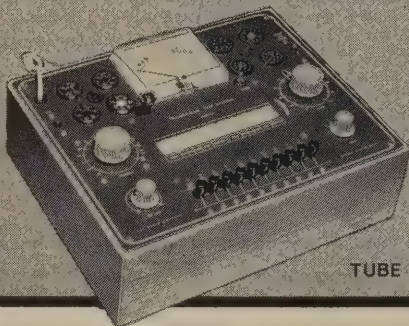

TUBE CHECKER

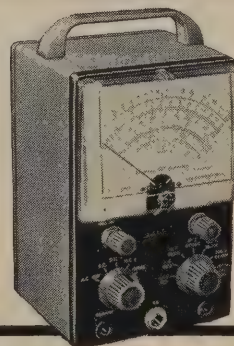

ETCHED
CIRCUIT VTVM

*High quality
test gear you
will be
proud to own*




HANDITESTER

*Priced low
to fit your
budget*



PICTURE TUBE
CHECKER

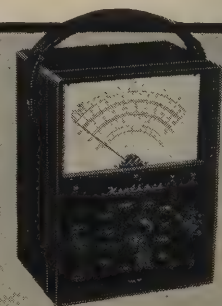

20,000
OHMS/VOLT VOM

HEATHKIT RF SIGNAL GENERATOR KIT

Even a beginner can build this prealigned signal generator, designed especially for use in service work. Produces RF signals from 160 kc to 110 mc on fundamentals in five bands. Covers 110 mc to 220 mc on calibrated harmonics. Low impedance RF output in excess of 100,000 microvolts, is controllable with a step-type and continuously variable attenuator. Selection of unmodulated RF, modulated RF, or audio at 400 CPS. Ideal for fast and easy alignment of radio receivers, and finds application in FM and TV work as well. Thousands of these units are in use in service shops all over the country. Easy to build and a real time saver, even for the part-time service technician or hobbyist. Shpg. Wt. 8 lbs.

MODEL SG-8

\$19⁵⁰

HEATHKIT LABORATORY RF GENERATOR KIT

Tackle all kinds of laboratory alignment jobs with confidence by employing the LG-1. It features voltage-regulated B+, double shielding of oscillator circuits, copper-plated chassis, variable modulation level, metered output, and many other "extras" for critical alignment work. Generates RF signals from 100 kc to 30 mc on fundamentals in five bands. Meter reads RF output in microvolts or modulation level in percentage. RF output available up to 100,000 microvolts, controlled by a fixed-step and a variable attenuator. Provision for external modulation where necessary. Buy and use this high-quality RF signal generator that may be depended upon for stability and accuracy. Shpg. Wt. 16 lbs.

MODEL LG-1

\$48⁹⁵

HEATHKIT DIRECT-READING CAPACITY METER KIT

Here's a fast, simple capacity meter. A capacitor to be checked is merely connected to the terminals, the proper range selected, and the value read directly on the large $4\frac{1}{2}$ " panel meter calibrated in mmf and mfd. Ranges are 0 to 100 mmf, 1,000 mmf, .01 mfd, .1 mfd full scale. Not affected by hand capacity. Shpg. Wt. 7 lbs.

MODEL CM-1

\$29⁵⁰

Heathkits...

By DAYSTROM

*are educational
as well as functional*


HEATHKIT "IN-CIRCUIT" CAPACI-TESTER KIT

With the CT-1 it is no longer necessary to disconnect one capacitor lead to check the part, you can check most capacitors for "open" or "short" right in the circuit. Fast and easy—to save your valuable time in the service shop or lab. Detects open capacitors from about 50 mmf up, so long as the capacitor is not shunted by excessively low resistance value. Will detect shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). (Does not detect leakage.) Employs 60 cycles and 19 megacycle test frequencies. Electron beam "eye" tube used as indicator. Compact, easy-to-build, and inexpensive. Test leads included. Shpg. Wt. 5 lbs.


MODEL CT-1

\$7⁹⁵

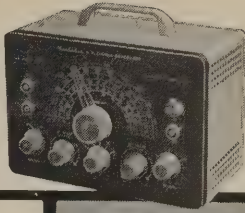
*Use these
kits for faster
and more
efficient testing*




RF SIGNAL
GENERATOR




DIRECT-READING
CAPACITY METER

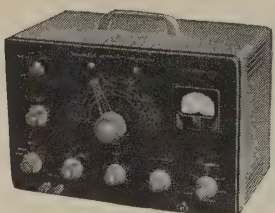


LABORATORY RF
GENERATOR

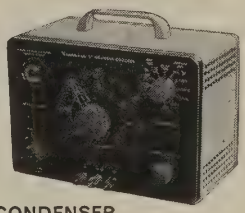

CONDENSER
CHECKER



"IN CIRCUIT"
CAPACI-TESTER



VISUAL-AURAL
SIGNAL TRACER

HEATHKIT CONDENSER CHECKER KIT

This handy instrument uses an electron beam "eye" tube as an indicator to measure capacity in ranges of .00001 to .005 mfd, .5 mfd; 50 mfd and 1000 mfd. Also measures resistance from 100 ohms to 5 megohms in two ranges. Checks paper, mica, ceramic and electrolytic capacitors. Selection of five polarizing voltages. Shpg. Wt. 7 lbs.

MODEL C-3

\$19⁵⁰

HEATHKIT VISUAL-AURAL SIGNAL TRACER KIT

Although designed originally for radio receiver work, the T-3 finds application in FM and TV servicing as well. Features high-gain channel with demodulator probe, and low-gain channel with audio probe. Traces signals in all sections of radio receivers and in many sections of FM and TV receivers. Built-in speaker and electron beam eye tube indicate relative gain, etc. Also features built-in noise locator circuit. Provision for patching speaker and/or output transformer to external set. Shpg. Wt. 9 lbs.

MODEL T-3

\$23⁵⁰

HEATHKIT IMPEDANCE BRIDGE KIT

The model IB-2A employs a Wheatstone Bridge, a Capacity Comparison Bridge, a Maxwell Bridge, and a Hay Bridge in one compact package. Measures resistance from 0.1 ohm to 10 megohms, capacitance from 100 mmf to 100 mfd, inductance from 0.1 mh to 100 h, dissipation factor (D) from 0.002 to 1, and storage factor (Q) from 0.1 to 1000. A 100-0-100 ua meter provides for null indications. The decade resistors employed are of 1% tolerance for maximum accuracy. Completely self-contained. Has built in power supply, 1000-cycle generator, and vacuum-tube detector. Special two-section CRL dial insures convenient operation. Instruction manual has entirely new schematic that clarifies circuit functions in various switch positions. A true laboratory instrument, that will provide you with many years of fine performance. Shpg. Wt. 12 lbs.

MODEL IB-2A

\$59⁵⁰

HEATHKIT "LOW RIPPLE" BATTERY ELIMINATOR KIT

This modern battery eliminator incorporates an extra low-ripple filter circuit so that it can be used to power all the newest transistor-type circuits requiring 0 to 12 volts DC,

and the new "hybrid" automobile radios using both transistors and vacuum tubes. Its DC output, at either 6 or 12 volts, contains less than .3% AC ripple. Separate output terminals are provided for low-ripple or normal filtering. Supplies up to 15 amps on 6 volt range or up to 7 amps on 12 volt range. Output is variable from 0 to 8 or 0 to 16 volts. Two meters constantly monitor output voltage and current. Will also double as a battery charger. Shpg. Wt. 23 lbs.

MODEL BE-5

\$39⁹⁵

HEATHKIT ISOLATION TRANSFORMER KIT

The model IT-1 is one of the handiest units for the service shop, home workshop or laboratory. Provides complete isolation from the power line. AC-DC sets may be plugged directly into the IT-1 without the chassis becoming "hot". Output voltage is variable from 90 volts to 130 volts allowing checks of equipment under adverse conditions such as low line voltage. Rated for 100 volt amperes continuously or 200 volt amperes intermittently. Panel meter monitors output voltage. Shpg. Wt. 9 lbs.

MODEL IT-1

\$16⁵⁰

Heathkits...

By DAYSTROM

*are designed with high-quality,
name-brand components to
insure long service life*

HEATHKIT "Q" METER KIT

At this price the laboratory facilities of a Q Meter may be had by the average service technician or home experimenter. The Q Meter permits measurement of inductance from 1 microhenry to 10 millihenry, "Q" on a scale calibrated up to 250 full scale, with multipliers of 1 or 2, and capacitance from 40 mmf to 450 mmf \pm 3 mmf. Built in oscillator permits testing components from 150 kc to 18 mc. Large 4½" panel meter is featured. Very handy for checking peaking coils, chokes, etc. Use to determine values of unknown condensers, both variable and fixed, compile data for coil winding purposes, or measure RF resistance. Also checks distributed capacity and Q of coils. No special equipment is required for calibration. A special test coil is furnished, along with easy-to-follow instructions. Shpg. Wt. 14 lbs.

MODEL QM-1


\$44⁵⁰

HEATHKIT REGULATED POWER SUPPLY KIT

Here is a power supply that will provide DC plate voltage and AC filament voltage for all kinds of experimental circuits. The DC supply is regulated for stability, and yet the amount of DC output voltage available from the power supply can be controlled manually from 0 up to 500 volts. At 450 volts DC output, the power supply will provide up to 10 ma of current, and provide progressively higher current as the output voltage is lowered. Current rating is 130 ma at 200 volts output. In addition to furnishing B+ the power supply also provides 6.3 volts AC at up to 4-amperes for filaments. Both the B+ output and the filament output are isolated from ground. Ideal unit for use in laboratory, home workshop, ham shack, or service shop. A large 4½" meter on the front panel reads output voltage or output current, selectable with a panel switch. Shpg. Wt. 17 lbs.


MODEL PS-3

\$35⁵⁰

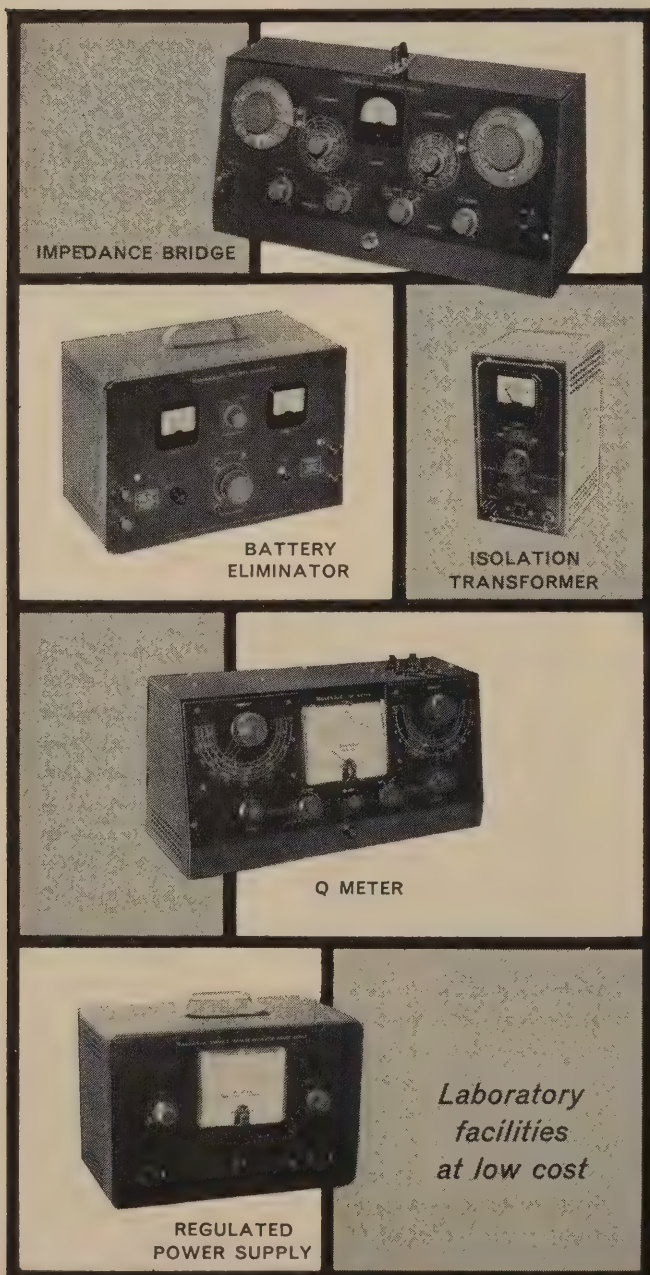



*Terrific values
in amateur
equipment!*

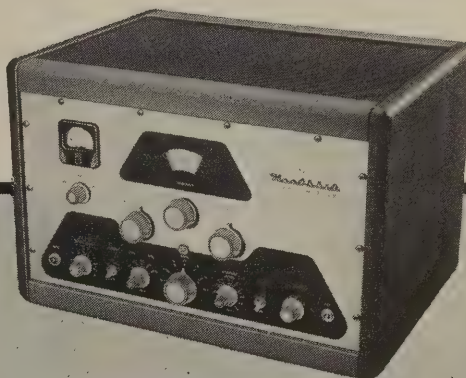

DX-100 TRANSMITTER



DX-20 TRANSMITTER



DX-35 TRANSMITTER

HEATHKIT DX-20 CW TRANSMITTER KIT

The Heathkit model DX-20 "straight-CW" transmitter features high efficiency at low cost. It uses a single 6DQ6A tube in the final amplifier stage for plate power input of 50 watts. A 6CL6 serves as crystal oscillator, with a 5U4GB rectifier. It is an ideal transmitter for the novice, as well as the advanced-class CW operator. Single-knob band switching is featured to cover 80, 40, 20, 15, 11 and 10 meters. Pi network output circuit matches various antenna impedances between 50 and 1000 ohms and reduces harmonic output. Top-quality parts are featured throughout, including "potted" transformers, etc., for long life. It has been given full "TVI" treatment. Access into the cabinet for crystal changing is provided by a removable metal pull-out plug on the left end of the cabinet. Very easy to build from the complete step-by-step instructions supplied, even if you have never built electronic equipment before. If you appreciate a good, clean signal on the CW bands, this is the transmitter for you! Shpg. Wt. 18 lbs.

MODEL DX-20

\$35⁹⁵

Heathkits...

By DAYSTROM

*are designed by
licensed ham-engineers,
especially for you*

HEATHKIT DX-35 PHONE AND CW TRANSMITTER KIT

The DX-35 transmitter can be thought of as the "little brother" of the DX-100. It features both phone and CW operation on 80, 40, 20, 15, 11 and 10 meters. A single 6146 tube is used in the final amplifier stage to provide full 65 watt plate power input on CW, or controlled carrier modulation peaks up to 50 watts for phone operation. Modulator and power supplies are built right in and single knob band switching is combined with a pi network output circuit for complete operating convenience. The tight fitting cabinet

presents a most attractive appearance, and is designed for complete shielding to minimize TVI. Back panel control provides convenient switch selection of three different crystals, reached through access door at rear of cabinet. A most remarkable power package for the price. Complete step-by-step instructions with pictorial diagrams to assure your success in assembly. Shpg. Wt. 24 lbs.

MODEL DX-35

\$56⁹⁵

HEATHKIT DX-100 PHONE AND CW TRANSMITTER KIT

Listen to any ham band between 160 meters and 10 meters and note how many DX-100 transmitters you hear! The number of these fine rigs now on the air testifies to the enthusiasm with which it has been accepted by the amateur fraternity. No other transmitter in this power class combines high quality and real economy so effectively. The DX-100 features a built in VFO, modulator and power supplies, complete shielding to minimize TVI, and pi network output coupling to match impedances from approximately 50 to 600 ohms. Its RF output is in excess of 100 watts on phone and 120 watts on CW, for a clean strong signal on all the ham bands from 10 to 160 meters. Single-knob band switching and illuminated VFO dial and meter face add real operating convenience. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. High quality components are used throughout, such as "potted" transformers, silver-plated or solid coin silver switch terminals, aluminum heat-dissipating caps on the final tubes, copper plated chassis, etc. This transmitter was designed exclusively for easy step-by-step assembly. Shpg. Wt. 107 lbs.

MODEL DX-100

\$189⁵⁰

FUNCTIONAL DESIGN . . .

The transmitters described on this page were designed for the ham, by hams who know what features are desirable and needed. This assures you of the best possible performance and convenience, and adds much to your enjoyment in the ham shack.


*Automatically turns off
transmitter and gives
visual signal*




"AUTOMATIC"
CONELRAD ALARM



GRID DIP METER

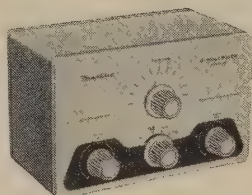

"Q" MULTIPLIER

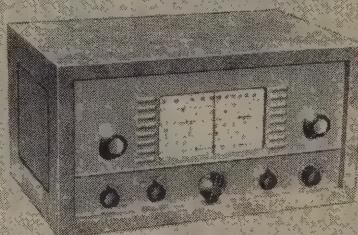

COMMUNICATIONS-TYPE
RECEIVER

*An ideal receiver
for the beginning
ham or short
wave listener*

HEATHKIT "AUTOMATIC" CONELRAD ALARM KIT

This conelrad alarm works with any radio receiver; AC-DC-transformer operated—or battery powered, so long as the receiver has AVC. Fully complies with FCC regulations for amateurs. When the monitored station goes off the air, the CA-1 automatically cuts the AC power to your transmitter, and lights a red indicator. A manual "reset" button reactivates the transmitter. Incorporates a heavy-duty six-ampere relay, a thyatron tube to activate the relay, and its own built-in power supply. A neon lamp shows that the alarm is working, by indicating the presence of B+ in the alarm circuit. Simple to install and connect. Your transmitter plugs into an AC receptacle on the CA-1, and a cable connects to the AVC circuit of a nearby receiver. A built-in sensitivity control allows adjustment to various AVC levels. Receiver volume control can be turned up or down, without affecting alarm operation. Build a Heathkit CA-1 in one evening and comply with FCC regulations now! Shpg. Wt. 4 lbs.

MODEL CA-1

\$13⁹⁵

HEATHKIT "Q" MULTIPLIER KIT

The Heathkit Q Multiplier functions with any AM receiver having an IF frequency between 450 and 460 KC, that is not "AC-DC" type. It derives its power from the receiver, and needs only 6.3 volts AC at 300 ma (or 12 VAC at 150 ma) and 150 to 250 volts DC at 2 ma. Simple to connect with cable and plugs supplied. Adds additional selectivity for separating signals, or will reject one signal and eliminate heterodyne. A tremendous help on crowded phone and CW bands. Effective Q of 4000 for sharp "peak" or "null". Tunes any signal within IF band pass without changing the main receiver tuning dial. A convenient tuning knob on the front panel with vernier reduction between the tuning knob and the tuning capacitor gives added flexibility in operation. Uses a 12AX7 tube, and special high-Q shielded coils. Instructions for connecting to the receiver and operation are provided in the construction manual. A worthwhile addition to any communications, or broadcast receiver. It may also be used with a receiver which already has a crystal filter to obtain two simultaneous functions, such as peaking the desired signal with the crystal filter and nulling an adjacent signal with the Q Multiplier. Shpg. Wt. 3 lbs.

MODEL QF-1

\$9⁹⁵

HEATHKIT GRID DIP METER KIT

A grid dip meter is basically an RF oscillator for determining the frequency of other oscillators, or of tuned circuits. Extremely useful in locating parasitics, neutralizing, identifying harmonics, coil winding, etc. Features continuous frequency coverage from 2 mc to 250 mc, with a complete set of prewound coils, and a 500 ua panel meter. Front panel has a sensitivity control for the meter, and a phone jack for listening to the "zero-beat." Will also double as an absorption-type wave meter. Shpg. Wt. 4 lbs.

MODEL GD-1B

\$19⁹⁵

Low Frequency Coil Kit: Two extra plug-in coils to extend frequency coverage down to 350 kc. Shpg. Wt. 1 lb. No. 341-A. \$3.00

HEATHKIT ALL-BAND COMMUNICATIONS-TYPE RECEIVER KIT

This communications-receiver covers 550 kc to 30 mc in four bands, and provides good sensitivity, selectivity, and fine image rejection. Ham bands are clearly marked on an illuminated dial scale. Features a transformer-type power supply—electrical band spread—antenna trimmer—head-phone jack—automatic gain control and beat frequency oscillator. Accessory sockets are provided on the rear of the chassis for using the Heathkit model QF-1, Q Multiplier. Accessory socket is handy, also, for operating other devices that require plate and filament potentials. Will supply +250 VDC at 15 ma and 12.6 VAC at 300 ma. Ideal for the beginning ham or short wave listener. Shpg. Wt. 12 lbs.

MODEL AR-3

\$29⁹⁵

(Less cabinet)

Cabinet: Fabric covered cabinet with aluminum panel as shown. Part no. 91-15A. Shpg. Wt. 5 lbs. \$4.95.

Heathkits...

By DAYSTROM

*are outstanding in performance
and dollar value*

HEATHKIT REFLECTED POWER METER KIT

The Heathkit reflected power meter, model AM-2, makes an excellent instrument for checking the match of the antenna transmission system, by measuring the forward and reflected power or standing wave ratio. The AM-2 is designed to handle a peak power of well over 1 kilowatt of energy and may be left in the antenna system feed line at all times. Band coverage is 160 meters through 2 meters. Input and output impedances for 50 or 75 ohm lines. No external power required for operation. Meter indicates percentage forward and reflected power, and standing wave ratio from 1:1 to 6:1. Another application for the AM-2 is matching impedances between exciters or R.F. sources and grounded grid amplifiers. Power losses between transmitter output and antenna tuner may be very easily computed by inserting the AM-2 in the line connecting the two. No insertion loss is introduced into the feeder system, due to the fact that the AM-2 is a portion of coaxial line in series with the feeder system and no internal connections are actually made to the line. Complete circuit description and operation instructions are provided in the manual. Cabinet size is 7-3/8" x 4-1/16" x 4-5/8". Can be conveniently located at operating position. Shpg. Wt. 3 lbs.

MODEL AM-2

\$15⁹⁵

HEATHKIT VARIABLE FREQUENCY OSCILLATOR KIT

Enjoy the convenience and flexibility of VFO operation by obtaining the Heathkit model VF-1 Variable Frequency Oscillator. Covers 160-80-40-20-15-11 and 10 meters with three basic oscillator frequencies. Better than 10 volt average RF output on fundamentals. Plenty of output to drive most modern transmitters. It features voltage regulation for frequency stability. Dial is illuminated for easy reading. Vernier reduction is used between the main tuning knob and the tuning condenser. Requires a power source of only 250 volts DC at 15 to 20 milliamperes and 6.3 volts AC at 0.45 amperes. Extra features include copper-plated chassis, ceramic coil forms, extensive shielding, etc. High quality parts throughout. VFO operation allows you to move out from under interference and select a portion of the band you want to use without having to be tied down to only two or three frequencies through use of crystals. "Zero in" on the other fellow's signal and return his CQ on his own frequency! Crystals are not cheap, and it takes quite a number of them to give anything even approaching comprehensive coverage of all bands. Why hesitate? The model VF-1 with its low price and high quality will add more operating enjoyment to your ham activities. Shpg. Wt. 7 lbs.

MODEL VF-1

\$19⁵⁰

Heathkits...

By DAYSTROM

are the answer for your electronics hobby.

HEATHKIT BALUN COIL KIT

The Heathkit Balun Coil Kit model B-1 is a convenient transmitter accessory, which has the capability of matching unbalanced coax lines, used on most modern transmitters, to balance lines of either 75 or 300 ohms impedance. Design of the bifilar wound balun coils will enable transmitters with unbalanced output to operate into balanced transmission line, such as used with dipoles, folded dipoles, or any balanced antenna system. The balun coil set can be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will easily handle power inputs up to 250 watts. Cabinet size is 9" square by 5" deep and it may be located any distance from the transmitter or from the antenna. Completely enclosed for outdoor installation. Shpg. Wt. 4 lbs.

MODEL B-1


\$8⁹⁵

HEATHKIT 6 OR 12 VOLT VIBRATOR POWER SUPPLY KITS

These little power supply kits are ideal for all portable applications with 6 volt or 12 volt batteries, when you are operating electronic equipment away from power lines. By replacing the power supplies of receivers, small public address systems, or even miniature transmitters with these units, they can be used with conventional 6 or 12 volt batteries. Use in boats, automobiles, light aircraft, or any field application. Each unit provides 260 volts DC output at up to 60 milliamperes. More than one power supply of the same model may be connected in parallel for increased current capacity at the same output voltage. Everything is provided in the kit, including a vibrator transformer, a vibrator, 6X4 or 12X4 rectifier, and the necessary buffer capacitor, hash filter, and output filter capacitor. Shpg. Wt. 4 lbs.


6 VOLT
MODEL VP-1-6
12 VOLT
MODEL VP-1-12

\$7⁹⁵ Each

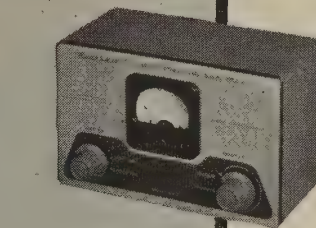


REFLECTED
POWER METER

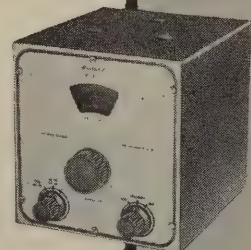
*Insure your
"on the air"
performance with
these fine accessories.*



VARIABLE FREQUENCY
OSCILLATOR

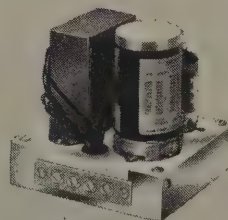

VIBRATOR
POWER SUPPLY

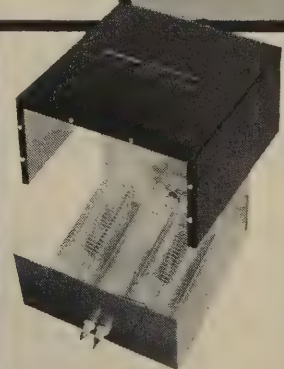

BALUN COIL SET

HEATHKIT ELECTRONIC IGNITION ANALYZER KIT

Previous electronic experience is not necessary to build this fine ignition analyzer. The construction manual supplied has complete step-by-step instructions plus large pictorial diagrams showing the exact placement and value of each component. All parts are clearly marked so that they are easily identified. The IA-1 is an ideal tool for engine mechanics, tune-up men, and auto hobbyists, since it traces the dynamic action of voltage in an ignition system on a cathode-ray tube screen. The wave form produced is affected by the condition of the coil, condenser, points, plugs, and ignition wiring, so it can be analyzed, and used as a "sign-post" to ignition system performance. This analyzer will detect inequality of spark intensity, a poor spark plug, defective plug wiring, breaker-point bounce, an open condenser, and allow setting of dwell-time percentage for the points. An important feature of this instrument is its ability to check dynamic performance, with the engine in operation (400 to 5000 RPM). It will show the complete engine cycle, or only one complete cylinder. Can be used on all types of internal combustion engines where breaker-points are accessible. Use it on automobiles, boats, aircraft engines, etc. Shpg. Wt. 18 lbs.

MODEL IA-1
\$59⁹⁵




IGNITION
ANALYZER



*Kit includes everything
you need for
construction — even
batteries!*

RADIATION COUNTER

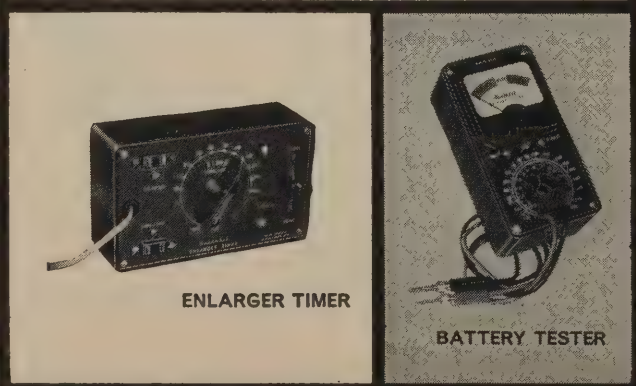

ENLARGER TIMER



BATTERY TESTER

HEATHKIT PROFESSIONAL RADIATION COUNTER KIT

This Heathkit professional-type radiation counter is simple to build successfully, even if you have never built a kit before. Complete step-by-step instructions are combined with giant-size pictorial diagrams for easy assembly. By "building it yourself" you can have a modern-design, professional radiation counter priced far below comparable units. Provides high sensitivity with ranges from 0-100, 600, 6000 and 60,000 counts-per-minute, and 0-0.02, .1, 1 and 10 miliroentgens-per-hour. Employs 900-volt bismuth tube in beta/gamma sensitive probe. Probe and 8-foot expandable cable included in kit price, as is a radiation sample for calibration. Use it in medical laboratories, or as a prospecting tool, and for civil defense to detect radioactive fallout, or other unknown radiation levels. Features a selectable time constant. Meter calibrated in CPM or mR/hour in addition to "beep" or "click" from panel-mounted speaker. Prebuilt "packaged" high voltage power supply with reserve capacity above 900 volt level at which it is regulated. Merely changing regulator tube type would allow use of scintillation probe if desired. Employs five tubes (plus a transistor) to insure stable and reliable operation. Kit price includes batteries. Shpg. Wt. 8 lbs.

MODEL RC-1
\$79⁹⁵

Heathkits...

By DAYSTROM

*are supplied with comprehensive
instructions that eliminate costly
mistakes and save valuable time*

HEATHKIT ENLARGER TIMER KIT


The ET-1 is an easy-to-build electronic device to be used by amateur or professional photographers in timing enlarger operations. The calibrated dial on the timer covers 0 to 1 minute, calibrated in 5-second gradations. The continuously variable control allows setting of the "on" cycle of your enlarger, which is plugged into a receptacle on the front panel of the ET-1. A "safe light" can also be plugged in so that it is automatically turned "on" when the enlarger is turned "off." Handles up to 350 watts with built-in relay. All-electronic timing cycle insures maximum accuracy. Timer does not have to be reset after each cycle, merely flip lever switch to print, to repeat time cycle. A control is provided for initial calibration. Housed in a compact plastic case that will resist attack of photographic chemicals. A fine addition to any dark room. Shpg. Wt. 3 lbs.

MODEL ET-1
\$11⁵⁰

HEATHKIT BATTERY TESTER KIT

The BT-1 is a special battery testing device that actually "loads" the battery under test (draws current from it) while it is being tested. Weak batteries often test "good" with an ordinary voltmeter but the built-in load resistance of the BT-1 automatically draws enough current from the battery to reveal its true condition. Simple to operate with "good-weak-replace" scale. Tests all kinds of dry cell batteries within ranges of 0-15 volts and 0-180 volts. Slide switch provides for either 10 ma or 100 ma load, depending on whether you're testing an A or B battery. Not only determines when battery is completely exhausted, but makes it possible to anticipate failure by noting weak condition. Ideal for testing dry cell hearing aid, flashlight, portable radio, and model airplane batteries. Test batteries in a way your customers can understand and stimulate battery sales. Shpg. Wt. 2 lbs.

MODEL BT-1
\$8⁵⁰

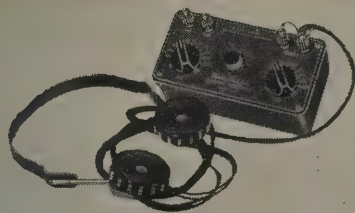


CRYSTAL RADIO



Now you can have radio
wherever you go —
with the portable
that plays anywhere!



BROADCAST BAND RADIO

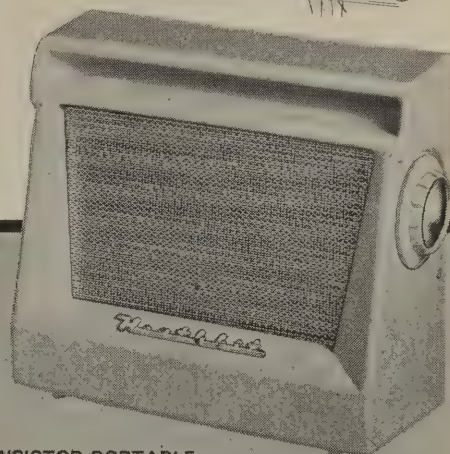

TRANSISTOR PORTABLE

HEATHKIT CRYSTAL RADIO KIT

The Heathkit model CR-1 crystal radio is similar to the "crystal sets" of the early radio days except that it has been improved by the use of sealed germanium diodes and efficient "high-Q" coils. The sealed diodes eliminate the critical "cats whisker" adjustment, and the ferrite coils are much more efficient for greater signal strength. Housed in a compact plastic box, the CR-1 uses two tuned circuits, each with a variable tuning capacitor, to select the local station. It covers the broadcast band from 540 to 1600 kc. Requires no external power whatsoever. This receiver could prove valuable to emergency reception of civil defense signals should there be a power failure. The low kit price even includes headphones. Complete step-by-step instructions and large pictorial diagrams are supplied for easy assembly. The instruction manual also provides the builder with the basic fundamentals of signal reception so that he understands how the crystal receiver functions. An interesting and valuable "do-it-yourself" project for all ages. Shpg. Wt. 3 lbs.

MODEL CR-1
\$7⁹⁵

result of these efforts. Six name-brand (Texas Instrument) transistors were selected for extra good sensitivity and selectivity. A 4" by 6" PM speaker with heavy magnet was chosen to insure fine tone quality. The power supply was designed to use six standard size "D" flashlight cells because they are readily available, inexpensive, and because they afford extremely long battery life (between 500 and 1000 hours). Costs you no more to operate from batteries than what you pay for operating a small table-model radio from the power line. An unbreakable molded plastic was selected for cabinet material because of its durability and striking beauty. Circuit is compact and efficient, yet components are not excessively crowded. Transformers are prealigned so it is ready for service as soon as construction is completed. Has built in rod-type antenna for reception in all locations. Cabinet dimensions are 9" L x 8" H x 3 3/4" D. Comes in holiday gray, with gold-anodized metal speaker grille. Compare this portable, feature by feature, to all others on the market, and you'll appreciate what a tremendous dollar value it represents! Shpg. Wt. 4 lbs.

MODEL XR-1
\$34⁹⁵
(Less batteries)
(With cabinet)

Heathkits...

By DAYSTROM

*are easy and fun to build,
and they let you learn
by "doing-it-yourself"*

HEATHKIT TRANSISTOR PORTABLE RADIO KIT

Heath engineers set out to develop a "universal" AM radio, suitable for use anywhere. Their objective was a portable that would be as much "at home" inside as it is outside, and would feature top quality components for high performance and long service life. The model XR-1 is the

HEATHKIT BROADCAST BAND RADIO KIT


This table-model broadcast radio is fun to build, and is a fine little receiver for your home. It covers the standard broadcast band from 550 to 1600 kc with good sensitivity and selectivity. The 5 1/2" PM speaker provides surprisingly good tone quality. High-gain IF transformers, miniature tubes, and a rod-type built in antenna, assure good reception in all locations. The power supply is transformer operated, as opposed to many of the economy "AC-DC" types. It's easy to build from the step-by-step instructions, and the construction manual includes information on operational theory, for educational purposes. Your success is assured by completely detailed information which also explains resistor and capacitor color codes, soldering techniques, use of tools, etc. A signal generator is recommended for final alignment. Shpg. Wt. 10 lbs.

Cabinet: Fabric covered cabinet with aluminum panel as shown. Shpg. Wt. 5 lbs. Part no. 91-9A. \$4.95.

MODEL BR-2
\$18⁹⁵
(Less cabinet)


*protects against possible
explosion and fire from
undetected fuel vapor*

**FUEL VAPOR
DETECTOR**

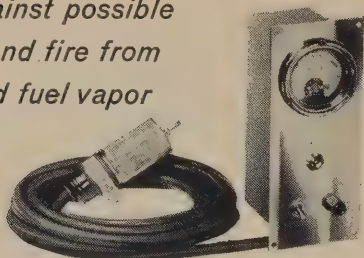


*detects electrolysis
currents which cause
deterioration of
underwater metal
fittings on your boat*

**ELECTROLYSIS
DETECTOR**

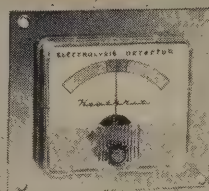

*indicates condition
and charge of batteries
for safe cruising*

**BATTERY CHARGE
INDICATOR**

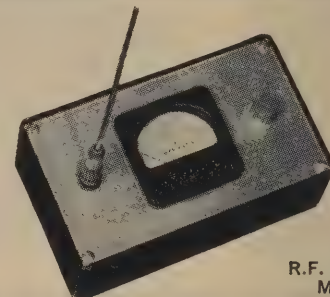

**R.F. POWER
METER**

HEATHKIT FUEL VAPOR DETECTOR KIT

Protect your boat and its passengers against fire or explosion from undetected fuel vapor by building and using one of these fine units. The Heathkit Fuel Vapor Detector indicates the presence of fumes on a three-color "safe-dangerous" meter scale and immediately shows if it is safe to start the engine. A pilot light on the front panel shows when the detector is operating, and it can be left on continuously, or just used intermittently. A panel control enables initial calibration of the detector when installed. Features a hermetically-sealed meter with chrome bezel, and a chrome-plated brass panel. It is very simple to build and install, even by one not having previous experience. Models FD-1-6 (6 volts DC) and FD-1-12 (12 volts DC) operate from your boat batteries. The kit is complete in every detail, even to the inclusion of a spare detector unit. Shpg. Wt. 4 lbs.

6 volt
MODEL FD-1-6
12 volt
MODEL FD-1-12

\$35⁹⁵
EACH

HEATHKIT BATTERY CHARGE INDICATOR KIT

The Heathkit model CI-1 Marine Battery Charge Indicator has been designed especially for the boat owner, although it has found use in service stations, power stations, and radio stations where banks of batteries are kept in reserve for emergency power. It is intended to replace the hydrometer method of checking storage batteries, and to eliminate the necessity for working with acid in small, below-decks enclosures. Now it is possible to check as few as one, or as many as eight storage batteries, merely by turning the switch and watching the meter. A glance at the meter tells you instantly whether your batteries are sufficiently charged for safe cruising. Dimensions are 2-7/8" W x 5-11/16" H x 2" D. Operates on either 6 or 12 volt systems using lead-acid batteries, regardless of size. Simple installation can be accomplished by the boat owner in fifteen minutes. Shpg. Wt. 3 lbs.

MODEL CI-1
\$16⁹⁵

HEATHKIT ELECTROLYSIS DETECTOR KIT

The Heathkit model ED-1 Electrolysis Detector indicates the extent of electrolysis currents between the boat's common ground and underwater fittings, except on boats having metal hulls. These currents, undetected, could

cause gradual corrosion and deterioration of the propeller or other metal fittings below the water line. It is particularly helpful when installing electrical equipment of any kind, or to determine proper polarity when power is obtained from a shore supply. Easy-to-build, the model ED-1 consists of a hermetically-sealed, waterproof meter, special sensing plate, and sufficient wire to install, including the necessary hardware. Mounts on instrument panel where it can be easily seen. Requires no power for operation, and gives instant warning to guard your boat for a lifetime. Shpg. Wt. 2 lbs.

MODEL ED-1
\$9⁹⁵

HEATHKIT RF POWER METER KIT

The Heathkit RF Power Meter Kit is designed to sample the RF field in the vicinity of your transmitter, whether it be marine, mobile, or fixed. Output meter is merely placed in some location close to the transmitter, to pick up RF radiation from the antenna. Requires no batteries, electricity, nor direct connection to the transmitter. It provides you with a continuing indication of transmitter operation. You can easily detect if power is dropping off by comparing present meter readings with past ones. Operates with any transmitter having output frequencies between 100 kc and 250 mc, regardless of power. Sensitivity is 0.3 volts RMS full scale, and a special control on the panel allows for further adjustment of the sensitivity. Meter is a 200 ua unit, mounted on a chrome-plated brass panel. The entire PM-1 measures only 3 3/4" W x 6 1/4" L x 2" D. An easy way to put your mind at ease concerning transmitter operation. Shpg. Wt. 2 lbs.

MODEL PM-1
\$14⁹⁵

Heathkits...

By DAYSTROM

*now offer you completely
modern marine equipment with
outstanding design features*

The Heathkit Transistor Radio Direction Finder model DF-1 is a self-contained, self-powered, 6-transistor super heterodyne broadcast radio receiver incorporating a directional loop antenna, indicating meter, and integral speaker. It is designed to serve primarily as an aid to navigation when out of sight of familiar landmarks. It can be used not only aboard yachts, fishing craft, tugs, and other vessels which navigate either out of sight of land or at night, but also for the hunter, hiker, camper, fisherman, aviator, etc. It is powered by a 9-volt battery. (A spare battery is also included with the kit). The frequency range covers the broadcast band from 540 to 1600 kc and will double as a portable radio. A directional high-Q ferrite antenna is incorporated which is rotated from the front panel to obtain a fix on a station and a 1 ma meter serves as the null and tuning indicator. The controls consist of: tuning, volume and power (on-off), sensitivity, heading indicator (compass rose) and bearing indicator (antenna index). Overall dimensions are $7\frac{1}{2}"$ W x $5\frac{1}{8}"$ H x $5\frac{3}{8}"$ D. Supplied with slip-in-place mounting brackets, which allow easy removal from ship bulkheads or other similar places. Shpg. Wt. 5 lbs.

\$54⁹⁵


Heathkits...

*are sold only by direct mail,
passing middleman
profits on to you*




The Heath Company maintains a technical consultation service, should you experience some sort of difficulty in construction or operation. Although only a very small percentage of our customers ever have occasion to use this service (usually only beginners in electronics) it is still reassuring to know that technical help is available when needed. A service department is also available, should you wish a complete factory check of operation and alignment or repair. After you build your first Heathkit you'll realize how easy it is.

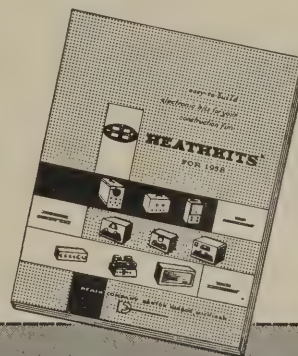Send for this
informative booklet
listing more than
100 "do-it-yourself" kits.



HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**

QUANTITY	ITEM	MODEL NO.	PRICE
		POSTAGE	
	<input type="checkbox"/> SEND FREE Heathkit Catalog	TOTAL	

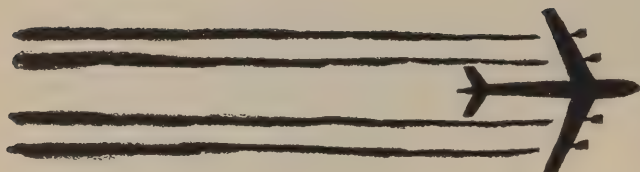

The cartridge of tomorrow is **HERE!**

To ride in America's first jet airliner, you'll have to wait until 1959—but the cartridge of tomorrow can be yours today! The sensational new ESL C-60 electrodynamic cartridge, as advanced as tomorrow's jet and musical as a rare Stradivarius, is now at your audio dealer's.

Hear it, and you'll be astonished at the C-60's dramatic superiority of reproduction quality. You'll be astonished, too, at its ruggedness in any record changer or arm. With a voltage output five times the minimum specified for the world-famed ESL Concert Series cartridge, the ESL C-60 will easily drive all modern preamplifiers.

Like all fine ESL cartridges, the C-60 can greatly increase the life of your records and styli. Write for free information on the cartridge that's years ahead: the ESL C-60. Better yet, make it yours today. Only \$39.50.



COMPARE THESE MINIMUM PERFORMANCE DATA:

- ▶ Frequency response flat within 1 db 18 cps to 20,000 cps (Elektra 35 test record)
- ▶ Response extends beyond 30,000 cps
- ▶ Minimum output 5 mv at 5 cm/sec
- ▶ Minimum compliance 6.8×10^{-9} cm/dyne
- ▶ Dynamic mass 1 mg
- ▶ IM distortion almost immeasurably small
- ▶ Vertical stylus force 2-6 gms
- ▶ Output impedance 40 ohms at all audio frequencies
- ▶ No transformer nor transistor amplifier ordinarily required
- ▶ Performance unaffected by load resistance

FOR LISTENING AT ITS BEST

Electro-Sonic Laboratories, Inc.

Dept. E • 35-54 Thirty-sixth Street • Long Island City 6, N.Y.

TELEVISION

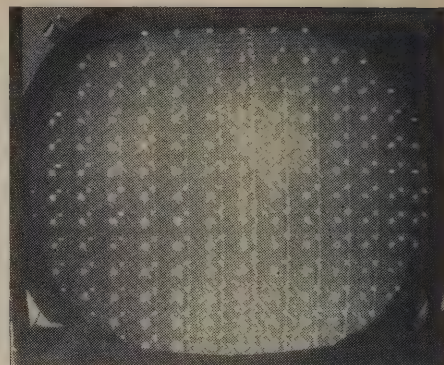


Fig. 3—Column lineup is not as evident when a dot pattern is used.

(Continued from page 59)

lucky. I harpooned it before it got up and ran off."

"Say, Red . . ."

"What now?"

"I hear they got a hoot-nanny out that you can plug on the base of the picture tube. It's supposed to have a switch that you use to turn on the red or blue or green by itself."

"Nothing wrong with your hearing," Red remarked. "Yep, what it does is to ground two grids at a time. The cathodes run positive in a color set, so that's the same as putting a negative bias on the grids."

"Seems like that would be real fine for checking field purity," Fuzzball suggested.

"It's a timesaver," Red agreed. "In fact we have half a dozen on order. We're going to use them on the bench, too."

"For what?"

"Well," replied Red, "it's got six other switch positions, too. You can switch a pair of binding posts into the different grid and cathode circuits of the picture tube for a quick voltage check all around."

"You connect a meter to the hoot-nanny?"

"Yep. Has a pair of binding posts for connecting the meter."

"What won't they think of next?" asked Fuzzball.

"Do you really want to know?" asked Red challengingly.

"Reckon I'll pass," Fuzzball replied. "What other gimmicks should I know about for installation work?"

"Well, in case you are working on your own set sometime, where you are interested in doing a good job, you'll find a low-power pocket microscope is handy."

"A microscope?"

"M-I-C-R-O-S-C-O-P-E," Red spelled out emphatically.

"All right, you don't have to throw your weight around," Fuzzball grumbled; "what would I be doing with a microscope?"

"It's for checking field purity," Red explained. "It's a sort of head shrinker that reduces a swelled head real fast."

"How do I use it?" asked Fuzzball.

"Let's get into that one another time," suggested Red. "Bess is getting ready to throw us out."

END

*build with
the best...*

JBL signature loudspeakers!

The careful work you do in building your high fidelity sound system will be shown off to best advantage if you use precision-made JBL SIGNATURE Loudspeakers. These are the most efficient units to be found anywhere, made with the most exacting care, meticulous attention to detail. Remember, it takes no more effort on your part to build with the best.

MODEL D130
15" Extended
Range
Loudspeaker

The only 15" extended range speaker made with a 4" voice coil is the world-famous JBL Signature D130. The large voice coil stiffens the cone for crisp, clean bass; smooth, extended highs. Your basic speaker, the D130 works alone at first, later becomes a low frequency driver when you add a JBL Signature high frequency unit and dividing network to achieve the ultimate excellence of a JBL Signature two-way system.

MODEL D208
8" Extended Range
Loudspeaker

A precision transducer in every sense of the word, the famed JBL Signature 8" D208 is made with the same care and precision as the larger units in the James B. Lansing Sound, Inc., line. If space and cost are major considerations, the D208, properly enclosed, provides the most lastingly satisfactory sound you can get. It is widely used in top quality systems where extension speakers are desired for areas other than the main listening room.

MODEL D123
12" Extended
Range
Loudspeaker

With outstanding "presence" and clean response throughout the entire audio spectrum, the D123 features an unusual shallow construction. Only 3 3/8" deep, it is designed to mount flush with the wall, between studding, in any standard wall or partition. Frequently, the D123 is used in multiples in "infinite baffle" wall installations. In this case the JBL Signature 075 is a logical high frequency unit to add when you advance to a two-way system.

MODEL 075
High
Frequency Unit

Another exclusive for James B. Lansing Sound, Inc., is the ring radiator in the JBL Signature 075 high frequency unit. A ring, rather than a diaphragm, radiates into the annular throat of an exponential horn. The result is high frequency reproduction of unmatched smoothness and clarity, absolutely free of resonances and strident peaks. The horn is beautifully machined from aluminum, the entire unit a gratifying, solid piece of fine craftsmanship. Designed for crossover at 2500 cycles with the JBL Signature N2500 Network.


MODEL 175DLH High Frequency Assembly

The acoustical lens is only available on JBL Signature high frequency units. The 14 element lens on the 175DLH disperses sound within the listening area over a 90° solid angle, smoothly, with equal intensity regardless of frequency. The acoustical lens is the greatest contribution to life-like high frequency reproduction in 20 years, and it was developed for use with high fidelity equipment by James B. Lansing Sound, Inc. In addition to the lens the 175DLH consists of a high precision driver with complex phasing plug and a machined aluminum exponential horn. Designed for crossover at 1200 cycles with the JBL Signature N1200 Network.

**JBL Signature
Two-way
Systems Are
Available
As Kits**

086 KIT This two-way system is made up of units which have been acclaimed by impartial authorities as the finest available anywhere today. Included in the kit are the 150-4C Low Frequency Driver, N500H Network, 375 High Frequency Driver, 537-509 Horn-Lens Assembly. These are the same units—including the serpentine acoustical lens—which are used in The Hartfield . . . units designed originally for installation in the most modern theaters in the world.

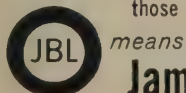There are many more kits and loudspeakers in the JBL Signature line. Whatever your needs, you will find exactly the right unit or system in the complete JBL Signature catalog. Send for your free copy. A limited number of technical bulletins are also available. Please ask only for those in which you are vitally interested.



James B. Lansing Sound, Inc.

JAMES B. LANSING SOUND, INC., 2439 Fletcher Dr. • Los Angeles 39, Calif.
Please send me the following:

☐ Free Catalog of JBL Signature Products ☐ Name and address of Authorized JBL Signature Audio Specialist in my community

TECHNICAL BULLETINS ON:


☐ D130 ☐ D123 ☐ D208 ☐ 175DLH ☐ 075 ☐ 375 ☐ 150-4C

Name _____

Address _____



City _____ Zone _____ State _____

TELEVISION HEARING AID

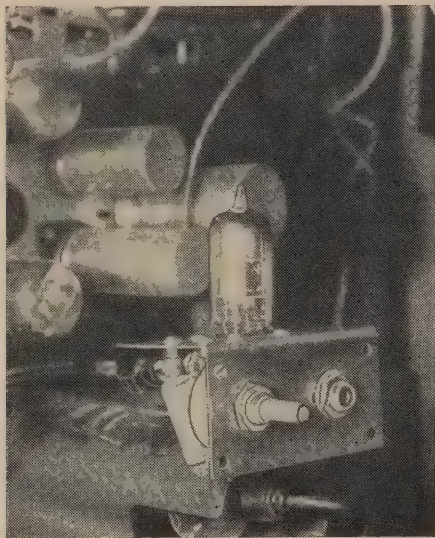

Front view shows control and jack.

Amplifier on rear of front panel.

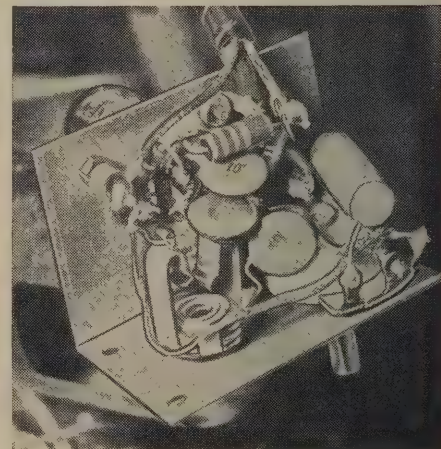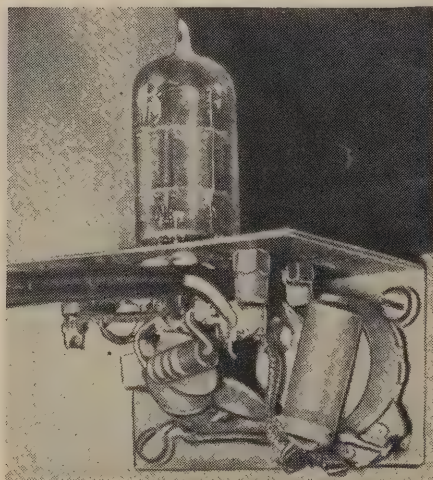

The underchassis of the amplifier.

ONE member of our family could get no pleasure out of the TV set because he is hard of hearing. No matter how high the volume was turned up it did no good and of course there were others to consider. A hearing aid didn't help much as it picked up too much noise from sources other than the TV set. A phono jack could have been used but the volume control then could be set only either for loudspeaker or phones.

Obviously, the answer was a separate amplifier and gain control. Preferably, the amplifier should be peaked at the higher frequencies for that is where most of the hearing range of the hard of hearing usually lies. (Many authorities believe that a flat response is more satisfactory to the usual hard-of-hearing person.—*Editor*)

This unit was the result. It is a simple two-stage amplifier (see diagram) and provides more than enough gain. No attempt was made at high fidelity, the only requirements being crispness and clarity.

The amplifier input is taken from the audio output tube so that there is always enough signal to drive the amplifier input section even though the speaker volume is turned down to the point where no one else can hear it. This makes it useful for late-hour listening when others are asleep, even for those whose hearing is not impaired.

I took the audio input from the plate (pin 5) of a 6AQ5. The B plus for the hearing aid came from the screen grid (pin 6). Pin 3 supplies the hot 6.3-volt side of the heater and ground return was made to the chassis. For other output tubes use the same system, connecting the leads to corresponding pins. The input lead should be shielded and the shield itself used for ground and heater return. Make all grounds to one point on the chassis. A word of caution: before


wiring in the hot heater lead, check to see which is the ground side. If this connection is not properly made, it will short the 6.3-volt winding of the power transformer to ground and probably burn out your transformer.

The chassis is a sheet-metal angle and can be made any convenient size. It is held to the inside of the TV cabinet by screws and the necessary holes drilled in the front of the cabinet for the gain control and earphone jack. If it is not desirable to drill holes in the cabinet, the amplifier can be built in a small box and kept near the receiver.

The circuit shown in the diagram was designed for a receiver having its heaters in parallel. Series-string heaters will require some modification, especially if the chassis is transformerless. In such case a .01- μ f capacitor should be placed between the output jack and the lead to the TV chassis. This will isolate the phones from the ac line.

The 12AV7 draws 450 ma with its heaters in parallel. This may exceed the safe operating limits of the existing power transformer or make it difficult to use in series strings. The problem can be overcome by using a separate heater transformer or a tube such as the 12AU7 which draws only 300 ma. If a 12AU7 is used, the plate and cathode resistor values may have to be varied slightly to obtain maximum gain.

END

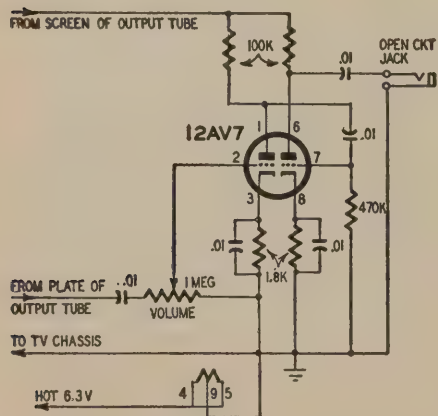

2—100,000-ohm $\frac{1}{2}$ -watt resistors; 1—470,000-ohm $\frac{1}{2}$ -watt resistor; 2—1,800-ohm 1-watt resistors; 1—meg-ohm potentiometer; 5—.01- μ f disc ceramics or tubular capacitors; 1—12AV7 tube; 1—9-pin miniature socket; 1—open circuit jack; 1—chassis.

Schematic diagram of the hearing aid.

THE

WING


DIPOLE



IS THE VERY

HEART

OF AN ANTENNA

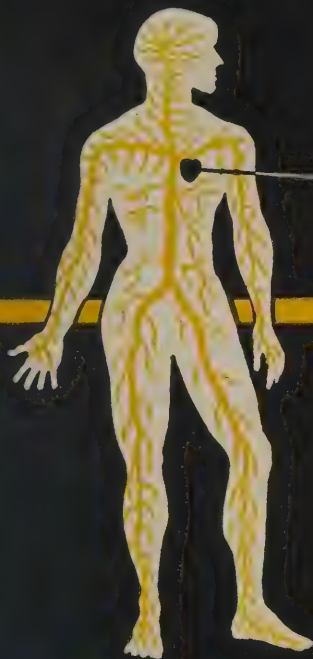

FOR DISTANCE

Flat Response That Gives
Good Reception on Both
Black & White & Color

EXTENDED "WING" DIPOLE

The Heart Of the Antenna
With The Increased Power and Sensitivity
Of The "WING" DIRECTOR
Exclusive Features Of The
TRIO ZEPHYR FAMILY ANTENNAS
THE LINE WITH PROTECTION



Zephyr[®]
PIONEER

FOR EXTREME DISTANCE

Uses The

EXTENDED "WING" DIPOLE

And The

"WING" DIRECTOR

COLLINEAR DIRECTOR
for increased gain
on the highs



ZEPHYR ROYAL[®]

FOR THE MAXIMUM

In TV Enjoyment

New

EXTENDED
"WING" DIPOLE

With The

"WING" DIRECTOR

COLLINEAR DIRECTOR

STAGGER - TUNED

THE NATION'S BEST PERFORMING ANTENNA ON BLACK & WHITE
EXCELLENT FOR COLOR RECEPTION



TRIO[®]

Manufacturing Company
ORIGOSVILLE, ILLINOIS

Export Sales Div., Scheel International Inc., 5909 N. Lincoln Ave., Chicago, U.S.A.

Cable Address: HARSHEEL

COPYRIGHT 1957 TRIO MFG. CO.

A Complete Line Of

CONICALS CONICAL-YAGI'S
SINGLE CHANNEL YAGI'S
MULTI CHANNEL YAGI'S
UHF Indoor & Outdoor

Understanding auxiliary TV circuits

By CHARLES GARRETT

The tail ends you rarely hear about, but often cause trouble

TV RECEIVERS are spotted with a number of special circuits and circuit components that can be troublesome to the service technician unless he is thoroughly aware of their normal and abnormal operation.

Horizontal peaking

The largest group of auxiliary circuits (circuits and components most often ignored or left out when discussing or simplifying the TV receiver's main circuitry) is located in the deflection oscillators and their associated circuitry. Some of these networks are shown in Fig. 1. The networks labeled a, b, c and d are all sawtooth-forming circuits. As their fundamental operation is the same, only network a is detailed. It is the sawtooth-forming network for a horizontal multivibrator.

The output from a multivibrator cannot be used directly to drive the horizontal output tube and deflection circuits as it is basically a square wave and not the sawtooth usually thought of in its connection. Photo A shows the output of the horizontal multivibrator with the sawtooth-forming network removed. The sawtooth has to be formed from this "square wave" to obtain a linear raster.

In normal operation the capacitor (called either charging or discharging capacitor) prevents the horizontal plate voltage from rising sharply by storing the rapid voltage change during its steady charging period. It releases its charge when the horizontal oscillator fires during the horizontal retrace period.

The series resistor in this circuit, by slowing down the capacitor's discharge, forms a negative pulse following the capacitor discharge. Photo B is the square wave found at the junction of the capacitor and resistor in circuits 1-a, 1-c and 1-d. This waveform combines with the capacitor waveform to form a modified sawtooth wave. The resistor determines the size of the negative pulse the sawtooth waveform will have. The size of the negative pulse that is needed is determined by the type of horizontal output tube used, and the design of the output transformer and output circuit whose inductance has to be overcome before the sawtooth portion can produce a linear sweep and raster. Photo C shows

the waveform at the horizontal multivibrator's plate, with the resistor in circuit 1-a removed and the capacitor going directly to ground. The modified sawtooth in Photo D appears at the plate of the horizontal multivibrator with circuit 1-a connected. This waveform is found in the older TV sets. Photo E shows another modified waveform found at the plate of a horizontal multivibrator with circuit 1-a connected. This is the normal plate waveform in most modern sets.

Improper operation of this circuit is not always obvious. The symptoms are very similar to those that can originate in other circuits and components. For example, in many receivers, when the capacitor or resistor opens, the only symptom is a slightly nonlinear raster on the left half of the screen. In this case, the damper or linearity circuit would normally be suspected instead of the sawtooth-forming network. However, overdrive bars in the center of the screen or even complete loss of raster are the more common symptoms of an open sawtooth-forming network. A shorted resistor or one that has decreased in resistance will cause the raster to narrow somewhat and be nonlinear near its center. But several other circuit defects or misadjustments can produce similar symptoms.

In every case of stubborn nonlinearity or insufficient width or height, an oscilloscope check should be made of the waveform at test points TP in Fig. 1 to determine if the source of the trouble is in the sawtooth-forming network.

Circuit 1-b is the sawtooth capacitor in a pulse-width type of horizontal oscillator. When this capacitor opens, it so greatly upsets the characteristics of this circuit that it usually kills the raster. This is because the normal waveform at the tap on the oscillator or transformer is destroyed and the oscillator is thrown way off frequency. Direct substitution is the easiest way to check this capacitor.

Stabilizing circuits

Networks a and b in Fig. 2 are horizontal stabilizing or ringing coils. Their function is not vital to the receiver's performance—horizontal oscillators could function without them, though not without some sacrifice of picture stability. Photo F shows the effect of a misaligned horizontal ring-

ing coil. Notice how the letters are distorted.

Their normal operation is as follows: When correctly tuned to the horizontal frequency of 15,750 cycles, they are shocked into sine-wave oscillation and this voltage combines with the normal circuit waveform.

This combined negative voltage (during cutoff) holds the second grid of the horizontal multivibrator or pulse-width oscillator more negative and more evenly negative until the tube is properly triggered by the positive-going sync pulses. Thus, positive noise pulses have to overcome an even greater negative voltage before they can prematurely fire the circuit. Also, the positive half of the sine wave will properly trigger the tube into conduction even if sync pulses are temporarily absent.

The sine wave formed by this circuit is finally eliminated by the sawtooth-forming capacitor, as previously described.

Circuit 2-a is normally aligned with a voltmeter. A jumper is first placed across the coil and the negative voltage on the multivibrator input grid test point is measured and recorded. The jumper is then removed and the coil aligned by adjusting it until grid voltage returns to the value it had with the jumper in place.

If the coil is not responsive to adjustment, it may be open, contain shorted turns or its shunting resistor or capacitor may be defective.

Circuit 2-b is aligned with an oscilloscope. The slug of coil L2 is adjusted until a waveform like that in Photo G is formed. This waveform should be present at the tap on L1. Adjustment of L1's slug may be required to hold the picture in horizontal sync during alignment of L2.

This circuit can produce severe raster tearing when it approaches correct alignment. Photo H shows raster breakup due to incorrect adjustment of horizontal stabilizing coils. Therefore, once the proper scope waveform is formed, some slight touchup may be required to keep the raster from breaking up within the normal horizontal-hold range of the set.

That about closes the shop for this month. Look for more on accessory circuits in a future issue. Retrace blanking, vertical peaking and yoke damping defects will be discussed. END

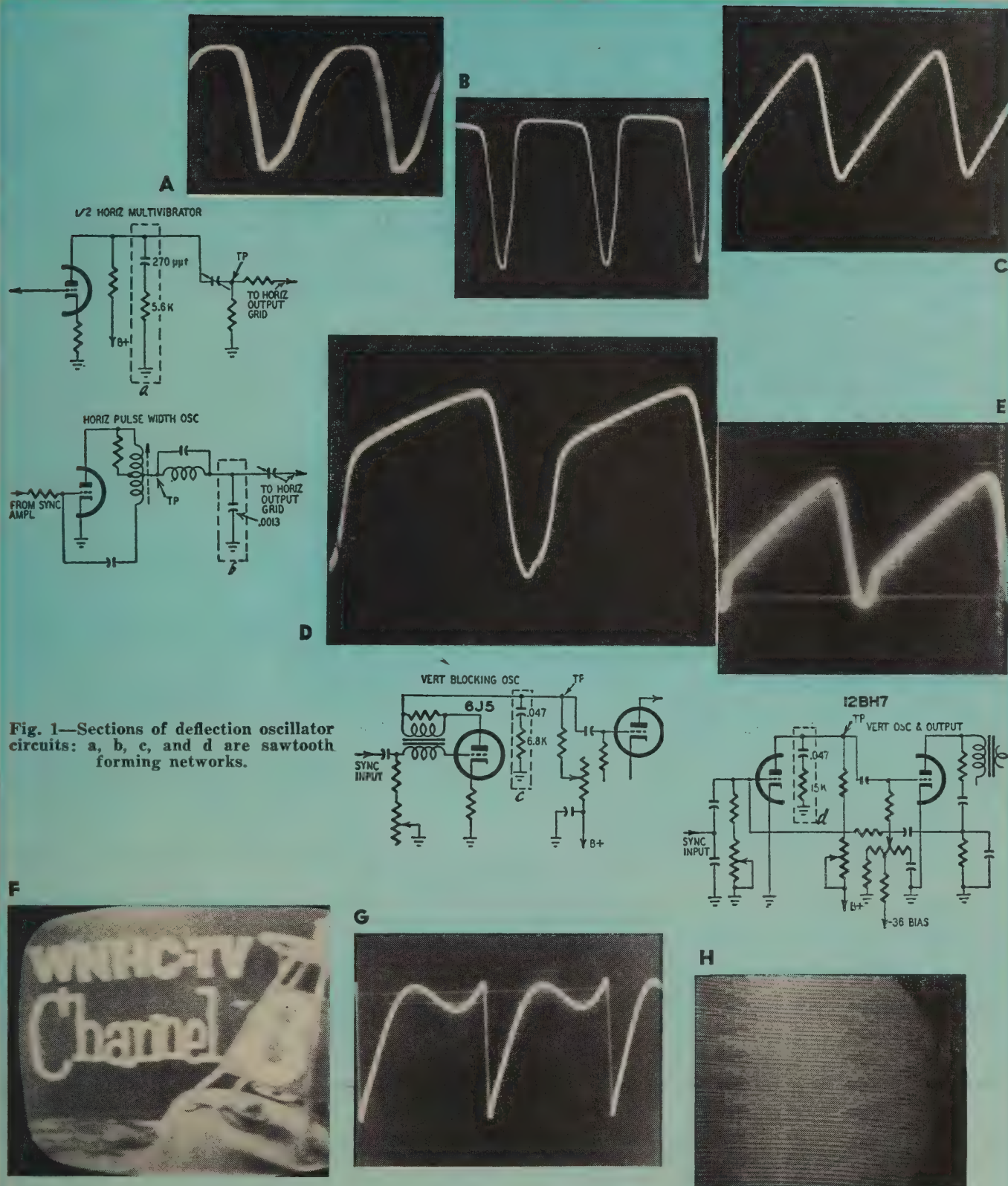


Fig. 1—Sections of deflection oscillator circuits: a, b, c, and d are sawtooth forming networks.

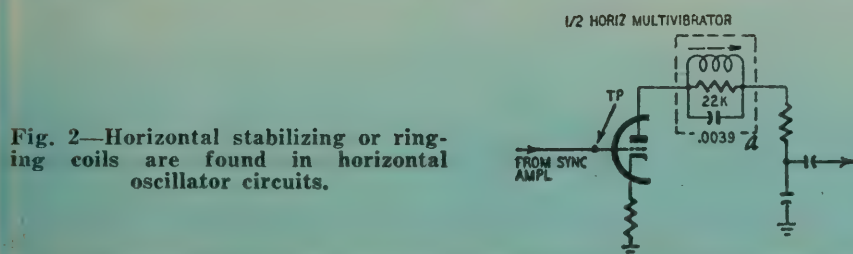


Fig. 2—Horizontal stabilizing or ringing coils are found in horizontal oscillator circuits.

Convince yourself at no risk that CENTURY instruments are indispensable in your every day work.

SHIPPED ON APPROVAL SEND NO MONEY — NO C.O.D.

Examine instruments for 10 days before you buy . . . Only then, when satisfied pay in "easy to buy" monthly installments.

Just 2 settings on the NEW FAST-CHECK TUBE TESTER

Model FC-1

tests all tubes completely, accurately
and in seconds — RIGHT ON THE SPOT

The FC-1 is the only tube tester in its price range to give a complete tube test of over 600 tube types in seconds without multiple switching or annoying checking of roll charts. You make every call pay extra dividends by merely showing your customer the actual condition and life expectancy of the tube. The extra tubes you sell each day will pay for the FAST-CHECK in a very short time.

WIDE RANGE OF OPERATION

Checks quality of over 600 tube types, which covers more than 99% of all TV and radio tubes in use today, including the newest series-string TV tubes, auto battery-type 12 plate-volt tubes, 0Z4s, magic eye tubes and gas regulators ■ Checks for cathode-heater and cathode-grid shorts and detects inter-element leakage up to 1.5 megohms ■ Checks for life expectancy.

Model AD-1 PICTURE TUBE ADAPTER — Also available for the FC-1. Checks all picture tubes (including the new short-neck 110 degree RCA-type picture tubes) for cathode emission, shorts and life expectancy. Also rejuvenates and restores cathode emission of weak picture tubes.

Model AD-1 (factory wired only) \$4.50



Save valuable servicing time and earn extra money with the FC-1

Model FC-1
factory
wired and
tested

\$58.50
(factory wired only)

OUTSTANDING VALUE FEATURES

Checks each section of multi-purpose tubes simultaneously. If one section is defective the tube will read "Bad" on the meter scale ■ 41 tube sockets accommodate all present and future tube types ■ Less than 10 seconds required to test any tube ■ Large D'Arsonval type meter is extremely sensitive, yet rugged . . . with two multi-color "Good-Bad" scales ■ Selection of 12 filament voltages ■ Line isolated ■ 7-pin and 9-pin straighteners mounted on panel ■ Large easy-to-read quick reference chart for over 600 tube types in use today ■ New tube listings furnished periodically.

Here's an in-circuit condenser tester that does the whole job!

The IN-CIRCUIT CONDENSER TESTER Model CT-1


Actually steps in and takes over where other in-circuit condenser testers fail. The tremendous range of operation makes it an absolute must for every serviceman.

Checks in-circuit: Quality . . . including leakage, shorts, opens, and intermittents ■ Value of all condensers 200 mmfd. to .5 mfd. ■ Electrolytics for quality — any size ■ Transformer, socket and wiring leakage capacity.

Checks out-of-circuit: Quality . . . including leakage, shorts, opens and intermittents ■ Value of all condensers 50 mmfd. to .5 mfd. ■ Electrolytics for quality — any size ■ High leakage to 300 megohms ■ New or unknown condensers.

JUST A FEW FEATURES OF THE CT-1

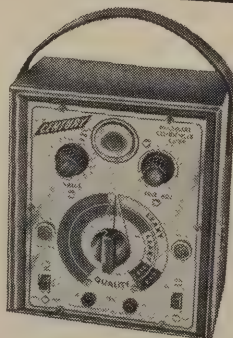Ultra-sensitive 2 tube drift-free circuitry ■ Multi-color scale gives simultaneous readings of both quality and value in-circuit or out-of-circuit ■ Cannot damage circuits ■ Electronic eye balance indicator for even greater accuracy ■ Line isolated ■ Fully shielded.



Model CT-1K
kit form

\$24.95

Model CT-1W
factory wired

\$34.95

CENTURY ELECTRONICS CO., INC.

111 Roosevelt Ave.,
Dept. 112, Mineola, N.Y.

Please rush the instruments checked for a 10 day examination period. If satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. If not completely satisfied I will return the instrument within 10 days and there is no further obligation. It is understood there will be NO CARRYING CHARGES. Should I fail to make payment when due, the full unpaid balance shall become due and payable at once.

CHECK INSTRUMENTS DESIRED

- ☐ Model FC-1 (wired) \$58.50
- ☐ \$14.50 within 10 days. Balance \$11.00 monthly for 4 months.
- ☐ Model CT-1W (wired) \$34.95
- ☐ \$9.95 within 10 days. Balance \$5.00 monthly for 5 months.
- ☐ Model CT-1K (kit) \$24.95
- ☐ \$9.95 within 10 days. Balance \$5.00 monthly for 3 months.

Prices Net F.O.B. Mineola, N. Y.

Name.....

Address.....

City..... State.....

TELEVISION

TWO-IN-ONE PROPOSITION

Two brothers had been in our store looking over TV receivers. After considerable haranguing between them—most of it unintelligible since they'd quiet down when a salesman approached—one of them bought an expensive TV set. We delivered it, installed the antenna system and were paid for the job.

Our record books showed more than the usual number of calls for service, far exceeding the average for the fine set we had sold.

Finally we got the story from a disgruntled neighbor of the loud-mouthed brother. Unwilling to pay the legitimate price for a receiver like the one his brother had bought from us, the mouthy man had purchased an exactly similar one from a fly-by-night discounter at a substantial price reduction.

He couldn't get service from the discounter, on the low price he'd paid. So, each time the set conked out, he'd cart it over to the brother's house and hook it up in place of the one we'd sold. Then the brother would phone us that his set was on the blink.

We were servicing two sets! The next time this happened, we took the set to the shop and held it for a good price.

We learned our lesson, and now we can identify any set we sell.—H. J. Miller

(The Miller concern has our sympathy, but not too much of it. We have always insisted that a service shop should have the serial number of every set that is repaired—Mr. Miller's experience is only one of the many reasons for that. For a dealer this precaution is many times more necessary than it is for a service technician.—Editor)

Cancelled!

This space was reserved for an advertiser who refused to state whether the tubes he was selling by mail were new, unused and perfect, or in any way substandard. The publishers of RADIO-ELECTRONICS have insisted on such a statement in all mail-order tube advertising since January 1956. This policy has lost us considerable advertising space—but it protects our readers.

what
could
be

more

exciting

to a

high

fidelity

enthusiast?



new

GLASER-STEERS

GS *Seventy Seven**

the fully automatic record changer with turntable quality performance

At last — what every audiophile has been waiting for — the convenience of a fully automatic record changer with the performance quality of a transcription turntable.

The new GS-77 provides a quality of performance unsurpassed by turntables up to double the price. Flutter and wow are virtually non-existent. Rumble has, for all practical purposes, been eliminated. And as for automatic conveniences — it is, without doubt, the most advanced record changer of our time.

There is more originality in the GS-77 than in all other changers combined! See for yourself.

'SPEEDMINDER'*...the amazing GS-77 feature that automatically selects correct turntable speed, and gives you record and stylus protection no other changer can equal.

You simply set the indicator to **'SPEEDMINDER'** and automation takes over...

- with the standard groove stylus in play position, the changer automatically plays at 78 rpm.
- with the microgroove stylus in position, the changer automatically intermixes and plays 33 and 45 rpm records without regard to speed, size, or sequence.

TURNTABLE PAUSES during change cycles and doesn't resume motion until next record has come into play position and stylus is in lead-in groove. Eliminates record surface wear caused by grinding action of record dropping on moving disc—a common draw-back in other changers. And the change cycle lasts only 5 seconds — fastest in the field.

* Trademark

† Patents Pending.

Every feature† spells—Greater Convenience and Better Performance — The ARM is shock suspended and damped, effecting complete acoustical isolation from deck plate and motor and practically eliminating resonance. An accessible vernier control adjusts stylus pressure to match any cartridge requirements. Once adjusted, the variation of stylus pressure between the first and tenth record on the table does not exceed 1 gram. Transcription arm convenience includes: finger lift for manual play, as well as indicator to facilitate location of stylus in groove. The MOTOR is 4-pole induction, dynamically balanced, hum shielded and shock mounted — all to assure accurate, constant speed, and smooth operation.

The IDLER and other rotating parts are precisely centered and mounted on low friction bearings. Idler automatically disengages in 'off' position. Prevents flat spots and wow. **MUTING SWITCH** and R/C filter network squelch all annoying sounds.

The GS-77 is absolutely jam-proof — built for years of trouble-free performance. A single knob controls all automatic and manual operations. The changer is pre-wired for easy installation, and is dimensioned to replace most changers.

less cartridge and base — **ONLY \$59⁵⁰**

Styling of the new GS-77 is gracefully simple — enhanced by its ebony and brushed gold finish and oyster white turntable mat. For a thrilling experience — see it — hear it at your high fidelity dealer. Descriptive literature available on request. Dept. RE-12.

GLASER-STEERS CORP. 20 Main Street, Belleville 9, N. J.
In Canada: Glaser-Steers of Canada, Ltd., Trenton, Ontario.
Export Div.: M. Simons & Son, Co., Inc., New York 7, N. Y.

TV Service Clinic

conducted by

ROBERT G. MIDDLETON

A COLOR TV receiver can be a rather frightening object, when we go out on our first service call. All the confidence that we feel back at the shop seems to sort of ooze out of our pores as we turn on the receiver and begin to study the symptoms.

However, most color receiver servicing requires only replacement of defective tubes. Fig. 1 shows a partial block diagram of a color receiver. You can see that a faulty tube can sometimes be localized by observing the reproduction (or lack of reproduction) of chroma, black-and-white and audio signals. Even the noise reproduction has a definite story to tell about the receiver's circuits.

A complaint of no sound and no picture may indicate a faulty tube in the front end or in the if stages prior to the sound takeoff point.

A complaint of no color picture, but with black-and-white reproduction and sound OK, points to a faulty tube in the chroma or possibly in the color sync sections. For example, if the chroma bandpass amplifier tube is dead, no chroma signal can pass. In some cases, when the color afc tube is defective, the

color signal rolls so fast on the screen that the colors produce a neutral gray, and the color drops out of the picture.

If the color picture is satisfactory but the sound is dead, the tubes in the sound channel should be checked, just as in a black-and-white receiver.

When the symptom is very poor definition, with colors dim and bluish, check the tubes in the Y channel between the color takeoff point and the picture tube.

Clear distinction must be made between *raster* colors and *signal* colors on the screen of the picture tube. Raster colors are present during black-and-white reception and in the absence of a signal. It is necessary to apply a color signal to the receiver before a check of the *signal* colors can be obtained. Signal colors appear superimposed upon the raster colors.

Raster colors are controlled by dc voltages on the cathodes, grids and screen grids of the color picture tube. Since modern color receivers often use dc coupling in the chroma channels, a tube fault which affects the signal may affect the background too. Here, the circuit diagram for the receiver is a valuable guide.

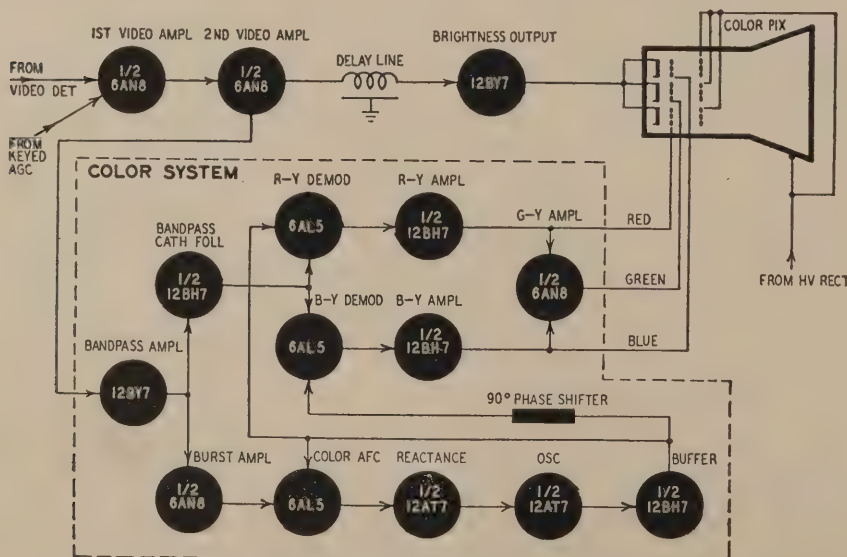


Fig. 1—Block diagram of color circuits in the Motorola TS-902.

Blown fuses

A few days after an Olympic 24-inch set (chassis 4CG26) was installed, it started blowing the $\frac{3}{8}$ -amp 250-volt fuses. A replacement fuse would last only a couple of days. The factory advised me to return to the flyback transformer. However, it seemed to me that the filter choke was grounding out. I replaced the choke with a resistor, slipped in a new fuse and the set operated OK for another day or so.

Then the damper tube blew and something in the horizontal output circuit is shorting out and smoking. The set is dead. Where should I start to nail this one down once and for all?—J. J. B., New Jersey.

I would suggest that the initial trouble with this receiver was a defect in the flyback, which occasionally drew excessive current from the horizontal output tube. However, there is also the possibility that the B-plus drain is marginal, due to an unsuspected leaky electrolytic capacitor in the power supply system. It is easy to confuse such a fault with an apparent grounding of the filter choke, which you noted. I suggest that you check through all the B-plus circuits to find out which one is drawing too much current (which causes the smoke that you mentioned). This check should lead you to the main difficulty. Even an ohmmeter check of the B-plus branch circuits should serve.

No sound

Complaint on a Crosley GC21TOL was "sound dead." The picture was normal. I found at the grid of the 25L6 a voltage of 170 instead of 142. Why is this voltage high and killing the sound?—A. F., Hamilton, Ont.

Use a .01- μ f series capacitor with a pair of headphones as an audio signal tracer. Find out where the sound stops, and go to work at that point in the circuit. It is certainly true that a voltage of 170 on the grid of the 25L6 will kill the sound, if the cathode is running at the specified 150 volts. The 25L6 in this receiver is used as a voltage divider. If the receiver is operating normally except for sound, look for trouble in the divider resistors which bring the 280-volt supply down to 142 volts.

Dim raster

I am working on a G-E model 21C208U with symptoms that would seem to indicate a simple repair job. However, I have worked myself blue in the face and cannot come up with the trouble. It is a condition of intermittent dimming of the raster with insufficient vertical sweep. The set may be OK for a day or the trouble may occur when it is first turned on. All voltages and resistances check OK except the cathode of the 6V3 which reads 740 volts instead of 645.—R. R., Westernport, Md.

This intermittent trouble sounds very much like a bad electrolytic which is breaking down on occasion. The de-

(Continued on page 93)

Build the Best— build ALLIED knight®-kits

the finest electronic equipment in money-saving kit form

LOWEST COST

ALLIED'S giant buying power passes biggest savings on to you—you do the easy assembly and your finished instrument equals the performance and appearance of equipment selling for several times the low KNIGHT-KIT cost. Your savings are BIG.

EASIEST TO BUILD

KNIGHT-KIT "Step-and-Check" instruction manuals with wall-sized picture diagrams are marvels of clarity—it's like having a good instructor at your side. No experience required—you can easily build any KNIGHT-KIT and get professional results.

LATEST DESIGN

Each ALLIED KNIGHT-KIT incorporates the very latest circuitry for top-quality performance. Tried and proved professional design and the use of premium quality parts throughout help insure your building success to bring you quality results.

COMPLETE KIT SELECTION:

- HI-FI
- HOBBY
- INSTRUMENT
- AMATEUR




MONEYBACK GUARANTEE. When properly assembled, KNIGHT-KITS fully meet published specifications or we refund your money in full.

EASY TERMS. If your KNIGHT-KIT order comes to \$45.00 or more, you can make your purchase on our attractive Easy Payment Plan.

High Fidelity Everyone Can Afford

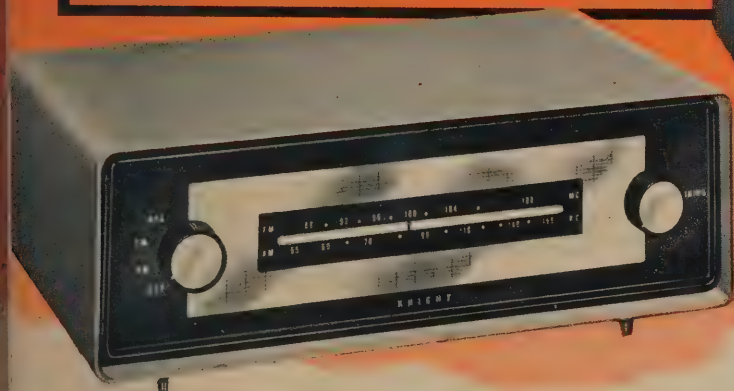- World's Finest Hi-Fi Kits
- Custom-Styled
- Easiest to Build Hi-Fi
- Money-Saving



knight-kit 18-Watt Complete Hi-Fi Amplifier Kit

Model Y-786

\$39.95

Only \$3.99 down

- The Last Word in Custom Hi-Fi Styling
- Full 18 Watts with Superb Hi-Fi Specifications
- 8 Inputs for Every Desired Signal Source
- Printed Circuit Switch and Printed Circuit Boards
- Full Equalization for All Record Types

Here is a custom-styled, easy-to-build complete Hi-Fi amplifier at a price that defies comparison. Delivers full 18 watts output with wide-range, flat frequency response for true hi-fi reproduction. Features 8 inputs for every possible signal source, including NARTB equalized tape head input. At full 18 watts output, distortion is only 0.5%; uses new RCA 6973 hi-fi output tubes. Frequency response is ± 1 db, 20-30,000 cps; tape head and magnetic cartridge sensitivity, 5 microvolts for 18 watts output; hum and noise level better than 60 db below 18 watts. Output taps for 4, 8 or 16 ohm speakers. Controls: Input and Record Equalization; Bass Boost and Attenuate; Treble Boost and Attenuate; Volume. Simplest assembly is made possible through the use of an exclusive printed circuit switch and two printed circuit boards—most of the kit wiring is already done for you. With custom-styled French-gray "space-saver" case on tapered feet finished in chrome, 4 x 13 x 8". Complete with case, tubes, all parts, and step-by-step instructions, for easy, error-free assembly. Shpg. wt., 15 lbs.

Model Y-786. 18-Watt Hi-Fi Amplifier Kit. Net only \$39.95

Model Y-787

\$49.95

Only \$4.99 down

- Latest Time-Saving Printed Circuit Design
- Flywheel Tuning
- Automatic Frequency Control
- 2.5 μ v FM Sensitivity
- True High Fidelity Response
- Beautiful Custom-Styled "Space Saver" Case

The best-looking, best-performing FM-AM tuner kit your money can buy! Carefully designed for quick, easy construction—a tuner you'll enjoy assembling and be proud to own, both for its amazing musical performance and outstanding beauty. Covers the full AM broadcast band and 88 to 108 mc FM. On FM, sensitivity is a remarkable 2.5 microvolts for 20 db of quieting; hum and noise, -60 db; IF bandwidth, 200 kc at 50% down on curve; response, ± 0.5 db, 20-20,000 cps. On AM, sensitivity is 3 microvolts for 10 db signal-to-noise ratio; IF bandwidth, 8 kc at 50% down on curve; response, 20-8000 cps. Outstanding features include: Inertia Flywheel Tuning or effortless, accurate tuning; Automatic Frequency Control (plus AFC disabling) to "lock-in" FM stations; printed circuit board with most of the kit wiring already done for you) assures time-saving, error-free assembly; pre-aligned RF and IF coils; tuned RF stage on FM; drift-compensated oscillator; neon glow tuning pointer; cathode follower output; two output jacks—one for recorder, one for amplifier; rotatable built-in ferrite antenna for AM. Includes beautiful French-gray case with chrome-finished tapered feet, 4 x 13 x 8". Ideal for use with 18, 20 or 30 watt KNIGHT-KIT amplifiers. Ready or easy assembly. Shpg. wt., 12 lbs.

Model Y-787. FM-AM Tuner Kit. Net only \$49.95

EASY TERMS TO FIT YOUR BUDGET. ALLIED KNIGHT-KITS may be purchased under our Easy Payment Plan. Your order need total only \$45.00 or more—only 10% down, small monthly payments thereafter. No red tape—fast handling assured.

Our 37th Year



® Registered Trade-Mark of Allied Radio Corporation

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL.

Now you can have Custom-Styled Hi-Fi in **ALLIED**



knight-kit 30-Watt Complete Hi-Fi Amplifier Kit

Model Y-762


\$76⁹⁵

Only \$7.69 down

- Full Equalization, $\pm \frac{1}{2}$ db of Recommended Accuracy
- Printed Circuit Switches • Printed Circuit Boards
- 8 Inputs For Every Possible Signal Source
- Full 30 Watts Output • Custom-Styled Beauty

Comparable to the best in Hi-Fi—at far less cost! Deluxe features include: Linear-deluxe Williamson-type circuit for flawless response; equalization for all records within $\frac{1}{2}$ db of recommended accuracy; 2 exclusive new printed circuit switches in preamp section (no complex wiring to do); 3 printed circuit boards for time-saving, error-free assembly; separate, continuously variable Level and Loudness controls; use of premium 12AY7 tube for low noise and hum; DC on all filaments of preamp tubes; exclusive A-AB-B speaker selector switch (use speakers of mixed impedances without mismatch). 8 inputs: Tape Head direct; G.E. and Pickering cartridges; Ceramic cartridge; Microphone; Auxiliary; Tape Preamp; Tuner (with separate Level Set control). Power amplifier response, $\pm \frac{1}{2}$ db, 15-100,000 cps at full 30 watt level; distortion—harmonic, 0.55% at 30 watts—IM, 0.74% at 20 watts. Separate Bass and Treble controls; rumble filter switch; variable damping. Output, 8 and 16 ohms. With smart French-gray cabinet, 4 x 15 x 15". Ready for easy, money-saving assembly. Shpg. wt., 32 lbs.

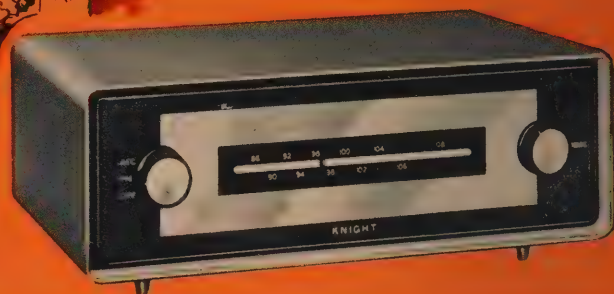Model Y-762. 30-Watt Hi-Fi Amplifier Kit. Net only.....\$76.95



knight-kit High Fidelity FM Tuner Kit

Model Y-751

\$38⁹⁵

Only \$3.89 down

- Authentic High Fidelity FM Response
- Flywheel Tuning • Automatic Frequency Control
- Printed Circuit • Pre-Adjusted Coils and IF's
- 4 Microvolt Sensitivity Guaranteed

Here is top value in creative engineering, impressive hi-fi performance and distinctive design—a tuner you'll be proud to build and own. Covers the full FM band, 88 to 108 mc. Features Automatic Frequency Control (with disabling feature) to "lock-in" stations and prevent drift; Inertia Flywheel Tuning for velvet-smooth, accurate station selection; pre-adjusted RF coils; pre-aligned IF's; cascode broad-band RF amplifier; drift-compensated oscillator; neon bulb pointer. All critical wiring is already done for you in the form of a printed circuit board—assembly is simple. Sensitivity is 4 microvolts for 20 db of quieting across entire band; output, 2 volts at 1000 microvolts input; IF bandwidth, 200 kc; response, 20-20,000 cps. with only 0.6% distortion. Output jacks for amplifier and tape recorder; cathode follower output. Ideal for use with the KNIGHT-KIT amplifiers, or any amplifier with phono-tuner switch. Features custom-styled case in French-gray, with tapered chrome-finished feet, 4 x 13 x 8". Includes all parts, tubes and step-by-step instructions for easy assembly. Shpg. wt., 12 lbs.

Model Y-751. Hi-Fi FM Tuner Kit. Net only.....\$38.95

knight-kit Deluxe 3-Way Speaker System Kit

Model Y-937


\$89⁵⁰

Only \$8.95 down

- Pre-Finished "Quik-Craft" Corner Enclosure
- Klipsch Designed and Licensed
- Famous Knight 12" 3-Way Speaker
- Easy to Assemble—Top Hi-Fi Quality
- Choice of Enclosure Finishes

Deluxe quality high fidelity speaker system at a money-saving low price. Easy to assemble—all you need is a screwdriver. System includes KNIGHT "Quik-Craft" corner-type folded-horn enclosure kit, and the famous-value KNIGHT 3-Way 12-inch speaker. Just assemble the enclosure—no finishing required—all surfaces are finished in hand-rubbed Korina blonde, mahogany or walnut. The speaker is the new 3-way type: 12" woofer cone for bass (full $1\frac{1}{4}$ pound woofer magnet), conical radiator for mid-frequencies, built-in compression-type tweeter (with wired calibrated dial) for highest frequencies. Unexcelled enclosure efficiency and superb speaker performance combine to cover the whole spectrum of audible sound for true hi-fi response from 35 to 15,000 cps, ± 3 db. Kit includes 12" 3-Way speaker, prefinished enclosure panels, grille cloth, hardware and instructions. Specify Korina blonde, mahogany or walnut when ordering. Shpg. wt., 44 lbs.

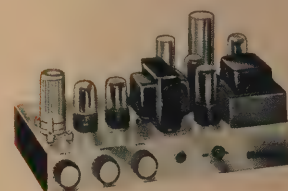Model Y-937. 3-Way Speaker System Kit. Net only.....\$89.50



knight-kit 10-Watt Hi-Fi Amplifier Kit

Y-753

\$23⁵⁰

Low-cost, authentic hi-fi amplifier. Response, ± 1 db, 30-20,000 cps. Input for crystal phono or tuner; chrome-plated chassis is punched for preamp kit below, to permit use of magnetic phono. Only 0.5 volt drives amplifier to full output. Separate bass and treble controls. Only 1% harmonic distortion. Matches 8-ohm speaker. 7 x 13 x 6". With all parts, tubes and instructions. Shpg. wt., 13 lbs.


Model Y-753. Net only...\$23.50
Y-235. Preamp Kit.....\$ 3.10
Y-757. Metal Cover....\$ 3.95

ALLIED RADIO

America's Pioneer in Electronic Kits

knight-kits

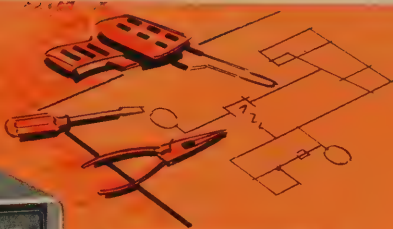THE VERY FINEST MUSICAL QUALITY—SO EASY TO BUILD
MONEY-SAVING HI-FI EVERYONE CAN AFFORD



So Easy To Build
Anyone can build
KNIGHT-KIT HI-FI.
No experience re-
quired to get top
results!



knight-kit High Fidelity Preamplifier Kit

Model Y-754


\$39.95

Only \$3.99 down

- Exclusive Printed Circuit Switches and Boards
- Equalization $\pm \frac{1}{2}$ db of Recommended Accuracy
- 8 Inputs Including Tape Head
- Self-Powered
- DC on All Tube Filaments
- Custom-Styled

Sensational Hi-Fi design at amazing low cost. Provides precise record equalization guaranteed within $\frac{1}{2}$ db of recommended accuracy!—more accurate than all but the most expensive factory-built preamps. Includes exclusive new KNIGHT-KIT printed circuit switches for easy, error-free assembly; 2 printed circuit boards eliminate all other wiring, except for power supply and control leads—so easy to build. Has built-in power supply; includes premium 12AY7 and ECC82 tubes. Frequency response, ± 0.5 db, 10-50,000 cps. Has 8 inputs: Tape Head; G.E. Phono; Pickering Phono; Ceramic; Microphone; Auxiliary; Tape Preamp; Tuner. Level adjustment for tuner input. Includes separate Bass and Treble controls; separate Level and Loudness controls; Rumble Filter switch; DC on all tube filaments; cathode follower output; 2 extra AC outlets. You get every advanced hi-fi feature in this easy-to-build preamplifier at the lowest possible cost. Includes beautiful custom-styled French-gray case, with tapered chrome-finished legs, 4 x 13 x 8". With all parts, tubes, step-by-step instructions; ready for easy assembly. Shpg. wt., 12½ lbs.

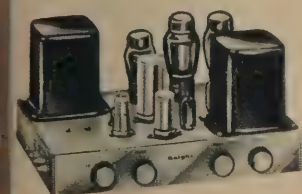Model Y-754. Hi-Fi Preamp Kit. Net only.....**\$39.95**



knight-kit 20-Watt Hi-Fi Amplifier Kit

Y-750

\$35.75

Only \$3.57 down

True hi-fi for less! Complete with full set of controls and built-in preamplifier. Response, ± 1 db, 20-20,000 cps; distortion 1% at 20 watts. Inputs for magnetic phono, microphone, crystal phono or recorder, and tuner. Compensation positions for 78 and LP records. Separate bass and treble controls. Output impedances, 4, 8, 16 and 500 ohms. Chrome-plated chassis. 7 x 13 x 14". Ready for easy assembly. Shpg. wt., 20 lbs.

Model Y-750. Net only...**\$35.75**
Y-758. Metal Cover.....**\$4.15**

knight-kit 2-Way Hi-Fi Speaker System Kit

Model Y-789

\$49.95

Only \$4.99 down

- Easy to Assemble—Pre-Finished Enclosure
- High Fidelity Response, 45 to 14,000 cps
- 12" Woofer and Horn-Type Tweeter
- A Wonderful Money-Saving Speaker Value

BIG SAVINGS—assemble your own quality KNIGHT-KIT 2-way speaker system—it's quick and easy! The cabinet is *pre-finished* in full-grained, high luster blonde or mahogany—you just assemble 7 pieces, mount the speaker components and enjoy rich, thrilling hi-fi sound—at incomparably low cost. Special Jensen-engineered baffle features "ducted port" construction to bring out the full beauty of bass notes, perfectly matching the Jensen woofer and compression tweeter; genuine L-pad control is rear-mounted to permit adjustment of tweeter for best tonal balance. Impedance, 16 ohms. The assembled unit delivers a frequency response of 45 to 14,000 cps. Enclosure measures 26 x 19 x 14". Beautifully styled to blend in any room. Kit includes Jensen 12" woofer, Jensen compression-type tweeter, pre-finished wood parts (with grille cloth installed), acoustic material, glue, hardware and step-by-step instructions. Absolutely no furniture finishing required. *Specify blonde or mahogany finish when ordering.* Shpg. wt., 33 lbs.

Model Y-789. 2-Way Speaker System Kit.

Net only.....**\$49.95**



12" Woofer



Tweeter with Controls



KNIGHT-KIT HI-FI IS AVAILABLE ON EASY TERMS TO FIT YOUR BUDGET

Fascinating

ALLIED **knight-kits**

FOR EXPERIMENTERS
AND HOBBYISTS



knight-kit 2-Transistor Pocket Radio Receiver Kit

- Model Y-262 • Loud, Clear Local Reception
• Newest Printed Circuit Board
• Built-In Loop Antenna
• Complete Kit—Nothing Else To Buy

\$14.65

It's fun to build this pocket-size two-transistor radio—and you'll enjoy its crystal-clear local broadcast-band reception wherever you go! Fits in your pocket, or with its button-down flap, can be worn from your belt. Completely self-contained with built-in ferrite loopstick antenna—no external antenna needed. Extremely efficient reflex type 2-transistor circuit actually does the work of 3 transistors! Printed circuit board reduces building time to about one hour. Has air-dielectric variable capacitor for easy, accurate station tuning. Operates for months and months on long-life alkaline battery supplied. Sensitive miniature earpiece provides crystal-clear tone. Handsome tan carrying case, plastic-impregnated, is styled to resemble leather; only 4x3½x1¼". Kit includes all parts, transistors, earpiece, battery and case. Shpg. wt., 1½ lbs.

Model Y-262. Net only\$14.65

knight-kit "Trans-Midge" Transistor Receiver Kit

- Model Y-767 Tiny, cigarette-pack-size one-transistor radio kit—fascinating to build—so low-priced. This novel miniature receiver will provide endless listening

\$2.45

pleasure the moment assembly is completed. Covers the local AM broadcast band with exceptional sensitivity and selectivity. Special features include: Efficient, slug-tuned coil for excellent station separation; external knob for easy station tuning; low-drain transistor operating for months from single penlight cell supplied; hinged-back, red plastic case. Kit includes all parts, transistor, battery, compact case and easy-to-follow instructions for quick assembly. (External antenna and headphones required.) Shpg. wt., 8 oz.

Model Y-767. Net only\$2.45
J-149. 4000 Ohm Headphones. 1 lb.\$2.15
C-100. Antenna Kit. 1½ lbs.\$1.03

knight-kit 10-Circuit Transistor Lab Kit

- Model Y-299 Sensational experimenters' transistor kit—an electronic marvel! Perfect for experimenter, student or hobbyist.

\$15.75

Assemble basic parts once, then complete project after project (10 in all), by simply plugging leads into proper jacks on printed circuit board—no wiring changes needed. You learn how transistors operate by "plugging in" to make any one of the following circuits; AM radio for strong headphone reception; 2-stage audio amplifier; wireless broadcaster; code practice oscillator; electronic timer; electronic switch; electronic flasher; photoelectric relay; voice-operated relay; capacity-operated relay. Includes all parts, 2 transistors, battery, headphones, circuit leads, relay, photocell, special guide cards for each project, explanation of each circuit. 3 lbs.

Model Y-299. Net only\$15.75


knight-kit 5-Transistor Superhet Personal Portable Radio Kit

- Model Y-766 • Styled to Equal the Finest
• Push-Pull Audio Drives 3½" Speaker
• Printed Circuit for Easy Building
• 200 Hour Battery Playing Life

\$29.95

Beautiful, easy-to-build transistorized personal portable with every ultra-modern design feature: 5 Texas Instrument Co. transistors; latest printed circuit chassis for easy, error-free assembly; bigger-than-average 3½" speaker; class B push-pull audio output; built-in high-gain ferrite loopstick antenna; plus phone jack output for private listening. Provides sensitive reception of the AM broadcast band with exceptional tone quality. Ultra-smart high-impact ivory plastic case has handsome gold trim with ebony accents; includes pull-out handle; only 7½x3½x1¼". With all parts, transistors, 9 volt transistor radio battery, carrying case and instructions anyone can easily follow. Shpg. wt., 2 lbs.



Model Y-766. Net only\$29.95

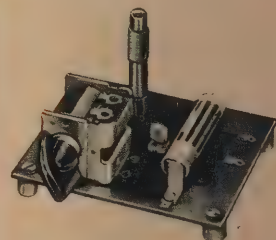

1-Transistor Radio Kit

\$3.95 Offers excellent AM local broadcast headphone reception. Printed circuit board for easy assembly. Operates from single penlight cell for months. Complete with all parts, transistor and penlight cell. (Antenna and headphones required.) Shpg. wt., 1 lb.


Model Y-765. Net only\$3.95

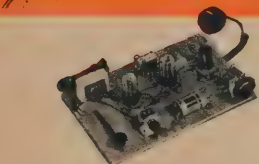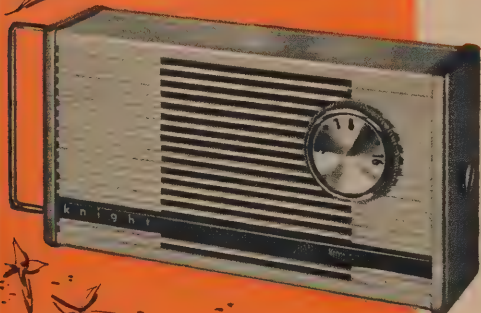

"10-In-One" Electronic Lab Kit

\$12.65 Famous experimenters' kit. Builds any of 10 fascinating projects, including broadcast receiver, wireless phono oscillator, code practice oscillator, signal tracer, relays, etc. Shpg. wt., 5 lbs.


Model Y-265. Net only\$12.65

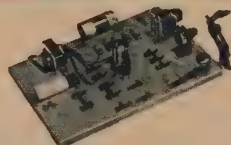

"6-In-One" Electronic Lab Kit

\$8.45 A favorite with beginners. After basic wiring is completed, you make circuit changes without soldering. Builds any of six favorite projects, including radio, wireless broadcaster, etc. Shpg. wt., 3 lbs.


Model Y-770. Net only\$8.45

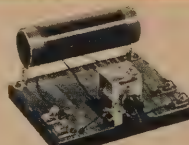

Crystal Set Hobby Kit

\$2.15 Entertaining, educational. Delivers clear headphone reception of local broadcast stations. With all parts, ready for easy assembly. (Antenna and headphones required.) Shpg. wt., 1 lb.

Model Y-261. Net only\$2.15

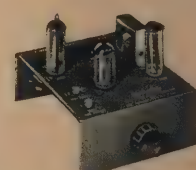

Wireless Broadcaster Kit

\$9.50 Play music or make announcements through your radio set—no connection to set required! Loads of fun—easy to build. Works up to 50 feet from set. Shpg. wt., 3 lbs.

Model Y-705. Net only\$9.50

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL.

FUN TO BUILD . . . INSTRUCTIVE . . . LATEST CIRCUITS FOR TOP PERFORMANCE
WIDEST CHOICE OF QUALITY HOBBYIST KITS



interruption of light beam triggers relay, which in turn sounds chime or bell, turns on lights, etc.



knight-kit Photoelectronic Relay Kit

Model Y-702 Advanced-design, ultra-sensitive photoelectronic relay—build it yourself and save! Dozens of uses: for automatic control of lights, door annunciator, burglar alarm, counting devices, etc. Provides dependable operation up to 250 feet with white light, up to 125 feet with "unseen" light (red filter) from Light Source Kit listed below. Selectable operation, with "trip" for burglar alarm to provide continuous ringing of alarm; and "auto" if relay is to operate each time beam is broken (for chimes, counting devices, turning on lights at darkness). Has SPST relay operated from thyatron; 6.3 v. terminals provide power for accessories. For 105-120 v. 50-60 cy. AC use. 6 lbs.


Model Y-702. Relay Kit. Net only. \$13.50
Model Y-703. Light Source Kit. With bulb and red filter. Shpg. wt., 3½ lbs. Net. \$6.75



"Ranger II" Superhet Receiver Kit

\$17.25 Popular Broadcast band receiver built and enjoyed by thousands. Features built-in antenna, automatic volume control, ball-bearing tuning condenser, PM dynamic speaker. Handsome plastic cabinet. Easy to assemble. AC or DC operation. Shpg. wt., 8 lbs.

Model Y-735. Net only. \$17.25

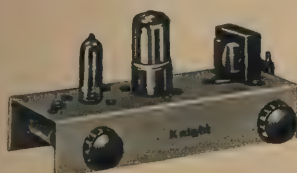

Phono Amplifier Kit

\$9.45 Build it yourself—and save! Ideal for use in a portable phonograph—just add record player and 3-4 ohm speaker. 1½ watts output. Inverse feedback circuit. Easy to assemble. Shpg. wt., 3 lbs.

Model Y-790. Net only. \$9.45



knight-kit "Ocean Hopper" All-Wave Radio Kit

Model Y-740 This top-performing regenerative receiver puts a world of listening pleasure at your finger-tips. Tuning range (using coils listed below) is virtually world-wide; covers 155 kc to 35 mc, including every type of radio transmission: AM broadcast, marine, aircraft, distress channels, direction-finding, Amateur, frequency standard, foreign broadcast, and police. With bandspread tuning. For use with headphones or 3-4 ohm PM speaker. Kit is supplied with standard broadcast band coil and all tubes and parts. (Less extra coils, headphones, speaker and cabinet.) Shpg. wt., 5 lbs.

Model Y-740. Net only. \$11.95

Y-746. Cabinet for above. 1½ lbs. Net \$2.90

Extra coils available: Long Wave Coil (155-470 kc), Net 79c. Short Wave (1.65-4.1 mc; 2.9-7.3 mc; 7-17.5 mc and 15.5-35 mc). Each 65c.



knight-kit "Space-Scanner" Bandswitching World-Wide Radio Kit

Model Y-243 • Broadcast or Short Wave Reception
 • Sensitive Regenerative Circuit
 • Convenient Bandspread Tuning
 • Built-In Loudspeaker

\$15.95 Imagine the thrill of hearing overseas broadcasts on a precision receiver you've built yourself—and then, at the flip of a switch, being able to tune to your favorite local broadcast station! Bandswitch selects exciting short wave, including foreign broadcasts, amateur calls, aircraft, police and marine radio on the 6.5 to 17 mc range, as well as standard 540-1700 kc broadcasts. Features highly sensitive regenerative circuit. Includes built-in 4" PM speaker and beam-power tube for strong volume and clear tone. Headphone connectors are available for private listening; switch cuts out speaker. Controls: Bandspread, Main Tuning, Antenna Trimmer, Bandswitch, Regeneration, Volume. 7x10x6". Easy to build from step-by-step instruction manual. For 110-120 v., 50-60 cy. AC or DC. (Less cabinet.) Shpg. wt., 5 lbs.

Model Y-243. Net only. \$15.95

Y-247. Cabinet for above. Shpg. wt. 2 lbs. Net. \$2.90

knight-kit 2-Way Intercom System Kit

Model Y-295 • Low Cost—Easy to Assemble
 • High Gain—Clear Tone
 • Handsome Metal Cabinets
 • Includes 50-Foot Cable

Easy to build at lowest cost—ideal for home, office, shop or school. Consists of Master unit and Remote unit. Remote unit may be left "open" for answering calls from a distance, for "baby sitting", etc. Remote also may be set for "private" operation—cannot be "listened-in" on, but it can be called and can originate calls. Master unit includes high-gain 2-stage amplifier, combination volume control and on-off switch, plus pilot light. Each unit has 4" PM dynamic speaker. System responds to even a whisper. Handsome Antique white cabinets, each 4¼x6½x4¾". With all parts, tubes and 50-ft. cable (up to 200-ft. may be added). For 110-120 v., AC or DC. 8 lbs.

Model Y-295. Master and one Remote. Net only. \$14.75

Y-296. Extra Remote Station Kit. 3 lbs. \$3.75



Electronic Photoflash Kit

\$28.50 Ideal for color or black and white photography. 1/700th-of-a-second flash; 50 watt/second output. Synchronizes with any camera with X or O shutter. (Less battery.) Shpg. wt., 4 lbs.

Model Y-244. Net only. \$28.50



Code Practice Oscillator Kit

\$3.95 Ideal for beginners learning the code. Transistorized circuit. Operates for months from single penlight cell supplied. Clear, crisp 500 cycle tone. Jacks for headphones; screw terminals for key. 1 lb.

Model Y-239. Net only. \$3.95



Phono Oscillator Kit

\$5.85 "Broadcasts" recorded music through any standard radio set up to 50 feet away. No direct connection to set required. Easy to build—fun to use. Shpg. wt., 2 lbs.

Model Y-760. Net only. \$5.85



knight-kit Low-Cost Tube Tester Kit

Model Y-143

\$29⁷⁵

- With 16 Filament Voltages
- 600 Latest Tube Types Listed
- Easy-to-Read 4 1/2" Meter
- Tests Series-String TV Tubes

Expertly designed for complete, up-to-date coverage of tube types. Tests *series-string* TV tubes; tests 4, 5, 6 and 7 pin large, regular and miniature types, octals, loctals, 9-pin miniatures and pilot lamps. Tests for open, short, leakage, heater continuity and performance (by amount of cathode emission). Big 4 1/2" square meter has clear "GOOD-?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 16 filament voltages from 0.63 to 117 volts to check virtually all receiving tubes; blank socket for future type tubes. Universal-type selector switches permit selection of any combination of pin connections. Single-unit, pre-assembled 10-lever function switch simplifies and speeds assembly. Up-to-date illuminated roll chart lists over 600 tube types. Counter model case, 5 x 14 x 10". Easy to build. 14 lbs.

Model Y-143. Net only **\$29.75**

Y-142. Portable Case model. 15 lbs. Net **\$34.75**

Y-141. Picture Tube Adapter. 1 lb. Net **\$ 4.25**

knight-kit RF Signal Generator Kit

Model Y-145

\$19⁷⁵

Build this wide-range, extremely stable RF signal generator—save two-thirds the cost of a comparable wired instrument! Large, semi-circular dial is clearly calibrated; range is covered in 5 separate bands for close accuracy in setting individual frequencies. Ideal for aligning RF and IF stages in radio and TV sets and for troubleshooting audio equipment. Delivers output on fundamentals from 160 kc all the way out to 112 mc; useful harmonics to 224 mc. Has built-in 400-cycle sine-wave audio oscillator for modulating RF; audio is also available externally. Features high-stability Colpitts circuit. Convenient jack for external modulation. Maximum audio output 10 volts; RF output over 0.1 volt on all ranges. Step and continuous-type attenuator controls. Supplied with precision-wound coils that require no adjustment. 7 x 10 x 5". Shpg. wt., 11 lbs.

Model Y-145. Net only **\$19.75**

knight-kit 1000 Ohms/Volt VOM Kit

Model Y-128

\$16⁹⁵

Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab or Amateur use. Large 4 1/2", 400 microamp meter with separate scales for AC and DC voltage and current, decibels and resistance. Uses 1% precision resistors; has 3-position function switch and 12-position range switch. 38 ranges include: AC, DC and output volts, 0-1-5-10-50-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-1000-100,000 ohms and 0-1 meg (center scale readings of 60, 150 and 1500 ohms); Current, AC or DC, 0-1-10-100 ma and 0-1 amp; Decibels, -20 to +69 in 6 ranges. Precision resistors are used as shunts and multipliers to assure exceptional accuracy of measurements. With all parts, battery, test leads and black bakelite case with convenient carrying handle, 6 3/4 x 5 1/4 x 3 3/4". A great value in an easy-to-build quality instrument. Shpg. wt., 2 1/2 lbs.

Model Y-128. Net only **\$16.95**

knight-kit Vacuum Tube Voltmeter Kit

Model Y-125

\$24⁹⁵

- 200 μ a Movement, 4 1/2" Meter
- Includes AC, Peak-to-Peak
- Balanced-Bridge, Push-Pull Circuit
- 1% Film-Type Resistors

Top buy in an extremely stable, highly accurate VTVM. Easy to assemble—entire chassis is printed circuit board. Perfect for radio-TV service work, lab and Amateur use. Features low-leakage type switches; 1% film-type precision resistors; balanced-bridge, push-pull circuit (switch to any range without readjusting zero set); zero center scale and direct-reading db scale; polarity reversing switch. Ranges: Input Resistance, 11 megs; DC and AC rms, 0-1.5-5-15-50-150-500-1500; AC Peak-to-Peak, 0-4-14-40-140-1400-4000; Response, 30 cycles to 3 mc; Ohms, 0-1000-10K-100K and 0-1-10-100-1000 megs; db, -10 to +5. Includes all parts, tubes, battery, test leads and portable case, 7 3/4 x 5 1/4 x 4 3/4". Easy to assemble. Shpg. wt., 6 lbs.

Model Y-125. Net only **\$24.95**

Y-126. Hi Voltage Probe; extends DC to 50,000 v. **\$ 4.75**

Y-127. Hi-Frequency Probe; extends AC to 250 mc. **\$ 3.45**



6V-12V Battery Eliminator Kit

\$32⁹⁵

High current rating; continuously variable filtered output; delivers 15 amps at 6 volts, 10 amps at 12 volts. May be used as battery charger. Two meters provide simultaneous current and voltage readings. Shpg. wt., 18 lbs.

Model Y-129. Net only **\$32.95**

Transistor Checker Kit

\$8⁵⁰

Checks gain ratio of all types of transistors; checks germanium and silicon diodes; checks for continuity and shorts. A valuable instrument at very low cost. Easy to assemble. Shpg. wt., 2 1/2 lbs.

Model Y-149. Net only **\$8.50**



Flyback Checker Kit

\$19⁵⁰

Checks condition of all types of horizontal output transformers and deflection yokes, as well as TV linearity and width coils. 4 1/2" meter; widest range in its field. Shpg. wt., 6 lbs.

Model Y-118. Net only **\$19.50**



Sweep Generator Kit

\$43⁷⁵

Extreme linearity on a par with costly lab instruments; fundamentals to 250 mc; output flat within 1 db; electronic blanking. Easy, money-saving assembly. Shpg. wt., 16 lbs.

Model Y-123. Net only **\$43.75**



Capacitor Checker Kit

\$12⁵⁰

Tests capacitors while in the circuit! Has widest range—20 mmf to 2000 mfd. Exclusive circuit for cancelling lead capacity. "Magic Eye" indicator. Save 60% over factory-wired units. 5 lbs.

Model Y-119. Net only **\$12.50**



ADVANCED-DESIGN INSTRUMENTS FOR SERVICE, INDUSTRIAL AND RESEARCH USE IN EASIEST-TO-BUILD, MONEY-SAVING KIT FORM



knight-kit 20,000 Ohms/Volt VOM Kit

Model Y-140 Outstanding quality and performance at money-saving low price. Features 1% precision multipliers; $4\frac{1}{2}$ " meter accurate within 2% of full scale deflection; 50 microamp sensitivity for 20,000 ohms/volt input resistance on DC; front panel "Zero adjust"; single switch to select function and range. 32 ranges: AC, DC and output volts, 0-2.5-10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-0.1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 in six ranges. Moisture-resistant film-type resistors for extreme accuracy. Carefully engineered circuit design achieves high sensitivity and extremely versatile application. Kit includes all parts, battery, test leads and black bakelite case with highly legible white markings; size $6\frac{3}{4}$ x $5\frac{1}{4}$ x $3\frac{3}{4}$ ". Easy to assemble. Shpg. wt., 5 lbs.

Model Y-140. Net only \$29.50

knight-kit High-Gain Signal Tracer Kit

Model Y-135 A remarkable value in an easy-to-build instrument which permits visual and aural signal tracing of RF, IF, video and audio circuits. Has *highest gain in its price class*. Traces signal from antenna to speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: usable gain of 91,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; combination 2-position probe, one for RF (6 mmf. input), the other for audio. Provides noise test; built-in watt-meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Binding posts provide output transformer and speaker substitution test, plus external 280 volts B+. With all parts, tubes and probe. 7x10x5". 12 lbs.

Model Y-135. Net only \$26.50

knight-kit 5" Wide-Band Oscilloscope Kit

Model Y-144

- 5 mc Width for Color TV
- Horizontal Sweep to 600 kc
- 25 mv/inch Sensitivity
- Z-Axis Input
- Printed Circuit Construction

Only \$6.90 down

Equals or betters the performance of commercially wired scopes costing far more. Two printed circuit boards and laced wiring harness assure wiring accuracy and cut assembly time. Ideal for lab use, color TV servicing and high frequency applications. Wide sweep range—15 to 600,000 cps. Vertical response, ± 3 db, 5 cps to 5 mc; only 1 db down at 3.58 mc color burst. High vertical sensitivity of .025 rms v/inch. Input capacity, 20 mmf. Outstanding features: cathode follower inputs; 2nd anode provides 1400 volts high-intensity trace; push-pull amplifiers; positive and negative locking; frequency-compensated attenuator; Z-axis input; one volt P-P calibrating voltage; astigmatism control; retrace blanking circuit; DC positioning control. Includes CRT. $14\frac{1}{2}$ x $9\frac{1}{2}$ x 16". 40 lbs.

Model Y-144. Net only \$69.00

Y-148. Demodulator Probe. Net \$ 3.45

Y-147. Low Capacity Probe. 12 mmf. Net \$ 3.45



Voltage Calibrator Kit

\$12.75 Permits use of any scope as precision peak-to-peak AC voltmeter. Puts a true square-wave voltage on scope screen. Selects any voltage between .01 and 100 volts; feeds external signal direct to scope for instant comparison. Shpg. wt., 5 lbs.

Model Y-136. Net only \$12.75

knight-kit 5" General-Purpose Scope Kit

Model Y-146

- Phantastron Linear Sweep
- 25 mv/inch Sensitivity
- Printed Circuit Board
- Retrace Blanking Circuit

Only \$4.20 down

Feature for feature the world's best oscilloscope kit value. A stand-out in its class with all these fine features: *Printed Circuit* wiring board and laced harness for quick, error-free assembly. *Phantastron Sweep Circuit* for high linearity of sweep from 15 to 150,000 cps. *25 Millivolts Per Inch Sensitivity*—3 times that of similarly priced scope kits. *Calibration Voltage*—1 volt peak-to-peak square wave, fully regulated. *Vertical Amplifier*—frequency response ± 3 db, 3 cps to 1.5 mc (± 6 db to 2.5 mc). Includes: Directly coupled positioning controls; retrace blanking circuit; frequency-compensated vertical input attenuator; positive and negative internal sync; high 2nd-anode voltage for high-intensity trace; input capacity, 45 mmf. Kit includes CRT. $9\frac{1}{2}$ x $13\frac{3}{4}$ x $17\frac{3}{4}$ ". 26 lbs.

Model Y-146. Net only \$42.00



Resistance Substitution Box

Easily determines resistor values required in a circuit. Makes available 36 standard 1-watt resistance values in 2 ranges between 15 ohms and 10 megohms, with 10% accuracy. Slide switch selects range; 18-position switch for value selection. Shpg. wt., 2 lbs.

Model Y-139. Net only \$ 5.95



Capacitance Substitution Box

Makes it easy to find capacitor values needed in a circuit. Provides 18 standard values from .0001 mfd to .22 mfd, $\pm 20\%$. All values are 600 volt, except .15 and .22, which are 400 volt. 18-position selector switch. Shpg. wt., 2 lbs.

Model Y-138. Net only \$ 5.95

Audio Generator Kit

\$31.50 Excellent design; range, 20 cps to 1 mc; less than .25% distortion; 600 ohm output. Ideal for hi-fi testing; offers the flat response of a lab standard. Shpg. wt., 16 lbs.

Model Y-137. Net only \$31.50

R/C Tester Kit

\$19.50 Measures capacitance and resistance. Balanced-bridge circuit; indicates power factor; tests capacitors at rated voltage. Large, easy-to-read dial and "magic eye." Shpg. wt., 10 lbs.

Model Y-124. Net only \$19.50



EASY TERMS AVAILABLE

Take advantage of the most liberal Easy Pay plan in electronics. On Knight-Kit orders totaling \$45 or more—just 10% down, small monthly payments thereafter. Low carrying charges—no "red tape."



knight-kit All-Band Amateur Receiver Kit

Model Y-726

\$104⁵⁰


Only \$10.45 down

- Tunes 540 kc to 31 mc
- Built-In Q-Multiplier
- Constant Running HF Oscillator
- Worthy of the Advanced Ham Operator
- Printed Circuit Bandswitch
- Printed Circuit Board • 1.5 μ v Sensitivity

A sensational communications receiver value with all the selectivity, sensitivity and features of high-priced commercial units. Uses printed circuitry throughout, including the exclusive new KNIGHT-KIT printed circuit bandswitch, for remarkably easy assembly. Covers 540 kc to 31 mc in 4 ranges; calibrated, electrical bandspread on 80-10 meter Ham bands; slug-tuned Hi-Q coils; continuous, VR tube-regulated B+ applied to HF oscillator lets you switch from standby to receive with no drift; built-in Q-multiplier peaks desired signal or nulls interference; delayed AVC; provision for crystal calibrator (below). Sensitivity, 1.5 microvolts for 10 db signal-to-noise ratio. Selectivity: variable from 300 cps to 4.5 kc at 6 db down. Exalted BFO injection. Controls: Main tuning, bandspread, band selector, Q-multiplier selectivity, Q-multiplier tune, null-off-peak, BFO pitch, RF gain, AF gain, BFO-MVC-AVC-ANL, off-stby-rec-cal, antenna trimmer, and phone jack. Cold-rolled $\frac{1}{16}$ " steel chassis. Handsome metal cabinet, 10 x 10 x 16 $\frac{1}{2}$ ". (Less phones, 8-ohm loudspeaker and S-meter.) 23 lbs.

Model Y-726. Amateur Receiver Kit. Net.....\$104.50

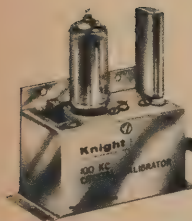Y-727. S-Meter Kit for above. 1 lb. Net.....\$9.50



knight-kit 100 Kc Crystal Calibrator Kit

Model Y-256


\$10⁵⁰

Crystal frequency standard at very low cost. Gives marker every 100 kc up to 32 mc. A "must" for marking band edges. Mounting flanges for installation in or back of receiver cabinet. Size only 1 $\frac{1}{2}$ x3". Requires 6.3 v. at 0.15 amp and 150-300 v. DC at 3-6 ma. Trimmer for zero-beating with WWV; On-Off switch. Complete with tube, crystal, all parts and easy-to-follow instructions. Shpg. wt., 1 lb.

Model Y-256. 100 Kc Crystal Calibrator Kit. Net only.....\$10.50

knight-kits FOR THE RADIO AMATEUR

knight-kit 50-Watt CW Transmitter Kit

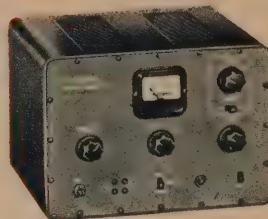

Model Y-255

\$38⁹⁵

Only \$3.89 down

- Ideal for the Novice
- Pi Antenna Coupler
- Bandswitching—80 to 10 Meters

There's exceptional value in this very popular bandswitching transmitter kit. Compact and versatile, it's the perfect low-power rig for the beginning novice as well as the seasoned veteran. Has bandswitching coverage of 80, 40, 20, 15 and 10 meters. Rated at 50 watts—actually operates at up to 60 watts on 80 and 40 meters. Oscillator is efficient 6AG7; final is reliable 807. Crisp, clean, cathode keying of oscillator and final. Built-in pi coupler permits use with random length antennas. Has highly effective TVI suppression. Other features not usually found in transmitter kits at this low price include: Ceramic-insulated final tank capacitor; pre-assembled switches; pre-wound parasitic chokes; ceramic coil forms; coax connector; crystal and VFO socket on front panel; power take-off jack for accessory equipment. Meter reads either plate or grid current of final. Takes crystal or VFO without circuit changes. Cabinet interior and chassis are copper-finished. Size, 8 $\frac{1}{2}$ x 10 $\frac{1}{2}$ x 8 $\frac{1}{4}$ ". With tubes and all parts for easy assembly. (Less crystal and key.) Shpg. wt., 19 lbs.

Model Y-255. 50-Watt Transmitter Kit. Net only.....\$38.95



Model Y-725

\$28⁵⁰

Only \$2.85 down

knight-kit Self-Powered VFO Kit

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristics for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread; separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output: 40v on 80, 20v on 40. With Spot-Off-Transmit switch for spot frequency tuning. Extra switch contacts for operating relays and other equipment. Attractive metal cabinet, 8 $\frac{3}{4}$ x 6 x 6". Ready for easy assembly. Shpg. wt., 8 lbs.

Model Y-725. VFO Kit. Net only.....\$28.50



Model Y-253

\$5⁸⁵

knight-kit Amateur RF "Z" Bridge Kit

Measures standing wave ratio (SWR) and impedance of antenna systems; ideal for adjusting antenna systems for optimum results. Measures impedances from 20 to 400 ohms up to 100 mc; SWR to 150 mc. Any VOM may be used for null indicator. With coax input and output connectors. Meters both input and bridge voltage. Calibrated dial gives direct impedance reading; includes 1% precision resistor for precise calibration adjustment. With all parts and handy plasticized SWR chart (less meter). 2 $\frac{1}{2}$ x 3 x 4 $\frac{1}{2}$ ". Shpg. wt., 1 $\frac{1}{2}$ lbs.

Model Y-253. "Z" Bridge Kit. Net only.....\$5.85

ORDER BLANK

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

ALLIED RADIO, Dept. PF, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$.....enclosed. (For parcel post, include postage—express is shipped collect).

☐ My Down Payment in the amount of \$..... is enclosed. Send Time Payment form.

Name.....

Address.....

City.....Zone.....State.....

ALL PRICES NET F. O. B. CHICAGO



Our 37th Year



FREE 1958
404-PAGE
ALLIED
CATALOG

See the 1958 ALLIED
404-Page Catalog for
complete listings of

more than 50 KNIGHT-KITS, covering Hi-Fi, Hobby, Test Instrument and Amateur Kits. The 1958 ALLIED Catalog is your complete Buying Guide to the world's largest stocks of everything in Electronics.

☐ Send FREE 404-Page 1958 ALLIED Catalog.

TELEVISION

(Continued from page 84)

fective electrolytic would be in either the vertical sweep or vertical oscillator circuit. Check the electrolytics carefully and replace those that do not have full capacitance and good power factor. It would also be advisable to make an over-voltage check of the electrolytics by running the line voltage up 15%. A bad electrolytic will break down faster on this test. It will get hot after a while, and you can find the bad one by touching its case.

Ringings

A Pacific Mercury chassis 150 has a severe case of ringing, with numerous vertical bars on the left side of the raster. The manufacturer states that the flyback transformer is probably defective. I replaced the horizontal output transformer and found that the improvement was so slight as to be negligible. I then checked all components in the horizontal output and damper circuits but this did not help either. An oscilloscope check clearly indicates a periodic oscillation in and around the flyback circuit, but the trouble cannot be pinned

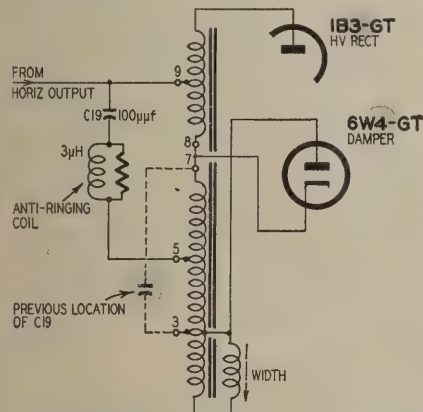


Fig. 2—Flyback circuit in the Pacific Mercury 150.

down. Perhaps I should try another flyback transformer but I am convinced that this is not the fault.

Since all the components check good, I would like to know of some circuit modification that would cure the trouble. Otherwise, perhaps you can recommend some way to re-dress the critical wires in this circuit.—G. B., Cranston, R. I.

The manufacturer's recommendation of replacing the flyback was probably based on this trouble appearing in other chassis in this series. Modifying the circuitry would be merely shooting in the dark in this case, and re-dressing wires could possibly make things worse. Because of the nature of the trouble, I feel that the most efficient way out of the trouble is to simply install an anti-ringing coil. (See Fig. 2.)

In installing this coil, you will have to remove capacitor C19, a 100- μ f unit connected between terminals 7 and 3 of the high-voltage transformer. Then connect the anti-ringing coil in series with C19, with C19 tied to terminal 9 of the transformer and the coil to terminal 5. This will place the coil

for ENGINEERED
exact
replacements
look to



Stancor exact replacement transformers are engineered—not copied. With manufacturers' original prints used as a basis for physical exactness, the circuit and operating requirements are carefully analyzed by the Stancor engineering staff. Where necessary, heavier wire, more insulation, protective coatings, corona rings, or heavier shielding are used to assure you of "better-than-new" performance. Even where the original may have been easily overloaded—it won't happen again with the Stancor replacement.

Chicago Standard has the largest engineering staff of any replacement transformer manufacturer—your assurance of a carefully and correctly designed transformer.

A free copy of the latest Stancor catalog and TV Guide is available at your distributor or direct from Stancor.

CHICAGO STANDARD TRANSFORMER CORPORATION


3509 ADDISON STREET

CHICAGO 18, ILLINOIS

Export Sales: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.

SUPER MAGNET SUPER SAVING!

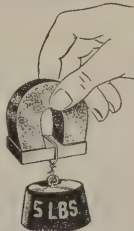Buy this Little Giant magnet, most powerful made, a sensational bargain! The low price of \$1.50 is less than 50% of what you'd pay for this magnet. Experimenters, hobbyists will find hundreds of uses for this powerful 4 oz. Alnico permanent magnet. LIFTS 5 LBS. EASILY. Limited quantity. Order several today. Measures 1 3/4 x 1 1/2". Item No. 86 Special Bargain (Shp. Chgs. 10c)



\$1.50

5 LBS

250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions.

ITEM NO. 123


\$2.95

(Shp. Chgs. 10c)



AMAZING BLACK LIGHT

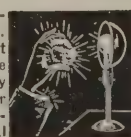250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects.



Shp. wt. 2 lbs.

ITEM NO. 87

\$2.45

(P. P. & Hdg. Chgs. 35c)

HUDSON SPECIALTIES CO., 160 W. 14th St. Dept. RE 11-57, New York 7, N. Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)

87 33 86 123

Name Please Print Clearly

Address

City Zone State



WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Shp. wt. 14 lbs.

ITEM NO. 33 NOW ONLY \$4.50

(P.P. & Hdg. Chgs. \$1.25)

TELEVISION

across a major portion of the flyback turns and choke off the ringing which is probably originating somewhere in the damper-yoke circuit. The anti-ringing coil should be approximately 3 μ h. If you wind it yourself, use a 1-watt resistor as a form.

Be sure the solder joint between the coil and capacitor C19 is smooth and round. Also, dress the coil and capacitor close to the transformer, as far as possible from the chassis to avoid corona.

Vertical sync instability

The complaint in a Philco TV-350 chassis is intermittent vertical roll. A thorough check of the vertical oscillator and output circuits showed everything to be per manufacturer's specifications.

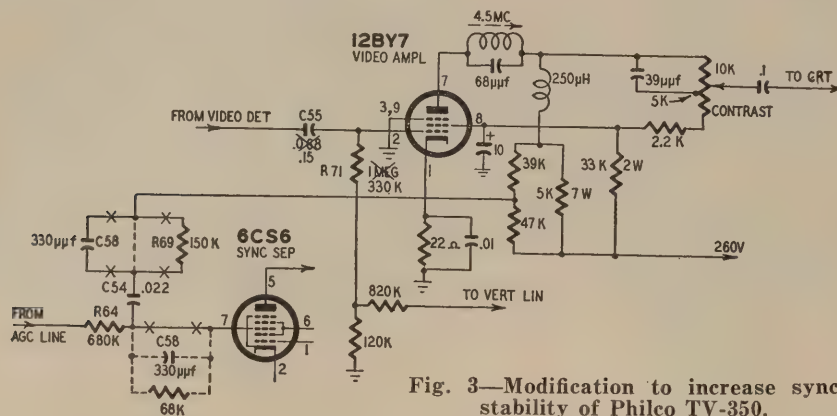


Fig. 3—Modification to increase sync stability of Philco TV-350.

The customer said that before moving here from a strong-signal area the set played perfectly. I then carefully checked the vertical integrator and the sync separator stage, but still without finding anything out of order. A few resistors were slightly off value, but replacing them did not help.

The horizontal sync on this set is extremely stable so I started replacing components in the vertical oscillator stage, and some in the sync stage, but

could not improve the situation. Short of replacing all components in the set, I would appreciate any suggestions that you may have.—P. R., Poughkeepsie, N. Y.

There is a possibility that the vertical sync pulses are of lower amplitude than the horizontal pulses. The attenuation could be due to slight misalignment. However, if alignment does not help, you should try the following circuit changes to improve sync stability. Before doing this, however, be sure to replace the 12BY7 (Fig. 3). A gassy tube can deform the vertical pulse and produce rolling.

You can improve the low-frequency coupling to the video amplifier by changing C55 from .068 μ f to 0.15 μ f. Also, reduce the value of R71 from 1

megohm to 330,000 ohms. Improve the sensitivity and stability of the sync circuit by removing capacitor C58 and resistor R69 from the circuit, and connect capacitor C54 as shown. Next, remove the leads from capacitor C54 and resistor R64 to pin 7 of the 6CS6 sync separator.

Take the removed 330- μ f capacitor C58 and connect it between pin 7 of the 6CS6 and the leads going to R64 and C54. Finally connect a resistor of about

68,000 ohms in parallel with C58. On several of these chassis the above modification has proved highly successful. And if the trouble is due solely to a signal of less than normal strength, the change will provide good vertical and horizontal synchronization.


Excessive drive

In servicing a Sylvania 1-515 chassis I replaced the horizontal output transformer because of shorted turns. The replacement flyback, obtained from Sylvania, restored the raster but the brightness was excessive and there is a drive line that cannot be eliminated by varying the drive control trimmer. I checked all components in the horizontal output and damper stages, and everything is in order. I tried changing a few component values but, while some helped a bit, they also caused other undesirable effects. Do you think the transformer is defective or is some other component damaged by the original defect?—P. R., Lynn, Mass.

The Sylvania replacement flyback transformer for this and similar chassis will often develop excessive high voltage and produce a drive line which cannot be removed by the drive control. The solution is to reduce the drive to the grid of the horizontal output tube. This can be done by replacing the 470,000-ohm resistor that shunts the drive control with one of about 150,000 ohms. This done, the drive control has adequate range to eliminate any drive bar and restore normal high voltage.

NEXT MONTH:

WHICH
COLOR BAR GENERATOR
IS BEST?

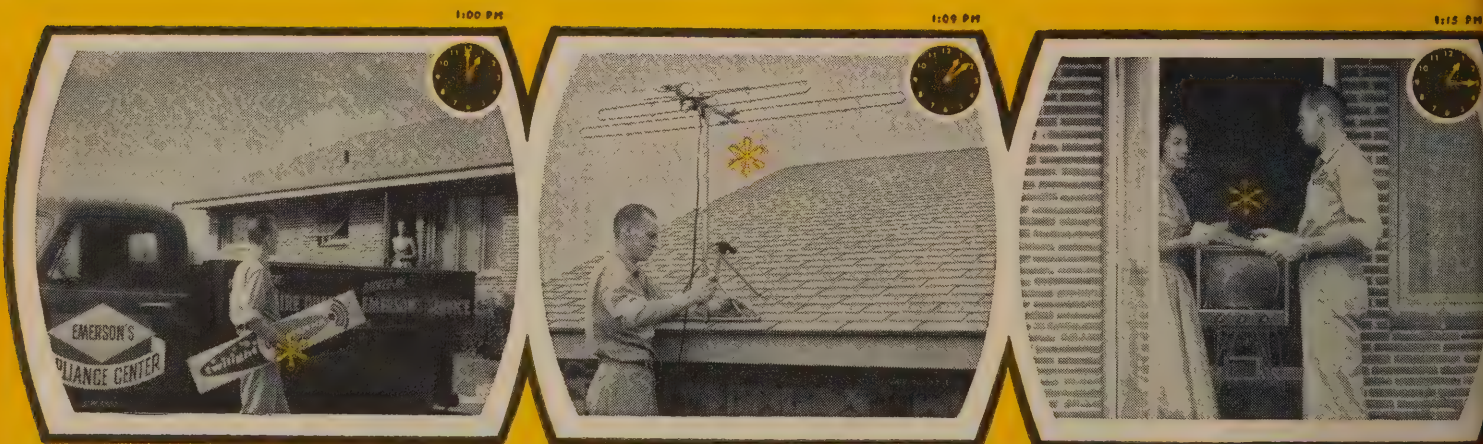

Picture of a smart TV technician
making a dollar a minute
on his way back from lunch

*
"Naturally...it's the
GOLD Twilight Antenna
by Winegard Co. RE-12
BURLINGTON, IOWA"

GUIDE

AUTRONIC-EYE®

TRAINING COURSES

MEAN MORE

BUSINESS FOR YOU!




Courses for experienced service technicians provide latest repair information—enable you to do the job faster and more efficiently.

Quick, accurate circuit diagnosis and repair to factory specifications boosts your profits. That's why so many qualified auto technicians attend these Guide training courses at no cost other than transportation and living expenses.

The Guide Lamp diploma, awarded only to those who successfully complete the course, is proof that you're equipped to give more and better service to more people—and that means business.

If you're an auto radio service dealer, come yourself, or send your technicians. There's one of 30 GM Training Centers near you. Apply through your local United Motors Service Division Distributor or write

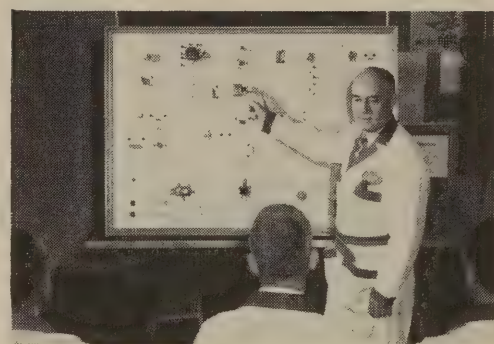GUIDE LAMP DIVISION • GENERAL MOTORS CORP. • ANDERSON, INDIANA



Jumbo-size operational panel of Guide's Autronic-Eye Circuit puts all parts out front for better, more efficient instruction.



Thirty modern GM Training Centers offer newest equipment and latest service techniques. There's one nearby... no matter where you live.




BLINKY MEANS BUSINESS!

Model TD-55 — Terms:
\$6.95 after 10 day trial then
\$5.00 per month for 4 months.

OPERATING INSTRUCTIONS
FOR MODEL TD-55
TUBE TESTER



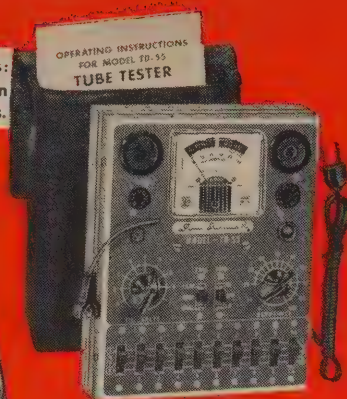Model TW-11 — Terms:
\$11.50 after 10 day trial then
\$6.00 per month for 6 months.



Model TV-12 — Terms:
\$22.50 after 10 day trial then
\$10.00 per month for 5 months.



Model TV-12 — Terms:
\$22.50 after 10 day trial then
\$10.00 per month for 5 months.

SHIPPED ON APPROVAL NO MONEY WITH ORDER NO C.O.D.

Superior's EMISSION TYPE New Model TD-55 TUBE TESTER

FOR

- The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester.
- The Professional Serviceman, who needs an extra Tube Tester for outside calls.
- The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by:

1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket. It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system. The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin or even the "top-cap."

Checks for shorts and leakages between all elements. The Model TD-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, especially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

Elemental switches are numbered in strict accordance with R.M.A. specification. One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Complete with carrying case.....

\$26⁹⁵
NET

Superior's New Model TV-40 PICTURE TUBE TESTER

Not a Gadget—Not a Make-Shift Adapter, but a Wired Picture Tube Tester With a Meter for Measuring Degree of Emission—at Only \$15.85

Of course you can buy an adapter for about \$5—which theoretically will convert your standard tube tester into a picture-tube tester; or a neon type instrument which sells for a little more and is supposed to be "as good as" a metered instrument. Superior does not make nor do they recommend use of C.R.T. adapters or neon gadgets because a Cathode Ray Tube is a very complex device, and to properly test it, you need an instrument designed exclusively to test C. R. Tubes and nothing else.

Tests ALL magnetically deflected tubes . . . in the set . . . out of the set . . . in the carton!

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

EASY TO USE: Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (ion trap need not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.

Only.....

\$15⁸⁵
NET

Superior's New Model TV-12 TRANS-CONDUCTANCE TUBE TESTER

TESTING TUBES

- Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.
- SAFETY BUTTON—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.
- NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

Extra Feature

Model TV-12 Also Tests Transistors!

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Housed in hand-rubbed oak cabinet.....

\$72⁵⁰
NET

Superior's STANDARD PROFESSIONAL New Model TW-11 TUBE TESTER

- Tests all tubes, including 4, 5, 6, 7, Octal, Lockin, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.
- The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.


EXTRAORDINARY FEATURE: SEPARATE SCALE FOR LOW-CURRENT TUBES. Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types. Housed in hand-rubbed oak cabinet.....

\$47⁵⁰
NET

USE APPROVAL FORM ON NEXT PAGE



Model TV-50 — Terms:
\$11.50 after 10 day trial then
\$6.00 per month for 6 months.

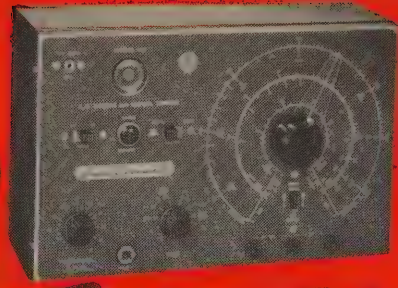

Model 76—Terms: \$6.95
after 10 day trial then \$5.00
per month for 4 months.



Model TV-60 — Terms:
\$12.50 after 10 day trial then
\$8.00 per month for 5 months.

TRY FOR 10 DAYS

before you buy! **then** if satisfactory pay in easy, interest free, monthly payments. See coupon below.

Superior's New Model TV-50 **GENOMETER**

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
 - ✓ R.F. Signal Generator for F.M.
 - ✓ Audio Frequency Generator
 - ✓ Bar Generator
 - ✓ Cross Hatch Generator
 - ✓ Color Dot Pattern Generator
 - ✓ Marker Generator
- R. F. SIGNAL GENERATOR:** 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.
VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.
BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.
CROSS HATCH GENERATOR: Pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.
DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.
MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)
Complete with shielded leads.

\$47⁵⁰ NET

Superior's New Model **76**

- ✓ IT'S A CONDENSER BRIDGE
- ✓ IT'S A RESISTANCE BRIDGE
- ✓ IT'S A SIGNAL TRACER
- ✓ IT'S A TV ANTENNA TESTER

✓ **CAPACITY BRIDGE SECTION** 4 Ranges: .00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. Will also measure the power factor of all condensers from .1 to 1000 Microfarads.
 ✓ **RESISTANCE BRIDGE SECTION** 2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms.
 ✓ **SIGNAL TRACER SECTION** With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc.
 ✓ **TV ANTENNA TESTER SECTION** Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? Locates a break in any TV antenna and measures the location of the break in feet from the set terminals.
Complete with R.F. and A.F. probes and test leads.

\$26⁹⁵ NET

Superior's New Model TV-60 **ALLMETER**

20,000 OHMS PER VOLT

Includes services never before provided by an instrument of this type. Read and compare features and specifications below:

FEATURES

- Giant recessed 6½ inch 40 Microampere meter with mirrored scale.
- Built-in Isolation Transformer.
- Use of the latest type printed circuit and 1% multipliers assure unchanging accurate readings.

SPECIFICATIONS

8 D.C. VOLTAGE RANGES: (At a sensitivity of 20,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500/30,000 Volts.
7 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500 Volts.
3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms, 0-20 Megohms.
2 CAPACITY RANGES: .00025 Mfd. to 30 Mfd.
5 D.C. CURRENT RANGES: 0-75 Microamperes, 0 to 7.5/75/750 Milli-amperes, 0 to 15 Amperes.
3 DECIBEL RANGES: —6 db to +58 db.
RF SIGNAL TRACER SERVICE: Enables following the R.F. signal from the antenna to speaker of any radio or TV receiver and using that signal as a basis of measurement to first isolate the faulty stage and finally the component or circuit condition causing the trouble.
AUDIO SIGNAL TRACER SERVICE: Functions in the same manner as the R.F. Signal Tracing service specified above except that it is used for the location of cause of trouble in all audio and amplifier systems.
Model TV-60 comes complete with book of instructions; pair of standard test leads; high-voltage probe; detachable line cord; R.F. Signal Tracer Probe and Audio Signal Tracer Probe. Pliofilm bag for all above accessories is also included. Price complete. Nothing else to buy. ONLY

\$52⁵⁰ NET

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
 Dept. D-411, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.


Name _____

Address _____

City _____ Zone _____ State _____

All Prices net. F.O.B. N.Y.C.

<input type="checkbox"/> Model TW-11.....	Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00	monthly for 6 months.
<input type="checkbox"/> Model 76.....	Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00	monthly for 4 months.
<input type="checkbox"/> Model TD-55.....	Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00	monthly for 3 months.
<input type="checkbox"/> Model TV-50.....	Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00	monthly for 6 months.
<input type="checkbox"/> Model TV-40.....	Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00	monthly for 3 months.
<input type="checkbox"/> Model TV-60.....	Total Price \$52.50
\$12.50 within 10 days. Balance \$8.00	monthly for 5 months.
<input type="checkbox"/> Model TV-12.....	Total Price \$72.50
\$22.50 within 10 days. Balance \$10.00	monthly for 5 months.

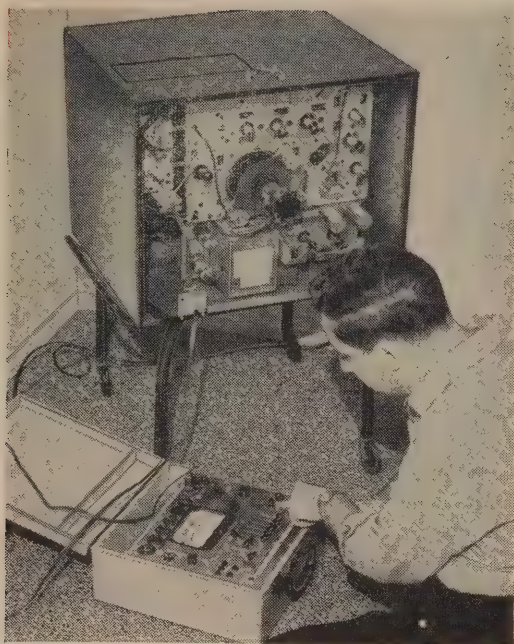

The meter needle indicated **REPLACE**. Now she felt she was getting her money's worth.

YOU walk in on a service call. The TV set has no sync. The picture is running in all directions at about 60 miles an hour. You take two screws off the top of the back, peel the fiberboard down and peep in. Right in the middle of the chassis, there is the sync separator, a 12AU7, with only one light burning.

You reach in, pluck out the old tube and insert a new one. The picture snaps into place with a boin-n-g. Your repair is complete. Total time elapsed 3½ minutes.

The set owner says, "While you're here, would you check the TV over and make sure everything is okay?"

What is your next move? Wrinkle up your nose in annoyance and beg off or begin pulling the set apart for a lengthy check? With a combination of the pressure of waiting calls, our natural laziness and a feeling of let well enough alone working on us; the tendency is to do the minimum job. But from both a business and technical point of view, it's just not the thing to do.

In our outfit we don't wait for the set owner to ask us to check out a set. With the exception of brand-new or just recently repaired TV's we ask the owner if he would like us to do a maximum job. We explain there is an additional labor charge plus any parts necessary. Here is what we give them.

The chassis is pulled out. The dust is wiped off, the controls lubricated, the tuner cleaned, the C-R tube face is cleaned. All the tubes are checked, resistors and capacitors visually checked, picture set for linearity and any trouble symptoms are traced and eliminated. Of course with the thousands of different makes and models

the procedure is tailored to fit the individual set but, in general, that is what we term a maximum job.

There is quite a bit more to completing a maximum job to the customer's satisfaction than a minimum. There is more salesmanship needed, as the price of the repair rises. It has often been said that one of the reasons why people hate to have their TV fixed is that the repair seems to them a negative thing. Just a restoration of status quo, not a new hat or pair of shoes. It's up to the technician to make the repair a positive thing, to provide definite actions or objects so the consumer feels he has received something tangible for his money.

It's hard for a customer to appreciate the complicated repair techniques that flash through your mind. All they can understand are the things they can see clearly. Some of these positive things that satisfy are the labor you go through, a lineup of defective parts or a meter that says something they can understand.

With all its faults, a tube tester is a good customer satisfier. I was serv-

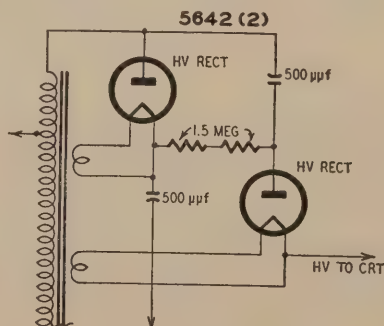


Fig. 1—The 500-μf capacitor measured 700,000 ohms. It caused blooming by lowering the high-voltage output.

do you do a MAXIMUM or MINIMUM job?

*There's more to
fixing a TV set
than replacing
one bad tube*

By **ART MARGOLIS**

ing a 21-inch Sylvania. The complaint was no raster. I found the 6CD6 out cold. I replaced it and the picture came on. The set was very dusty and the screen filthy. I asked the customer, who happened to be a real estate agent, if she would like me to do a maximum job. She told me to go ahead.

After cleaning it all up, I began checking out the set. There were two weak if's that I changed. As I was adjusting the agc I noticed a bad blooming condition had developed. I checked the two subminiature 5642 high-voltage rectifiers. They were both weak so I replaced them. The bloom cleared a little but there was still some left.

I dug into the high-voltage cage and measured the resistance of the two 500-μf 10,000-volt capacitors. One of them measured 700,000 ohms (see Fig. 1). I replaced it. The blooming ceased. After that I made up the bill with the additional charges. The female land seller was naturally curious as to what she was paying for. I showed her how the capacitor measured 700,000 ohms on my ohmmeter. She looked at me blankly, completely snowed. I don't think she was too happy about not understanding either.

I finally gave up that tack and demonstrated all the weak tubes, one by one on the tube tester. The meter needle sitting in the red **REPLACE** zone brought a satisfied smile. Now she felt she was getting her money's worth.

Sell each dollar separately

The majority of your customers will put up no argument and will go along with whatever you, the expert, advise. But, there are always the tough "I'm from Missouri" set owners who don't trust a soul. I have one such customer who is a bill collector. Maybe his job makes him that way, but anyway here's what we do with clients like him.

I arrived after an absence of close to 2 years. When I took the back off of his 21-inch G-E, I could see it hadn't been touched since I was there last. He growled, "The sound is reverberating in the picture."

Sure enough, he had sound bars in the video that could be varied with the volume control. After a few minutes of checking I found the cover can on the fourth if video detector was loose. As the volume control was turned up, the



HIT THE JACKPOT



IN THE COLOR TENNA

SELL-A-BRATION

Sweepstakes

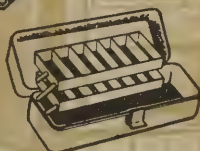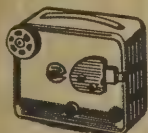

You're in the money when you sell JFD Colortennas. Thousands of profit-conscious service-dealers proved it to themselves last year making *more* profits... picking up \$100,000.00 in merchandise and trip prizes. So can you in '58!

PERFORMANCE!...Results—not claims! Hundreds of thousands of Helix Colortenna installations throughout the U.S.A. best tell their story of matchless VHF performance. Your selection of 5 "area-engineered" Helix Colortennas helps you meet and *beat* any location requirements without waste of 1 db in performance or 1 cent in cost.

PROMOTION!...Year-round national advertising...local advertising over *your* store name expands *your* volume...tells *your* prospects to see *you* for their antenna replacements and new antenna installations.


GOLD ANODIZED CONSTRUCTION!...Now with brilliant diamond-hard Gold Anodizing that gives you *more* to show and *more* to sell in today's color-conscious market...*plus* 15 inch dowel reinforcement of all elements over 30 inches...*plus* indestructible, unbreakable insulators made of ultra low-loss Kralastic B material...*plus* dozens of other top-flight construction features.

PROFITS!...because you sell *every* prospect with the full line of Helix Colortennas.

PREMIUMS!...every Colortenna you sell counts for *free* brand name merchandise. For example, sell only 11 Wonder Helix WX811S for a Chatham blanket...only 11 Star Helix SX711S for Aluminum Fishing Tackle Box.

PLEASURE TRIPS!...redeem your points in trip-tickets here or abroad.

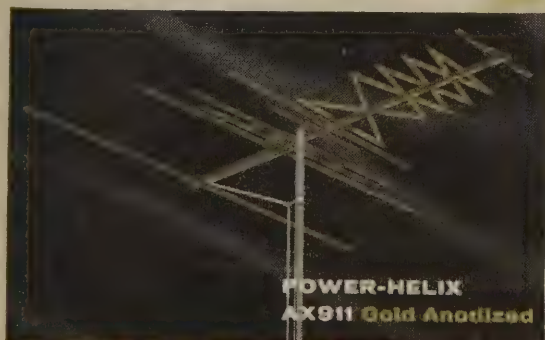THREE GRAND PRIZES TO SERVICE-DEALERS WITH MOST SELL-A-BRATION POINTS: ALL-EXPENSES PAID TRIPS FOR TWO TO PARIS, BERMUDA, WALDORF-ASTORIA, NEW YORK!



JFD Colortennas now available with Alcoa alumilite gold anodizing so bright it sells on sight!

JFD Electronics Corporation
6101 Sixteenth Ave., Brooklyn 4, N. Y.

- ☐ Show me how I can cash in on the Colortenna Sell-A-Bration.
- ☐ Give me the name of nearest JFD Colortenna Distributor.

Company _____

Address _____

City _____ Zone _____ State _____

cabinet would vibrate, vibrating the can which modulated the video. Snapping the can into place cured the condition.

Only about 5 minutes had elapsed. I advised the customer he could use a maximum job. He gave me the go-ahead, not missing a move. After the routine cleaning, I noticed the vertical sync was a little weak. The picture would roll every now and then. I mentioned this to the customer. He said, "It does roll sometimes but I adjust it back in."

I checked through the vertical circuits. After about a half-hour I found one of the line filters leading into the vertical B plus, a 40- μ f electrolytic, was defective. It had evidently decreased in value, allowing some ripple into the vertical sync which rolled the picture (see Fig. 2). A new filter gave the vertical sync much better holding power. Before replacing it I showed my client a before-and-after on the vertical stability. He nodded OK.

The 6BQ7 rf amplifier read weak on the tube tester. I showed the customer a before-and-after on how some of the snow was cleared out of the video. The vertical output tube was weak. And I gave him a before-and-after on the additional vertical sweep that allowed a perfect linearity adjustment.

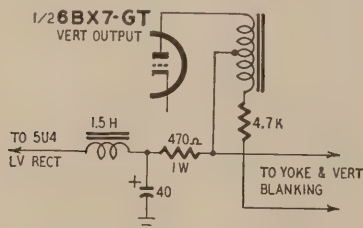


Fig. 2—Defective electrolytic passed dc ripple; picture rolled.

I tapped the damper, it started to arc. I called him over. He amazed me by saying, "OK, OK, I believe you. Do what you think it needs." I completed the maximum job. The only objection I received to the bill was a swallow.

Because you do check over the entire TV set during a maximum job, you might give the impression that your standard guarantee is now unconditional. You must make the point beyond any doubt that the guarantee is only on the actual labor performed and parts installed. You must let the set owner know that checking a part does not guarantee it. *Only replacing it or repairing it carries some form of guarantee.* I learned this lesson the hard way.

I was called by an old customer who has a 12-inch Emerson. His call came in early asking for service before noon. I arrived about 11:30. He had his hat and coat on when I arrived. He said, "It's in bad shape, fix it all up and Dad will pay you." With that he drove off, the only one left in the house besides me was his father, who was reading in another room.

There was no video and a four-sided shrunken picture. I changed a 12AU7 video amplifier and the selenium rectifiers. That restored all. I cleaned and checked the set out, but I couldn't find

another defective part. I made up a bill and his father paid me.

About a week later he called again, patient but annoyed, "The picture is much better but it still doesn't work right." I went over on the double. The set was perfect. I had an intermittent on my hands. He described the symptoms, but his words had little meaning. I did manage to make out there was no audio or video, just a shrunken raster. I pulled the chassis.

After the usual waiting, checking and heartache the intermittent condition appeared. Sound and video left and the picture developed extreme horizontal foldover. I changed the damper, the condition cleared. I reinstalled the old damper, the condition reappeared. An open cathode in the damper was converting the sawtooth waveform into a sine wave. I had it.

That was until I presented the set owner with another bill. He legitimately said, "I thought you'd given me a 90-day guarantee on that overhauling job you did for me."

Since I hadn't made the conditions absolutely clear, he had a leg to stand on. I swallowed this time and chalked it up to overhead. A few words of clarification before he left the house in the beginning would have avoided this loss.

Catch the little things

If you do a maximum job for a set owner, he naturally expects perfection. There are always many tiny details about his TV that have been annoying the viewer. These faults have not been major enough for the set owner to call you for these annoyances alone. But while you are there, if you can catch these tiny faults, you will really leave a satisfied customer.

Lots of them are so minor to you that you're not even aware of them. They might be dead pilot bulbs, springs missing from knobs, a dead mosquito under the glass face, some TVI you can eliminate or explain away, or an actual trouble symptom. The only way you can get at these minor complaints is to interrogate the set owner.

I was repairing a 17-inch G-E. The original complaint was no raster. I found this was due to no high voltage. Regular tube checks proved fruitless so I pulled the chassis on the floor. There was no B plus on the screen of the horizontal output tube. I found the 4,700-ohm 4-watt screen resistor open. I changed it and the raster returned.

I said to the set owner, "While I have the chassis on the floor, would you like me to check it over?" She gave me the go ahead. While I was tube checking, I gave her the third degree. I managed to pry loose that the contrast hadn't been as good as it used to be. I resolved to check out the video circuits for defects.

About five tubes were in dilapidated shape and the Global was ready to konk. I changed them all, cleaned all the controls and went through the rest of my maximum-job procedure. Then I turned on the set. The picture was much clearer

but the contrast level was down quite a bit. I checked voltages in the video amplifiers. On the plate of the first video amplifier there was supposed to be 75 volts. I measured about 40. I checked all the components in that plate leg. I found a .05- μ f cathode bypass that measured 10,000 ohms (see Fig. 3). I changed it. You should have seen the contrast come up then.

She became very excited with the newly found contrast. She remarked, "The picture looks now like when the set was brand new." It's funny, but the restoration of the high voltage didn't faze her one way or the other. That she took as her due. But the bringing back of the contrast that had been needing her for months and months, that in her estimation was really an achievement. It was something that she had accepted as having to be. Something she wouldn't have tried to have fixed.

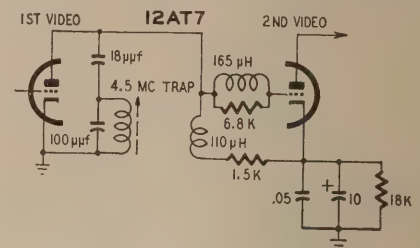


Fig. 3—Low resistance short in the .05- μ f capacitor lowered plate voltage and caused lack of contrast.

Contrary to what you may think, doing a maximum job that costs so much more than a straight service call is not unpleasant to set owners. Sure, laying out the cash hurts them for a minute but, if they can feel that their TV is operating at peak performance, that's really what they want.

But the maximum job has to be done correctly. You have to make the repair a positive thing. Sometimes you have really to exert yourself selling the improvements one by one. Spell out whatever guarantee you are going to give and make sure you catch all annoyances, even the little ones.

After a maximum job your customers will get the idea that you are thorough. It is hard for them to remember exactly what you did but the main thing is you will get across the idea of completeness. This idea of completeness is important; don't underestimate it. Even if it comes back to you in a seemingly silly way. Like it did to me after I had done a maximum job on a 16-inch Philco.

A new 12AZ7 local oscillator brought back the high band. A new 6T8 cleared up the garbled sound. A new 6CD6 got rid of some black spaces on the sides. A screen cleaning restored a 50% brilliance loss. Each and every change was positive and made a whale of a difference.

When I received a recommendation call from their neighbor, I was curious enough to ask the neighbor what the original customer had remembered about my repair. The answer, "She told everybody how you put all the screws back into the set." END



To help you...

4 NEW CBS TECHNICAL AIDS

Here are four new CBS technical publications on tubes and semiconductors. Each is especially designed to make life easier for electronic technicians and engineers:

Technician's Handbook...

compact, comprehensive ready-reference data by and for the electronic service technician. Only \$1.50 net.

Engineer's Handbook...

complete EIA data and two-color curves by and for engineers — and technicians who want all the facts. Only \$7.50 net.

Transistor Course...

fast, fascinating home-study course — teaches basic fundamentals of transistors through use. Available from CBS Tube distributors.

Tube Tips...

monthly inside information on tubes and semiconductors — especially for service technicians. From CBS Tube distributors only.

You'll want all four of these CBS technical aids. See them . . . examine them . . . get them at your CBS Tube distributor's . . . today!

ELECTRON TUBES




CBS-HYTRON, Danvers, Mass.
A Division of
Columbia Broadcasting System, Inc.

For the best in entertainment tune to CBS

relay averts toyland tragedy

Simple photoelectric relay is an educational toy and practical robot

By JAMES A. McROBERTS

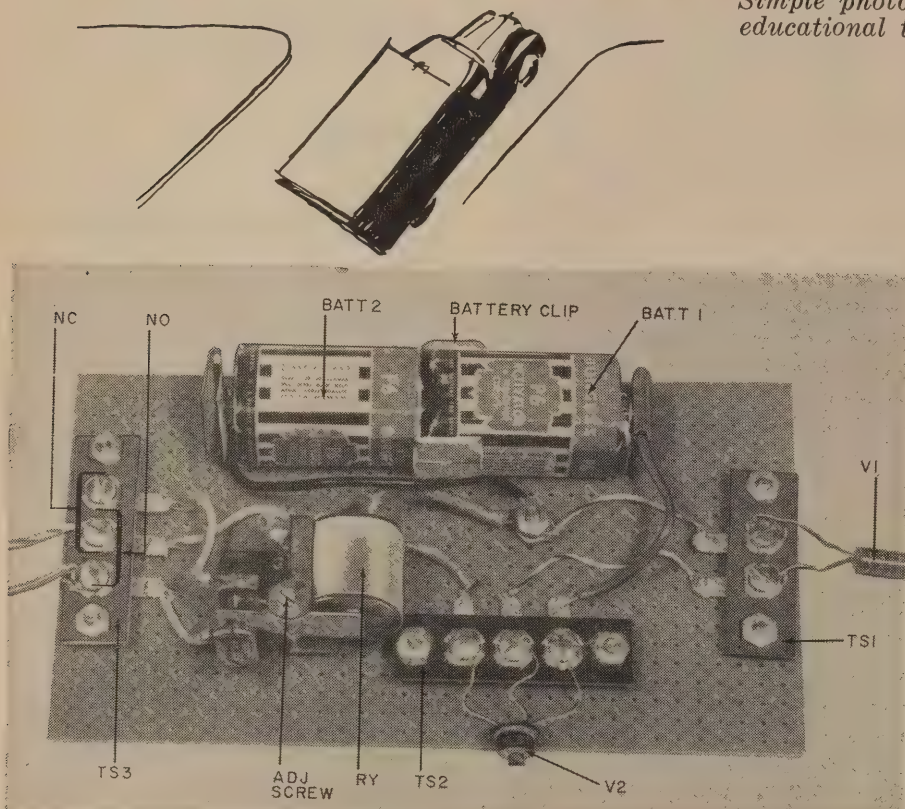

Closeup shows parts layout and wiring detail.

NO, the toyland flyer looming out of the night on our cover photo did not hit Santa's new auto. The train was stopped short of that tragedy by an automatic crossing guard (see photo above).

As an educational toy, this device furnishes many hours of enjoyment for Junior and perhaps Papa too. It was built breadboard style for this reason. Besides cutting off power to the train when the crossing is obstructed, it can be made to ring a bell, light a block signal, stop a following train, ring a station bell, or do any one of a number of other things.

For practicality, build the unit into a metal or other sturdy container along with a self-contained power supply. The most obvious gainful use is annunciator service. Whenever light to the cell is broken, a chime rings, announcing the presence of a guest or customer. It will indicate the presence of unwanted visitors, too, such as burglars. To discourage the latter group, use the device to turn on lights automatically whenever night comes, with a second piece of apparatus for burglar or visitor alarm duty.


Fig. 1 shows the simple circuit which you can put together in an hour. And

the closeup photo shows the parts layout and wiring details.

The cover picture demonstrates how a CL-3 Clairex photocell is illuminated by a small bulb whenever the crossing is not obstructed. As long as the crossing is clear, relay RY stays closed (energized), and power is supplied to the track's control section through the NO contacts. (This circuit is normally open when coil is not energized.) Interruption of the light beam reduces current through the relay, which opens, cutting the circuit from train transformer to track, and stops the train.

Two or more sections of the track's middle rail (either rail in a two-rail system) may be insulated by pulling the connecting pins. Put a piece of tape over the ends to insulate the broken connection. As the train approaches an obstructed crossing, it stops but it will run on the remainder of the track. The number of track sections controlled depends on the train's speed and length. Two or three experiments quickly determine the required distance.

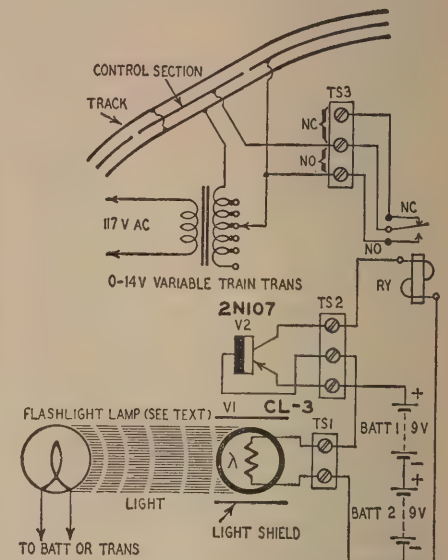The CL-3 photocell is a conductive type whose resistance decreases in proportion to an increase in the light on it. When unilluminated, almost no current passes through the transistor's base



BATT 1, 2—9-volt battery (Burgess P-6 or equivalent)
RY—8,000-ohm coil, adjusted to operate at about 1.3 ma or less and release at around 0.7 ma (Sigma 4F-8,000-S or equivalent)
TS1—terminal strip, 2 contacts
TS2, 3—terminal strip, 3 contacts
VI—Clairex CL-3 cadmium-selenide photocell
V2—2N107
Battery harness (Lafayette MS-421)
Tool and battery clip (Lafayette 119-701)
Perforated bakelite board, 3-11/16 x 6 7/8 inches (Lafayette MS-305 or equivalent)
Flashlight lamp (see text)
Miscellaneous hardware

Fig. 1—Circuit of the automatic crossing control.


circuit. Consequently little current flows in the collector circuit including relay RY. Increased light on the photocell increases the transistor's base and collector current. When the relay's pull-in point is reached, the relay closes, applying current to the track. Reverse action occurs as the light decreases, with the relay dropping out and opening these contacts.

For some purposes, the de-energized position activates the controlled circuit through the NC contacts. For this reason, the NC contact has been brought out to a lug on terminal strip TS3.

The light source may be a prefocused flashlight bulb operated below its voltage for the short distance by a single flashlight cell. Or it may be energized from hot contacts of the train transformer through a suitable dropping resistor. (Two flashlight cells driving a 2.8-volt bulb will pull in the relay at 8 feet. With one cell, the range is about a foot.)

Now build it

The breadboard model, most instruc-

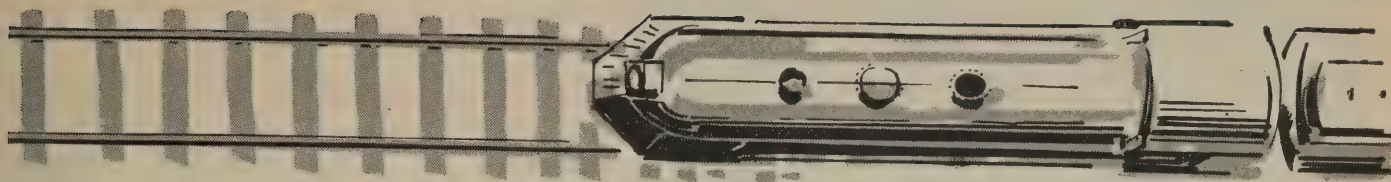

tive for Junior, takes about an hour to assemble. Parts placement is not critical and may follow the photo. Hidden beneath the batteries are two No. 2/56 screws holding the battery clip to the board. Cut off any extra screw length and cover the end with plastic tape to prevent scratching floors and furniture.

About a $\frac{1}{4}$ -inch length of a 6/32 screw is needed for the relay. Cut off the excess with a hacksaw while a nut is on the screw. Unscrew the nut to clean the threads. Install carefully, checking to prevent this screw from digging into the relay coil. An extra nut is used, with the screw and nut forming the negative tie point. For convenience you can slip a soldering lug on the screw. Position the relay for easy wiring to TS3, TS2 and the negative tie point.

Cut the fiber insulation of the battery harness in half. One polarized end fits the negative terminal of the battery and goes to the negative tiepoint. This is the black lead. The red lead runs to the transistor's emitter. *Do not reverse polarity to see if it works—it won't!* The transistor probably won't work again either!

Two 9-volt batteries snap together to form an 18-volt power source. The battery clip (a spring type clip used to hold small tools) holds them rigidly in place. Simply unsnap the batteries or either lead to cut off power.

The light source is shielded with a piece of black tape in the photo. You can use a lamp tower for a neater appearance and some type of building could be placed over the relay unit if desired. A single cell will light a 2.8-volt prefocused flashlight bulb brightly enough to operate the relay from about 6 to 10 inches. Two cells and a reflector extend this distance to about 7 or 8 feet. A lens further increases the range, and can be used on either the light or photocell.

If you want to work the bulb from the train transformer, use a locomotive headlight bulb rated about 14 volts. A 12–14 volt bulb may also be utilized with a bell transformer as the light source. Do not overexpose the photocell by bringing the source closer than about $2\frac{1}{2}$ inches or excessive current may be passed to the base of the transistor. Use just enough light to hold the relay on.

Some relays have to be adjusted to

increase their sensitivity. This is done by decreasing the tension on the armature spring and possibly decreasing the spacing between the contacts. The tension-adjusting screw on the Sigma type 4F relay is indicated in the photo.

Less tension lets the relay close more easily. Relay RY will not drop out if spring tension is too weak. Clockwise turning of the adjustment screw increases tension; counterclockwise turning reduces it. Turn the adjustment screw a little at a time and note results. If a voltmeter is handy, check to see that the relay pulls in with about 11 volts across its coil and drops out at about 6 volts. The circuit is designed for these normal relay operational

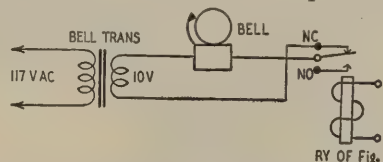


Fig. 2—Auxiliary circuit rings doorbell or chimes.

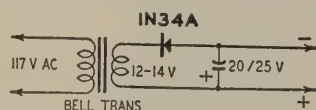


Fig. 3—Convenient power supply replaces batteries.

points with an 18-volt supply. *Do not use higher voltages.*

Other uses

The locomotive's headlight beam can energize the relay. If the light is obstructed, the relay does not go on and the train stops. Here again the number of track sections controlled is determined by the speed of the train. Also take into account the intensity of the locomotive headlight. It must be bright enough to trigger the relay.

As an annunciator, interruption of the beam de-energizes the relay. This time, you would use the NC (normally closed) contacts instead of the normally open set used at the crossing. An auxiliary power supply rings the bell or chimes with the relay circuitry acting only as an electronic switch. Fig. 2 shows this type of operation.

To turn on houselights when it gets dark, place the photocell where it will be indirectly illuminated by daylight. The relay's NC contacts are used. Drooping light values allow the relay to drop out and actuate the auxiliary

circuit. Up to 200 watts may be directly controlled by a Sigma 4F relay. For heavier loads, use an auxiliary relay.

The photocell's sensitivity may be too great in some applications. Whenever this becomes a problem, connect a 1-megohm potentiometer in series with the photocell and the negative end of the power supply. The added resistance lowers the photocell's sensitivity.

A somewhat similar arrangement makes the relay an electronic counter. The relay controls a circuit containing a stepper relay or a solenoid moving a mechanical counter. Objects that interrupt the light beam cause a count for each interruption. The count will be exact if some spacing exists between the objects being counted. Should two pass at about the same time, the photocell may see them as only one.

Power supply

Although less than 2 ma is drawn from the battery supply of the crossing relay circuit, you may prefer to use a batteryless power supply for continuous operation. Fig. 3 shows the circuit of such a supply. The bell transformer is stocked by most hardware stores. It is the higher voltage type delivering a nominal 12–14 volts instead of the more common 8–10 volts. Failing to secure such a transformer, use a low-current 12.6-volt filament transformer.


In wiring the power supply, take care that diode and electrolytic capacitor polarities are correct. Connect the negative terminal of the capacitor and diode.

If the same transformer also powers a lamp for lighting the photocell, its output voltage may be rather low due to the load. If this hinders relay action, simply adjust the relay for a lower pull-in point. Do not overdo it or the relay may not drop out. Make a check for drop-out after all such adjustments.

Caution

One side of the line may be connected to the relay frame in some of the circuit applications. Exercise care in touching the relay or allowing it to touch metal objects possibly grounded. A small plastic box placed over the relay and electrical tape over the mounting screws will offer added protection. If the unit is built on a metal chassis or into a metal box, keep the relay isolated from the box or chassis. **END**

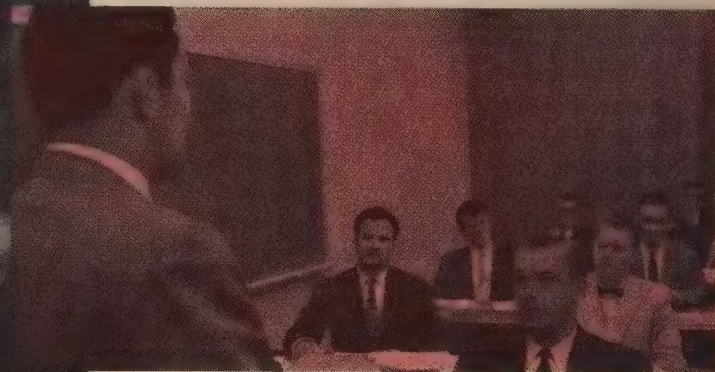How Far Can You Go in Electronics Without a Degree?



"Student" Fred Gunther in the IBM school

Fred Gunther has no degree. Yet, today, at IBM, Fred is a Technical Engineer working on America's biggest electronics project. His story is significant to every technician who feels that lack of formal training is blocking his road to the top.

Let's go back to 1950 and watch Fred Gunther, at 18, as he goes about the business of determining his life's work. Fred spent almost a year trying his hand at various jobs. None of these turned out to be the one that Fred wanted to devote his life to. So, still undecided about his career, Fred entered the Navy for a four-year hitch.

Fred learned something very valuable in the Service, as have many other men who eventually discover the electronics field. His aptitude tests revealed him as an excellent electronics prospect, and he received ten months' training in electronics fundamentals and radar. Upon his discharge in 1955, he was an Electronics Technician, First Class.

Something even more important to Fred's career occurred during his Service hitch. He began to hear such terms as "automation" . . . "data processing" . . . "electronic computer." "Then, one evening, while glancing through the paper," he recalls, "I spotted a story about Project SAGE."

What is Project SAGE?

SAGE means Semi-Automatic Ground Environment. It is part of America's radar warning system—a chain of defense that will ultimately ring our country's entire perimeter. At the heart of this system are giant electronic computers which digest data filtered in from Texas towers, picket ships, reconnaissance planes, ground observers. The computers analyze this information for action by the Strategic Air Command and other defense units. These computers are the largest in the world. Each contains 58,500 vacuum tubes plus 170,000 diodes. They are built for the project by IBM.



Answering instructor's questions

Fred joins IBM

SAGE fascinated Fred, for it embodies the most advanced electronic concepts in giant computer work. And, when he learned that IBM would train him at full salary, plus a living allowance, to become a Computer Units Field Engineer, he seized the opportunity. Fred started his new electronics career in the IBM school, with twenty other technicians. He attended classes 8 hours a day. Courses consisted of some 20 subjects—computer circuitry and units, maintenance techniques—everything he would need to become a full-fledged Computer Units Field Engineer.

Assigned to McGuire AFB

His training completed, Fred was assigned in May, 1956, to McGuire Field, where the first of the giant SAGE computers is located. Here he assisted in the cable installation for this vastly complicated electronic giant. He helped to set up the computer, interconnect its many sections, check it out and make it ready for operation. Fred spent five months

at McGuire Air Force Base, but his education was not yet completed.

Becoming a Computer Systems Engineer

"I like to think it was due to my interest and grade of work," Fred says, "but at any rate, last October I was invited to return to Kingston for further training—to become, in fact, a Computer Systems Engineer. Naturally, I was proud and pleased, for this training would give me a much greater range of understanding . . . make me more valuable to the company and myself . . . and give me a chance to assume actual engineering responsibility." Fred completed the



At the operating console of the computer

Computer Systems course. After several months of outstanding work in his new capacity, he received a *third* promotion—to Technical Engineer—in a field engineering liaison group.

What does the future hold?

What does the future hold for Fred Gunther, now that he has become a Technical Engineer? "It's hard to even set a goal in a field as rapidly moving as this," Fred says, "but with my IBM training back of me, the future sure looks good. I've advanced from Radar Technician to Computer Units Field Engineer to Computer Systems Engineer to Technical Engineer in two years—and received a valuable electronics education besides!"

How about YOU?

Since Fred Gunther joined IBM Military Products and the Project SAGE program, opportunities are more promising than ever. This long-range program is destined for increasing national importance, and IBM will invest thousands of dollars in the right men to insure its success.

If you have two years' education and/or experience in electronics gained through technical schooling or military service, you can become a member of this important, permanent, expanding project as a Computer Units Field Engineer.

You'll receive twenty weeks' training at Kingston, N. Y., with full pay, plus living allowance, before assignment to a permanent location of your choice. You'll receive salary, not wages, plus overtime pay.

This intensive training leads to positions of unusual responsibility. Thousands of IBM electronic engineers, graduates of this course, can vouch for its effectiveness.



Home to the family, Pemberton, N. J.

And, of course, you'll receive the famous IBM company-paid benefits that set standards for industry today.

• • •

WRITE TODAY to:

Mr. N. H. Heyer, Room 649L
Military Products Division
IBM Corp., Kingston, N. Y.


You'll receive a prompt reply. Personal interviews arranged in all areas of the United States if your résumé of experience and education indicates you have the qualifications.

IBM

**MILITARY
PRODUCTS**

- DATA PROCESSING
- ELECTRIC TYPEWRITERS
- MILITARY PRODUCTS
- SPECIAL ENGINEERING PRODUCTS
- SUPPLIES
- TIME EQUIPMENT

BINARY PHOTO TIMER

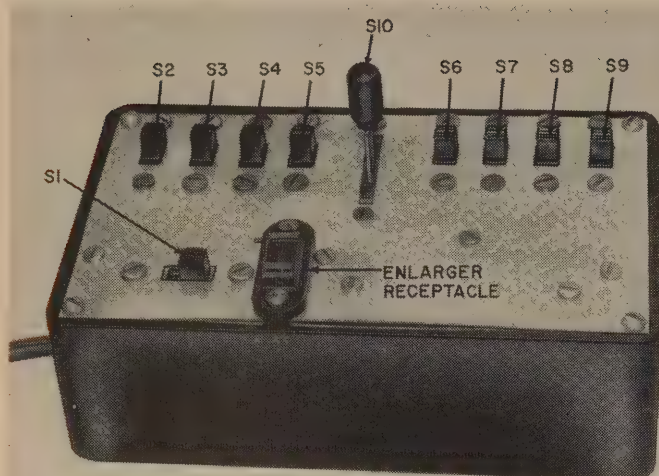


The completed timer.

*This timer
is easy to use,
even in
complete darkness*


By ALVIN F. RYMSHA

PROBABLY hundreds of circuits have been published illustrating as many different approaches to an electronic timer. The majority have been designed for darkroom use, for timing enlargers and contact printers. As an amateur photographer, I have found one failing common to all. They cannot be seen in the dark! Unless the user has considerable dexterity, the lights must be turned on to change the time setting. The timer described in this article overcomes this fault because it doesn't require sight for its setting. Any delay from 1 to 165 seconds can be set by touch alone. The timer will repeat its setting each time it is tripped, and the setting may be "read" by the fingers in total darkness. The entire unit is encased in a plastic meter box and measures only $6\frac{1}{4} \times 3\frac{3}{4} \times 2$ inches.


Starting with a circuit which is simple and reliable (used in the Heath-kit timer), several changes are made. First, the socket for the safelight is eliminated, since there seems to be no need to turn it off in the first place. Second, the variable resistor type of control is replaced by a step-resistor bank. It is this change that increases the convenience of operation. A group of fixed resistors are connected in series across the timing capacitor to change its discharge time and thereby the "on" time of the enlarger. Each resistor is

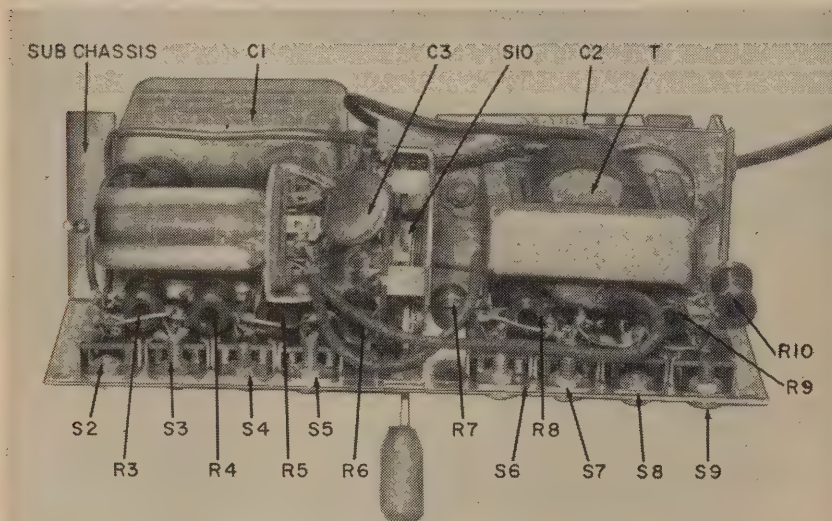

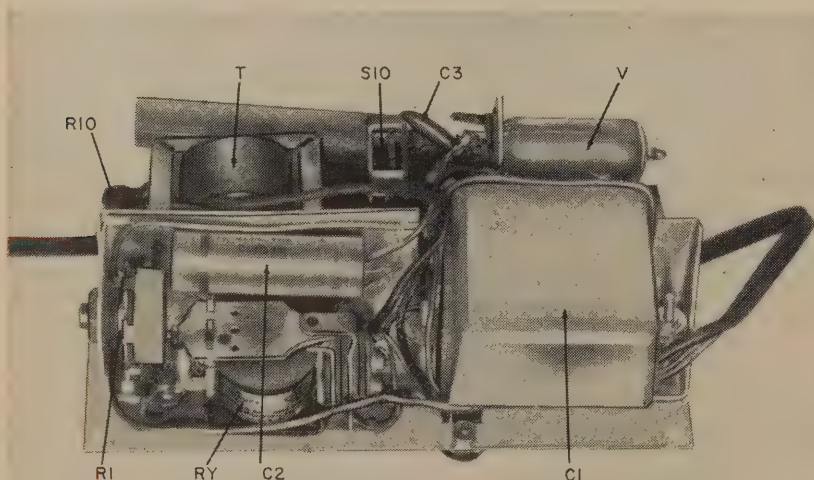Top view of the timer chassis, showing subchassis assembly.



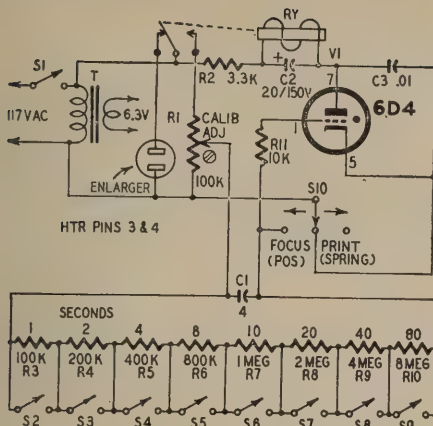Rear view of the chassis. Note the compact layout.



- R1—pot, 100,000 ohms, midjet
 R2—3,300 ohms, 1 watt
 *R3—100,000 ohms
 *R4—200,000 ohms
 *R5—100,000 ohms or two 200,000 ohms in series
 *R6—800,000 ohms or 470,000 and 330,000 ohms
 *R7—1 megohm
 *R8—2 megohms
 *R9—4 megohms or two 2 megohm units in series
 *R10—8 megohms or 4.7 and 3.3 megohms
 R11—10,000 ohms, 1/2 watt
 C1—4-μf, 200-volt electrolytic
 C2—20-μf, 150-volt electrolytic
 C3—.01-μf ceramic
 RY—5,000 ohms spdt
 S1—9-spst slide switch
 S10—single-pole 3-position lever switch, spring return and positive
 T—filament transformer, 6.3 volt, 1/2 amp
 V—6D4 thyratron
 Miniature ac socket (1)
 Miniature tube socket, 7 pins (1)
 Plastic case 6 1/4 x 3 3/4 x 2 inches
 Aluminum panel 6 x 3 1/2 inches
 *These resistors are 1% or 5%, 1/2-watt units

Circuit of the binary timer.

shorted by a slide switch, permitting any combination to be inserted.

The values of the resistors are determined by a binary series: that is, in powers of 2. The constants of the circuit are so arranged that 100,000 ohms across the 4-μf timing capacitor results in a 1-second delay. Therefore, 200,000 ohms produces a 2-second delay; 400,000 ohms, 4 seconds; 800,000 ohms, 8 seconds; 1 megohm, 16 seconds; 2 megohms, 32 seconds; 4 megohms, 64 seconds; 8 megohms, 128 seconds, and so forth. If all except the 100,000-ohm resistor are shorted, a 1-second delay results. By placing any other resistors in the circuits, the delay is increased by a factor of 2 for each 100,000 ohms. To obtain a 5-second delay, the 100,000- and the 400,000-ohm resistors are inserted. One minute would be obtained by inserting the 2-megohm (for 32 seconds) and the 4-megohm (for 64 seconds) resistors. By inserting all the resistors at once, a total resistance of 16.5 megohms results in a 165-second delay.

The slide switches are connected so that in their "up" position the associated resistor is out of the circuit. Sliding it down inserts the resistor. With only eight switches, it is a simple matter to code-set the desired time and to feel the positions of the switches to read their setting.

In addition to its other advantages, the unit's calibration is extremely simple. No dial needs hand calibration. After construction an electric clock with a second hand is connected to the enlarger terminal, the switches set for 10 seconds and the timer started. The

calibration control (R1) is then adjusted so the clock indicates exactly 10 seconds movement. For fine adjustment a longer time (perhaps 120 seconds) may be set up and the final "touchup" given the calibration. If the resistors are sufficiently precise, they will all fall exactly in line and no further adjustment is necessary.

For the sake of economy, 5% 1/2-watt carbon resistors can be used, in series combinations shown in the parts list. A more precise and reliable unit will result if 1% deposited carbon or boron-carbon resistors are used. One word of caution: use care when soldering the resistors in place. If possible, leave the leads fairly long and do not overheat the resistors as a permanent change in value may result.

Construction details

An aluminum panel cut to fit the meter case and a small subchassis support the components. If the parts are laid out beforehand, possible interference (or downright lack of space) will be avoided. The timing capacitor, filament transformer and relay are the largest components and should be selected for the smallest size available. To conserve space, timing capacitor C1 should be metallized-foil type and need not be over a 200-volt rating. For the transformer, any 6.3-volt unit rated at 1/2 amp will do.


Lay out the slide switches, lever switch, ac connector, timing capacitor and the relay on the front panel. The capacitor is mounted on tubular stand-offs behind the power switch and connector. Bend up a subchassis shelf to support the tube socket and transformer. The calibrating potentiometer may be mounted either on a separate bracket or the bent-over end of the subchassis. This also applies to the tube. In the prototype, the slide switches were secured by machine screws but smooth-headed rivets would retain the "feel" of the unit better.

After all panel drilling, cutting and filing is complete, mount the slide switches and ac connector. Wire the switches in series and solder the resistors in proper order across the switch terminals. Keep the parts snug against the panel as other components will be mounted adjacent to them. Mount the tube socket on the subchassis and install the subchassis, timing capacitor, lever switch and transformer. Complete as much of the wiring as possible, leaving wire ends for the relay and calibrating potentiometer. Wire the potentiometer and the relay (with its capacitor) and install them, the relay going in last. The power cord is fed through a hole in the side of the plastic case.

The unit is a fairly tight squeeze into the box. Due care should be taken to insulate any parts which may touch. The relay-calibration potentiometer area should be particularly watched. You can lose a 6D4 through carelessness here. (I know!) END

for Ultimate Fidelity

SHERWOOD*

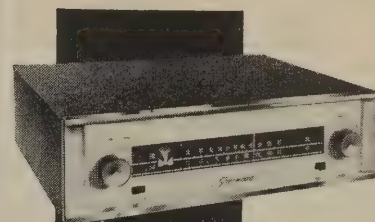

*outstanding honors bestowed, unsolicited, by most recognized testing organizations.

No matter what your source of music—FM, your own discs, or tape—you will enjoy it at its best coming from Sherwood's complete home music center... most honored of them all! Sherwood tuners for example...

First to achieve under one microvolt sensitivity for 20 db FM quieting increases station range to over 100 miles. Other important features include the new "Feather-Ray" tuning eye, automatic frequency control, flywheel tuning output level control and cathode-follower output.

Model S-2000 FM-AM Tuner \$139.50 net

Model S-3000 FM (only) Tuner \$99.50 net


For complete specifications, write Dept. RE-12

SHERWOOD

ELECTRONIC LABORATORIES, INC.

2802 West Cullom Avenue, Chicago 18, Illinois

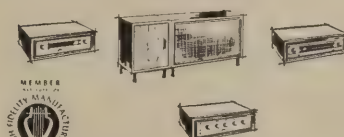The "complete high fidelity home music center."



In New York hear "Accent on Sound" with Skip Weshner, WBAI-FM, week nights, 9 P.M. In Los Angeles, KRHM-FM, 10 P.M.

more about transistor types

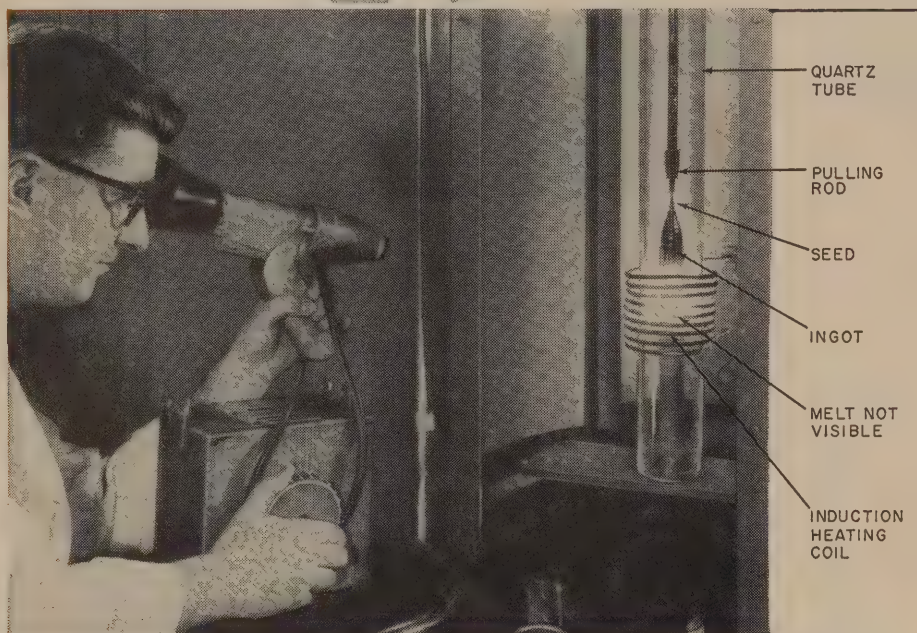


Fig. 2—Growing a single germanium crystal.

LAST month you took a close look into the workings of drift and Uni-junction transistors. You also learned how some alloy and diffusion types are made. Now, the discussion of manufacturing techniques is continued, covering additional types.

An interesting variation of alloying produces *bonded* or *bonded-barrier transistors*. Here the material to be alloyed in, instead of being in the form of a dot, is plated or otherwise attached to the end of a wire. The necessary heat is produced by passing a surge of current through the wire.

A bonded transistor looks much like a point-contact (or coaxial) unit, except that it is truly a junction transistor, the emitter and collector regions being produced by alloying, not electroforming.

Micro-alloy transistor

Here the material to be alloyed in as collector and emitter is produced by plating it directly on the surface of the germanium. The slab of germanium (see Fig. 1) is etched, with a jet spray, till very thin, just as for surface-barrier transistors. The emitter and collector are then plated on the surface, also like surface-barrier transistors. However, now the device is heated and alloying takes place, giving a very shallow alloyed region.

The only advantage of the surface-barrier transistor, remember, is that special etching techniques are used to get a very thin base. Micro-alloy transistors have the same advantage. There are also subtle advantages in micro-alloying one or both of the contacts. The disadvantage is that the base is made so very thin that maximum collector voltage is very low.

Because of the low voltages, the micro-alloy transistor is severely limited in power and its only advantage is good frequency response.

Grown transistor types

Germanium and silicon for transistors must be in the form of a single crystal—one very large array of precisely arranged atoms. About the only practical way to obtain these crystals is to grow them. The Czochralski technique, by which a small single crystal is slowly pulled out of a vat of molten germanium, is generally used. The melted germanium crystallizes in exactly the right order on the single crystal or seed. The photograph shows a germanium crystal being pulled. The coils, wrapped around the outside, are for heating the molten germanium, and only the top of the ingot is visible through the quartz tube which encloses the apparatus. The technician is using an optical pyrom-

By PAUL PENFIELD, JR.

Part II—Manufacturing techniques used to make bonded, micro-alloy, grown-junction, rate-grown, grown-diffused and meltback transistors are discussed

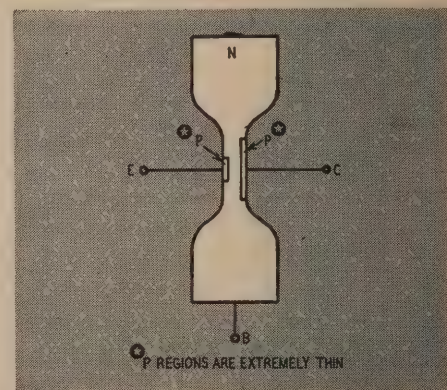


Fig. 1—Micro-alloy unit uses same shape germanium as surface barrier types.

eter to read the temperature of the melt.

If the material in the melt is pure germanium, then intrinsic type germanium will be pulled. But if there are more donors than acceptors, the n-type will result, and vice versa.

Using this idea, *grown-junction transistors* are made by starting off with n-type material. At a certain point a small pellet of acceptor material is dropped into the melt, and p-type germanium is grown. After a short while, a pellet of donor material is added which more than balances the acceptors present.

The result is an n-p-n sandwich in the pulled crystal (see Fig. 2, which has suitable properties to be a transistor. The finished ingot is cut up after

the junctions are located, and many transistors are cut from the sandwich.

Unfortunately, it is rather difficult to locate and make a connection to the p-type base. And only a limited number of transistors can be made from each pulling operation. The scrap germanium must be purified before it is used again. The base region can be made quite thin, meaning fairly good high-frequency operation. Also, the collector capacitance is rather small.

An interesting technique exists for making several grown junctions in one ingot. This is done by growing the crystal from three reservoirs of molten germanium, each doped appropriately for one of the three regions. When it is time to change the doping, one reservoir is moved away and the other shifted into place, leaving the crystal always in contact with a germanium surface. This is done by mounting the reservoirs on a turntable with narrow channels between them. The turntable is rotated while a clever gate system keeps the three melts from mixing. This technique allows many sandwiches to be made from each pulling.

Rate growing

Another way to get n-p-n sandwiches in a grown ingot is to use the rate-growing method. Here a nearly equal mixture of donors and acceptors is put into the melt. Whether we get n-type or p-type depends on the delicate balance between donors and acceptors,

grown transistor compares with the grown-junction model in high-frequency response. Both types are available commercially.

It is possible to combine the effects of growing a junction with diffusion techniques to get very small base regions. If the materials and their densities are just right, it is possible to get a p-p junction in a grown bar—either by rate growing or by adding pellets. The p-p junction (one side of which has more of both acceptors and donors than the other side) is not itself useful, but, if the ingot is heated, some of the donors diffuse, giving a very small n-region right where the p-p junction was. By locating these junctions and cutting up the bar of germanium, a *grown-diffused transistor* is made.

All the grown type transistors have the advantage of a small base region, but have a rather high cost. Partly this is due to the difficulty of locating the junctions in the completed transistor, and of soldering a connection to the extremely thin base region.

Meltback types

If a piece of germanium is placed between a hot and a cold temperature, it will melt back partway, remaining partly molten, partly solid. Now if the temperature is reduced, the germanium will refreeze as a single crystal, but with a changed impurity distribution. By properly using a delicate balance

n-region at the location of the junction. The p-n-p sandwich can now be cut apart to make good high-frequency transistors.

Tetrode transistors

Transistor tetrodes (which have two base connections) are customarily made from a meltback or meltback-diffused sandwich, although in principle they could be made from any of the grown types as well. Furthermore, p-n-p-n hook transistors can be made by a slight variation of the meltback-diffused technique.

By cooling a meltback sample rapidly instead of slowly, *melt-quench* transistors are formed. The original bar may be p-type, and immediately after refreezing the material may be n-type. The refreezing is allowed to proceed only a small distance, however, and then the germanium is rapidly cooled or quenched. In effect, the impurities are trapped wherever they happen to be, and the quenched region is p-type again. Thus only a small controlled n-type region is produced. Melt-quench transistors are not yet available, and it is doubtful if they ever will be, because they offer no particular advantage over other high-frequency models.

The major difficulty with transistors is poor high-frequency response. It seems probable that future high-frequency transistors will be drift units made with the special jet-etching techniques used for surface-barrier types,

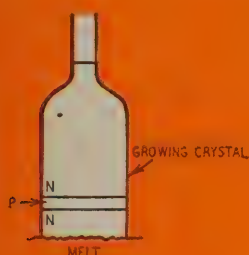


Fig. 2—A grown n-p-n sandwich suitable for transistors.

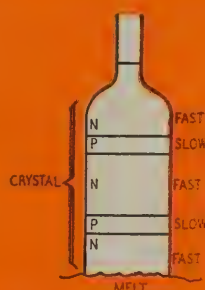


Fig. 3—Many junctions can be rate-grown in one crystal.

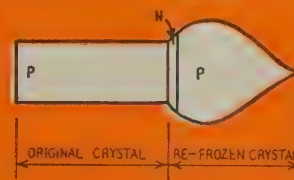


Fig. 4—A meltback p-n-p sandwich

which is affected by the rate of pulling and the temperature. Thus slow rates of growth may yield p-type, and fast growing gives n-type.

Fig. 3 shows an ingot with n-p-n sandwiches made by merely slowing down the growth rate for a minute. This can be cut apart and each sandwich yields many transistors. Dozens of sandwiches can be obtained from each melt.

If the growth rate and temperature are adjusted correctly, the growth rate may actually be negative for a while—the crystal melts back. When the positive growth rate appears again, a very thin p-region results, and the junction formed is abrupt. Both factors help raise the frequency response.

With or without meltback, the *rate-*

of donors and acceptors, it is possible to start with a p-region, refreeze it as an n-region for a short distance, and then change over to a p-region. This produces a p-n-p sandwich (Fig. 4) which can be cut apart for *meltback* transistors.

It is difficult to control the base width accurately this way. So an improved method is used to make the *meltback-diffused transistor*. Correct doping is provided so that after meltback a p-p junction, of the type discussed in the grown-diffused transistor, is formed. The two sides of this p-p junction are p-type but have different amounts of impurities. If correct doping is used, a gentle heating of the germanium will cause a diffusion of the donors, giving a very thin

the diffused base region used in the alloy-diffused transistor, and micro-alloy emitter and collector regions. Such a transistor should not be too expensive and is expected to go beyond 1,000 mc.

Techniques for making junction transistors that have been popular in the past, specifically the grown type methods, will be less important. Meltback techniques will never amount to too much because the base region is of poor quality.

Alloy transistors will continue to be the best sellers for ordinary applications. Power transistors may be silicon diffused emitter-collector models. Diffusion techniques are just coming into their own, so expect good diffused transistors in the future. END

the VOM that outsells all others combined

... now better than ever!

For years, the rugged dependability of the Simpson 260* has made it the world's most popular volt-ohm-milliammeter. Now . . . Simpson offers a new and improved 260 . . . easier to operate, more sensitive, more accurate . . . a better buy than ever before.

To date, over 3/4 million Simpson 260s have been purchased by technicians, service organizations, laboratories, factories, and the armed forces. Such overwhelming preference is proof that the 260 best meets the needs of VOM users. Sound basic design gives it day-in, day-out dependability and ruggedness. "Extras," such as the Adjust-A-Vue handle (standard on 260s), not only provide convenience but save time. When you are in the market for a VOM, you can be sure that a 260 is your best buy. Have your jobber show you this new model of the world's most popular volt-ohm-milliammeter—the Simpson 260.

*TRADEMARK

MANY NEW FEATURES

make the new 260 more valuable than ever!

NEW FEATURES

- **POLARITY REVERSING SWITCH:** Makes d.c. measurements easier and faster . . . no lead reversal.
- **50 MICROAMPERE-250 MILLIVOLT RANGE:** Gives more sensitive measurements . . . provides complete current coverage in six easy steps!
- **EASIER-TO-READ SCALES:** Black and red scales have been spread out for faster reading, less chance of error!
- **LESS CIRCUIT LOADING:** Sensitivity of a.c. voltage ranges increased to 5000 ohms-per-volt!
- **POPULAR DBM RANGES:** -20 DBM to +50 DBM, one milliwatt in 600 ohms!
- **IMPROVED FREQUENCY RESPONSE IN A. C. MEASUREMENTS:** 5 to 500,000 cycles per second!
- **FULL-WAVE BRIDGE RECTIFIER SYSTEM:** Provides more accurate a.c. voltage measurements!
- **RUGGED PRINTED CIRCUIT**
- **ALL COMPONENTS EASILY ACCESSIBLE**

RANGES

D.C. VOLTAGE (20,000 ohms-per-volt): 0-250 mv; 0-2.5 v; 0-10 v; 0-50 v; 0-250 v; 0-1000 v; 0-5000 v.

A.C. VOLTAGE (5000 ohms-per-volt): 0-2.5 v; 0-10 v; 0-50 v; 0-250 v; 0-1000 v; 0-5000 v.

A.C. VOLTAGE (With 0.1 uf internal series capacitor): 0-2.5 v; 0-10 v; 0-50 v; 0-250 v.

VOLUME LEVEL IN DECIBELS (Zero DB equal to 1 milliwatt across a 600 ohm line): -20 to +10 DB; -8 to +22 DB; +6 to +36 DB; +20 to +50 DB.

D.C. RESISTANCE: 0-2000 ohms (12 ohms center); 0-200,000 ohms (1200 ohms center); 0-20 megohms (120,000 ohms center).

DIRECT CURRENT: 0-50 ua; 0-1 ma; 0-10 ma; 0-100 ma; 0-500 ma; 0-10 amp.



Simpson ELECTRIC COMPANY

5200 West Kinzie Street, Chicago 44, Illinois
Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

SERVICE CASES ELECTRIC--

professional look



SERVICE TOOL CASE, 16" by 8" by 6 3/16". Weighs 5 1/2 lbs. without contents.

SPECIAL "160". Holds over 160 tubes. 17 7/8" by 8 3/8" by 11 7/16". 8 lbs. without contents.

SERVICE MASTER "240". Holds over 240 tubes. 22 1/8" by 9 9/16" by 12 3/4". 9 1/2 lbs. when empty.

These new matched service cases are a G-E "first". You can get them nowhere else. They are built just as strongly as their smart appearance indicates . . . with rugged construction, heavy-duty hardware, craftsmanship in every detail. And planned by service experts! You carry with you—compactly—everything you need for home service calls.

The cases are fully matched in design and in their attractive orange-and-gray colors. The

leatherette-type finish is scuff-resistant for plenty of hard wear. You will be proud to carry these handsome cases into the finest home. Their smart, up-to-the-minute appearance stands for the quality television service you offer.

Waiting for you . . . now . . . is your set of matched service cases. Your General Electric tube distributor will tell you how to obtain them. Phone him! *Distributor Sales, Electronic Components Division, General Electric Co., Owensboro, Ky.*

Progress Is Our Most Important Product

GENERAL  ELECTRIC

AMPHENOL

vi-fi Indoor Antenna true VIDEO FIDELITY

Announcing Vi-Fi—two years in development, a new Indoor TV Antenna with new ideas in appearance, electrical and mechanical performance, and mounting versatility.

True Video Fidelity: powerful picture-pull for sharper images, on color or black & white, 'slide rule' tuning and transformer coupling for best impedance matching and maximum signal pickup.


Slender Line Styling: only nine and a half inches long, as thin and as modern as the new TV sets.

Fold-from-sight Elements: shorter, easier-to-handle antenna elements hidden from sight when not in use.



3-Way Mounting: on top, flush or hidden in back for consoles, table models and portables.

Vi-Fi is available in three color choices and in VHF and VHF/UHF models—there are many other features you will want to know about. You and Vi-Fi will want to get acquainted!

contact your AMPHENOL distributor

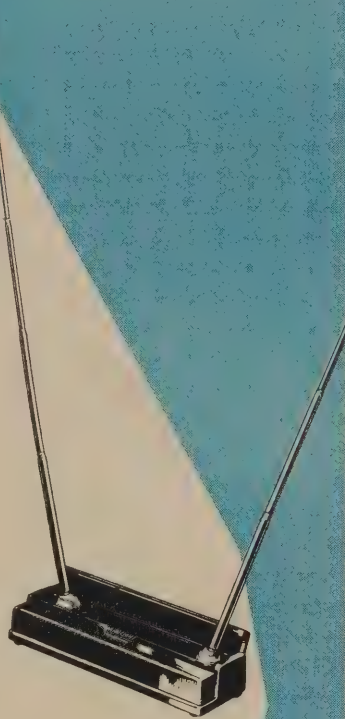


SLENDER LINE
styling

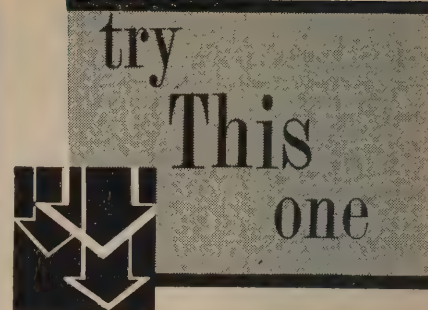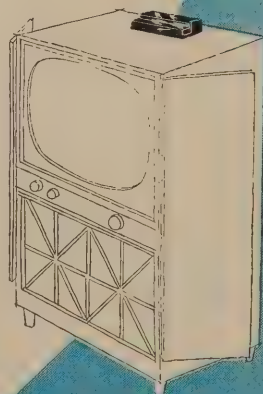

ANCHORING AMPLIFIER COVER

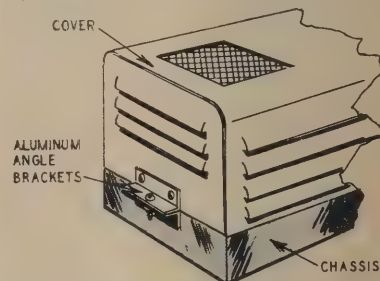If the cover of your amplifier chassis is held by spring clips be very careful when anyone else is to lift the unit. The chances are they'll get a grip on the cover and you'll hear a crash as the amplifier hits the floor! The fastening shown was installed after two such accidents. While the amplifier managed to survive, there's no sense in its being subjected to another shock test.



Pieces of aluminum angle stock were fastened to the cover and chassis at each end. They form flanges that may be bolted together, and also serve as handles for lifting. Keeping the bolts tight tends to have a beneficial effect, too—it discourages knob twisters from disturbing critical screwdriver adjustments under the cover!—*Hugh Lineback*

CHASSIS DRILLING

When holes are drilled in the metal chassis of electronics gear, there is always the danger of the chips falling in unwanted places, causing short circuits and other troubles.

To prevent this I always magnetize the drill so that it will attract and hold the particles. If the chassis is of a nonmagnetic material such as aluminum, I make a dam out of putty or clay around the spot where the hole is to be drilled to catch the chips.


Incidentally, the clay or putty also works well in removing metal chips from a magnetized drill.—*John A. Comstock*

PROBE SAVER

An ordinary clip type broom or tool holder fastened to the side of the vtvm case or a nearby spot on the bench makes a convenient holder for the high-voltage probe and protects its plastic shell from damaging contact with other tools on a crowded bench.—*Harry J. Miller*

SOLDERING PHONE TIPS

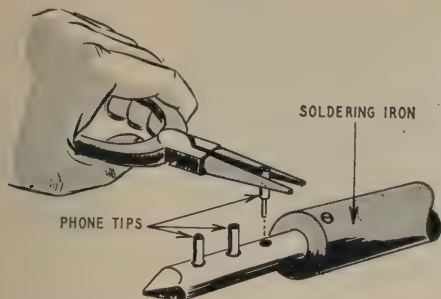
Soldering phone tips to wires makes the experimenter wish for more than two hands—but here is a simplified



method: Drill several holes in an old soldering iron, large enough to accommodate the tips. Rest the iron in its stand and fill the heated tips with solder. Then, with the wire end inserted, grip the tip with pliers and lift out to cool, holding the wire in place with the free hand.—Hugh Lineback

RECTIFIERS FROM SALVAGED TUBES

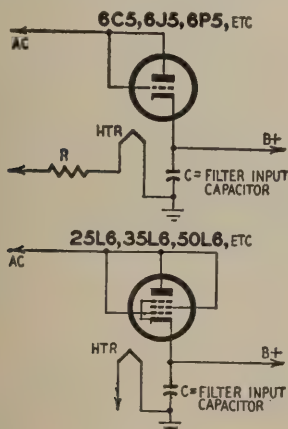Vacuum tubes that have internal shorts or introduce unwanted noises into a circuit may have to be replaced, even though they are not actually burned out. Many such tubes can be used as rectifiers in a great many experimental circuits by reducing the effective number of circuit elements




to the two found in a simple diode. Some tube types, like those illustrated, can be converted by the changes shown. The cathode is one element of the diode and all grids are connected to the plate to form the other. In some cases it may be necessary to insert a voltage-dropping resistor (R) in series with the heater lead.—Warren J. Smith END



"He was an electronics engineer."

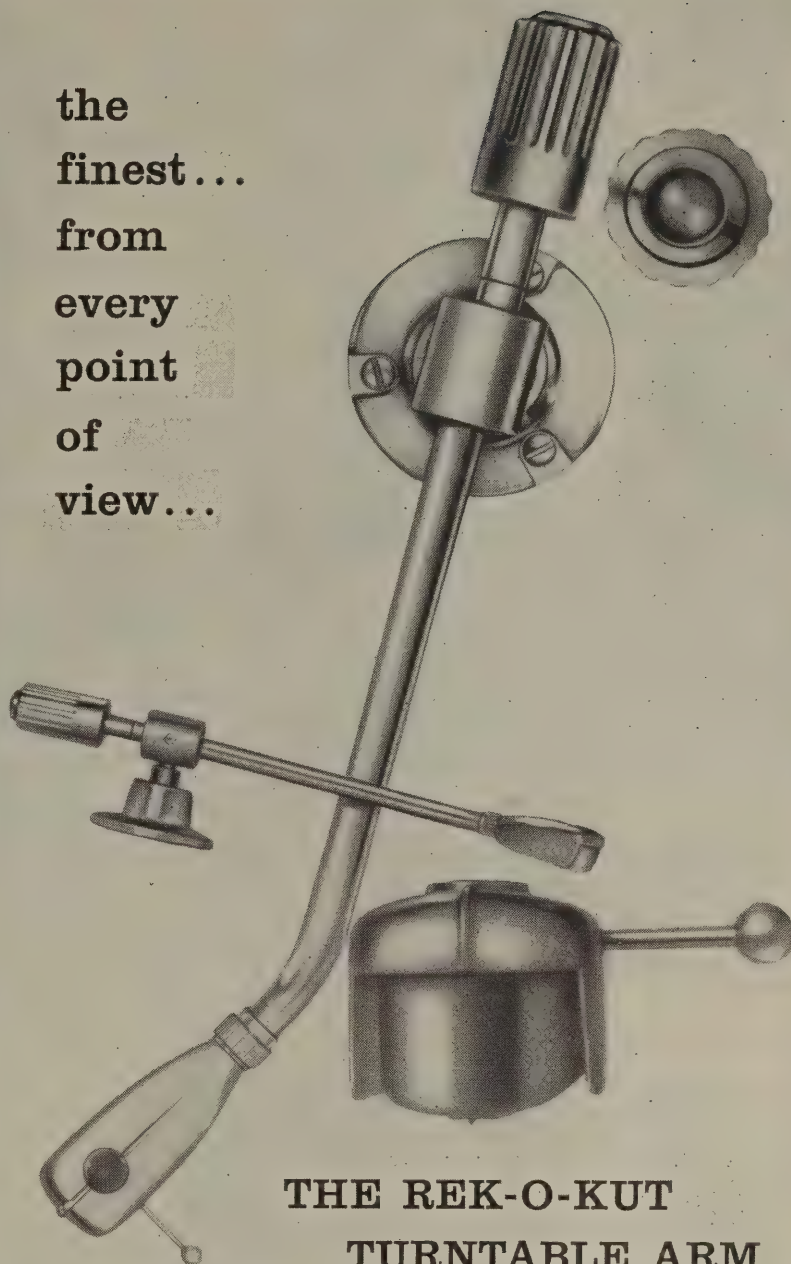the
finest...
from
every
point
of
view...



THE REK-O-KUT TURNTABLE ARM

Most superbly styled of all arms — this is also the *one* turntable arm that offers best compliance, lowest resonance, optimum tracking... to give you better sound! That is why it is the *one* arm invariably sold with every turntable — *outselling all other turntable arms combined!* Write for catalog and free Strobe disc. \$26.95 12" Arm, \$29.95 16" Arm.


EXCLUSIVE FEATURES! • Patented sealed Versa-Twin bearing pivot provides superior horizontal compliance. • For free vertical motion, arm pivots are mounted in chrome steel ball-bearing races. • Micrometer gram weight adjustment gives correct stylus pressure without need for stylus gauge. • Has easy arm-height adjustment. Takes all popular cartridges.



REK-O-KUT

HIGH FIDELITY TURNTABLES—TURNTABLE ARMS
38-19 108th St., Corona 68, N.Y.

NEW STANDARD OF PERFORMANCE

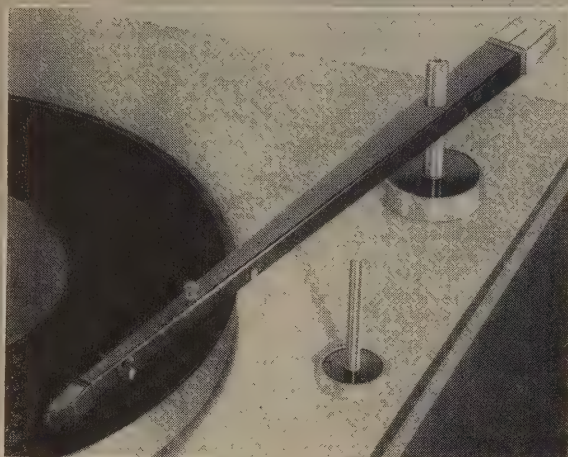

**SHURE
STUDIO**

Dynetic

PHONO REPRODUCER

**IT TRACKS AT ONE GRAM!
ITS FREQUENCY RESPONSE IS
20 TO 20,000 CPS ($\pm 2\text{db}$)!**

ONLY WITH THE STUDIO DYNETIC

- Record and needle wear are drastically reduced!
- You can completely avoid record scratches!
- You never have to level your turntable!
- You don't have to worry about groove-jumping!
- You can get superb fidelity, even from warped records!

You get the excellent response, low distortion and high compliance of dynamic cartridge construction, plus high output, minimum hum pick-up and the elimination of tone arm resonance and needle talk. There are also the additional benefits of the elimination of the pickup of low frequency rumble and motor noise. This superb unit sells for \$79.50 net. Your hi-fi dealer will be happy to arrange a demonstration.

**Write to Sales Department for
reprints of informative,
published articles.**


SHURE

The Mark of Quality

IN ELECTRONICS SINCE 1925

SHURE BROTHERS, INC., 212 HARTREY AVENUE, EVANSTON, ILL.

radio-electronic Circuits

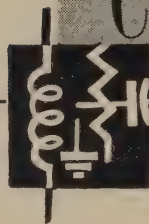


BATTERY ELIMINATOR

A line-operated battery eliminator with adjustable A and B voltages is handy when servicing portable radios. By dropping the output voltages below the levels required by the set you can spot erratic oscillator tubes and often isolate the causes of intermittent operation.

B-plus lead and 5- and 150-volt meter across the A and B output leads, respectively.

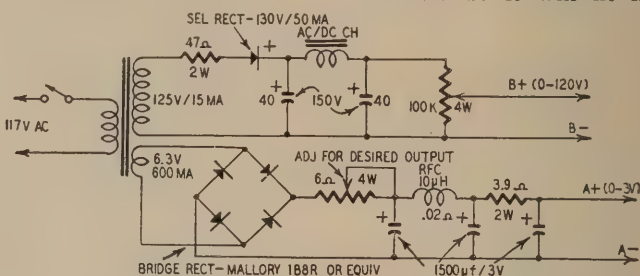The same circuit can be used when electrifying battery radios. If you are careful when selecting parts you may be able to construct the eliminator so it will fit in the space



The circuit of a suitable eliminator is shown in the diagram. It can be used with most portables with parallel-connected 1.5-volt filaments. B voltage can be as high as about 120 with normal drain and A voltage can be adjusted to supply some sets requiring 3 volts. The eliminator can be improved by installing a 25-ma dc meter in the

formerly occupied by the batteries. The power transformer may be a Stancor PS-8415 or equivalent, the B-plus rectifier a Sarkes Tarzian model 50, the low-voltage rectifier a Mallory 1B8R and the A filter capacitors a triple section unit such as the Sprague TVL 3015 or individual units with values of 1,500 μf or more.

BOOSTING 152-162-MC SIGNALS

I have a Gonset model 3012 FM tuner for the 152-162-mc band. Its sensitivity is satisfactory for powerful base stations but not for low-powered mobile transmitters. I raised the overall sensitivity of the system to an acceptable level by replacing the ground-plane antenna with a high-gain omnidirectional type and adding a booster. The antenna is a vertical collinear array like that in Fig. 1. This is a three-element array with a gain of about 3 db and a feed-point impedance that provides a good match to 300-ohm transmission lines. The antenna will cover the entire band adequately when cut for 157 mc. The dimensions shown are for this frequency.

The gain of the array can be increased about 1 db for each half-wave element added to it but it is hardly worth while to add fewer than three. The feed-point impedance will approximately 100 times the number of half-wave elements. The two outside elements remain the same length. The added elements are inserted between the end ones and are each the length of the center element. One-quarter wavelength stubs like those shown in Fig. 1, are used between each half-wave element.

The antenna and phasing stubs are made from rigid rods or tubing. The array can be mounted by fastening the cold (shorted) ends of the stubs to a metal mast. Be sure the mast is grounded to provide protection against lightning.

Fig. 2 is the diagram of a single-stage neutralized rf amplifier similar to a simple TV booster. Tuning capacitors C1 and C2 are butterfly type midget units with capacitance of about 10 μf per section. You can use E. F.

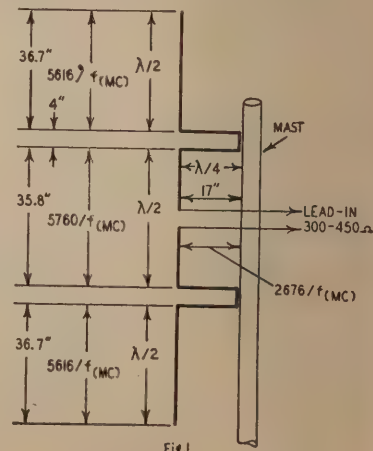



Fig. 1

LITTELFUSE

Des Plaines, Illinois



**PUT YOUR MONEY
WITH THE WINNER**

LITTELFUSE

Quality, Service, Range, and such winning service aids as the Fuse Caddy, One-Call Kits, LC Fuse Caddy, Packaged Snap-On Holders, Fuse-Retainer Assortments, Single-Fuse Channels, participation in Howard Sams Photofact Folders.

spectacular...new Tape System Components PENTRON

• STEREO • MONAURAL

Select the Tape units to meet your needs

Pentron combines professional features and custom styling with building-block flexibility. You buy what you want and add to your system when you desire—from the simplest monaural system to the all inclusive stereo systems.


PENTRON LEADERSHIP FEATURES

- Precision made and tested professional head assembly with Azmur-X spring loaded screw adjustment.
- Simple single rotary control.
- Four outputs plus two AC convenience outlets.
- Mounts VERTICALLY, horizontally, or at any angle.
- Speed change lever at front panel.
- Removable pole pieces in heads, as easy to change as a phono needle.
- Automatic self-energizing differential braking.


basic specifications

TM series mechanisms

COMBINATION HEAD:
Frequency response: 40-14,000 cps with proper equalization. Signal-to-Noise: 55 db with CA units.
Track width: .093"; gap width: 1/4 mil; impedance of record section: 6000 ohms; inductance of erase section: 60 mh • **STACKED HEAD:** track width: .080"; gap width: .15 mil; impedance: 3500 ohms • **FLUTTER:** under 0.4% at 7 1/2 ips; under 1% at 3 1/2 ips • **CAPSTAN DRIVE:** Idler driven • **MOTOR:** 4 pole induction type, individually balanced • **OUTPUTS:** 4 standard pin jack outputs to accept shielded phono plug • **CONVENIENCE OUTLETS:** two auxiliary AC outlets controlled by mechanism power switch. Supplied with removable mounting brackets with shock mounts.

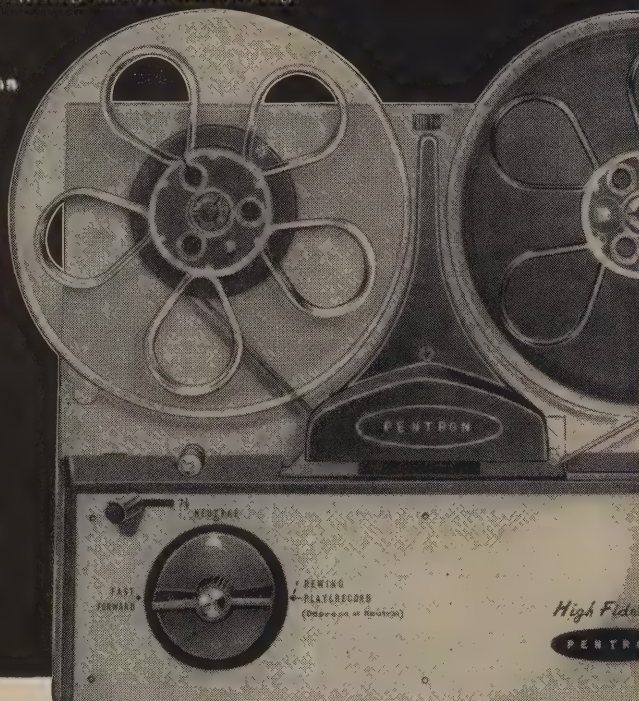


preamplifiers

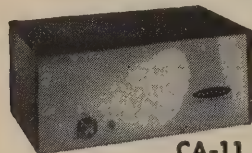

CA-11

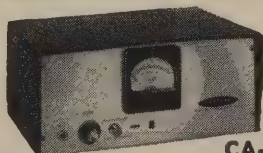Tape Playback only. Response: 20-20,000 cps. Signal-to-Noise: 55 db



CA-13

Tape playback preamp and record amplifier. Response: 20-20,000 cps. Signal-to-Noise: 55 db



CA-15

Stereo dual channel playback. Response: 20-20,000 cps. Signal-to-Noise: 60 db

ALL CA UNITS HAVE SAME PHYSICAL DIMENSIONS AND REQUIRE SAME CUTOUT.

HEAR PENTAPE RECORDED TAPES—"GREATEST SOUND EVER FOUND"

PENTRON®

779 S. Tripp Avenue
Chicago 24, Illinois
Canada: Atlas Radio Ltd. Toronto

Send brochure on tape components

Name _____

Address _____

City & State _____

RADIO-ELECTRONIC CIRCUITS (Continued)

Johnson type 11MB11 or equivalents. Neutralizing capacitors C_N are twisted-wire gimmicks or 0.5- μ mf tubular ceramic trimmers.

L1 and L2 each consist of five turns of No. 18 enameled wire wound in two sections of 2 1/2 turns each. The sections are 3/8 inch in diameter and 1/2 inch apart with a tap at the center. The antenna input and output link windings are each three turns of No. 18 wire wound 3/8 inch in diameter and 1/4 inch long. These links are inserted between the halves of L1 and L2.

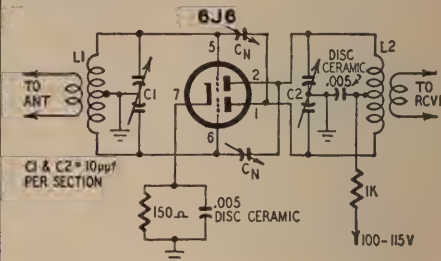



Fig. 2

To adjust the booster, connect it between the antenna and tuner—former to match the tuner's 52-ohm using a balun or TV elevator transformer to match the tuner's 52-ohm input. Tune the tuner to a frequency in the center of the band and squeeze or spread the turns of L1 and L2 so the signal comes in. To neutralize the booster, disconnect the antenna lead-in and replace it with a 300-ohm resistor. Turn up the tuner's volume control and adjust the neutralizing capacitor for minimum noise.—Henry O. Maxwell

RE: PHASING EARPHONES

It is interesting to note that the technique of phasing earphones—described by Art Trauffer on page 40 of RADIO-ELECTRONICS, June, 1957—can be elaborated to reproduce direction of sound origin.

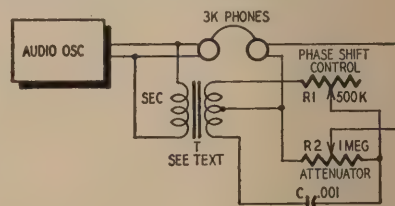For example, if one earphone is fed a tone which is constant in phase, while the other earphone is fed the same tone which passes through a phase-shifting circuit, the apparent direction from which the tone is coming moves about the listener as the operator varies the amount of phase shift.



A suitable demonstration arrangement is shown in the diagram. T is a conventional audio output transformer with its low-impedance winding connected to the audio oscillator. R2 operates as an ATTENUATOR and should be set to provide approximately the same level of sound in the right earphone as in the left. R1 is the PHASE-SHIFT CONTROL, and causes the apparent direction of sound origin to move around the listener as its setting is varied.—Robert G. Middleton END

MF C	50+30 MF 150 WVDC	15+15 MF 300 WVDC	40/25 MF 250/25 WVDC	40+40 MF 150 WVDC	60/35 MF 350 WVDC
	SPRAGUE	SPRAGUE	SPRAGUE	SPRAGUE	SPRAGUE
	TWIST-LOK*LYTIC TVL-2510 30+10 MF 150 WVDC	TWIST-LOK*LYTIC TVL-2575 40+40 MF 300 WVDC	TWIST-LOK*LYTIC TVL-2515 20+20 MF 250 WVDC	TWIST-LOK*LYTIC TVL-2579 60+60 MF 300 WVDC	
	SPRAGUE	SPRAGUE	SPRAGUE	SPRAGUE	
	TWIST-LOK*LYTIC TVL-2438 60+60 MF 150 WVDC	TWIST-LOK*LYTIC TVL-2435 50+50 MF 150 WVDC			
	SPRAGUE	SPRAGUE			
	TWIST-LOK*LYTIC TVL-2420	TWIST-LOK*LYTIC TVL-2435			

for the **RIGHT**
'LYTIC replacement

...Use an exact
SPRAGUE replacement



YOU GET EVERYTHING IN A SPRAGUE TVL! *Every* TVL for *every* voltage rating is made with the more expensive high-purity etched-foil anode construction using ultra-stable film formation techniques. Cathodes are etched to meet high ripple requirements. Sprague TVL's give maximum trouble-free service—NO HUM—as well as long shelf life. And they perform just as well in the cold North as they do in the sub-Tropics. Yet this premium quality costs you no more!

That's why Sprague Twist-Lok® electrolytic capacitors are the first choice of leading radio-TV set makers and independent service technicians alike. Insist on TVL's for more exact ratings . . . quality that meets original equipment specifications . . . and all the latest results of capacitor research. WRITE FOR NEW CATALOG C-612


don't be vague...insist on

SPRAGUE®

world's largest capacitor manufacturer

SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

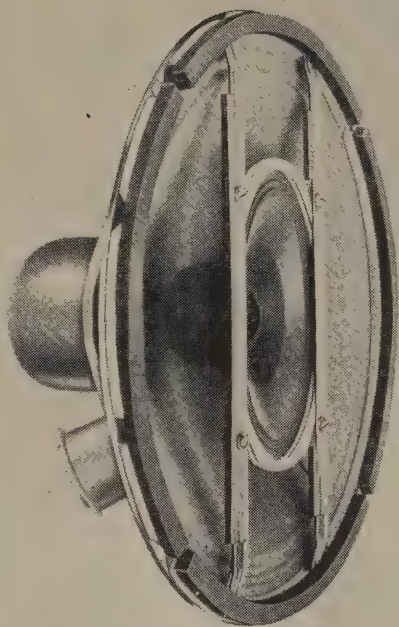Sprague Products Company • Distributors' Division of the Sprague Electric Company • North Adams, Massachusetts.



**The price will be
music to your ears, too!**

NEW SONOTONE CA-12 12" CO-AXIAL LOUDSPEAKER

40-14,000 cycles—elliptical cone tweeter—complete dividing network. And the price...\$19.50. That's right, \$19.50. Yet it out-performs speakers selling at three times the price. Interested? Listen to the CA-12 and be convinced.

Ask your dealer for a demonstration, or send your name and address for full details.


Electronic Applications Division

SONOTONE[®] CORPORATION
ELMSFORD, N. Y.

SONOTONE CORPORATION, Dept. LE-127, Elmsford, N. Y.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____


New Tubes & Semi-conductors

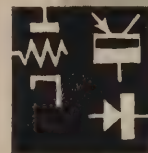

An all-glass color picture tube, a diode-tetrode designed for 12-volt automotive radios and some more transistor-characteristic abbreviations highlight this month's releases.

21CYP22

A directly viewed, round-glass, shadow-mask type picture tube for use in color television receivers, made by RCA. It is designed with an all-glass envelope which reduces high-voltage insulation requirements of the color receiver. It also has an external conductive coating which, with a portion of the internal conductive coating, forms a supplementary filter capacitor. This 3-gun tube has a 6.3-volt 1.8-amp filament.

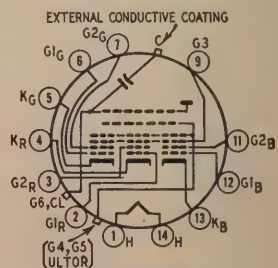

21CYP22
SUBSCRIPT R,G,B REFER TO RED, GREEN & BLUE GUNS

The 21CYP22 is electrostatically focused and magnetically converged. Its maximum ratings are:


*Ultor-to-cathode voltage†	25,000
Grid 3-to-cathode voltage†	6,000
Grid 2-to-cathode voltage† (of each gun)	600
Grid 1-to-cathode voltage† (Neg bias value)	400
(Pos bias value)	0
(Pos peak value)	2
Peak heater-cathode voltage† (htr neg respect to cath)	
(during warmup, 15 seconds)	410
(after warmup)	180

*Between the ultor terminal and the high-voltage supply terminal, it is necessary to connect a 50,000 ohm resistor. The high voltage must be connected to the high-voltage supply terminal (G6, CL)—never directly to the ultor.

†Of each gun.

12R5, 17R5

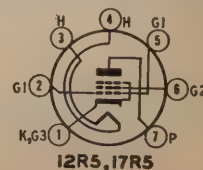These seven-pin miniatures are beam pentodes designed for use as a vertical amplifier in television receivers. Both



12R5, 17R5

NEW TUBES & SEMICONDUCTORS (Cont.)


tubes are identical except for heater ratings. The 12R5 has a 12.6-volt 600-ma and the 17R5 a 16.8-volt 450-ma heater. Both have controlled-warmup characteristics for use in series-string circuits.

Manufactured by Raytheon, typical operating characteristics are:

V_P	110
V_{G2}	110
V_{G1}	-8.5
I_P (ma)	40
I_{G2} (ma)	3.3
R_P (ohms) (approx)	13,000
g_m (μ ohms)	7,000

12DF5

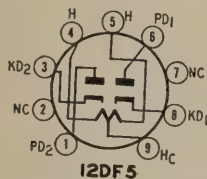A nine-pin miniature tube containing a cathode type, full-wave rectifier. Its center-tapped heater can be operated



12DF5

at 12.6 volts, 450 ma or 6.3 volts, 900 ma. It is manufactured by Sylvania.

Typical operating characteristics are:


Input to filter
Capacitor Choke

V_P (rms ac supply to each plate)	325	450
Filter capacitor (μ f)	40	
Filter choke (h)		10

Effective plate supply resistance (ohms)	82	
Dc output current at filter (ma)	100	100
Dc output voltage at filter	330	360

2N340

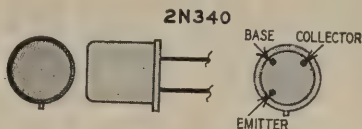This grown-junction n-p-n silicon transistor is especially designed for use




in audio or servo amplifier stages requiring medium power output. The 2N340, made by Texas Instruments, will operate over a temperature range of -55°C to 150°C

Maximum ratings are:

V_{CB}	85
I_C (ma)	50
P_C (mw) (at 100°C)	400
(at 125°C)	200
Power gain (db)	30

6DT8, 12DT8

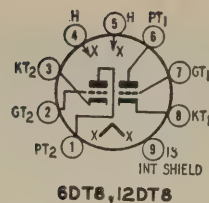General-purpose high-mu twin triodes of the nine-pin miniature type intended for use as an rf amplifier and as a combined oscillator-mixer in FM tuners. The 6DT8 has a 6.3-volt 0.3-amp heater. The 12DT8's heater is rated at 12.6 volts at 0.15 amp. Both are made by RCA.



6DT8, 12DT8


The triode units are isolated by an internal shield having a separate base-pin terminal. Operating characteristics, when used in Class-A1 amplifier service are:

Values are for each triode section

V_P	100	250
Cathode-bias resistor (ohms)	270	200
μ	60	60
g_m (μ mhos)	4,000	5,500
R_P (ohms approx)	15,000	10,900
I_P (ma)	3.7	10
V_s (for I_P of 10 μ a)	-5	-12

12EM6

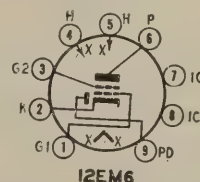A combined detector diode and a tetrode with a common cathode. The tetrode section is intended for use as a power amplifier where heater, plate and screen grid potentials are obtained di-



12EM6

Get This Valuable Book

FREE



Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!


At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 6—NEW Coyne TECHNICAL DICTIONARY with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.

EXTRA! 900 Page TV Cyclopedic Included! For speedy on-the-job use, you also get famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation, etc. in easy ABC order. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

FREE! New Supplements With your set you also get Coyne's annual FREE Supplement Service. Always keeps you up-to-date on latest radio and TV developments. Yours, absolutely FREE, if you act now!

NOW!
7 BIG BOOKS
IN ONE GREAT SET!

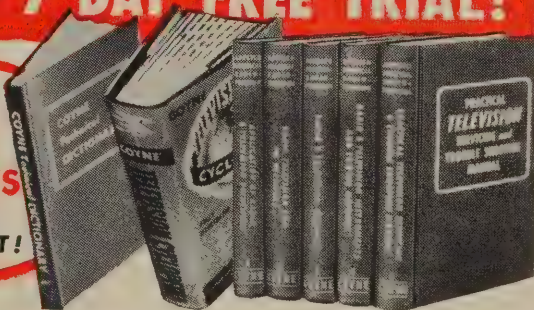

SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. C7-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name..... Age.....

Address.....


City..... Zone..... State.....

Where Employed.....


☐ Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

COYNE

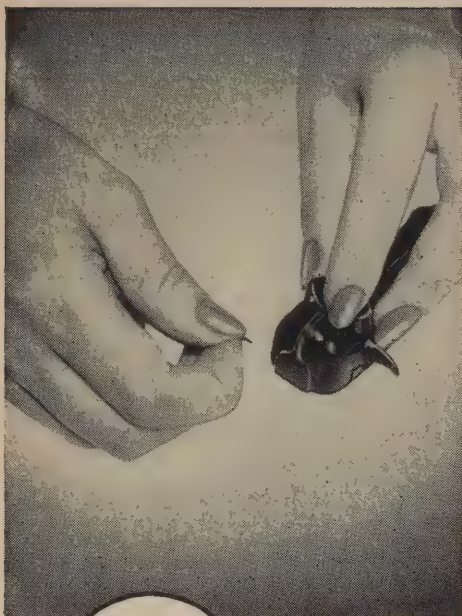
ELECTRICAL SCHOOL
500 S. Paulina St., Dept. C7-T1, Chicago 12, Ill.




NO FINGERNAIL FUMBLING!

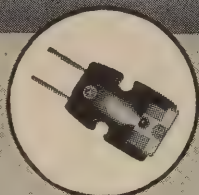

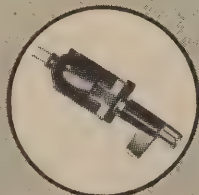FLUXVALVE SINGLE SERIES 370—A miniature high quality cartridge for use in any type of auto-changer or manual player arm. Available in 5 models, prices start at a low \$17.85.



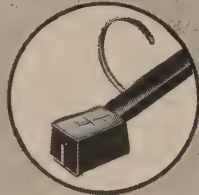FLUXVALVE TWIN SERIES 350—A turnover cartridge providing a rapid change of stylus point radius. Available in 12 models featuring many combinations of styli, prices start at a modest \$24.




Model 194D UNIPOISE Pickup Arm—This new... lightweight... integrated arm and cartridge assembly containing the FLUXVALVE with exclusive "T-Guard" stylus—is only a fraction of the weight of conventional tone arms. High compliance and single friction-free pivot bearing assure distortionless tracking of microgroove and standard groove recordings. Available with the 1/2, 1 or 2.7 mil diamond stylus. Prices from \$59.85.

Exclusive

"T - GUARD"

STYLUS

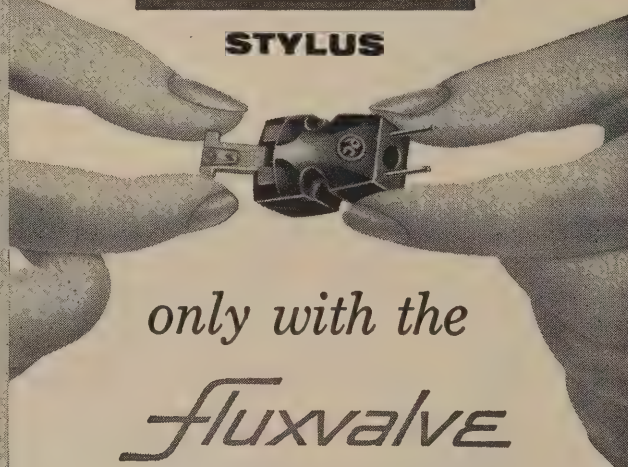

*only with the
fluxvalve*

PICKERING'S introduction of the truly miniature FLUXVALVE magnetic phonograph cartridge represents a new era in high fidelity cartridge design. This newest of PICKERING cartridges brings the music lover the most exciting and *safest* idea in a stylus assembly since PICKERING introduced the first lightweight high fidelity pickup more than a decade ago.

The "T-Guard" stylus assembly is a quick-change, easy to slip-in unit which eliminates precarious finger-nail fumbling. Its practical "T" shape provides a firm and comfortable grip for safe and easy stylus change.

The most flexible cartridge in the world... the FLUXVALVE is the *only* cartridge with the remarkable 1/2 mil stylus... exclusive *only* with PICKERING. The FLUXVALVE can be used with any one of *five* styli, to meet any requirement or application... to play any record, at any speed.

If you are planning to buy a new cartridge—the fact that PICKERING developed this revolutionary stylus is *important to you!* All of the research, development and planning that went into the "T-Guard" stylus is conclusive proof of the superlative engineering skill in every FLUXVALVE model you buy.

For those who can hear the difference FINE QUALITY HIGH FIDELITY PRODUCTS BY

PICKERING & COMPANY, INC., Plainview, N. Y.



NEW TUBES & SEMICONDUCTORS (Cont.)

rectly from an automotive battery.

Announced by Raytheon, typical operating characteristics of the 12EM6 are:


V_{btr}	12.6
I_{btr} (ma)	500
V_{PT}	12.6
V_{g2}	12.6
V_{g1} (af) (rms)	1.0
I_P (ma)	2.5
Power output (mw)	10
Total harmonic distortion (%)	10

Abbreviations

I_{CO} —Collector current when collector junction is reverse-biased and emitter is dc open-circuited.
 I_{EO} —Emitter current when emitter junction is reversed-biased and collector is dc open-circuited.
 I_{CEO} —Collector current with collector junction reverse-biased and base open-circuited.
 NF—noise figure.
 G_c —Common-emitter power gain.
 G_b —Common-base power gain.
 P_c —Collector power dissipation.
 h_{ib} —Common-base input impedance, output ac short-circuited.

17CAP4

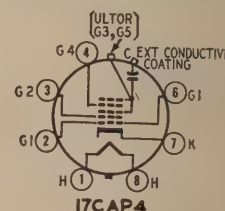Another addition to 110° picture tubes, the 17CAP4 is a direct-viewed 17-inch rectangular glass type made by Sylvania. It has a spherical faceplate, aluminized screen and needs no ion trap. Its 6.3-volt 600-ma heater has a warmup time of 11 seconds.



Maximum voltage ratings for the 17CAP4 are:

Ultor	17,600
V_{g4} (pos value)	1,100
(neg-value)	550
V_{g2}	550
V_{g1}	

(neg bias value)	154
(neg peak value)	220
(pos bias value)	0
(pos peak value)	2

Peak heater-cathode voltage (htr neg with respect to cath)

(15-sec warmup)	450
(after warmup)	200
(htr pos with respect to cath)	200

Other types

A high-current medium-mu triode, the 6528, has been presented by the Chatham Electronics Div. of Tung-Sol Electric. It is intended for series regulator service in dc power supplies.

A 1,000-watt ceramic tetrode for single-sideband operation, the 4CX-1000A, has been announced by Eitel-McCullough.

END

New Transcription-Type Tone Arm Makes *Collaro* World's First True High Fidelity Changer



The Turntable That Changes Records

From Collaro, Ltd., world's largest manufacturer of record playing equipment—comes the most significant development in the field in years—the new transcription-type tone arm.

This arm, exclusive with Collaro, literally changes the conventional record changer into a brand new instrument—a TRANSCRIPTION CHANGER—with features of the finest professional equipment.

The arm is a one-piece, spring-damped, counter-balanced unit which will take any standard high fidelity cartridge. It is free of any audio spectrum resonances. It permits the last record to be played with the same low stylus pressure as the first. Between the top and bottom of a stack of records there is a difference of less than a gram in tracking pressure as compared with 4 to 8 grams on conventional changers. Vertical and horizontal friction are reduced to the lowest possible level. These qualities, found only in the Collaro Transcription Changer, insure better performance and longer life for records and styli.

In its superb performance, the new Collaro Continental, Model TC-540, meets the rigid requirements for high fidelity

equipment. Here, for the first time in a changer is professional quality at a record changer price. The Continental is \$46.50. Other Collaro changers are priced from \$37.50 up. (Prices slightly higher west of the Mississippi.)

In addition to the new tone arm, the Collaro Continental features include: 4 speeds, manual switch for turntable operation; wow and flutter specifications—0.25% RMS at 33½ RPM—superior to any changer in the world; automatic intermix; automatic shut-off after last record; heavy duty 4-pole, shaded pole induction motor; heavy rim-weighted balanced turntable; muting switch and pop-click filter for elimination of extraneous noises; jam proof machinery; pre-wiring for easy installation; attractive two-tone color scheme to fit any decor; tropicalization to operate under adverse weather and humidity conditions; easy mounting on pre-cut board or base; custom testing at the factory for wow, flutter, stylus pressure and correct set down position.

FREE: Colorful new catalog describes complete Collaro line. Includes helpful guide on building record collection.



WRITE TO
ROCKBAR CORPORATION

Dept. D-012

650 Halstead, Mamaroneck, N.Y.

Rockbar is the American sales agent for Collaro and other fine companies.



... another
MALLORY
service-engineered
product



MALLORY VIBRATORS

to meet every service requirement

1 FOR THE VERY BEST IN PERFORMANCE...

Mallory Gold Label Vibrators are the result of over 27 years of vibrator pioneering and leadership. Employing the exclusive Mallory buttonless contact design, they eliminate problems of sticking contacts... insure positive starting... provide far longer life... are unbelievably quiet. For utmost dependability, and to build your reputation for service, make Mallory Gold Label Vibrators your standard of quality.

Depend on Mallory
for vibrator dependability
—for any job



2 FOR ECONOMY JOBS...

The Mallory Highlander is a new line designed expressly for the jobs that must be done at a lower price. It delivers trouble-free service longer than any vibrator in its price class—second only to the Gold Label line. Ask your Distributor for the new Mallory Highlander—in the handy new 10-pack carton.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters

Technicians' News



OPPOSES PAY TV TESTS

The National Alliance of Television and Electronic Servicing Associations' (NATESA) executive secretary, Frank J. Moch, has expressed the organization's stand against any tests of pay TV "which would in any way encourage the acceptance of this system." This was in a letter to John C. Doerfer, FCC chairman.

NATESA has asked the FCC and the House Interstate Commerce Committee to get all details of the workings of pay TV before permitting tests or authorizing it in any form.

Six points are emphasized by Mr. Moch. He states that approving pay TV will be a mortal blow to the independent service industry, since pay TV promoters would demand the right to maintain the sets. He continues that we (NATESA) have not been able to get assurances to the contrary.

He also states that approval would encourage the promoters to assume a utility attitude, and like the phone company would then supply the sets on a rental basis, thus raising havoc with the entire manufacturing, distribution, retail and servicing industries.

In explaining other points of the NATESA stand, Mr. Moch wrote that pay TV is opposed to historical concepts is not in keeping with the spirit of laws, like those authorized by the FCC; that despite its weaknesses, the present system of telecasting has been accepted by the public; that pay TV cannot guarantee elimination of existing shortcomings and that pay TV does not guarantee that commercial practices now distasteful to viewers will not be continued.

TECHNICIAN'S ADVERTISING

The National Alliance of Television & Electronics Service Associations (NATESA) now offers every member of every local affiliate an opportunity to participate in the NATESA National Advertising and Publicity Program, an article in the September issue of *TESA (Missouri) News* proclaims.

The program calls for ads in several top magazines, newspaper ads on a local level, radio and TV spots on a national level, listing in the yellow pages of the phone directory, Operator 25 service and use of direct-mail pieces.

Individual members of local affiliates will be franchised to participate, and window valences, truck decals, letterheads, billheads, mailing pieces, etc., will be available at cost. The cost will be very low as advertising materials

TECHNICIANS' NEWS (Continued)

will be purchased in mass quantities.

The Cody Advertising Agency, Chicago, Ill., headed by Jim Cody, will handle the program and is already preparing ad copy. The yearly cost of this program, because of its size, is expected to be extremely low. Individual members can participate for a few cents a day over a period of several months.

URGES STRONG GROUP

Addressing the annual convention of the National Alliance of Television and Electronics Service Associations (NATESA), E. P. Atcherley, assistant manager of Sylvania's Electronic Products Distributor Sales Dept., said that, in his opinion, television service technicians require fewer, or one strong nationally known organization, to insure proper coordination of ideas and adequate interchange of technical information.

"To fulfill its role in electronics," Mr. Atcherley stated, "the service industry should have the equivalent of an American Medical Association or a National Association of Cost Accountants. At the present time there is no single organization equipped to fulfill the servicemen's needs and protect his interests."

HAZARDOUS ANTENNA

Those who believe TV repairing is a cinch were proved wrong again when Dr. Sidney Gaft, Bronx, N. Y., was killed while fixing a television antenna. Working on the roof of a 6-story building, Dr. Gaft slipped and fell off the roof to his death.

END

Thirty-Five Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of **ELECTRICAL EXPERIMENTER** on file for interested readers.

In December, 1923, *Science and Invention* (formerly *Electrical Experimenter*)

Loudspeaker Without Microphone, by Dr. Alfred Gradenwitz.

Radio for the Beginner, No. 22, by Armstrong Perry.

Broadcast Stations.

A Compact "Single Six" Circuit, by H. E. Hayden.


Multi-Wave Reinartz Receiver, by Kenneth Harkness.

How to Build a Rogers' Cage Loop, by Dr. James Harris Rogers.

Well Made Radio Cabinet.

Radio Oracle.

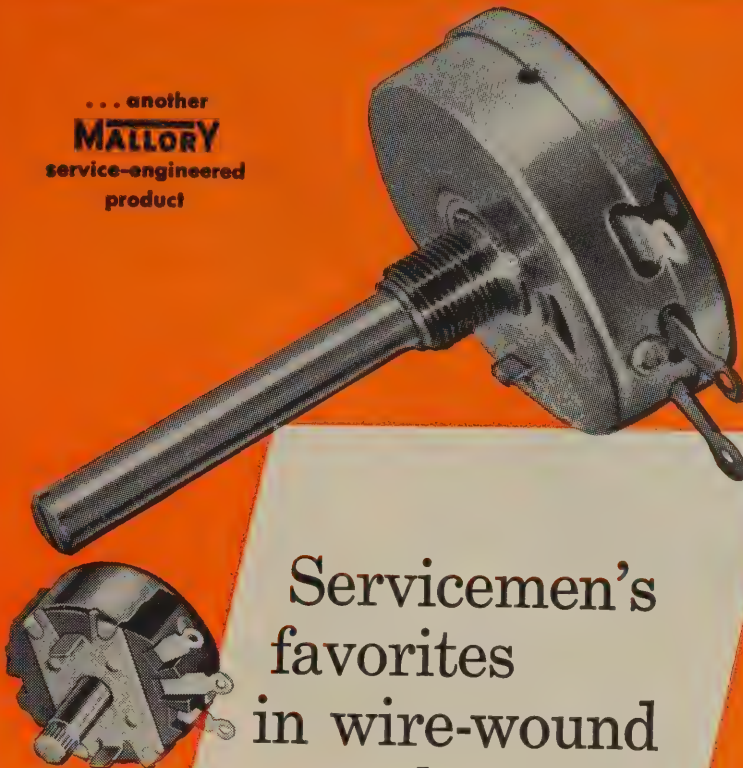... another
MALLORY
service-engineered
product



Servicemen's favorites in wire-wound controls

You're sure of giving your customers the best when you use Mallory wire-wound controls. The choice of servicemen and manufacturers everywhere, they have set the standards of the industry for value and performance.

They're conservatively rated—to assure you of cool operation without need for using over-sized units.

They're compact—fit readily into crowded chassis locations.

They're long lasting—give years of stable, dependable service.

They're uniform—made to strict specifications to meet or exceed original equipment requirements.

Mallory 2-watt and 4-watt controls are available in resistance values and tapers to match every replacement need. Your local Mallory distributor has a complete stock—see him today!

P. R. MALLORY & CO. Inc.
MALLORY


P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Controls
- Vibrators
- Switches
- Resistors
- Rectifiers
- Power Supplies
- Filters
- Mercury Batteries

another



quality
engineered
product

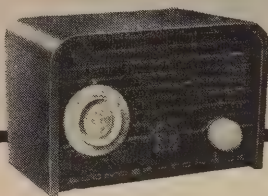

all channel UHF converter

Model 99 is your best buy in a UHF converter. Features include tuned input, precise impedance match, UL approval, one-knob tuning and drift-free performance. Largest selling UHF converter in the country at \$22.95 list ...In difficult reception areas use the BTU-2.....only \$39.95

another



quality
engineered
product



2-set coupler

Model TV-42 a 2-set coupler approved for color, UHF, VHF and FM. Matched resistive circuit with 12db interset isolation and flat response—0-900 megacycles. Another quality TV accessory engineered by B-T Labs.....\$2.95 list

Sold by electronic parts distributors

for further information
use coupon below

BLONDER-TONGUE LABS, INC. RE12
9-25 Alling Street, Newark 2, N. J.

Please send me literature covering

☐ B-T TV Accessories

Name.....

Address.....

City.....Zone.....State.....


Patents



ADJUSTABLE MULTIVIBRATOR Patent No. 2,788,449

Richard L. Bright, Adamsburg, Pa. (assigned to Westinghouse Electric Corp., E. Pittsburgh, Pa.)

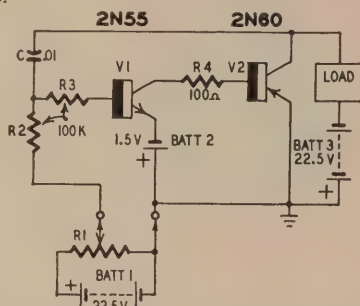When this circuit is first switched on, BATT 1 and BATT 3 act in series through the load to charge C. A rush of current through R2 produces a voltage drop that drives the junction of C, R2 and R3 negative and blocks V1. Absence of current through R4 keeps V2 nonconducting also.



As C charges, junction C-R2-R3 goes less negative. When the base voltage has dropped to about 1.5, V1 begins to conduct. Current flows through R4 to unblock V2 as well. C now discharges through R3 and saturates V1, and in turn V2. Thus, a second discharge path exists through R2 and V2.

At completion of the discharge, the cycle repeats. Voltage of BATT 1 has an important effect on the timing of the cycle, for it determines the instant V1 begins to conduct. Therefore this circuit is a pulse generator variable over a wide frequency range with but a single potentiometer control, R1.

DOG-TRAINING DEVICE

Patent No. 2,800,104

Robert C. Cameron, and John W. Hopkins, Jr., Leavenworth, Kans.

With this invention a dog's life can be made more miserable by remote control. The trainer carries an uhf portable transmitter (Fig. 1). A receiver is strapped to his dog within a



Fig. 1

harness, with a pair of electrodes touching the dog's shoulders. When the dog disobeys a command or fails to do something expected of him, the trainer presses a key to impart a "mild and unharmed, but effective" shock to his dog.

The radio detector may be superregenerative, with audio output coupled to a relay (Fig. 2). This stage is biased to cutoff, so it conducts only when modulated by a tone. Normally the relay armature touches the upper contact, allowing C to charge through R from the filament supply.

The relay is energized when the transmitter key is depressed. C discharges through the primary of stepup transformer. A high voltage

STAN-BURN

CATHODE RAY TUBE SPECIALS ONE YEAR GUARANTEE

G.E.	Type	STAN BURN	G.E.	Type	STAN BURN
\$15.80	10BP4	\$10.00	24.75	17LP4	\$18.00
19.10	12LP4A	13.95	29.00	19AP4A	24.00
30.25	13QP4	11.50	28.35	20CP4A	18.95
20.75	14CP1	15.00	33.60	20CP4B	21.95
33.75	15DP4	14.50	29.75	21EP4A	20.15
23.50	16AP4	18.50	34.85	21EP4B	23.25
32.20	16DP1A	15.25	30.90	21FP4	21.15
33.75	16GP4	18.75	37.00	21MP4	26.25
23.50	16KP4	15.75	29.75	21P4	22.00
28.40	16KP4A	18.75	34.85	21YP4A	25.00
31.50	16LP4A	16.25	28.30	21ZP4	21.00
31.50	16WP4	16.25	33.60	21ZP4B	24.00
23.50	17BP4	15.75	100.00	21AP4	56.00
28.40	17BP4B	18.75		(6 mos. guar.)	
30.75	17CP4	20.50	48.40	24CP4A	38.00
33.90	17GP4	21.50	50.00	24DP4A	39.00
*ALUMINIZED—INQUIRE FOR ANY TUBE TYPE NOT LISTED. STAN-BURN CRT TUBES RCA LICENSED.					
MFD. BY LINCOLN. All orders of 6 or more STAN-BURN CRT TUBES 100% GUARANTEED.					
PRICES SUBJECT TO CHANGE WITHOUT NOTICE.					

*ALUMINIZED—INQUIRE FOR ANY TUBE TYPE NOT LISTED. STAN-BURN CRT TUBES RCA LICENSED—MFD. BY LINCOLN. All orders of 5 or more STAN-BURN CRT are subject to additional 10% discount. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

WHY PAY MORE?

HI-FI COMPONENTS • KITS
RECORD PLAYERS • TAPES
RECORDERS • TUNERS
AMPLIFIERS • SPEAKERS
ELECTRONIC PARTS & TUBES • Etc.

Top brand nationally adv. merchandise in this and other Radio & TV mags. is yours at low cost. Send us your list. Give Mfr's name and Model No. of item. Write for '57 catalogs to Dept. RE-12 today.

BRAND NEW IMPORTED TAPE RECORDERS

Clear, sharp music and speech reproduction. Dual track, 5 tube balanced amp., 6" tape reel, Magic Eye tube, numerical footage counter, 2 tone maroon & grey leatherette case, portable, compact mechanism, weighs under 17 lbs. AMAZING VALUE!

SINGLE SPEED (3 1/4).....\$64.95
DUAL SPEED (3 1/4 and 7 1/2).....74.95
FREE reel of tape with each recorder!

HI-FI DIAMOND NEEDLES—1 Yr. Guar.

Diamond needles reduce record wear and needle noise thus retaining full frequency response and tonal qualities of your records for a longer period of time.

SINGLE DIAMOND needle.....\$7.95
DIAMOND SAPP dual needle.....8.95
Shipment PPD. (specify cartridge make)

RECORD CHANGERS

COLLARO RC-456 4 speed changer....\$33.81
GARRARD RC-88 4 speed changer....53.41
GARRARD RC-98 4 speed changer....66.15

FREE wood mounting base, record wiping cloth and 45 RPM spindle with all orders for Collaro and Garrard changers, with this ad.

VM 4 SPEED HI-FI CHANGER—Model 1210

with Ronette or Astatic flip-over cartridge.....\$22.95

MONARCH Model UA8U 4 SPEED AUTO. INTERMIX CHANGER less crystal cartridge.....\$19.95

RONETTE (phono fluid) cartridge flip-over type.....\$2.98

SONOTONE cartridge, flip-over.....\$2.98

45 RPM SPINDLE for V.M. or Monarch.....\$1.98

WOOD MOUNTING BASE for V.M. or Monarch.....\$3.95

MOUNTING BOARD unfinished for V.M. or Monarch.....\$1.50

NEW GENERAL ELECTRIC HI-FI VARIABLE RELUCTANCE CARTRIDGE. Replaces discontinued RPX050 type. Full range reproduction 20-20,000 cycles. Four gram tracking force for minimum record and stylus wear.

4G050—Dual Sapphire needles.....\$8.77

4G052—Diamond, Sapphire needles.....\$18.99

KITS!

We stock the following manufacturers complete line of kits—see reference pages.

EICO see pages 29-30
QUALITY see page 148
PRECISE
BORGES
GROMMES
TECHMASTER see page 131

All domestic orders will be shipped prepaid. Send us your list. Order by Mfr. and Model No. of item.

\$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: Porcelain sockets, coils, speaker, transistor, cond. ONLY.....\$1.98 (plus 50c postage)

1957 PHONOLOGRAPH

All models have 4 speed automatic changers in portable carrying cases, shuts off after last record, jam proof, turnover cartridge, sapphire needles, attractive modern styling with tone and volume controls:

#757 ECONOMY MODEL—mist blue and white.....\$37.50

#857 DUO-FI—2 speakers, 2 tone grey leatherette, 45 RPM spindle, ceramic cart.....49.00

#957 HI-FI—2 special HI-FI speakers, ebony starlite leatherette, 45 RPM spindle, ceramic cart.....56.50

#1057 HI-FI—3 special HI-FI speakers, 3 controls (base, treble & Vol.), ceramic cart., Diamond/Sapp needles, 45 RPM spindle, Luggage Tan leatherette.....78.00

NATIONALLY ADVERTISED IN LIFE, POST, ESQUIRE

YOU NAME IT—WE HAVE IT

Complete line of T.V. & Radio receiving tubes, coils, transistors, controls, antennas & accessories—No Minimum Order—DEALER DISCOUNT! Thousands of satisfied HI-FI enthusiasts and dealers will vouch that STAN-BURN GIVES THE BEST DEAL POSSIBLE!

EXPORT INQUIRIES AND OFFERS INVITED. Terms: 20% with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse. Write for our latest price list and HI-FI Catalog RE-12. All Prices Subject to Change Without Notice.

STAN-BURN RADIO and ELECTRONICS CO.
558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

RADIO-ELECTRONICS

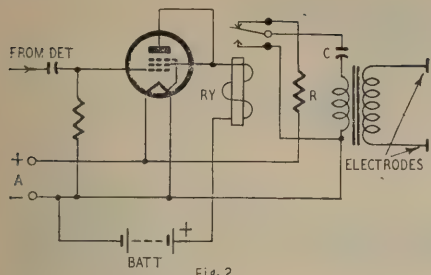


Fig. 2

The inventors recommend subminiature tubes and tiny batteries. This is the least that can be done for the poor dog. Forcing him to carry heavy equipment would be adding insult to injury.


WIDE-BAND AMPLIFIER

Patent No. 2,781,423

Chester G. Kuczun, Brighton, and Paul A. Husman, Reading, Mass. (Assigned to Laboratory for Electronics, Inc., Boston, Mass.)

Two separate amplifiers team up to provide flat response from dc to 10 mc. One amplifier (A) is effective from zero to 300 kc. The other (B) responds from 100 cycles to 10 mc. A crossover network smooths the overlap range for flat transition.

It is easy to maintain a constant gain through A, but B presents more of a problem because of the high frequencies. Therefore, its gain is regulated. A standard or pilot frequency (10 cycles) is fed to B. Some transmission occurs even though this amplifier is designed for high frequency. Initially, the pilot frequency output from B is made equal to that from the pilot oscillator. Any departure from this condition is the fault of B. An automatic control corrects its gain as needed.

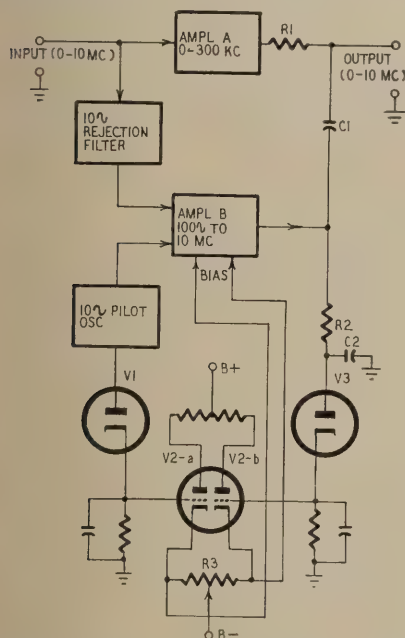


There must be no coupling between A and the pilot generator. Also, the pilot frequency must not reach B directly from the input. Both purposes are accomplished by a rejection filter

R1, C1 is a crossover unit. It reduces high frequencies from A and also low frequencies from B. R2 and C2 form a low-pass filter that transmits only the pilot frequency to V3.

V2 is a difference amplifier that receives two signals, both of pilot frequency. One is the output of the pilot generator itself, detected by V1 and filtered. The other is the output from B, rectified by V3 and filtered. These signals appear at the grids of V2. When they are equal, there is no potential difference between the cathodes of V2. Therefore no additional bias voltage is fed to B at this time. Any change in the output from the pilot generator has no effect on the bias, since it affects the grids of V2-a and V2-b equally.

If the 10-cycle output from B changes (without corresponding change from the oscillator), it must be the fault of amplifier B. For example, if the output increases, V2-b receives a more positive signal at its grid. Its cathode also goes more positive. As a result B receives a bias voltage that reduces its gain. **END**

PHASTRON

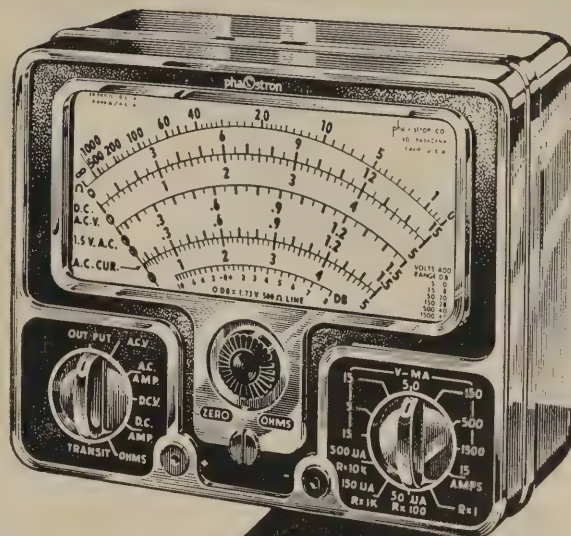

**Here Is The
Best Value
Ever Offered In
An Electrical
Measuring
Instrument...**

METER PROTECTION

The meter movement is protected up to 1000 times overload by rectifier network.

"555A"

A.C.-D.C. V.O.M.

ONLY THE PHAOSTRON "555A" V.O.M. (VOLT OHM MILLIAMMETER) MEASURES A. C. and D.C. CURRENT and VOLTAGE AS WELL AS RESISTANCE AND HAS ALL THESE FEATURES:

- Unbreakable Metal Case of Highly Polished Chrome
- Separate Range and Function Switches
- Anti Magnetic Shielding
- Easy-to-Read, Large 4-Color Scales
- 43 Unduplicated Ranges
- Only 2 jacks
- 3% D. C....4% A. C. Permanent Accuracy

Other Fine Phaostron Products

MODEL "777"—Vacuum Tube Voltmeter...42 unduplicated ranges with permanent accuracy—3% D.C., 5% A.C.

CUSTOM PANEL INSTRUMENTS—
2½", 3½", 4½", 6"...all shielded
by their metal cases from stray
magnetic fields. 2½" and 3½"
models available in round or
square face.

PORTABLE LABORATORY INSTRUMENT...with double probe outlets and full overload protection.

**RUGGEDIZED AND SEALED
PANEL INSTRUMENTS**...available
in 1½" (Square Bezel) and 2½",
3½", 4½" Round Bezel models in
AC, DC or Null Indicators.

ACCESSORIES AVAILABLE

Genuine Leather Carrying Case \$7.95
Panel Mounting Adapter \$1.50

NEW LOW PRICE

Not \$49.50, but priced lower than ever before. Complete with probes and batteries. (Replaces former model 555)

NOW ONLY

\$44⁹⁵


Write today for full details or ask your dealer

PHAOSTRON INSTRUMENT AND ELECTRONIC COMPANY

151 Pasadena Avenue, South Pasadena, California


"FOR
OUTSTANDING
PERFORMANCE
AND
TROUBLE-FREE
OPERATION
YOU CAN DEPEND ON
BENCO
TV EQUIPMENT"

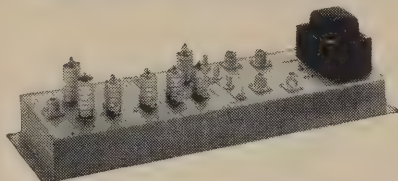A complete range of TV equipment for hotels, motels and community systems.




SUPER-40—BROAD BAND AMPLIFIER

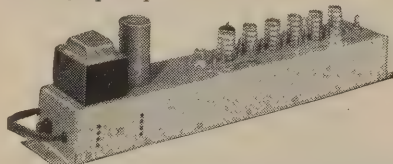Completely new design—Four 75 ohm inputs, each separately controlled—Modified cascode input, giving extremely low noise figure—Most versatile amplifier for present day conditions. Total output up to 4 volts. **\$115⁰⁰**




P. A.—SINGLE CHANNEL PRE-AMPLIFIER

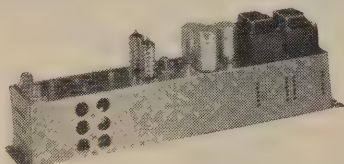The ultimate in head end equipment—60 db gain—Extremely low noise, full A.G.C. Exceptional results with signals as low as 50 microvolts. **\$135⁰⁰**



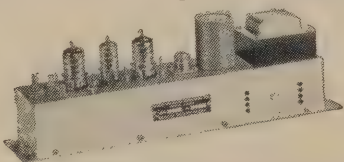H. C. A.—VERY HIGH OUTPUT AMPLIFIER

Designed for all applications where a high output voltage is required. Capable of driving a low band signal through 2½ miles of K-14 type cable. 5 volts maximum output. **\$250⁰⁰**



S. P. A. SINGLE CHANNEL PRE-AMPLIFIER

For head end of multiple systems. 40 db gain—built-in overload control. Low noise cascode input. Economically priced at **\$59⁹⁵**

Prices are suggested user net.

USE THIS HANDY COUPON

Benco Television Associates Ltd.,
27 Tabor Road,
Rexdale, Ontario, Canada
Please send me full information on

- ☐ Super "40" ☐ P.A.
☐ H.C.A. ☐ S.P.A.

Name

Address

City..... Prov. State.....



Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

PROKOFIEV: Peter and the Wolf
SAINT SAENS: Carnival of Animals
Rodzinski conducting Philharmonic of London
Scherchen conducting Vienna State Opera Orchestra

Westminster XWN-18525

Few combinations of music present as delightful material for testing, demonstration and show-off (as well as listening) as these two. Westminster does its wonderful best, presenting marvelous drums and solo double bass and a brilliant and clean overall sound. Unfortunately, it undoes its work by an error which I cannot forgive in a company with so much hi-fi savvy. The commentary by Garry Moore, dubbed in after the recording of the orchestras, is at a level higher than the peaks of the orchestras. It is impossible to set the volume to bring the musical portions to best effect without raising the voice to the level of a fog horn. I urge Westminster forthwith to redub the job with the voice at least 6 db, and preferably 10 db lower. If it does so, it should have a best selling hi-fi hit. The solo bass in the *Elephants of Carnival of Animals* alone is worth the price. Here, at last, is a double bass not as big as life but as big as many hi-fi fans would like it to be, with fearsome capacity to rattle the loose china and window panes and to find any point of resonance in the system—or the house structure. Its rosy guttiness is entirely natural, too. The drums, too, are both prodigious and natural. Other elements contribute to its superiority. As a dividend—which may annoy some—it includes the very awesomely natural sounds of the animals. The roar of the lion will especially delight owners of really fine speaker systems. It has the genuine thunderous ominousness. But, I repeat, as long as the voice is at its present ridiculous level, these virtues will either have to be hidden or paid for with headache and family strife.

HOLST: The Planets

Stokowski conducting Los Angeles Philharmonic

Capitol P-8389

This second release makes plain that the new association of Capitol and Stokowski is going to be a highly rewarding one for listeners with fine hi-fi systems. This music is extraordinary in its variety of tonal effects. Requiring a very augmented orchestra, it provides opportunity for almost every instrument to show off its particular forte and in several fearsome peaks produces a concatenation of orchestral sound which is hard to match. This recording does a superb job of bringing it all to the ear, with complete freedom from distortion, great faithfulness of tone and an extremely fine definition. It will take a really fine system to do it justice, but on such a system it is hard to imagine what advantage a live performance could have. For those who can learn to like the music well enough to become familiar with the detail, this would be a superlative test recording—par-

ticularly for distortion, definition and naturalness. And it would be a fine demonstration record for musicians or sophisticated listeners. For my money, the best recording Capitol has issued so far.

DVORAK: Slavonic Dances (Nos. 1-10)
Malko conducting Philharmonia Orchestra of London

RCA Victor LM-2096

DVORAK: Slavonic Dances (Nos. 11-16)
GRIEG: Lyric Suite
Same orchestra

RCA Victor LM-2107

Now that everybody has recorded Strauss waltzes in hi-fi, it appears that another cycle may be in the making with *The Slavonic Dances*. If so, it's a good idea, for these dances have a fine variety of music and tone coloring. This one is good enough musically, but the bass is rather vague for hi-fi demonstration. *The Lyric Suite* makes an excellent pairing. The surfaces of my copies were very noisy and nothing I could do would quiet them.

ROZSA: Jungle Book Suite
Thief of Bagdad Suite
Composer conducting Frankland State Symphony Orchestra

RCA Victor LM-2118

The background music to the Alexander Korda filming of Kipling's *The Jungle Book* was recorded by RCA Victor with the voice of its hero for the narration before the war on 78's and proved very popular with the young fry. The music itself has been frequently performed in concert suite version. Here we have a new version, but with an adult voice in narration. The original was far more effective, but this should be pleasing to those who have not been conditioned by the original recording. The same composer's music to the movie, *Thief of Bagdad*, also with narration, has the flip side. The balance of voice to music is excellent. Not remarkable in hi-fi effects but pleasant and clean.

BIZET: Carmen Suite
L'Arlésienne Suite No. 1


Paray conducting Detroit Symphony
Mercury MDS 5-3

KODALY: Hary Yanos Suite
Dorati conducting Minneapolis Symphony

Mercury MDS 5-1

Mercury's entry into the stereo tape field is a welcome one. For one thing its Olympian recording technique with its great dynamic range is particularly suited for showing off the advantages of tape reproduction. Whereas on the discs the peaks are very likely to overload even the best pickups, on tape they come through with a brilliant cleanness. For another, the Mercury three-channel recording technique is a step toward but not a complete solution of the "hole-in-the-middle effect" of two-channel stereo reproduction. Finally, and perhaps best

New LOW Prices for CBS Power Transistors

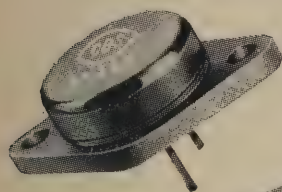

2N255
\$1.35



2N256
\$1.50

Stepped-up sales and production made them possible. The savings go to you. Your net prices for the CBS 2N255 and 2N256 are cut in half!

Now radio amateurs and experimenters can build a variety of economical transistorized equipment, fixed or mobile, capable of real power output:

- Ten-watt mobile modulator
- Mobile power inverters
- Six-watt hi-fi amplifier
- Code practice oscillator
- Compact mobile p-a system
- Portable phono amplifier
- Sensitive relay circuit
- D-c voltage multiplier
- Regulated power supply



Write for Bulletin PA-16, CBS Power Transistor Applications, giving complete details. Or pick it up along with your low-cost 2N255 and 2N256 transistors at your CBS Tube distributor's.

CBS-HYTRON

Semiconductor Operations, Lowell, Mass.
A Division of
Columbia Broadcasting System, Inc.

DECEMBER, 1957

NEW RECORDS (Continued)

of all, the initial offerings present the spectacular type of material which makes the most vivid impression whether on stereo or single channel. This pair of tapes will present present-day stereo at its very best. The Hary Yanos, especially, has some very spectacular spots which, on the best stereo systems, will yield a most persuasive and brilliant presence. The more familiar *Carmen Suite* also has some very effective portions. The cost is high but pays for some of the very finest stereo tapes so far issued.

Dancing and Dreaming Jay Norman Quintet

Concertapes 24-2 (stereo)
456 (monaural)

There is nothing very demanding or spectacular about the music, but this tape is capable of bringing a five-piece supper club ensemble right into your living room. The high highs and percussives of the rhythm are extremely good, and the monaural version would be excellent for demonstrating really fine single-channel systems.

Russkaya Dragon conducting Hollywood Bowl Orchestra

Capitol P-8384

Another of the excellent combination salads in the Hollywood Bowl series which ought to find a very wide audience, especially among those who are just beginning to enjoy both classical music and high fidelity. This consists of a half dozen such proven Russian favorites as the *Overture from Russian and Ludmila*, *Volga Boatman*, *Dance of Buffoons*, *Kamennoi-Ostrow*, *Tchaikovsky's Melody* and the folksong-based *Meadowland*. There is plenty of both hi-fi fireworks and melody. The recording is fully up to the high standards of this series—clean even in the biggest peaks, with a realistic balance of highs and lows, and a nice liveness. Nothing here to try a system severely, but much to make even a moderate system sound good; easy to listen to at low levels and respectfully impressive for demonstration at loud levels, especially *Meadowland*.

Guitariana Espagnol Richard Pick on Solo Guitar

Concertapes 24-1 (stereo)
455 (monaural)

Recording a solo guitar in stereo looks like a silly performance and, in fact, sounds silly in spots. But few recordings communicate so high an immediacy—even in the monaural version. If you've never listened to a guitar at a distance of a few inches, this will give you the very same experience. The reproduction of the guitar transients is almost painfully real, and I recommend the monaural version as a demonstration piece with first-class single-channel systems.

Lena Horne at the Waldorf-Astoria With Nat Brandywine's Orchestra

RCA Victor LOC-1028

On-the-spot recording of an actual performance. The recording of Lena is extremely intimate and her breathing, etc. are very audible. There is a most strange effect, however, in the spots when she opens up double F. To prevent overloading, the engineers reduced gain of the closeup mike, which has the effect of seeming to make her move about 20 feet back during the loud spots. Exceptionally clean for a pop. The audience was well disciplined except for one table whose ebullience is plainly audible on the flip side.

TCHAIKOVSKY: *Serenade for Strings* BARBER: *Adagio for Strings* ELGAR: *Introduction and Allegro for Strings*


Munch conducting Boston Symphony
Strings

RCA Victor LM-2105

Though we seldom pay any great attention to the quality of the strings in recordings, the fact is that it is not easy to record or reproduce massed strings with any great verisimilitude. They seem able to find any discontinuity or resonant peak in a speaker system and indeed few tweeters really come through with flying

t-m KITS

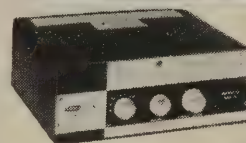
- Advanced designs for the best in high fidelity reproduction
- Build and save do-it-yourself
- See them at your local radio parts distributor



New 60 WATT
HIGH FIDELITY
**AMPLIFIER-
PREAMP KIT**

An integrated high power amplifier package for the audio perfectionist—complete with versatile pre-amplifier in one compact high styled unit—at a budget price. Undistorted power output is guaranteed to be 60 watts from 20 to 20,000 cps. Intermodulation is 1% at 60 watts and below 0.25% at ordinary listening levels.

Model 19K.....\$79.95
Cabinet.....7.50

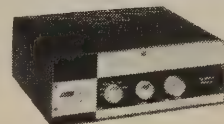


New 25 WATT
HIGH FIDELITY
**AMPLIFIER-
PREAMP KIT**

Top quality integrated amplifier preamplifier system on a single chassis at exceptionally low price. Performance equals or exceeds any available amplifier up to rated power of 25 watts.


Model 21K.....\$59.95
Cabinet.....7.50

WILLIAMSON TYPE 20-WATT AMPLIFIER

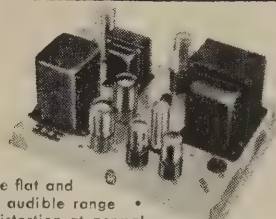


Frequency response flat and smooth thru entire audible range • Less than .0025 distortion at normal listening levels • Excellent transient characteristics.
Model TM-15A, complete with tubes—sockets, terminal strips, and connectors mounted.....\$49.95

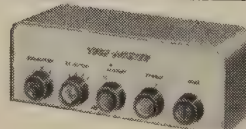PREAMPLIFIER with Cathode Follower Output



4 input channels • Separate bass and treble controls • 3-position equalizer • AC outlet for auxiliary equipment • Powered by main amplifier.
Model TM-17P, complete.....\$19.95

HI-FI FM TUNER

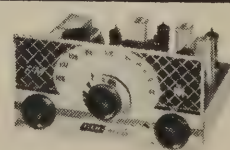

Self-contained power supply • Tuning range 87-109 Mc • 200Kc IF bandwidth • Grounded-grid RF stage • AFC with front-control cutoff • Microvern timer • No-drift ratio detector • 4 uv sensitivity for 20 db quieting • Standard de-emphasis network • .8 volt RMS cathode-follower output • 3.2 volt RMS high-impedance output • 300 ohm input impedance • Switch-controlled AC receptacle for auxiliary equipment.

Model FM-18, complete with punched chassis, tubes, and hardware (less wire and solder).....\$29.50

**t-m
KITS**

Write for latest catalog to:
a product of
TECH-MASTER CORPORATION
75 Front St., B'klyn 1, New York

GIVE YOUR EARNINGS A BIG B-O-O-S-T!

Let these 2 Great Manuals Train You to Service
any Radio or TV Set faster.more profitably



The way to earn more is to learn more! These Ghirardi manuals make it easy for you to be a well-paid expert on all types of Radio-TV service. And they cost only a fraction of the price you might expect for such complete, easily understood training. If sold as a course, you'd regard them as a bargain at \$100.00 or more. Instead, you buy both big books for only \$13.00... and don't risk a cent until you see how good they really are!

SAVE \$1.25

Get this complete 1500-page modern service training library for only \$13.00. Use coupon.

3 MONTHS TO PAY

Cut service time in half!

COMPLETE 889-PAGE TRAINING IN TIME-SAVING PROFESSIONAL METHODS

For beginners, this famous **RADIO & TV TROUBLESHOOTING AND REPAIR** manual is a complete, top-notch course in money-making professional service methods. For experienced servicemen, it is the ideal way to develop better troubleshooting techniques and shortcuts, find quick answers to puzzling problems, and to handle tough jobs faster.

Block diagrams, response curves, 417 illustrations and other features speed your work... make each step doubly clear. Here are some of the subjects: Component Troubles; "Static" and "Dynamic" and "Visual" Troubleshooting Methods; Shortcuts and Tips; Complete Guide to Television Service; Realignment Made Easy; FM, Communications Receivers, Record Players, etc.; Auto Radios; Loudspeakers; Servicing Tuner and Switching Mechanisms... and many more. Price \$7.50 separately. See MONEY-SAVING OFFER in coupon.

TELLS YOU HOW! SHOWS YOU HOW!

Handy "Quick Guide" Charts cover practically every type of troubleshooting and servicing... from television testing to AM and FM realignment, IF and Detector Sections, car radios... and many more.

THE COMPLETE 'KNOW-HOW' OF CIRCUITS AND THEIR SERVICE PROBLEMS

You can repair any radio or TV set ever made far better, faster and more profitably when you know its circuits from A to Z. That's where this 669-page **RADIO & TV CIRCUITRY AND OPERATION** manual is worth its weight in gold.

You locate troubles quicker... because circuitry "know-how" teaches you exactly what to look for and where. Useless testing and guesswork are eliminated. Covers every receiver circuit and variation to common use. Teaches you their peculiarities and likely trouble spots. Over 110 pages explain every detail of Television circuitry for all receiver sections.

Throughout, this famous book brings you the kind of above-average training that really pays off. Price \$6.75 separately... or see MONEY-SAVING OFFER in coupon.

'GOODBYE' TO SERVICE HEADACHES!

Become an expert on circuits... and watch your service headaches disappear! This book contains the kind of training that counts big in helping you work faster and make more money.

---PRACTICE 10 DAYS FREE!---

Dept. RE-127, RINEHART AND COMPANY, INC.
232 Madison Ave., NEW YORK 16, N.Y.

Send books checked for 10-DAY FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing. (NOTE: Send cash with order and we pay postage. Same 10-day return privilege with money promptly refunded.)

☐ MONEY SAVING COMBINATION

Both books only \$13.00... you save \$1.25. Payable at rate of \$4 (plus postage) after 10 days and \$3 a month thereafter until \$13.00 has been paid.

- ☐ Radio & TV Troubleshooting and Repair (\$7.50)
☐ Radio & TV Circuitry and Operation (\$6.75)

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A.—\$8.00 for TROUBLESHOOTING AND REPAIR; \$7.25 for CIRCUITRY AND OPERATION; \$14.00 for both. Cash with order only. Money refunded if you return books in 10 days.

NEW RECORDS (Continued)

colors when faced with the high end of the string register. Furthermore, there is a peculiar rosy shimmer or murmur to massed strings which seldom comes through as it should in records. The string section of the Boston Orchestra, with its precision and excellent tone, is eminently suitable for an attempt at faithful reproduction and in this record RCA does a very good, though not yet perfect, job. With top-notch equipment, you should be able to reproduce it with no distortion and no wiriness, but with a plainly audible rosy tone.

TCHAIKOVSKY: Violin Concerto in D
Heifetz, Soloist
Reiner conducting Chicago Symphony
RCA Victor LM 2129

The solo violin is not as easy to record and reproduce as some think, either. Tweeters have a special gift for changing its coloration, and pickups seem especially subject to becoming rattled by portions of its range. This recording of one of the most favored of all fiddle concerti by one of the masters of the instrument is perfect enough to present a completely fair test to any system. If you hear any unpleasant edge or distortion or if the color seems uncharacteristic, you can safely blame your system. This disc continues the somewhat artificial combination of closeup mike on fiddle and more remote one on orchestra which I have noted previously, but the effect is nevertheless quite impressive and the intimacy of the violin will enable any fiddler to discern (and criticize) Heifetz' technique in detail. Listen for the fingering transients in the rapid runs.

FRANCK: Symphonic Variations
RIMSKY-KORSAKOV: Piano Concerto
SCRIABIN: Piano Concerto
Badura-Skoda, Piano
Vienna Symphony and Philharmonic of
London
Westminster XWN 18521

BEETHOVEN: The Five Piano Concertos
Artur Schnabel, Piano
Krips conducting Symphony of the Air
RCA Victor LM-6702 (5 12-inch LP's)

The Victor offering is an almost monumental collection of five records of the complete Beethoven concerti at a special price and represents a bargain all the more worth while because of the excellence of the recording. Experts may prefer other pianists for some of these, but the layman can be assured of hearing these great examples of the concerto in authoritative performance and interpretation.

Paul Badura-Skoda and Westminster present the seldom heard Scriabin and Rimsky-Korsakov concerti and the more familiar Franck variations also with great competence and a possibly more stunning recording of the piano—especially its bottom end. The big, very damped tympani are a pleasant dividend.

MOZART: Symphonies Nos. 29, 30, 31 and 32
Leinsdorf conducting Philharmonic Orchestra of London
Westminster XWN-18216

This, too, is for listening, not testing or showing off. It is part of a series which will eventually include all of Mozart's symphonies. These are not as familiar as the later ones but all have the characteristic Mozartian charm. The recordings present the music to its best advantage with fine definition and a spacious and clean sound.


Relax With Larry Ferrari
Hammond Organ and Schulmerich
Harp-Celesta

RCA Victor LPM-1496

A typical restaurant type potpourri of popular tunes on a Hammond organ distinguished by the addition—for the first time, it is said, on records—of the Schulmerich harp-celesta, which offers both harp and celesta tones. Pleasant background music. END


Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

Technotes

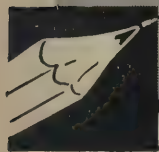

WEAK COLOR

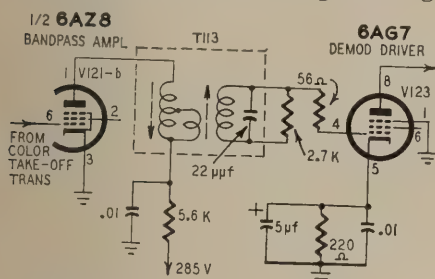
We've come across what seems to be a fairly common trouble in the RCA 21-CT-663U. The set comes in with weak color, all washed out even with the chroma control turned all the way up. Circuit checks and voltage readings



reveal low plate and screen voltage at V121-b, the bandpass amplifier. A positive voltage is found at the grid of V123, a demodulator driver. Turns out that T113, the bandpass transformer develops a high-resistance short between its primary and secondary—usually more than 1 megohm. Replacing the transformer is the only cure, and a quick one.—Joe Shane

INTERMITTENT OSCILLATION

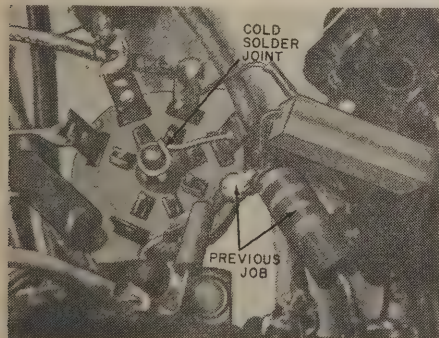An Emerson was brought into the shop with a complaint of occasional jellyfishing. The symptom would vary. Violent shaking was one type while complete loss of sync was another. A negative picture with smear was a third, even though the negative picture was not over the entire raster. The symptom could be excited by jarring and the



set's speaker did the exciting while in the customer's home. The speaker was disconnected temporarily to prove this point of a loose contact someplace.

A meter on the agc indicated a rise whenever the symptom occurred. And the same increase in voltage was noted across the detector load resistance. As a result of this check, the trouble seemed to lie ahead of the video detector.

The voltmeter was left connected to

IT'S NEW!
IT'S A BARGAIN!
IT'S "IN THE BAG"!

VACO®

5-PIECE
ALL HOLLOW
SHAFT

Nut Driver Kit

No. K 505

Only
\$3.68
NET

Break-Proof Shock-Proof Comfortome Handle

All-Hollow Heavy Duty Shaft

Extra Hard Long Wearing Hex Head

Convenient! Compact!

Here's a practical, quality built nut driver kit . . . economically priced, too! 5 popular sizes . . . $\frac{3}{16}$ ", $\frac{1}{4}$ ", $\frac{5}{16}$ ", $\frac{11}{32}$ ", $\frac{3}{8}$ " ideal for every service need . . . in one convenient plastic bag with button-down flap to keep drivers in place! Made to VACO professional quality standards throughout backed by our famous unconditional guarantee.

See Your Parts Distributor, Today!

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: ATLAS RADIO CORP., Toronto 10, Ontario

Christmas Seals

ARE THE AMERICAN PEOPLE'S
FAVORITE SYMBOLS OF CHRISTMAS GIVING

HI-FI ACCESSORIES BY

Dynamic

ELECTRONICS

FOR BETTER RESULTS

RECORD COMPENSATOR

Model RC 180 \$9.50 List

THERE IS A DYNAMIC ACCESSORY FOR ALMOST EVERY NEED. SOLD ON A MONEY BACK GUARANTEE!

At Leading distributors everywhere. Full Line Catalog on Request!

Manufactured By
DYNAMIC ELECTRONICS-NEW YORK, INC.
Forest Hills, Long Island, N. Y.

COYNE

TRAINS YOU
IN SPARETIME
AT HOME

TELEVISION

RADIO-COLOR TV

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. *Practical Job Guides* to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly "put together kits."

SEND COUPON FOR FREE BOOK
SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.

B. W. COOKE, Jr., Pres. **COYNE ELECTRICAL SCHOOL** FOUNDED 1899

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina, Dept. 97-HT4, Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. 97-HT4

Send FREE BOOK and details of your Television Home Training offer.

Name _____

Address _____


City _____ State _____

when you think of speakers,


think of OXFORD Speakers

Oxford Speakers are at
recognized distributors.

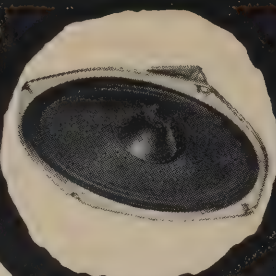
A FREE CATALOG is available
... write for yours NOW!



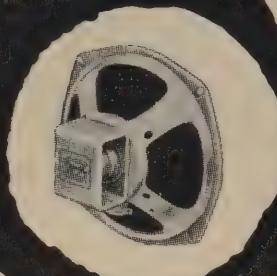
DUAL CONE HI-FI SPEAKER
a new development to provide
top performance. Available in
OXFORD REAR DECK SPEAKER
KITS for all automobiles.



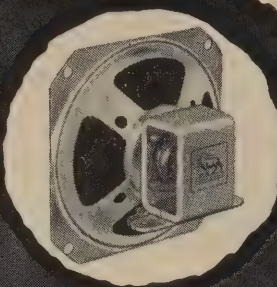
RADIO and TELEVISION SPEAKERS ... as the source for more
speakers to original set manufacturers — you can't go wrong when
you specify ... OXFORD for original
equipment or replacement applications.



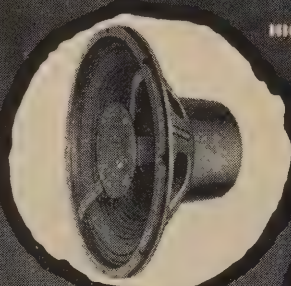OUTDOOR SPEAKERS ... regardless
if you need speakers for drive-in
theater applications, OR any other
use where you want rugged, steady
performance, specify the OXFORD
WEATHER-PROOF SPEAKERS ...
you'll be glad you did.



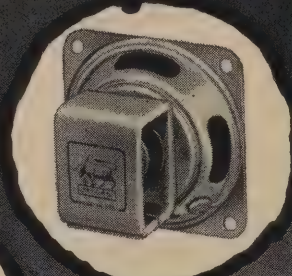HIGH FIDELITY SPEAKERS
demand the unsurpassed
sound reproduction which
OXFORD SPEAKERS
not only promise,
BUT guarantee
and at prices that will
amaze you.



SPEAKERS FOR PORTABLES
there must be many reasons
why more Oxford Speakers
are used in portable radios
than ever before in over 30
years of manufacturing the
finest speakers.

AUTO RADIO SPEAKERS
Oxford assures you of the most
enjoyment in your automobile
when you have one of the
many Oxford auto speakers.



OXFORD Components, Inc.

Subsidiary of Oxford Electric Corp.

556 West Monroe Street • Chicago 6, Ill.

In Canada: Atlas Radio Corp., Ltd. Toronto • Export: Roburn Agencies New York City

OPPORTUNITY ADLETS

Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for February issue must reach us before December 15, 1957.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

BE A SPY! Correspondence course on wire tapping, bugging, telescopic sound pickup, recording techniques, micro-photography, invisible and remote photography, telescopic and serial photography. Lessons in surveillance, trailing, and use of equipment. Complete course \$22.50. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

DIGITAL COMPUTERS AND DATA PROCESSING. Complete correspondence course covering theory of operation and applications with a comparison of 10 different medium sized systems. Complete course \$25.00. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

GUIDED MISSILES AND SATELLITES. Correspondence course covering Missile Aerodynamics, Internal Control and Navigation Systems, Ground Control & Telemetering, and Rocket Engines. Complete Correspondence course with plans for Hottest Missile \$38.50. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

BUILD YOUR OWN "A" BOMB. Complete correspondence course covering Atomic "Fission" and "Fusion" Bombs and Reactors; Fundamentals, Applications, and Nuclear Engineering. Complete 2,500 page industrial course \$10 with order & \$4 per lesson. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPRITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

TRANSISTOR GENIUS! Learn transistor fundamentals, applications. Audio, RF, High Frequency design. Complete correspondence course with laboratory experiments and parts included. \$32.50. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

RADAR & PULSE Communication. Correspondence course covers Principles, Antennas, Transmitters, Receivers, Magnetrons, Klystrons, Backward Wave Tubes, Sea Search, Air Search, Fire Control, Voice Multiplex. Includes section for FCC Radar endorsement. \$58.75. A. Carrier Co., 734 15th St., N.W., Washington 5, D.C.

MANUFACTURERS SURPLUS Build your own electronic organ from these basic units: 60 note triple stacked shunt keying mechanisms, octave wired isolating resistor to each palladium contact. Three types available: Great 16', 8', 4' dimensions 5" wide, 2 1/2" high, 36" long; Swell 8', 4', 2 1/2" dimensions 3 1/2" wide, 3 1/4" high, 36" long; Single Manual 16', 8', 4' including 12 pedal bass notes dimensions 4" wide, 3" high, 36" long; keying mechanisms. \$10 each. Tone generators, 5 octaves each, sold only in sets of 12 units; notes C through B. These units consist of 3 nine pin tube sockets, one 5K wire wound tuning control, not less than 18 condensers, 400 and 600 volt, 18 resistors, 2 five pin plugs, all parts mounted in generator chassis. Each set \$12. C.O.D. orders not accepted. No schematics or photos available. MINSHALL ORGAN INC., Brattleboro, Vermont.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. Walker 5-7000.

20-50% DISCOUNTS on Hi-Fi, tape recorders, tape, accessories, photographic equipment, individual quotations only. No catalogs. CONMAR CAMERA & HI-FI, 121-07 237th Street, Rosedale 22-R, N. Y.

TECHNOTES (Continued)

the detector load and the first if's grid was grounded with a jumper. The chassis was shaken again and the rise of voltage definitely indicated oscillation in the if section. Successive grounding and many tappings with shakes localized the trouble to one stage.



The photo shows the bottom view of this stage with a miniature tube as the amplifier. Some previous repair work had been done. Evidently a resistor had been replaced.

In so doing, the iron had heated the center contact of the tube socket. And the lead to it was probably shaken while cooling. The result was a cold soldered joint at the center contact. Resoldering cured the symptoms once and for all.

The center contact is grounded to prevent undue capacitance between the input and the output forming a small shield. Stage gain was enough on weak stations to force the set into oscillation due to this added capacitance. Most of the time the joint made good enough contact to prevent the oscillation.—
James A. McRoberts

PHILCO CHASSIS 7L40

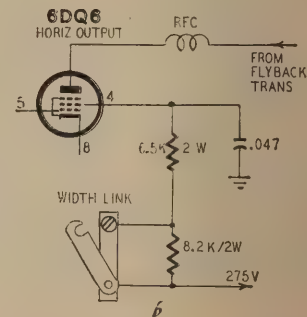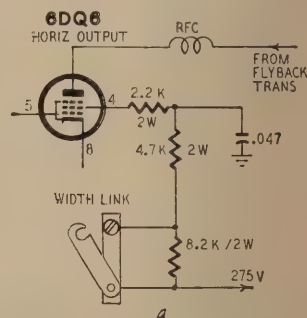
On these sets you will occasionally run into a horizontal drive line which cannot be eliminated. If all horizontal tubes have checked good, take a look at the 6DQ6's screen circuitry. The correct hookup should include a 2,200-ohm and a 4,700-ohm resistor as shown in *a*. On several of these models, the circuit had been changed so that a 6,500-ohm resistor replaced the two shown in *a*.



This circuit (*b*) supplies approximately the same screen voltage but puts the .047- μ f capacitor directly between screen and ground, effectively removing the isolating or screen suppressor resistor and reducing the width. Replace the single resistor with the two proper values. The 6DQ6 socket has two spare pins which can be used as tie points.—
John B. Ledbetter

FIELD COIL RESISTANCE?

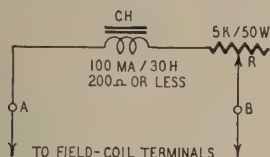When you run into a loudspeaker with a burned-out field coil and don't know what the coil's resistance is; relax, there is a way to find out.



Connect a 5,000-ohm variable resistor (R) in series with a filter choke (CH) across the field-coil terminals. Vary R until proper plate and screen voltages appear. Then turn the power off and measure the resistance between points A and B. Now just hook up a coil with the same value.—Stanley Clark

DU MONT RA-165

The complaint was no picture. I found a burntout 6BQ6 and replaced it. This restored the picture, but there was a slight horizontal displacement and critical vertical sync. I checked the sync, video, if and tuner tubes—all were very good. The customer said that the trouble had been there as long as she could remember and the chassis had received shop repairs without the difficulty being corrected.

This presented a challenge, so I convinced the customer to let me take the set to the shop. I set it up on the bench with a test tube and yoke. It performed perfectly. All waveforms and voltages were normal. After letting it cook for a few days, I returned it.

The set still had a slight horizontal displacement and critical vertical sync. I pulled the chasis again, this time with the yoke and picture tube. Set up on the bench it played perfectly. I brought the cabinet to the shop and found the trouble would appear only when the set was in its cabinet. Further checking showed that the trouble started when the chassis was about two-thirds in the cabinet.

Several enjoyable minutes were spent pushing the chassis in and out of its cabinet and watching the trouble come and go. Then I checked the bottom of the chassis for parts which might be hitting the cabinet. I had absolutely no luck!

The only conclusion was that the trouble could not be happening. But it was! Then I noticed a blue lead running on top of the chassis to the local-fringe switch. The trouble would start when this lead was under the front of the picture tube. I rerouted the lead under the chassis and the trouble was permanently cured.

The picture tube was a glass 21-inch type with its outer coating grounded. There was only a fraction of an inch between the top of the chassis and the front bottom of the C-R tube. Evidently the capacitance between the blue lead and the grounded C-R tube coating was enough to disturb the sync pulse.—Harry D'lott, Terrace Radio & Television

END

YOU NEED THIS...

FREE GIANT ALL NEW 1958 BA CATALOG

172 KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR 1st TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

RUSH COUPON TODAY!

INDEX PAGE 1/2

BURSTEIN-APPLEBEE CO.

BURSTEIN-APPLEBEE CO. Dept. M, 1012-14 McGee St., Kansas City 6, Mo.

☐ Send Free 1958 B-A Catalog No. 581.

NAME _____

ADDRESS _____

CITY _____ STATE _____

OPPORTUNITY ADLETS (Continued)

RENTALS, The Best in Stereo Tapes. Write, CALIFORNIA TAPED MUSIC ASSN., 1971 Cordilleras Road, Redwood City, Calif.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 672-RE, Hartford 1, Conn.

WANTED: Electronics technicians desiring educational achievement accreditation in electronics. CRAMWELL RESEARCH INSTITUTE, INC., EM-7, Adams, Mass.

FREE Illustrated Catalog, postpaid printing. D M PRESS, Sebastopol, Calif.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT Co., 128 Liberty Street, New York, N.Y.

1500 PERSONALIZED 5/8" x 1 1/8" Labels \$1. Your 3 line name & address printed with blue ink on fine quality white gummed paper. Money back guarantee. HAMILTON-WARD, Dept. 11B, Westfield, Mass.

LOOKING FOR CLEAN RESPONSE to 20 Cycles? Listen to the radically new "Racon Hi-C" foam suspension speaker. Write for free literature, RACON ELECTRIC CO., INC., 1261 Broadway, N.Y. 1, N.Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 696 Sunrise Highway, Babylon, N.Y.

COMPLETE Television Sets \$11.95. JONES TV, 1115 Rambler, Pottstown, Pa.

LEARN WHILE ASLEEP! Details free. RESEARCH ASSOCIATION, Box 610-RE, Omaha, Nebraska.

PORT ARTHUR COLLEGE—Training for FCC Licenses. Enrollment Monthly. PORT ARTHUR, Texas.

PRINTING PRESSES, Type, Supplies, lists 3c. TURNBAUGH SERVICE, Mechanicsburg, Pa.

RECORDERS, Hi-Fi, Tapes. Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counters, etc. \$1 each. List Free. PARKS, Box 946 Redwood City, Calif.

LONG PLAYING RECORDS 20 to 50% Discount Brand-New Factory Fresh Unplayed—All Labels—Send 20c for catalogue to RECORD SALES, 1110 Winburn, Houston 4, Tex.

Patents, Copyrights. SANDERS, Registered Patent Attorney, 6430 Evans, Chicago 37, Ill.

DIAGRAMS! Repair Information! Radios—Amplifiers—recorders \$1. Televisions \$1.50. Give make, model, chassis. TV MILTIE, Box 101EA, Hicksville, N.Y.


DEALERS SELL Your Trade-In TV Sets: WANTED—PACKARD-BELL (B-W 1953), HOFFMAN (B-W 1951), STROMBERG CARLSON (B-W 1953), HOFFMAN (Color 1953) Price includes heavy packing—shipping charges to be collect. Do Not Ship Sets Now—Send Only Details. PANJONY SERVICE, C. J. DEMAREST, Box 644, Flushing 52, N.Y.

DISCOUNTS UP TO 50% except fair trade items—Cameras, projectors, tape recorders, lenses, Hi-Fi, components. Write for individual quotations on your specific needs, no catalogs. CLASSIFIED HI-FI EXCHANGE RE, 2375 East 65th St., Brooklyn 34, N.Y.


LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

UNUSUAL CONFIDENTIAL QUOTATIONS on all your "Hi-Fi" requirements. No Catalogs. KEY ELECTRONICS, 120 Liberty Street, N.Y. 6, N.Y. EVERgreen 4-6071.

new Devices

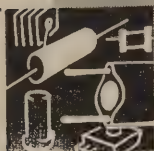

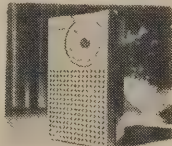TRANSISTOR RADIO, model TR-4. Superhet, printed circuitry. 3 x 5 x 1 1/4 inches. 12 ounces.



—I. D. E. A., Regency Div., 7900 Pendleton Pike, Indianapolis, Ind.


AUTO RADIO. All-transistor model. Fits 1958 Oldsmobiles and



Pontiacs. Can be slipped out and used as portable radio. 9 transistors. Automatically plugs into car's electrical system. Uses car's speaker, antenna and extra transistor audio system.—Delco


Radio, Div. General Motors, Kokomo, Ind.

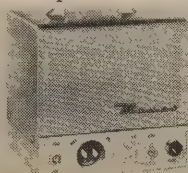ELECTRONIC CONVERTER, model CV-612. 6- or 12-volt input. Delivers 117 volts at 130 watts constantly, 150 watts intermittently. 7 x 8 1/2 x 8 1/2 inches. 18 pounds.—Mark Simp-




son Manufacturing Co. Inc. (MASCO) 32-28 49th St., Long Island City 3, N.Y.

WINDOW SPEAKER SUP-

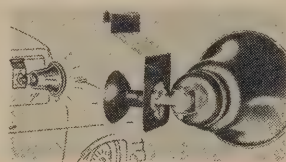


PORT, WM-1. Fastens speakers to auto window. Made from sheet steel finished in gray enamel.—Atlas Sound Corp., 1451 39th St., Brooklyn 18, N.Y.

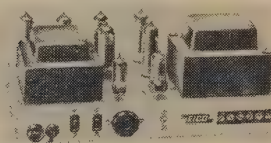BASIC AMPLIFIER, HF-30, kit and wired. 30-watts. 15-50,000



cycles \pm 0.5 db at rated output. Harmonic distortion less than 1%.—Electronic Instruments Co. (EICO), 84 Withers St., Brooklyn 11, N.Y.

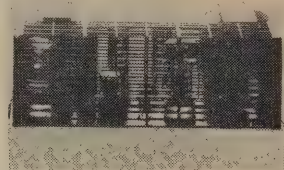HI-FI AMPLIFIER, Super Seventy. 70 watts, 20-20,000 cycles at full output \pm 0.1 db. 1M distortion less than 1% at rated




output.—Sargent-Raymont Co., 4926 E. 12 St., Oakland, Calif.

PHONO CARTRIDGE, Ceramic




V-8 line. Sapphire-tipped needles, 1 and 3 mil. Combination of 1-mil diamond and 3-mil sapphire. 30-15,000 cycles. Tracking pressure, 8-10 grams.—Webster Electric Co., 1900 Clark St., Racine, Wis.

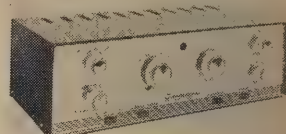HI-FI KITS, Little Genie, model 207AK (illustrated) preamp. LJ-6K, 10-watt amplifier; 250K, 50-watt basic amplifier.—Grommes, Div. of Precision Electronics



Inc., 9101 King St., Franklin Park, Ill.

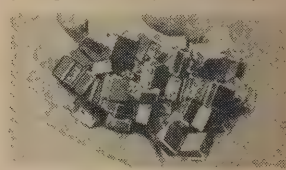MINIATURE MICROPHONE, MC30. 100 fit in palm of the hand. Controlled magnetic type. 400-4,200 cycles. Output is -72 db, impedance 2,000 ohms, both



measurements at 1,000 cycles.—Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill.

RIBBON VELOCITY MICROPHONE Ribbonette. 30-14,000 cycles. For tape recorders. Replaces crystal mike without need for input transformer. Microphone output is -54.



"CHRISTMAS BONUS" BOOK OFFER

SAVE 29%

on famous G/L Technicians' Books

NOW—right at the peak of the Christmas season, when most prices are up, we are making this astounding offer. G/L Service Technicians' books, regularly \$4.60—

ONLY \$3.28 each—a 29% CASH DISCOUNT!

These handsomely-bound books cover all the important phases of servicing.

OFFER GOOD UNTIL DECEMBER 31 ONLY

On January 1, 1958, these books go back to \$4.60. So act now—select the books you want at \$3.28 each and send in your order with your remittance today. This is the book buy of the year—don't miss it.

EXTRA SAVINGS ON QUANTITY ORDERS

Order 3 or more books and save an extra 10%! Build your own library—buy them as gifts for friends, but don't miss this offer it won't be repeated!

3 booksregularly	\$13.80
4 booksregularly	\$18.40
5 booksregularly	\$23.00
6 booksregularly	\$27.60
7 booksregularly	\$32.20
8 booksregularly	\$36.80

Special price
'til Dec. 31

\$ 8.86
11.81
14.76
17.71
20.66
23.62

- Cloth-Bound Editions
- Latest Titles
- First Quality Books
- Top Authors

CHOOSE FROM THESE BEST SELLERS

- **RAPID TV REPAIR**—By G. Warren Heath. Lists more than 500 TV troubles alphabetically. Shows you how to put your finger on the toughest trouble in minutes. Cross-referenced, indexed. Troubleshooting charts.
- **SERVICING COLOR TV**—By Robert G. Middleton. This popular engineer-writer answers all your questions on color TV—chroma circuits, matrix testing, the flyback system and other phases of this up-and-coming branch of servicing.
- **TV—IT'S A CINCH**—By E. Aisberg. An international sensation! Gives you all the answers on TV theory in an easy-to-understand dialogue style.
- **SERVICING RECORD CHANGERS**—By Harry Mileaf. Shows you how to make extra money in this growing branch of servicing.

The following books explain the function, construction and use of modern test instruments and show you how to get more out of them in modern servicing:—

- **THE VTVM** by Rhys Samuel
- **SWEEP AND MARKER GENERATORS FOR TELEVISION AND RADIO** by Robert G. Middleton
- **PROBES** by Bruno Zucconi and Martin Clifford
- **THE OSCILLOSCOPE** by George Zwick

MONEY-BACK GUARANTEE

Because of the tremendous savings, we can not bill on this offer. But, YOU RISK NOTHING. If not completely satisfied return the books within 10 days FOR A FULL REFUND.

MAIL THIS COUPON TODAY

Gernsback Library, Inc., Dept. 127 T
154 West 14th St.
New York 11, N. Y.

My remittance of \$_____ is enclosed. Please send me postpaid the books checked below. If not satisfied I may return them within 10 days for a full refund.

- | | |
|--|--|
| <input type="checkbox"/> RAPID TV REPAIR | <input type="checkbox"/> THE VTVM |
| <input type="checkbox"/> SERVICING COLOR TV | <input type="checkbox"/> SWEEP AND MARKER GENERATORS |
| <input type="checkbox"/> TV—IT'S A CINCH | <input type="checkbox"/> PROBES |
| <input type="checkbox"/> SERVICING RECORD CHANGERS | <input type="checkbox"/> THE OSCILLOSCOPE |


Name _____ (please print)

Street _____ City _____ Zone _____ State _____



db.—Fentone Corp., 106 Fifth Ave., New York, N.Y.

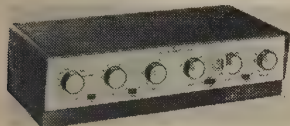STEREO—MONAURAL PRE-AMP, Knight KN-700. For use with stereo or monaural hi-fi system. Two equalized tape head playback preamps. Inputs for G-E and Pickering magnetic




cartridges, ceramic cartridges, microphone, tuner, tape preamp or crystal cartridge and two auxiliary sources.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

RECORD PLAYERS, portable hi-fi units. *Model CVS-12* (illustrated) permits continuous speed




variations from 25-100 rpm. *Model L-34* plays at 33 1/3 and 45 rpm. Both use the A-120 arm.—REK-O-KUT Inc., 38-19 108th St., Corona 68, L.I., N.Y.

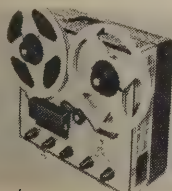TAPE RECORDER, Concertone Globomatic 60. Pushbutton controls. Half-track, full-track or stereophonic record and play-




back. Takes up to 10 1/2-inch reels. Plays at 7 1/2 and 15 inches per second.—American Electronics Inc., 655 W. Washington Blvd., Los Angeles 15, Calif.

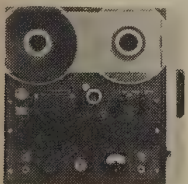TAPE RECORDER, model 90, 40-15,000 cycles. Wow and flutter



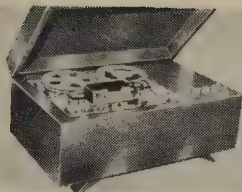
0.18%. Hysteresis synchronous motor.—Roberts Electronics, Inc., 1028 N. La Brea Ave., Los Angeles 38, Calif.

STEREO TAPE RECORDER, Tancordex. 3 motors for drive, fast forward and rewind. 3 shielded heads for record playback and erase. 40-15,000 cycles (down 4 db at 15,000). Wow and flutter less than 0.17%. In-line heads. Self-contained binaural playback preamps.—La-




fayette Radio, 165-08 Jamaica Ave., Jamaica 33, N.Y.

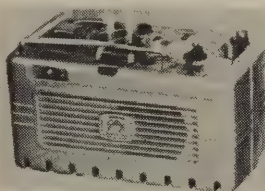PORTABLE TAPE RECORDER, model G-255/S. Made in Italy.



3 3/4 or 1 1/2 ips. Dual track. Push-button recording. 7 1/2 pounds.—American Gelo Electronics, Inc., 312 Seventh Ave., New York, N.Y.

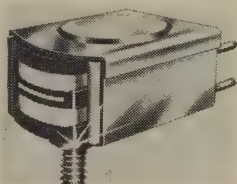STEREO TAPE HEAD. Recording and playback. Interchannel magnetic shield provides cross-talk rejection. Can be compensated to provide essentially flat response from 30-10,000 cycles.




—Nortronics Co., 1015 S. 6 St., Minneapolis 4, Minn.

NEW TAPE REEL. Molded with




extra-heavy flanges which give a balanced flywheel-like action, minimizing wow. Molded of opaque warp-proof plastic.—St. Cecilia Co. Ltd., Westwood, N.J.

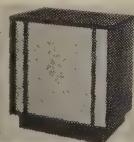SPEAKER SYSTEM, model S-121, 5 speakers, 4 channels,




12-inch woofer, 8-inch lower mid-range, 6-inch upper mid-range and two 3-inch tweeters. Semi-infinite baffle enclosure, treble balance control. Input impedance 8 ohms, power (max.) 25 watts. 35-20,000 cycles.—Pilot Radio Corp., 37-06 36th St., Long Island City 1, N.Y.

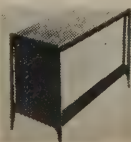SPEAKER—AMPLIFIER SYSTEM, Integrand. Integrated system of speakers and transistor



YOU CAN BUILD A TOROID TRANSISTOR POWER SUPPLY*

(D.C. to D.C. Converter)

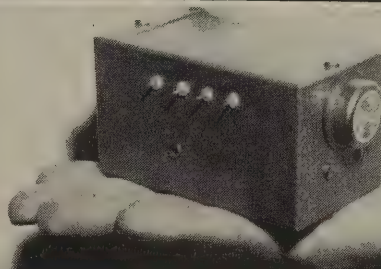

*using this
TOROID TRANSFORMER

\$16.00*

*Plus 50c for packing and mailing
Quantity prices on request

Delivers 225 to 450 volts D.C. simultaneously. Available in 12 or 24 volts. Maximum power 90 watts (transmitter intermittent service). 40 watts continuous.

AND
TRANSISTORS

2 Recommended Types—Both for

\$11.00

MORE EFFICIENT!
(80-90%)

LESS WEIGHT!
(1/10 weight of equivalent Dynamotor Power Supply)

LESS SPACE!
(90-watt output from 2" X 2" X 4" unit)

LOW HEAT GENERATION!

GREATER RELIABILITY!

- ✓ Designed especially for mobile and portable equipment.
- ✓ Each transformer tested in actual power supply unit and FULLY GUARANTEED!
- ✓ Complete construction details furnished.
- ✓ Special TOROID units and components to specifications on request.
- ✓ Manufactured by makers of world-famous SUNAir Aircraft Transceivers.

SUNAIR ELECTRONICS, INC.

Dept. 03
Broward International Airport
Fort Lauderdale, Florida

I am enclosing ☐ check ☐ money order in the amount of \$16.50 for a TOROID TRANSFORMER, or in the amount of \$27.50 for a Toroid Transformer and two matching power Transistors. ☐ 12 volts ☐ 24 volts

Name

Address

City.....Zone.....State.....



A low-cost high-use gift

FOR
HOBBYISTS
HAMS AND
EXPERIMENTERS
HI-FI
ENTHUSIASTS



MODEL 8100K

only
\$7.95
list

Weller SOLDERING KIT

featuring the famous **WELLER** Soldering Gun

Here's a gift that'll bring a hearty "thanks" from any man who receives it this Christmas. For the Weller Soldering Kit means quick, easy, expert soldering... even for the amateur. The Weller Soldering Gun heats instantly, has fingertip "on-off" control and dual spotlights. Over 100 watts, it's UL approved and guaranteed for 1 year. Gift packaged kit also includes cleaning brush, soldering tool and solder.

Professional, Heavy-Duty Weller
Soldering Guns up to 275 Watts **\$13.50**
list and up

Weller Heavy-Duty Soldering Kit **\$14.95**
in Sturdy Metal Storage Case list

Order for Christmas from your electronic parts distributor

WELLER ELECTRIC CORPORATION
601 Stone's Crossing Road, Easton, Pa.

NEW DEVICES (Continued)


amplifiers for hi-fi sound reproduction. 15-inch woofer and mid-range ring radiators. Stereo and monaural models.—**Brand Products Inc.**, Westbury, N.Y.

TONE ARM model 212, Micro-




Balanced. Viscous-damped vertical and horizontal pivots.—**Gray Manufacturing Co.**, Arbor St., Hartford, Conn.

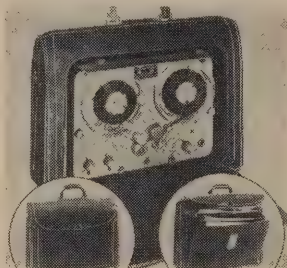SECRET RECORDER, battery-operated. Fits in briefcase, weighs 11 3/4 lbs. 5 mercury bat-



teries power motor. Single-speed (1 1/2 ips) and 2-speed (1 1/8 and 3 3/4 ips) available. One 5-inch reel holds 3 hours' dual track recording.—**Amplifier Corporation of America**, 398 Broadway, New York 13, N.Y.

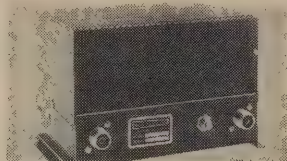RF AMPLIFIERS, for TV signal distribution in apartment houses, hotels, motels, housing



developments, etc. **Model ABB-8** (illustrated) covers channels 2-6; **ABB-4** channels 2-13.—**Westbury Electronics Inc.**, 300 Shames Dr., Westbury, N.Y.

WIDE-BAND RF AMPLIFIER, **Golden Cascader**. Bandwidth: 35 mc, from 53.5-88.5 mc. Gain: 30 db minimum. Noise figure: less than 9 db. Incorporates line bridging. For closed-circuit TV or community antenna systems.—**Jerrold Electronics Corp.**, 23d and Chestnut Sts. Philadelphia 3, Pa.

BRIDGE KIT, resistance-capacitance-ratio, **model C-20**. Resistance ranges from 0.5 ohms-200 megohms; capacitance from



10 µf-2,000 µf; ratio compared with an external standard from .05-20.—**Paco Electronics Co. Inc.**, 70-31 84th St., Glendale 27, N.Y.

FUSE KIT, contains 60 fuses covering most popular fuse replacements for electronic technicians. In pocket-sized case.—




Sightmaster Corp., 85 Beechwood Ave., New Rochelle, N.Y.

MULTIMETER, **model 120-M**. 44 ranges. Sensitivity 20,000 ohms per volt dc and 5,000 ohms per volt ac. 44 ranges including ac




and dc volts, ohms and milli-amperes. 5 1/4-inch meter.—**Precision Apparatus Co. Inc.**, 70-31 84th St., Glendale 27, N.Y.

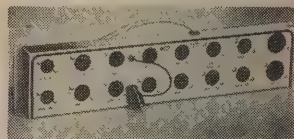SOCKET PANEL, **model 510**. Extends the use of the **B & K model 500** tube tester. Adds 50% more sockets to quick-check many more old and new tube




types.—**B & K Manufacturing Co.**, 3726 N. Southport Ave., Chicago 13, Ill.

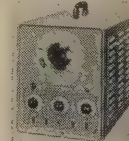COLOR BAR GENERATOR, **model 430**. All standard outputs plus G-Y at 90°. Single master control to select outputs. Control positions identified by




color picture of pattern which should appear on screen of properly adjusted receiver.—**Simpson Electric Co.**, 5200 W. Kinzie St., Chicago 44, Ill.

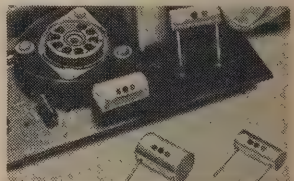MOLDED RF CHOKES. Radial leads, color coded, 0.47-10,000 µh. Encapsulated in alkyd plas-



tic.—**Delevan Electronics**, Roycroft Campus, East Aurora, N.Y.

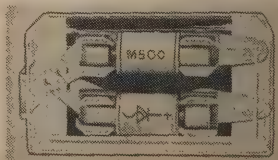RECTIFIER REPLACEMENTS. **M-500 conversion kit**. Silicon rectifiers replace existing selenium units. Delivers more B plus.



—**Sarkes Tarzian Inc.**, 415 N. College Ave., Bloomington, Ind.

RADIO-ELECTRONICS

NEW FROM PYRAMID

DRY ELECTROLYTIC CAPACITOR FOR EXTREME TEMPERATURE RANGE REQUIREMENTS TYPE TR


For applications previously reserved for Tantalum capacitors, Pyramid announces a new high reliability, dry electrolytic to be designated as Type TR. These are extended life capacitors using high purity aluminum foil, and can be supplied for any capacity requirements desired. Units are available in both polarized and non-polarized construction.

4 OPERATING TEMPERATURE RANGES: Type 20-85 TR -20°C to $+85^{\circ}\text{C}$. Type 20-100 TR -20°C to $+100^{\circ}\text{C}$.
Type 40 TR -40°C to $+85^{\circ}\text{C}$. Type 55 TR -55°C to $+85^{\circ}\text{C}$.

CAPACITANCE TOLERANCES: Pyramid type TR units are made with commercial capacitance tolerances.

POWER FACTOR: TR units rated less than 15 working volts have a maximum power factor of 25% at 25°C and 120 cps. Type TR units rated 15 working volts and over have a maximum power factor of 15% at 25°C and 120 cps.

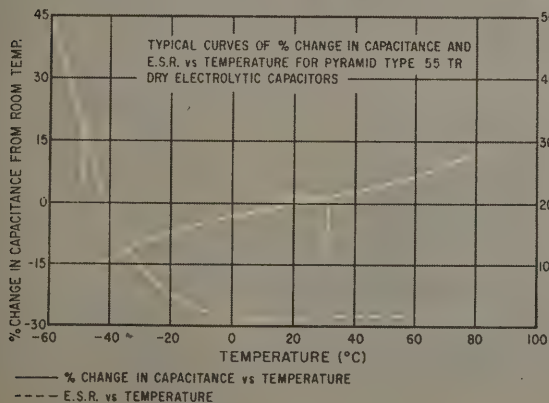D.C. LEAKAGE: Leakage current limits for Pyramid type TR capacitors measured after the working voltage has been applied for 5 minutes may be determined from the following formulas: At 25°C ; $I = 0.04CV$, At 85°C ; $I = 0.35CV$, At 100°C ; $I = 0.63CV$. Where: I = leakage current in microamperes, C = capacitance in microfarads, V = rated working voltage.



WORKING VOLTAGE: Pyramid type 20-85 TR can be supplied up to 450 working volts. Pyramid types 20-100 TR, 40 TR and 55 TR can be supplied up to 150 working volts.

SURGE VOLTAGE: The surge voltage rating of Pyramid type TR capacitors at 85°C and 100°C is 115% of the rated working voltage.

LIFE TEST: After 1000 hours at 85°C or 100°C , and working voltage applied, Pyramid type TR capacitors meet the following specifications at 25°C and 120 cps. The capacitance is within $\pm 40\%$ of the capacitance measured before life test. The power factor is less than 150% of the power factor measured before the life test. The leakage current is within the limits specified above.

For circuit application information and a copy of TR Engineering Bulletin write to Industrial Division:

PYRAMID
FILTRIC COMPANY
1445 HUDSON BOULEVARD
NORTH BERGEN, NEW JERSEY

Build 16 Radio

CIRCUITS at Home with NEW DELUXE 1958 PROGRESSIVE RADIO "EDU-KIT"

\$22.95
Now
Reg. U.S.
Pat. Off.



A Practical Home Radio Course

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

Now Includes

- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

FREE SET OF TOOLS, PLIERS—CUTTERS, TESTER, SOLDERING IRON, ALIGNMENT TOOL

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. You will receive a basic education in radio, worth many times the small price you pay, only \$22.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of

Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions and parts are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing."

Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn. You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our kit contains tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book.

TROUBLE-SHOOTING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have. J. Statalis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a course but I found your ad and sent for your kit."

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER
- ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK
- FCC AMATEUR LICENSE TRAINING • RADIO BOOK
- PRINTED CIRCUITRY

—90 DAY UNCONDITIONAL MONEY-BACK GUARANTEE—

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00

- ☐ Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
- ☐ Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- ☐ Send me FREE additional information describing "Edu-Kit." Include FREE valuable Radio and TV Servicing Literature. No obligation.

Name.....

Address.....

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave.,
Room 135G, Brooklyn 11, N.Y.

NEW DEVICES (Continued)

REPLACEMENT UNITS. TV power transformers, P-2813 replaces G-E RTP-326; P-2819, Admiral 80C35-1,7; P-2869, Philco 32-8673 vertical output transformer A-2816, G-E RTO-064.—Merit Coil & Transformer Corp., 4427 N. Clark St., Chicago 40, Ill.

VIBRATORS, Highlander. Replacement units. Packaged in 10-



pack cartons.—P. R. Mallory & Co. Inc., 34 S. Gray St., Indianapolis, Ind.

BATTERY-ELIMINATOR FILTER, model BE-4, provides additional filtering of output of 6- or 12-volt battery eliminators



for use with transistor equipment, 5 amps maximum current output.—Heath Co., 305 Territorial Ave., Benton Harbor, Mich.

LOCTITE, for securing nuts to bolts. Prevents loosening.



Locked nuts can be removed with ordinary tools, retreated and reused.—American Sealants Co., 103 Woodbine Ave., Hartford 6, Conn.

MAST GRIPPERS. Lightweight clamps for antenna installa-



tions. Pair converts 1 1/4-inch tubing into slidable trombone mast. Weather-resistant, cast aluminum alloy.—Helix Rotor Co., Marlin, Tex.

SCREW-HOLDING DRIVER. Small twin bits expand and hold the screw when tool is inserted




into screw-head slot. Aids in reaching hard-to-get-at spots. Variety of lengths and sizes.—H. J. J. Co., 268 Marlow Dr., Oakland, Calif.

SOLDERING AIDS, miniaturized. Two types. Specially de-


signed for printed-circuit applications.—Available from CBS tube distributors.

SOLDERING GUN, model 100.

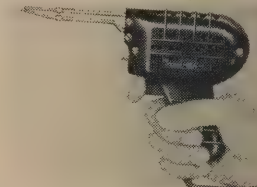

Heats in 2.5 seconds. Rated at 100 watts. Replaceable tips.—Wen Products Inc., 5806 North-west Highway, Chicago 31, Ill.

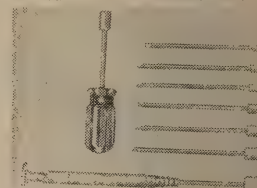SOCKET WRENCHES, subminiature. 1 1/2 inches long. 7 sizes: 5/64, 3/32, 7/64, 1/8, 5/32, 3/16 and 1/4 inch.—Desco Manufac-



turing Co., 551 W. Glenoaks Blvd., Glendale 2, Calif.

WIRE STRIPPER, Strip-It. Adjusts to strip size 10-20 single or stranded wire. Will also snip




wire.—Hunter Tool Co., Box 584, Whittier, Calif.

AM-FM STEREO TUNER, model 330. FM section includes a 150-kc bandpass, 2-mc detector, steep if response, 80-db rejection of spurious cross



modulation and automatic gain control. FM sensitivity, 2 μ v for 20 db of quieting. AM section has 1 μ v sensitivity, 3-position adjustable if bandwidth and 10-kc whistle filter.—H. H. Scott Inc., Dept. P. Powdermill Rd., Maynard, Mass.

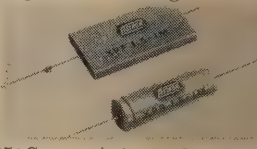MYLAR CAPACITORS, type XPR (round) and XPF (flat). Voltage rating: 150 volts at 85°C and 100 volts at 125°C. Temperature range: -55°C-



125°C.—Astron Corporation, 255 Grant Ave., E. Newark, N. J.

END


All specifications given are from manufacturers' data.

FREE CHRISTMAS GIFTS on all sales of \$5 or over.
RADIOS — TOOLS — PENS — ETC. (depending on size of order)

Excitingly new! DX-16 Super Deluxe TV KIT

70° or 90° — operating all 21", 24" and 27" PICTURE TUBES

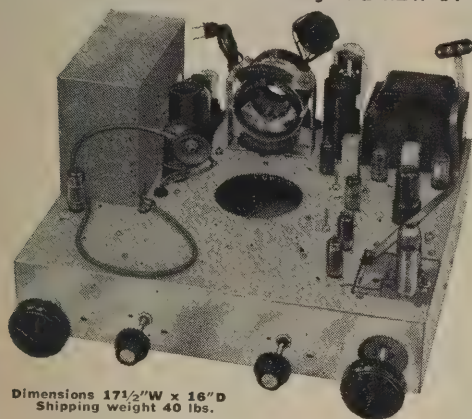The DX-16 SUPER DELUXE TV KIT is a worthy successor to the famous #630 TV KIT... a product in which we took a leading role. In designing and engineering this NEW KIT, we used the #630 as a standard of comparison for POWER, STABILITY and FRINGE AREA RECEPTION... resulting in a NEW TV CHASSIS equal in performance and with even greater versatility.



Dimensions 17 1/2" W x 16" D
Shipping weight 40 lbs.

NEW IN DESIGN — Mounts Horizontally, Vertically or Sideways.

- ★ Produces a Superior 16-Tube Chassis with 30-Tube performance.
- ★ Latest advanced Inter-carrier Circuitry and Multi-section Tubes.
- ★ Standard Cascode Tuner for Selectivity and Fine Definition.
- ★ 5 Microvolts Video Sensitivity (20 volts peak to peak at CRT grid).
- ★ Fast Action AGC for Drift Free, Steady and Clear Pictures.
- ★ 3 Hi-gain Video I.F. Stages for excellent Contrast and Details.
- ★ AGC Level and Area Control, for adjusting reception to signal area.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Horizontal Sweep Circuit is the famous RCA Synchroguide Network.
- ★ Large 250 ma Power Transformer—not a hot chassis.
- ★ Large 12" Concert-tone Speaker.

ALL COMPLETE with LIFE-SIZE step-by-step Building Instructions (less tubes & CRT) .. **\$69.97**

ALL COMPLETE with SET of WESTINGHOUSE TUBES (less CRT) **\$79.97**

ALL COMPLETE with SET of WESTINGHOUSE TUBES and WESTINGHOUSE 21" 70° or 90° Aluminized CRT... **\$99.97**

WESTINGHOUSE OR CBS PICTURE TUBES

BRAND NEW in Factory Sealed Cartons—With a Full Year Guarantee

17" 70° #17BP4A \$22.66 90° #17AVP4A Aluminized	21" 70° #21YP4A Aluminized \$32.21 90° #21ALP4A Aluminized	24" 90° #24CP4A Aluminized \$48.99	27" 90° #27EP4A Aluminized \$74.31
--	--	---	---

"ONE DOLLAR"

buys as much as \$15 worth


Deduct 10% ON ANY ORDER of \$10 or over (on items listed below)

100 - ASSORTED FUSES popular sizes \$1
100 - ASSORTED 1/2 WATT RESISTORS \$1
70 - ASSORTED 1 WATT RESISTORS \$1
35 - ASSORTED 2 WATT RESISTORS \$1
10 - 6' ELECTRIC LINE CORDS with plugs \$1
5 - TV CHEATER CORDS with both plugs \$1
4 - 50' SPOOLS HOOK-UP WIRE 4 colors \$1
100 - TWIN LEAD-IN WIRE 300Ω heavy duty \$1
50' - FLAT 4-CONDUCT. WIRE, many purposes \$1
1 - \$7 INDOOR TV ANTENNA hi-gain 3 section \$1
20 - ASST. TV KNOBS, ESCUTCHEONS, Etc. \$1
15 - ASSORTED ROTARY SWITCHES \$15 worth \$1
100 - FINEST NYLON DIAL CORD best size \$1
200 - SELF TAPPING SCREWS #8 x 1/2" \$1
50 - ASST. TUBULAR CONDENSERS \$1
5 - ELECTROLYTIC COND. 100/50 - 50/25v \$1
35 - ASST. RADIO KNOBS screw and push-on \$1
100 - KNOB SPRINGS standard size 3/4" x 1/2" \$1
100 - ASSORTED KNOB SET-SCREWS \$1
25 - ASSORTED CLOCK RADIO KNOBS \$1
400 - ASST. H'DWARE, screws, nuts, rivets, etc. \$1
50 - ASST. SOCKETS octal, noval and miniature \$1
50 - ASST. MICA CONDENSERS some in 5% \$1
50 - ASST. CERAMIC CONDENSERS \$1
10 - ASST. VOLUME CONTROLS less switch \$1
5 - ASST. VOLUME CONTROLS with switch \$1
20 - ASST. PILOT LIGHTS popular types \$1
10 - PILOT LIGHT SKTS. bayonet type, wired \$1
50 - ASST. TERMINAL STRIPS 1, 2, 3, 4 lug \$1
10 - ASST. RADIO ELECTRO. CONDENSERS \$1
5 - ASST. TV ELECTROLYTIC CONDENSERS \$1
15 - ASST. TV COILS vnc, penking, width, etc. \$1
25 - ASST. MICA TRIMMER CONDENSERS \$1
50 - TUBULAR CONDENSERS .02-.400v \$1
50 - TUBULAR CONDENSERS .001-.600v \$1
20 - TUBULAR CONDENSERS .047-.600v \$1
50 - TUBULAR CONDENSERS .01-.400v \$1
3 - ELECTROLYTIC COND. 40/40-450v \$1
3 - ELECTROLYTIC COND. 80-450v \$1
3 - ELECTROLYTIC COND. 50/30 - 150v \$1
3 - ELECTROLYTIC COND. 40/10/10 - 450v \$1
3 - ELECTROLYTIC COND. 50/25/10-150v \$1
10 - HV TUBULAR CONDENSERS .03-2000v \$1
10 - HV TUBULAR CONDENSERS .005-6000v \$1

35 - MICA COND. 20 - 100 mmf & 15 - 250 mmf \$1
35 - MICA COND. 20 - 470 mmf & 15 - 1000 mmf \$1
35 - MICA COND. 20 - 680 mmf & 15 - 10K mmf \$1
35 - CERAMIC COND. 20-25 mmf. & 15-47 mmf. \$1
35 - CERAMIC COND. 20-68 mmf & 15-1500 mmf. \$1
35 - CERAMIC COND. 20-250 mmf and 15-680 mmf \$1
50 - 100Ω 1/2 WATT RESISTORS 5% \$1
75 - 680Ω 1/2 WATT RESISTORS 10% \$1
75 - 470KΩ 1/2 WATT RESISTORS 10% \$1
50 - 3.3Ω 1 WATT RESISTORS 10% \$1
50 - 15KΩ 1 WATT RESISTORS 10% \$1
50 - 470KΩ 1 WATT RESISTORS 10% \$1
25 - 2.2Ω 2 WATT RESISTORS 5% \$1
25 - 3.3Ω 2 WATT RESISTORS 5% \$1
25 - 100KΩ 2 WATT RESISTORS 10% \$1
10 - ASST. WIREWOUND RES. 5, 10, 20 watts \$1
3 - AUDIO OUTPUT TRANSFORMERS 50L6 type \$1
3 - AUDIO OUTPUT TRANS. 6K6 or 6V6 type \$1
3 - I.F. COIL TRANSFORMERS 456kc \$1
3 - I.F. COIL TRANSFORMERS 10.7 mc FM \$1
4 - OVAL LOOP ANTENNAS ass't. hi-gain types \$1
3 - LOOPSTICK ANT. new ferrite, adjustable \$1
12 - RADIO OSCILLATOR COILS 456kc \$1
3 - 1/2 MEG VOLUME CONTROLS with switch \$1
1 - 5" PM SPEAKER alnico #5 magnet \$1
5 - SETS SPEAKER PLUGS, wired \$1
10 - SETS PHONO PLUGS and PIN JACKS \$1
2 - \$2.50 SAPPHIRE NEEDLES 4000 playings \$1
5 - DIODE CRYSTALS 2-IN21 2-IN23 1-IN64 \$1
1 - TV VERT. OUTPUT TRANS. 10 to 1 ratio \$1
5 - TV CRT. SOCKETS with 18" leads \$1
5 - HI-VOLT. ANODE LEADS with 18" leads \$1
1 - TV SYNCHROGUIDE TRANSFORMER #208TB \$1
1 - TV SYNCHROLOC TRANSFORMER #208TB \$1
1 - TV RATIO DETECTOR TRANS. 4.5mc \$1
1 - SET TV KNOBS standard type incl. decals \$1
1 - LB SPOOL ROSIN CORE SOLDER 40/60 \$1
6 - SPIN TIGHT SOCKET SET 3/16" to 7/16" \$1
3 - TV ALIGNMENT TOOLS 5", 7", 12" \$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted, enclose with money order or check. You will receive a new copy of this ad for re-orders.

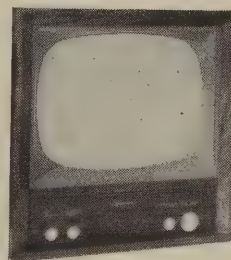ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.



BUILD YOUR TV CABINET

Comparable to the type that Top Mfrs. use on their finest TV Sets.

You receive—The FRONT PANEL ASSEMBLY complete as pictured in genuine Mahogany, Walnut or Blond Korina in a beautiful hand-rubbed finish with MASK, SAFETY GLASS, DECALS and undrilled KNOB PANEL.

You also receive—the TOP & SIDES finished in matching color, the perforated BACK with CRT CUP, GLUE, SCREWS, BRADS and amazing Easy-To-Follow Instructions. 90% of the job is done for you... All you add are the BOTTOM & simple 1" connecting STRIPS.

21" CABINET... H-26" W-25" D-22" ... **\$24.95**

EICO... World's Largest Selling KITS & Instruments

See EICO ad pages 29-30

HF12 HI-FI AMPLIFIER 12-watt (kit) \$ 34.95
HF12 HI-FI AMPLIFIER 12-watt (wired) 57.95
HF50 HI-FI AMPLIFIER 50-watt (kit) 57.95
HF50 HI-FI AMPLIFIER 50-watt (wired) 87.95
HF52 2-WAY AMPLIFIER 50-watt (kit) 69.95
HF52 HI-FI AMPLIFIER 50-watt (wired) 109.95
HF61A HI-FI PREAMPLIFIER (kit) 24.95
HF61A HI-FI PREAMPLIFIER (wired) 37.95
HF61 HI-FI PREAMP. w/power supply (kit) 29.95
HF61 HI-FI PREAMP. w/power supply (wired) 44.95
HF60 HI-FI AMPLIFIER 60-watt (kit) 72.95
HF60 HI-FI AMPLIFIER 60-watt (wired) 99.95
HF20 HI-FI AMPLIFIER 20-watt (kit) 49.95
HF20 HI-FI AMPLIFIER 20-watt (wired) 79.95
HFS1 2-WAY HI-FI SPEAKER SYSTEM 39.95
666 TUBE & TRANSISTOR TESTER (kit) 69.95
666 TUBE & TRANSISTOR TESTER (wired) 109.95
368 TV-FM SWEEP GEN. & MARKER (kit) 69.95
368 TV-FM SWEEP GEN. & MARKER (wired) 119.95
460 COLOR & MONO. 5" SCOPE (kit) 79.95
460 COLOR & MONO. 5" SCOPE (wired) 129.95
324 RF SIGNAL GENERATOR (kit) 26.95
324 RF SIGNAL GENERATOR (wired) 39.95
232 PEAK to PEAK VTVM w/probe (kit) 29.95
232 PEAK to PEAK VTVM w/probe (wired) 49.95


EICO CATALOG mailed on request

BROOKS RADIO & TV CORP., 84 Vesey St., New York 7, N.Y.

TELEPHONE
Cortland 7-2359

SAMS "BEST SELLER" BOOKS

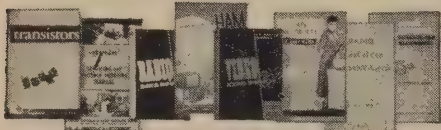FOR THE TECHNICIAN • STUDENT
EXPERIMENTER • HOBBYIST



USE THIS HANDY ORDER FORM

- ☐ **Pinpoint TV Troubles in 10 Minutes.** Amazingly practical procedures for solving TV troubles. Includes over 50 time-saving check charts, dozens of diagrams and test Methods, circuit explanations, etc.—a real timesaver for TV repairs. 299 pages; 5½ x 8½"; fully illustrated. Only.....\$3.95
- ☐ **TV Servicing Guide.** Quick reference guide for Technicians. Trouble symptoms are illustrated by picture tube screen photos and proper repair procedures are clearly described. Covers all sections of the TV circuit. 132 pages; 8½ x 11"; illust. Only.....\$2.00
- ☐ **Tape Recorders.** Explains recorder theory, tape characteristics, how recorders work; covers motorboard mechanisms, drive motors, volume indicators, bias oscillators, amplifiers, magnetic heads, equalization circuits. 176 pages; 5½ x 8½"; illust. Only.....\$2.75
- ☐ **Transistor Circuit Handbook.** The authoritative book on transistor types, construction, characteristics, applications, circuitry, techniques for wiring and testing. Covers every phase of the subject. 430 pages; 6 x 9"; illust. Only \$4.95
- ☐ **Hi-Fi Handbook.** Invaluable data on Hi-Fi design, selection and installation, including fidelity, sound theory, analysis of all components (speakers, enclosures, amplifiers, tuners, etc.), systems design, proper selection and installation. 240 pages; 5½ x 8½"; illust. Only.....\$3.00
- ☐ **Servicing AGC Systems.** Describes operation and circuit variations of AGC systems; explains applicable servicing techniques. Illustrated by actual case histories and photos of symptoms. 132 pages; 5½ x 8½"; illust. Only.....\$1.75
- ☐ **Learning Electricity Fundamentals.** The complete, fascinating story of electricity: history, electron theory, static electricity, uses of switches and fuses, resistance, Ohm's Law, magnetism, electro-magnetism, transformers, generators and motors, circuits and controls, practical wiring, etc. 416 pages; 6 x 9"; illust. Only.....\$5.95
- ☐ **Transistors.** A very practical, complete book on Transistors and their application in TV-Radio-Electronics. Explains theory, circuitry, installation, testing techniques and servicing. 100 pages; 5½ x 8½"; illust. Only.....\$1.50
- ☐ **Color Television.** An outstanding training course for Technicians. Covers principles of the color TV system; color receiver circuits; installation and servicing of color receivers. Includes color blocks outlining use of color test equipment. 260 pages; 8½ x 11"; profusely illustrated. Only.....\$6.95
- ☐ **Electronic Metal Locators.** Explains basic types and their operation; tells how to construct your own units; describes applications. Covers interesting uses in industry as well as in prospecting and mine location. 124 pages; 5½ x 8½"; illust. Only.....\$2.50

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber, or mail to
Howard W. Sams & Co., Dept. 2-M7
2201 E. 46th St., Indianapolis 5, Ind.

Send books checked above. My (check) (money order)
for \$.....is enclosed.


Name.....

Address.....


City.....Zone.....State.....

(outside U.S.A. priced slightly higher)

Business and People

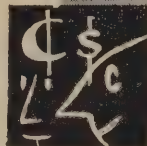

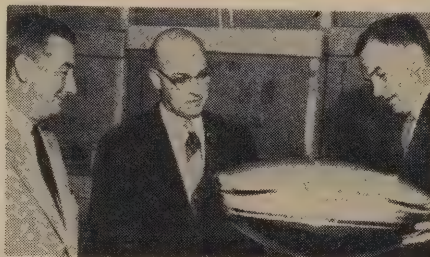Sylvania Electric Products, Seneca Falls, N. Y., recently produced its 15 millionth TV picture tube. Shown on hand for this production milestone are,



left to right, Donald W. Gunn, general manager of the Electronic Products Sales Department; Matthew D. Burns, vice president electronic tube operations, and W. Herbert Lamb, general manager of the Television Picture-Tube Division.

Pyramid Electric Co., North Bergen, N. J., held an engineering symposium on "Long Shelf Life of Capacitors in

GET INTO ONE OF THESE
TOP OPPORTUNITY FIELDS

ELECTRICITY — Electronics or TELEVISION — Radio-Color TV

TRAIN IN THE GREAT SHOPS OF

COYNE OLDEST, BEST EQUIPPED
SCHOOL OF ITS KIND IN U.S.

Veterans and Non-Veterans—Prepare for a better job NOW that offers a real future, too! Get practical training in TELEVISION—RADIO—ELECTRICITY—ELECTRONICS—(Refrigeration & Electric Appliance Repair can be included). Learn on real equipment—no advanced education or previous experience needed. Lifetime employment service to graduates.

Finance Plan—enroll now, pay most of tuition later. Part time employment help to students.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B.W. COOKE, JR., President **COYNE** FOUNDED 1895
ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED
NOT FOR PROFIT
500 S. PAULINA ST., CHICAGO, Dept. 97-81H
ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B.W. COOKE, JR., Pres., COYNE ELECTRICAL School
500 S. Paulina St., Chicago 12, Ill., Dept. 97-81H

Send FREE BOOK and details on:

- ☐ TELEVISION-RADIO
☐ ELECTRICITY-ELECTRONICS

NAME.....

ADDRESS.....

CITY.....STATE.....

Relationship to Low Temperature Characteristics" in Los Angeles. Karl Moeglich, Pyramid's director of re-



search and development, conducted the meeting and Jack Berman, California representative, acted as host. Thirty people from 14 different firms attended.

Cleveland Institute of Radio-Electronics, Cleveland, Ohio developed an Employers' Plan for training technical personnel while on the job. The plan helps employers relieve the two-way radio-microwave technician shortage without hiring new personnel. A booklet describing the service has been prepared by the school.

Weller Electric Corp., Easton, Pa.,



SENCORE Handy "36" R-C Substitution Unit



Most Often
Needed
Components
At YOUR
Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12-1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12-½ watt 10% resistors from 10K ohms to 5.6 megohms
- ★ 10-600 volt capacitors from 100-mfd. to .5mfd.
- ★ 1-10mfd., 450V Electrolytic
- ★ 1-40mfd., 450V Electrolytic

For Shop, Lab, or outside service
AVAILABLE AT ALL PARTS
DISTRIBUTORS!

SERVICE
INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.

ONLY
\$12.75
DEALER NET

POPULAR
SENCORE
PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

BUSINESS AND PEOPLE (Continued)

is offering electronic distributors a four-color three-dimensional sign featuring its soldering gun.

General Cement Manufacturing Co., Rockford, Ill., made a special price offer




on its grille cloth. In addition, a wire display rack is offered with 100 packages.

Vaco Products, Chicago, created a new display featuring its solderless



terminals. The display also has slots for exhibiting the Vaco crimping tool and for holding descriptive literature.

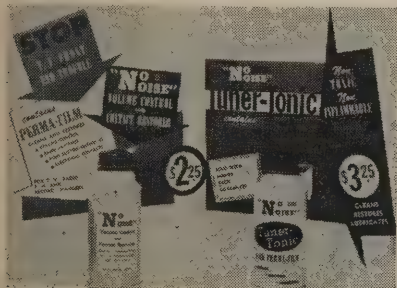Electronic Chemical Corp., Jersey City, N. J., is offering dealers two



two-color single can displays for its volume control and contact restorer, and Tuner-Tonic products.

George Gemberling, former general district manager of Alliance Manufacturing Co., Alliance, Ohio, has been promoted to sales manager of the Con-



NOTE: This offer good only until DEC. 25th in the U. S. (Foreign orders until JAN. 25th)

LEKTRON'S BIGGEST-EVER CHRISTMAS DOUBLE BONUS OFFER!

Our annual "Thank You" to our thousands of customers

FREE WITH EVERY \$10 ORDER

BONUS #1
Your choice of ANY \$1 KIT
FREE

BONUS #2
\$15 worth of RADIO PARTS
FREE

DOUBLE BONUS

Sixteen Dollars' worth of parts free with \$10 order

WORLD FAMOUS KIT KING DOLLARBUYS!

- ☐ **HOBBIY METER.** 2 1/4" rd. Bakelite panel meter, 0 to 32 VDC. Reg. \$6. **\$1**
- ☐ **60 TRANSFORMERS.** COILS. Reg. \$15. IF, RF, ant., slug-tuned coils, chokes. 25 types. Wt. 3 lbs. **\$1**
- ☐ **VEEDER-ROOT COUNTER.** 000-999. Ideal for all counting operations. Reg. \$4.99. **\$1**
- ☐ **3 LBS. HARDWARE.** Reg. \$8. Approx. 2000 pcs. Assd. screws, brackets, etc. **\$1**
- ☐ **2 TRANSISTOR TRANSFORMERS.** UTC "ounce-er" type. Reg. \$10. Inter-stage, 1x3/4x3/4". Imp. ratios unknown. Color-coded leads. **\$1**
- ☐ **EMERSON TUNER.** Hi-Q, permeability-tuned ANT & OSC coils w/padders on 2x4" plate; variable tuning mech. Reg. \$5. **\$1**
- ☐ **7 MERCURY SWITCHES.** for silent switching; glass sealed w/mercury. 115 V. Reg. \$6. **\$1**
- ☐ **WORLD'S SMALLEST RADIO KIT.** 2 1/2x1 3/4x 3/4" w/permeability tuner. Reg. \$3.50. **\$1**
- ☐ **175-FT. HOOKUP WIRE.** Reg. \$3.75. In 25-ft. rolls. Assd. colors, stranding, insulation. #18 to #24. Wt. 2 lbs. **\$1**
- ☐ **6 RAYTHEON GERMANIUM DIODES.** Type CK-705; like IN34, IN34A, IN48, IN51, IN69, IN66. Reg. 85c each. **\$1**
- ☐ **"Postagestamp" CRYSTAL MIKE.** 3/4" sq. Crisp, clear to \$,000 cps. **\$1**
- ☐ **2 SUB-MINI SOLENOIDS.** 1 x 5/8 x 3/8". Change elec. energy to mechanical. 12 VDC @ 300 ma actuates plunger. Wt. 2 oz. Reg. \$5. **\$1**
- ☐ **60 RESISTORS.** Insulated. Many 1% & 5%. 1/2 to 2 W; 10 ohms to 10 megs. 30 values. Wt. 1/2 lb. Reg. \$16. **\$1**
- ☐ **SUB-MINI P-N-P TRANSISTOR.** 1/4 pencil eraser size. Used in "name" portables. W/spec. sheets. \$5 value! **\$1**
- ☐ **10 3-SEC. TIMING MECHANISMS.** Reg. \$3 each. Multi-ganged for all kinds of gadgets. Wt. 2 lbs. **\$1**
- ☐ **4 MINIATURE RECTIFIERS.** 1/2-wave, selenium. Reg. \$1 each. **\$1**
- ☐ **60 TUBULAR CONDENSERS.** .0002 to .1 mf. to 2000 V. Oils incl. Wt. 2 lbs. Reg. \$12. **\$1**
- ☐ **60 PORCELAINIZED RESISTORS.** Carbofilm, precision-type. 15 values; 1/2 to 1 W. 50 ohms to 1 meg. Reg. \$12. **\$1**
- ☐ **30 TUBE SOCKETS.** Transistor, printed circuit, 4-14 probe; mini, standard types. Some mica filled. Wt. 1 lb. Reg. \$1. **\$1**
- ☐ **SIX DIODES.** Assd. sizes, crystal and silicon. Reg. \$15. **\$1**
- ☐ **8 TRANSISTOR SOCKETS.** Mica-filled. For sub-mini tubes, too. Reg. \$3. **\$1**
- ☐ **40 PRECISION RESISTORS.** Carbofilm, Wilkors. etc. 1/2 W. 50 ohms to 1 meg. Wt. 1/2 lb. Reg. \$18. **\$1**
- ☐ **40 MOLDED CONDENSERS.** Black Beauties, porcelain, etc. Reg. \$8. To .1 mf to 1000 V. Oils incl. Wt. 1 lb. **\$1**
- ☐ **75-PC. RESISTOR SPECIAL!** All types assd. to 10 ohms. Precision, 30 values. WORTH \$15. Wt. 1 lb. **\$1**
- ☐ **40 TRANSISTOR RESISTORS.** Only 1/4" long. 20 values; 15 ohms to 10 megs. Color-coded. Reg. \$6. **\$1**
- ☐ **8-PC. NUTDRIVER SET.** Plastic handle, 3/16, 7/32, 1/4, 5/16, 11/32, 3/4, 7/16" steel socket wrenches in plastic case. Wt. 1 lb. \$3 value. **\$1**
- ☐ **100 RADIO PARTS.** Surprise assortment. Reg. value over \$15. Wt. 3 lbs. **\$1**
- ☐ **4 OUTPUT TRANSFORMERS.** 50L6, 35L6, 6V6, 50B4 to 3-4 ohm v.c. Wt. 1 lb. Reg. \$6.50. **\$1**
- ☐ **30 PRINTED CIRCUIT PARTS.** Boards. Wide variety, exclusive! Reg. \$17. Wt. 1 lb. **\$1**
- ☐ **15-PC. TWIST DRILL SET.** 1/16 thru 1/4" x 64ths. In graduated plastic holders. Reg. \$4. **\$1**
- ☐ **60 TERMINAL STRIPS.** Posts. Wide variety solder lug, binding, etc. Wt. 1 lb. **\$1**
- ☐ **15 ROTARY SWITCHES.** Ceramic & bakelite; 2, 3-gangs. Std. shafts. Wt. 3 lbs. Reg. \$14. **\$1**
- ☐ **30 DISC CONDENSERS.** Transistor & printed circuit types. Reg. \$8. **\$1**
- ☐ **60 STANDARD KNOBS.** Bakelite & plastic in assorted colors. Set-screw types incl. Wt. 2 lbs. **\$1**
- ☐ **50 PLUGS & RECEPTACLES.** Audio, power, chassis, panel & spkr. types. Wt. 2 lbs. **\$1**
- ☐ **50 MICA CONDENSERS.** Silver, 5% incl. 30 values; .00001 to .01 mf. To 1000V. Wt. 1 lb. **\$1**
- ☐ **10 ELECTROLYTICS.** Assd. can, tubular types to 500 mf. Wt. 3 lbs. **\$1**
- ☐ **30 POWER RESISTORS.** WW, candohm, sand-coated, vitreous. 15 values; 5 to 50 W. 35 to 11000 ohms. Wt. 2 lbs. **\$1**
- ☐ **100 CERAMIC CONDENSERS.** Assd. types, color-coded. Discs, too. **\$1**
- ☐ **15 VOLUME CONTROLS.** Reg. \$10. Singles and duals to 1 meg. **\$1**
- ☐ **10 "POLY" BOXES.** Assd. sizes; clear plastic, hinged, w/snap locks. Reg. \$2.50. **\$1**
- ☐ **65-PC. CONDENSER SPECIAL!** All types assd.; molded, oil, ceramic, paper, mica, variable. discs. Reg. \$15. **\$1**
- ☐ **5 FERRI-LOOPSTICK CORES.** Hi-Q, assd. flat & tubular. 5 to 1/2" long. Wt. 1 1/2 lbs. **\$1**
- ☐ **125 RESISTORS.** 1/2, 1 W. 40 values; 5 ohms to 10 megs. 5%, too. **\$1**

SANTA CLAUS SPECIALS!



SUPER SOLAR BATTERY

REG. \$10. Generates greater energy than famed B2M! 2 1/2x1 3/4x 1/2" plug-in type, in handy case. **\$2.88**

TRANSISTOR PORTABLE RADIO KIT

No experience necessary! Famous make kit, with powerful HI-Q ferrite antenna, diode det., 2 transistor ampl. stages, 4" spkr. 7 1/2x5 1/2x2 1/4" styrene case. For broadcast band. Instructions, diagrams, pictorials, all parts. **\$12.94**

9V battery, 69c extra.

HEARING AID PHONES w/cord

Crystal 5,000 ohm \$1.39

Dynamic 5,000 ohm \$1.69

CROSSOVER NETWORK

Crossover freq. 2500 to 3500 kcs. For 8 and 16 ohm v.c. to match tweeter, below. Reg. \$14. **\$6.99**

HI-FI TWEETER

Metal cased, cone. Freq. response, 3,000 to 16,000 cps. Max. rating, 20 W. 2 7/8x2 1/2" w/flat surface mtg. bracket. Elsewhere, \$5.95 to \$12. **\$3.99**

TWO TWEETERS:

8 ohm, 16 ohm imp. **\$2.99**

3-TUBE AC-DC AMPLIFIER

Fully wired. Reg. \$5. Sep. vol. tone controls. Lowest price ever! **\$2.99**

TUBES, \$1.91 extra

"SLIM JIM" CRYSTAL MIKE

60 to 10,000 cps. Sleek, lightweight aluminum; 4 5/8x1 1/2" dia. ON-OFF sw. cable conn. Ship **\$4.88**

AMAZING "PILLOW" SPEAKER

"Silent-sound" by bone conduction to inner ear. 3/4 ohm v.c. 100% personal listening. Com. **\$2.88**

12" HI-FI SPEAKER

50 to 10,000 cps. Use w/tweeter v.c. only. **\$4.44**

POCKET MULTI-TESTER

3 1/2 x 2 x 1 1/2" bakelite case, 100 ohms/V. Zero adj. 0/15/150/1000 AC & DC V; 0/150 ma; 0/100,000 ohms. W/test leads in orig. pack. **\$6.99**

SCOOP! SOLDERING GUN

Lightweight, controlled heat for transistor & printed circuit **\$4.99**

REGENCY ALL-TRANSISTOR VEST POCKET RADIO

COMPLETELY WIRED READY TO PLAY.....ONLY **\$14.95**

Imagine! Cigarette-case-sized (3 x 2 x 1 1/2") radio fits your shirt pocket! Spectacularly engineered by famous Regency. Reflex circuitry with RF, DET., AMP. stages. Amazing sensitivity, selectivity and volume. No external antenna or hanging wires. W/super sensitive hearing aid phone. Broadcast band, 540 to 1500 kcs. 1000-hour batteries, GUARANTEED SATISFACTION!

FREE! GIANT 12-PAGE CHRISTMAS FLYER!

Check items wanted. Return entire ad w/check or MO, including sufficient postage; excess returned. C.O.D. orders, 25% down. Rated, net 30 days. Print name, address, amount money enclosed, in margin. (Canada postage: 45c 1st lb., 28c ea. addl. lb.)

EXPORT ORDERS INVITED!

LEKTRON

131 EVERETT AVE. CHELSEA 50, MASS.

PHOTOGRAPHS

RADIO-ELECTRONICS can use good photographs of service benches, service shops, high-fidelity audio layouts, and any other interesting and original radio-electronic devices. We will pay \$6.00 each for good professional photos or equivalent, suitable for reproduction. Full information on subject photographed will increase their acceptability.

The Editor, RADIO-ELECTRONICS
154 West 14th Street, New York 11, N.Y.



sumer Products Division. Ray Buhrman (right), advertising manager, was appointed assistant sales manager of the division as well as advertising manager.

H. F. Randolph continues as manager, receiving tube operations, of the RCA Electron Tube Division, Harrison, N.J., in a reassignment of the staff of






What's your line?

Hi Fi? TV? RADIO?

TRANSISTORS?

Whatever your interest is in electronics, you'll find a Gernsback Library book that caters to it. The books are authoritative of course, but written in a clean, crisp style that's easy to understand. And don't let the low prices fool you. Look over the titles. Note the authors—the best in the business. See the books at your distributor's. Prove to yourself that there are no better popular technical books at any price.

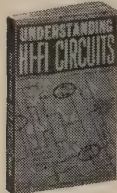

No. 64 Understanding Hi-Fi Circuits
Norman H. Crowhurst. A book that had to be written. Tells you how to choose the best circuit for your own tastes—and

HIGH FIDELITY
budget. Covers damping, feedback, matching and all the other points that may trouble you. 224 pages. Paper cover \$2.90. Deluxe hard cover \$5.

No. 58 Maintaining Hi-Fi Equipment
Joseph Marshall. Describes the specialized approach needed to service hi-fi equipment. Covers acoustic as well as electronic troubles. 224 pages. Paper cover

\$2.90. Deluxe hard cover \$5.

No. 56 High-Fidelity Circuit Design
Norman H. Crowhurst and George Fletcher Cooper. How to plan and build amplifiers on paper. Includes the famous Cooper series on feedback from RADIO-ELECTRONICS. 304 pages. Hard cover only. \$5.95.

No. 66 Basic Audio Course
Donald C. Hoefler. Cov-

ers everything from the nature of sound to recording techniques, including an explanation of hi-fi systems from preamp to speaker. 224 pages. Paper cover \$2.75. Hard cover \$5.

No. 48 High Fidelity—Design, Construction, Measurements.
Three-way approach to better hi-fi performance. 128 pages. Paper cover only. \$1.50.



No. 63 Transistor Circuits
Rufus P. Turner. Transistors for the practical man! One of the best known practical writers on the subject describes and tells you how to work with hundreds of transistorized circuits. Invaluable for the experimenter, hobbyist and do-it-yourselfer who wants to use transistors. 160 pages. Paper cover only. \$2.75.

No. 61 Transistor Techniques
A practical handbook for the man who wants to work with transistors. Keeps theory and math to a minimum and gives scores of hints on how to use transistors to best advantage in modern equipment. Covers testing, performance, construction, and measurements. 96 pages. Paper cover only. \$1.50.

No. 51 Transistors—Theory and Practice
Rufus P. Turner. This practical book on transistors is one of our all-time best sellers. Covers theory, characteristics, use in well-known circuits, characteristics of commercial transistors, etc. 144 pages. Paper cover only. \$2.00.

THEORY AND PRACTICE

No. 44 Basic Radio Course
John T. Frye. Teaches you more about fundamentals in an easy-going style than you can learn from many conventional textbooks. Covers everything from Ohm's law to circuit analysis including inductance, capacitance, resonant circuits, vacuum tubes, etc. 176 pages. Hard cover only \$2.25.

No. 45 Radio Tube Fundamentals
George Christ. Tubes from the technician's point-of-view! How and why they behave as they do in modern radio circuits. Complete coverage from basic theory to an analysis of different types. 96 pages. Paper cover only \$1.00.

No. 46 Television Technotes
Cuts trouble-shooting time. Gives the causes, symptoms and cures of over 600 specific TV troubles. Based on the experience of service technicians and manufacturers' service departments. 128 pages. Paper cover only \$1.50.

No. 47 Radio and TV Hints
Over 300 hints, kinks, gimmicks and short cuts to help you save time and energy in TV, radio, hi-fi, amateur, or experimental work. 112 pages. Paper cover only \$1.00.

No. 49 Radio and TV Test Instruments
Gives complete details on how to build 22 test instruments including picture tube

Christmas shopping got you stumped?
Why not give Gernsback books!

tester, VTVM, scope, signal generator, etc. 128 pages. Paper cover only. \$1.50.

No. 50 TV Repair Techniques
Top technician-writers give you the benefit of their experience in solving tough TV servicing problems. Covers signal tracing, servicing in the home, control troubles, etc. 128 pages. Paper cover only. \$1.50.

RADIO CONTROL

No. 53 Radio-Control Handbook
Howard G. McEntee. A practical handbook for controlling model planes, trains, and boats by radio. No theory—just detailed information on how to build and maintain complete systems as well as components. 192 pages. Paper cover only. \$2.25.

No. 43 Model Control by Radio
Edward L. Safford, Jr. An excellent companion book to Radio-Control Handbook. Covers theory and construction of components and complete systems. 112 pages. Paper cover only. \$1.00.

BUSINESS AND PEOPLE (Continued)



entertainment tube products. H. R. Seelen, manager, color kinescope operations, is now manager, kinescope operations. Right, M. J. Carroll former manager, cathode-ray and power-tube marketing, becomes manager, marketing.

Roy A. Juusola joined CBS-Hytron, Danvers, Mass., as manager, marketing administration. He has over 15 years experience in electronics and comes to the company from Sylvania, where he was a plant manager.



John Prutton joined the capacitor sales section of Centralab Division of Globe-Union, Milwaukee, Wis. He has wide experience in the industry and was formerly associated with the P. R. Mallory Co. and Westinghouse Corp.

Frank Hadrick joined the engineering staff of Simpson Electric Co., Chicago, as chief field engineer-test equipment. He comes to Simpson from Admiral Corp. where he had been chief television field engineer.



George I. Long, Jr., president of Ampex Corp., Redwood City, Calif., was elected to the board of directors of Orradio Industries, Opelika, Ala.

Obituary

Robert Lee Stephens, a pioneer in electronics and high fidelity, recently in Iowa City, Iowa, following surgery for a chronic hip ailment. He founded Stephens Tru-Sonic Co., Los Angeles. Although he sold his interest in 1956, he was a consultant to the firm. END

TV TINKERER

By Jeanne DeGood

He knows exactly what is wrong
And says repairmen take too long
And so he grabs a tool and starts
To pull out tubes and scatter parts.

It doesn't take him very long
To find exactly what is wrong—
It's really simple to explain
A screw is loose—up in his brain.



GERNSBACK LIBRARY, INC., 154 West 14th St., New York 11, N.Y.

- ☐ 43 ☐ 44 ☐ 45 ☐ 46
- ☐ 47 ☐ 48 ☐ 49 ☐ 50
- ☐ 51 ☐ 53 ☐ 56 ☐ 58
- ☐ 61 ☐ 63 ☐ 64 ☐ 66

These hard cover editions by mail only

- ☐ 58H ☐ 64H ☐ 66H

See your distributor—or use this coupon.

Enclosed is my remittance of \$.....

Please send me the books checked, postpaid.

Prices 10% higher in Canada

Name please print

Street

City Zone State

127

technical Literature



Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

ELECTRONIC PARTS, Catalog No. 68. A grouping of many types of electronic parts with brief descriptions and illustrations fill its 156 pages.—Newark Electric Co., 223 W. Madison St., Chicago 6, Ill.

ELECTRONIC COMPONENTS, General Catalog 305. Complete listing of electronic components from resistors to elaborate high-fidelity units. Among the 180 illustrated pages are sections on transistors and subminiature components, stereophonic equipment, amateur items and tools.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

TV TUNERS, Catalog 201. Pocket-sized, 28-page booklet contains the latest listing of this manufacturer's tuners and shows exploded views of each type. A replacement guide covering TV sets made between 1948 and 1957 is also available.—Standard Coil Products Co. Inc., 2085 Hawthorne Ave., Melrose Park, Ill.

COIL AND TRANSFORMER CATALOG, 1957. Filters, high-Q coils, toroids variable inductors and power, pulse, audio and miniature transformers are described and illustrated in this 34-page booklet.—United Transformer Corp., 150 Varick St., New York 13, N. Y.


TUBE TESTER, model 107Q is described and illustrated in a colorful folder. Operating instructions, circuitry and other important features of the tester are presented.—Seco Manufacturing Co., 5015 Penn Ave. South, Minneapolis 19, Minn.

ELECTRICAL CATALOG of 78 pages lists over 1,500 electrical wiring devices, lamps and specialty products.—Eagle Electric Manufacturing Co., Inc., 23-10 Bridge Plaza South, Long Island City 1, N. Y.

MAGNETIC FILMS and Magna-Strips are described in a full color brochure.—Reeves Soundcraft Corp., 10 E. 52 St., New York 22, N. Y.

INDUSTRIAL TUBES provides source material on the general characteristics of power tubes, beam-power tubes, thyatrons and other industrial types. Also lists maximum ratings of these tubes.

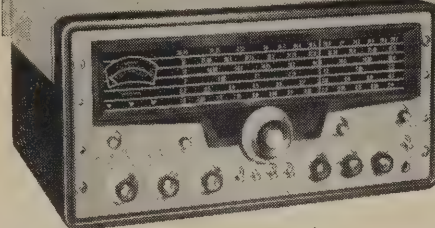In Stock . . . at "the place to buy"
hallicrafters
Only \$31⁴¹
PER MO. JUST 10% DOWN
NET PRICE: \$395.00



Top flight receiver in the field; seven ham bands, large slide rule dial; 1.8-2.4 mc., 3.2-4.1 mc., 7.0-7.3 mc., 14.0-14.4 mc., 21.0-21.5 mc., 26.95-27.35 mc. and 28.0-29.7 mc., plus special 10 mc. position for WWV. Covers most important MARS frequencies. Dual conversion receiver with exclusive upper/lower side band selection, T-notch filter, 50:1 tuning knob ratio with absolute resetability, built-in precision 100 kc. marker crystal. Illuminated dual scale S-meter functions with AVC off. Five steps of selectivity from 500-5000 cycles and precision temp. compensation. 52 ohm antenna input. 14 tubes plus voltage regulator and rectifier. Size: 20x10½x16". Shp. wt. 74 lbs.

R-46B Speaker, wt. 13½ lbs. — \$17.95



Please send me Free Catalog . . . and complete info on Hallicrafters SX-101.

NAME: _____

ADDRESS: _____

CITY & STATE: _____

SX-101


at **WORLD RADIO**

"The World's Largest Distributor of Amateur Radio Equipment!"

- ✓ Top Trades!
- ✓ Prompt Shipment!
- ✓ Easy Terms!

**FREE 1958
Catalog**

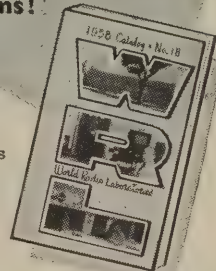200 pages, hundreds of illustrations, 15,000 top value items write for yours, today!



"Why, Rudolph!
You're almost human
since we bought the
JENSEN NEEDLE".

E B E
**COMPUTERS, ROBOTS
AUTOMATION**

TRANSISTOR DIGITAL COMPUTER KIT. Build the newest circuits. Multi-brators, counters, logic circuits, 'and', 'or', flip flops and use them. This is the first time we offer this kit after months of testing and preparation. A 'first' on the market for EBE, we thank our engineers. Can be expanded with standard parts to increase range and capacity. For speedy reply order by air mail. Send \$59.50 for kit plus instructions.

- **ELEMENTARY RELAY COMPUTERS;** learn the principles of operation and programming, including the boolean algebra. You can build actual computers from the circuits given. Complete at \$12.50.
- **AUTOMATION,** instruction in circuits, systems and design, for both industry and the home. Learn how to apply instrumentation to all types of processes. No prerequisite. Complete course: \$19.50 including answers to all questions.
- **ROBOTS,** manual on construction, building projects. Use standard parts for circuits. Save money by building your own relays and timers. You receive 200 pages and additional data for one year for FREE. \$5.00 ppd.
- **ELECTRONICS,** learn the principles of radio, television, radar, test equipment, transistors, computers. 40 lessons plus three text books, \$22.50 down and \$10.00 per month for five months. This is the lowest price for the entire field!
- **DIGITAL COMPUTERS,** learn circuits used in giant brains. Build small computers that add, subtract, multiply and higher algebra by special programming. Includes memory devices, binary counting, programming and free research. Complete course \$18.50.

ELECTRONIC BRAIN ENTERPRISES, INC.
1015 Atkin Ave., Salt Lake City 6, Utah

Name: _____

Address: _____

HI-FI ENGINEERED FOR THE FUTURE ENGINEERING-STYLE- PERFORMANCE ARKAY STEREO HI-FI KITS AND PREWIRED



ARKAY FM-8
Professional
Standard
FM TUNER

Engineered for precise FM reception Arkay "Miracle Ear Sensitivity" provides 1.9 uv for 20 db quieting. Freq. Response 20-20,000 cps. Outstanding features include 3 tuned RF stages, rimi-limiters, Armstrong FM Foster Seeley tuning system, variable AFC Silent tuning system, high-level & Binaural motor, cathode follower, 0-100 log scale for FM (multiplex) outputs, 0-100 log scale for stereo pinpointing, self-contained AC power supply plus many other extras.

KIT \$39.95 WIRED \$59.95
ARKAY AM-5 AM TUNER Most sensitive AM tuner. "Miracle Ear" 2 uv for 20 db s/n Wide & Narrow Band 3 gang tuning cond 10KC whistle filter
KIT \$23.45 WIRED \$35.95
HFT-7 AM-FM Tuner, AFC, Sensitive.
KIT \$32.00 WIRED \$49.95



**ARKAY STEREO AT
SENSIBLE PRICES!**
At last the economical
audiophile can enjoy
"living sound"

**ARKAY MODEL FL-30
HI-FI AMP PRE-AMP**
An engineering masterpiece TRANSISTORIZED front end assures finest in Hi-Fi sound. Freq. response 1/2 db 30-10,000 cps. 30-50 watts, 50 watt peak inputs for magnetic pickup, tuner, tape & 2 aux. Complete with step-by-step plans, handsome black cabinet & rose gold panel.
KIT \$49.95
WIRED \$74.95

SEE N'HEAR THESE ARKAY UNITS!

Arkay FL-10—12 watt amp pre-amp—only \$28.95	Arkay A-12—Amp pre-amp for budget-minded. Output 12 watts. Easily assembled \$22.95	Arkay FL-5—5 watt amp gives true hi-fi performance kit for beginner \$12.25
Arkay B-125—High Efficiency Speaker System Kit 17x17x15 1/2" Simple: Nail, glue and stain \$12.95. Model B-125 with Co-ax spkr. and Bal. \$25.00	Arkay TR-6—All-transistor port superhet kit output better 275 mill watts 540-1620 kc. Superb tone. Const. extremely simple \$37.50	Arkay TR-5—Personal Portable-5 transistor. Printed circuit printed layout component b.d. assembled 3 hr High impact styrene case. jack for pvt. listening \$31.45

Prices 5% higher west of Mississippi
FREE! At your dealer or write for complete catalogues of Stereo & Monaural HI-FI, Radio & TV, Kits & Wired.

arkay
LEADERS IN
AUDIO, TV & HI-FI
EQUIPMENT

120 CEDAR STREET
NEW YORK 6, N. Y.

At Your Dealer Insist on Hearing the
Fabulous "LIVING SOUND" STEREO

TECHNICAL LITERATURE (Continued)

A second booklet, *Guide to Replacement*, lists basic designation, tube class and various manufacturers' type numbers of many industrial tubes.—Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

REPLACEMENT CHART shows part of manufacturer's line of exact replacement power transformers, yokes, flybacks and vertical output transformers.—Merit Coil & Transformer Corp., 4427 N. Clark St., Chicago 40, Ill.

SPEAKER ENCLOSURES, ready-to-use cabinets and prefinished types. A complete line is shown in this 1958 catalog.—Cabinart, 99 N. 11 St., Brooklyn 11, N. Y.

ELECTRONIC COURSES are outlined and employment opportunities with their requirements are presented in this handy brochure.—Cleveland Institute of Radio Electronics, 4900 Euclid Ave., Cleveland 3, Ohio.

EIA (RETMA) STANDARDS. RA-196: Fixed Film Resistors (High Stability), from Standards Proposal 507. **RS-197:** Power Filter Inductors for Electronic Equipment, from Standards Proposal 511 and 526, a revision of TR-110-B.—EIA (Formerly RETMA), Engineering Dept., 650 Salmon Tower, 11 W. 42 St., New York 36, N. Y. RA-196, 60c. RS-197, 50c.

LINEARITY IN TRANSMITTER TUBES is

stressed in a 9-page bulletin entitled "Transmitting Tubes for Linear Amplifier Service."—Penta Laboratories, Inc., 312 N. Nopal St., Santa Barbara, Calif.

CONTROL GUIDE, No. 5, makes control replacement information available. Covers replacements for radio, TV, auto sets as well as audio equipment.—Centralab, Div. of Globe Union Inc., 900 E. Keefe Ave., Milwaukee 1, Wis. 20c.

ELECTRONIC PHONO FACTS is a 21-page booklet by Maxmilian Weil which answers many questions about high-fidelity equipment. It covers subjects like stylus alignment, peaks and dips, turntable and record care.—Rek-O-Kut Inc., 38-19 108th St., Corona, 68, L. I., N. Y. 25c.

FIXED COMPOSITION RESISTORS, type BT. Construction, characteristics, terminations, heat dissipation, color coding, power and voltage ratings are found in *Catalog Data Bulletin B-1C*.—International Resistance Co., 401 North Broad St., Philadelphia 8, Pa.

NEW BOOK CIRCULAR describes Beitman's *Additional 1957 TV Servicing Information Manual*. Also lists other helpful servicing literature.—Supreme Publications, 1760 Balsam Rd., Highland Park, Ill.

CRYSTAL-FILTER SPECIFICATIONS, outline drawings, typical characteristic curve and circuit diagram are set forth

FIX OLD RADIOS IN A JIFFY!

Fix 'em
good as new . . .
without lost
time or
needless testing



Often, it takes more time than it's worth to fix old radios . . . but NOT when you own this 3 1/2-pound, 744-page **RADIO TROUBLESHOOTER'S HANDBOOK**! Just look up the old make and model. Handbook tells exactly what is likely to be wrong—shows exactly how to fix it. No wasted time. No needless testing. Gives common trouble symptoms for over 4,800 old home receiver models, auto radios and record changers by 202 manufacturers. Includes hundreds of pages of old tube and component data no longer available from any other source.

CUT SERVICE TIME IN HALF!

Even beginners can repair old sets which might otherwise be thrown away because service data is lacking! Handbook more than pays for itself first time you use it! Covers old sets made by Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. The only service guide of its kind.

10 DAY FREE EXAMINATION

Dept. RE-127, RINEHART & CO., Inc.
232 Madison Avenue, New York 16, N. Y.

Send RADIO TROUBLESHOOTER'S HANDBOOK for 10-day examination. If I decide to keep book, I will then send \$6.95 plus postage. Otherwise, I will return book promptly and owe you nothing. (SAVE! Send \$6.95 with order and we pay postage. Same 10-day return privilege with money refunded.)

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A.—Price \$7.50 cash with order only. Money back if you return book in 10 days.

CONVERT TO COLOR TV

COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any-size black-and-white TV, direct view or projection, to receive compatible color TV. **COLORDAPTOR** is simply attached to TV set, does not affect normal operation and can be built from parts experimenters have on hand.

Complete specifications including theory of operation, complete simplified construction plans, schematic and sample color filters..... **\$1.95**

Essential parts kit containing all special parts—coils, delay line, crystal, color filters—

Up to 16" sets— **\$19.95** 17" and larger— **\$20.95**

All other **COLORDAPTOR** parts, kits, motors, etc. available. Write for information and prices.

COLORDAPTOR, 3471 Ramona, Palo Alto, Calif.

LMB "SAL-MET"

LMB Presents The New

FREE 1957 CATALOG covering the full precision engineered line of original box chassis as manufactured by LMB including new Miniature, new Jiffy, new T.F., new Utility Boxes. Eleven different types, 160 different shapes and sizes. A ready reference for engineers, experimenters or anyone using metal boxes. Send for your FREE CATALOG now! "SAL-MET" Non-corrosive Flux—solders copper to aluminum, aluminum to aluminum, any metal to any metal using conventional solder and regular soldering methods. Send for both LMB and "SAL-MET" Catalogs.

LMB, 1011 Venice Blvd., Los Angeles 15, Calif.



MORSE CODE

SENDING • RECEIVING • SPEED

Complete Instructions.

Made Easy with 45 or 78 RPM Record.

7 INCH 45 RPM... SEND \$1.25 12 INCH 78 RPM... SEND \$2.25
Prices include Postage and Handling

UNCLE SAM RECORDINGS • Dept. B-12
59 East Van Buren Street Chicago 5, Illinois

Sold by leading hobby shops, radio-electronic dealers, hi-fi record shops, chain and department stores everywhere. Dealers, Jobbers and Mail Order firms inquiries invited.

TECHNICAL LITERATURE (Continued)

in this 4-page catalog.—Hycon Eastern Inc., 75 Cambridge Parkway, Cambridge 42, Mass.

ELECTRONICS CATALOG, No. 170, lists over 27,000 items in its 404 pages. A complete line of hi-fi components and Knight kits are included. Industrial equipment is also shown.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

HIGH-FIDELITY CATALOG contains a listing of this manufacturer's line of hi-fi equipment in kit and factory-wired form. — Electronic Instruments Co. (EICO), 84 Whithers St., Brooklyn 11, N. Y.

MAGNETIC TAPES for instrumentation recording are the subject of this illustrated booklet. Six tape types used in telemetering, computers and other instruments are detailed. — Minnesota Mining & Manufacturing Co., 900 Bush St., St. Paul 6, Minn.

CONSTANT-VOLTAGE TRANSFORMERS for 6.3-volt filament supplies are offered in circular CVP-269. Four informative pages describe the operation of these units.—Sola Electric Co., 4633 W. 16 St., Chicago 50, Ill.

AUDIO-FREQUENCY AMPLIFIERS are detailed in *Catalog No. 16-C* which stresses laboratory type units for scientific laboratories, tape or disc recording equipment and other purposes. —Cimena Engineering, Div. of Aerovox, 1100 Chestnut St., Burbank, Calif.

TRANSISTOR SPECIFICATIONS of this manufacturer's line of alloy-junction types and an interchangeability guide are offered in a 4-page pamphlet.—Industro Transistor Corp., 649 Broadway, New York 12, N. Y.

PRECISION WIREWOUND RESISTORS are presented in this illustrated 2-color catalog. Axial, lug, printed-circuit and radial-lead versions are described.—General Resistance Inc., 557 E. 156 St., New York 55, N. Y.

MINIATURE PAN-I-LITES and Pan-I-Lite switches are shown in two illustrated spec sheets.—Alden Products Co., 117 N. Main St., Brockton 64, Mass. **END**

CORRECTION

There is an error in the text of the article "Hi-Fi Twin-Coupled Amplifier" in the November issue. In the second paragraph on page 44 the text states that R5 and C1 should be removed when using an electrostatic tweeter. The reference should be to R6 instead of R5.

Our thanks to Mr. L. R. Cartwright of Unionville, Mich., for reporting the error.

The author of "Build This Amplifier—Rectifier Vtvm for Audio Testing" (October, page 59) points out that capacitor C7 was erroneously listed as an electrolytic in parts list. C7 should be a paper type capacitor to minimize leakage and erroneous meter readings. A bath tub type capacitor was used in the original instrument.

"OUTPERFORMS THEM ALL"



I. J. Saltzman, *Globe Sound Service, Jamaica, N. Y.*, experienced commercial sound engineer, says: "On side by side comparison test, the CJ-44 outperforms them all."

NEW! ATLAS "King Cobra-Jector"

CJ-44



Shown with GB-1 Universal Mounting Bracket

Complete with "Acousti-Match" Built-in Driver Unit

List \$72.50

NET \$43.50

A wide-angle, all-purpose, all-weather Public Address Speaker, complete with integral high-power super-efficient "Acousti-Matched" driver unit. "Acoustic-Matched" means "Controlled Response" within the frequency limits most useful in P. A. and high level music reproduction. "Controlled Response" offers conversion efficiency never before obtainable in high-powered speakers. "Controlled Response" results in smooth reproduction — free from peaks which so often create and sustain acoustic feedback.

The CJ-44 conserves costly amplifier output power — fewer speakers do a complete job. The speaker horn is easily rotated for horizontal or vertical dispersion patterns.

The CJ-44 is the only high-powered P. A. speaker that can be equipped with the new Atlas Universal Mounting Bracket, permitting quick and secure directional adjustment on both planes. Simple to make a horizontal or vertical adjustment as a final "touch-up" to the installation.

The CJ-44 is designed for the "tough jobs." No gimmicks, no fluffs, no wild claims — just a reliable super-efficient speaker for all applications.

Input Power:	30 watts constant 50 watts peak
Input Impedance:	16 ohms
Response:	150-9,000 cps
Dimensions:	Bell 23" x 13"; Over-all length 19"
Net Weight:	16 lbs.

Write for free Catalog 57.



ATLAS SOUND CORP.

1443-39 St., Brooklyn 18, N. Y.
Atlas Radio Ltd., Toronto, Canada

Dave Rice's

OFFICIAL

ORDER BOOK

for every TV-Radio
service call



Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10.

... and for customer's prices on every replacement part, Dave Rice's

OFFICIAL PRICING DIGEST

listing over 60,000 items. \$2.50

In stock at your distributor, or write


ELECTRONIC PUBLISHING CO. INC.

180 North Wacker Drive Chicago 6, Illinois

FREE! 360 pages of the Newest in

ELECTRONICS

HIGH FIDELITY • RADIO • TV

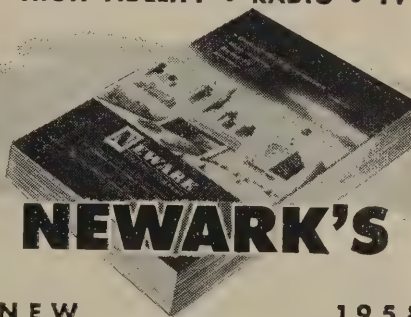

NEWARK'S

NEW CATALOG 1958

Offers you a fast, efficient, dependable way of selecting the finest components in the field at the lowest prices.

NEWARK

ELECTRIC COMPANY

Write Dept. RE-12

223 W. Madison St. • Chicago 6, Illinois
4736 W. Century Blvd. • Inglewood, Calif.

DYNAKIT

Amplifier Kits

A proven circuit of finest sound quality in a new deluxe 60 watt model and standard 50 watt model



MARK III 60 watts 79⁹⁵*
4, 8, 16 ohm outputs net

The new Mark III includes all the sensational attributes of the popular Mark II plus these outstanding deluxe features

- ★ 60 watts at less than 1% distortion. Instantaneous peak power of 140 watts. IM less than .05 at average listening levels.
- ★ Choke filtering and low noise circuitry reduce hum and noise to 96 db below 60 watts.
- ★ New rugged KT-88 tubes and other heavy duty parts used conservatively.

MARK II 50 watts 69⁷⁵*
8, 16 ohm outputs net

The Mark II is the best buy in high power high fidelity kits

- ★ Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
- ★ Highest stability using patented stabilizing networks with minimum number of phase shifting stages. Suitable for all loud-speaker systems including electrostatic.
- ★ Dyna Biaset (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components. No balancing adjustments required to meet published specifications.
- ★ Dynaco Super-Fidelity output transformer with patented para-coupled windings. This is the finest available transformer of its type for the most critical audio uses.

Available from leading Hi-Fi dealers everywhere

Descriptive brochure available on request.

DYNA COMPANY

617 N. 41st Street, Philadelphia, Pa.

Slightly higher in West

Books



TV REPAIR QUESTIONS AND ANSWERS, Vol. 5 (Sound and Low-Voltage Circuits), by Sidney Platt. John F. Rider Publisher, Inc., 480 Canal St., New York 13, N.Y. 5 1/2 x 8 1/2 inches, 120 pages. \$2.10

Many of us find it easier to absorb and retain information that is presented in question-and-answer form. This book, written that way, is for practical technicians. Theory is held to a minimum. Questions and answers are followed by a discussion which explains the procedure. Where adjustment or alignment is outlined, it is given step by step. To save time and effort, separate chapters are written for the if stages, detector, amplifier, speaker and power supply.

TV TUBE LOCATOR, Vol. 2. Harry G. Cisin, Amagansett, N. Y. 8 1/2 x 11 inches, 32 pages. \$1.50.

This newest volume of the TV Tube Locator starts where Vol. I stopped. Shows tube layouts of recent TV sets

from 1955 models up to and including the newest 1957 sets. Each diagram gives the location and exact type number for every tube in the receiver and its function. A handy feature of the book is a table listing 135 common TV troubles caused by defective tubes. Series-string heaters and selenium rectifiers are indicated. If you've ever wondered which tube is the video output, this book can save you time.—LS

THE GRAMOPHONE HANDBOOK, by Percy Wilson. Methuen and Co., Ltd., 36 Essex St., London W. C. 2, England. 5 x 8 inches. 227 pages text, 42 pages advertiser's announcements, 15 shillings.

This work by the technical editor of the British periodical *The Gramophone* is billed on the jacket as "intended for the ordinary man of an inquiring turn of mind who wants to know something of the ideas behind this modern development of high-fidelity reproduction of sound." Mr. Williams presents the basic purposes of high fidelity, the conditions for achieving it and a summary of the means of arriving at it, clearly and free from personal prejudice or enthusiasm. The first four chapters comprise an excellent presentation of the ideas behind high fidelity. The several chapters on pickups, styli, arms and turntables, record wear, etc., are a little more advanced than the rest and should be of value to a somewhat more technical reader. Though specific references are

CATALOG OF Professional Quality Kits
"DIRECT FROM FACTORY"

FREE

TRANSVISION SPLIT/KITS

- TV KITS
- INSTRUMENT KITS
- HI-FI KITS, SPEAKERS
- HI-FI CABINETS (Largest Selection)
- Electronic PHOTOFLASH Kits

PAY AS YOU WIRE with Transvision "SPLIT-KITS." A few dollars gets you started. Each Kit is split into a few packages. You can order one at a time as you wire.

Also **RECORDS** RCA - CBS All Labels

at BIGGEST DISCOUNT!

TRANSVISION, INC., New Rochelle, N.Y.

Rush FREE Catalog of KITS. HI-FI Equipment. Cabinets, Records, etc

Name _____


Address _____

City _____ State _____

Almost everybody remembers to make Christmas Seals a part of his giving . . . because they give the greatest gift of all, health, life itself, to so many.

How about you?

BE QUALITY WISE . . . BUY QUAL-KITS!

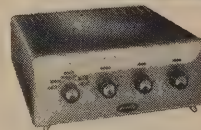

HI-FI AMP. KIT
Complete 6 tube-10 watt amplifier Push-pull beam power output, built-in pre-amp. 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response 1/2 db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion. **\$28.50**

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional.

*Add 10 percent for new federal tax



HI-FI AM-FM TUNER KIT
Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM, 25 uv AM. Armstrong FM Circuit with limiter. Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control — no drift. Easy assembly. **\$28.95***

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

QUALITY-ELECTRONICS
319 Church St. Dept. RE12 New York 13, N. Y.

BOOKS (Continued)

to British equipment, this does not take away from the usefulness of the book to American readers.—JM

SERVICING AND CALIBRATING TEST EQUIPMENT, by Milton S. Kiver. Howard W. Sams & Co., Inc., Indianapolis 5, Ind. 5½ x 8½ inches, 184 pages. \$2.75.

A successful service technician really has two jobs: He must keep his own test equipment in good operating condition as well as keep his customers' sets in good repair. Unless the first requirement is satisfied, there is not much likelihood that his customers will be. Even the highest-quality meters, generators, scopes and probes do not remain reliable unless they are properly maintained and regularly checked.

This book shows how to take care of, calibrate and repair various test instruments. It tells how to keep test records and the best methods of preventive maintenance. Typical service instruments are described with photos and schematics.—IQ

FM LIMITERS AND DETECTORS, edited by Alexander Schure, John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 5½ x 8½ inches, 44 pages. 90c.

Four basic FM circuits are described in detail. They are the limiter, Foster-Seely discriminator, ratio detector and gated-beam tube circuit. Theory and operation are covered in each case, together with information for adjustment for optimum results.—IQ

RESONANT CIRCUITS, Edited by Alexander Schure. John F. Rider Publisher, Inc., 116 W. 14th St., New York 11, N. Y. (No. 166-16). 5½ x 8½ inches, 72 pages. \$1.25.

Resonant circuits; combinations of L, C and R are found in many types of electronic instruments and radio devices. Presuming little previous knowl-

edge, this booklet starts with basic concepts. It clearly describes such topics as impedance, Q, power factor and coupling. Distributed as well as lumped constants are covered.—IQ

INVENTORS AND INVENTIONS, by C. D. Tuska. McGraw-Hill Book Co., Inc., 330 W. 42 St., New York, N.Y. 6 x 9 inches, 174 pages. \$3.75.

Whether you admire the inventive genius in others or you yourself have a creative spirit, this book will be interesting. The author describes effects of environment, education and age on patent productivity. Case histories of many important patents such as the superheterodyne radio, telephone and X-rays show how inventions may result from inspiration, curiosity, accident or sheer necessity.

Inventors will find suggestions for protecting, patenting and marketing their brain-children.—IQ END

CORRECTION

The author of "Build This Amplifier-Rectifier VTVM for Audio Testing" (October, page 59) points out that capacitor C7 was erroneously listed as an electrolytic in the parts list. C7 should be a paper type capacitor to minimize leakage and erroneous meter readings. A bathtub-type capacitor was used in the original instrument.



"BREEZE THROUGH"

FCC LICENSE EXAMS

ONLY \$5.00

No lessons to wait for

Train for better pay in communications—most interesting jobs

LICENSE MANUAL FOR RADIO OPERATORS

By J. R. Johnson
A complete, simplified study guide for getting your "ticket" as a commercial operator.

Covers all necessary examination data from electrical and radio fundamentals to navigation and related subjects. Anyone with basic radio training will find Johnson's LICENSE MANUAL FOR COMMERCIAL OPERATORS the ideal training book for making this all important step in getting one of communication's most interesting, best paid technical jobs.

10-DAY FREE EXAMINATION

Dept. RE-127, RINEHART & CO., Inc., 232 Madison Ave., New York 16, N. Y.

Send Johnson's LICENSE MANUAL FOR RADIO OPERATORS for 10-day examination. If I decide to keep book, I will send \$5.00 (plus postage) in full payment. Otherwise, I will return book and owe nothing. (SAVE! Send \$5.00 with order and we pay postage. Same 10-day return privilege with money refunded.)

Name.....


Address.....

City, Zone, State.....

OUTSIDE U.S.A.—\$5.50 cash with order. Same 10-day return privilege with money refunded.

DYNAKIT PREAMPLIFIER

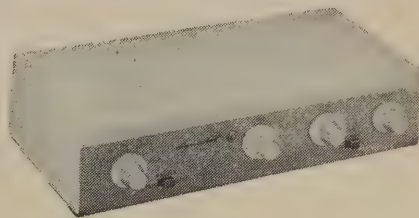An Outstanding Companion Kit to the World Famous Dynakit Amplifiers



This handsome new control unit gives crystal clear, noise-free reproduction from any modern program source. Its unique all feed back design by David Hafler sets a new standard of preamplifier performance. The design of the Dynakit preamplifier is a synthesis of outstanding features which produce smoother, more natural sound. Compare these features with any other units regardless of price.

★ Unequaled performance

Actually less than .1% distortion under all normal operating conditions. Response ±.5 db 6 cps to over 60 kc. Distortion and response unaffected by settings of volume control. Superlative square wave performance, and complete damping on any pulse or transient test.

★ Easiest assembly

All critical parts supplied factory-mounted on XXXP printed circuit board. Eyeleted construction prevents damage to printed wiring. This type of construction cuts wiring time by 50% and eliminates errors of assembly. Open simplified layout offers complete accessibility to all parts.

★ Lowest noise

Integral dc heater supply plus low noise components and circuitry bring noise to less than 3 microvolt equivalent noise input on RIAA phono position. This is better than 70 db below level of 10 millivolt magnetic cartridge.

★ Finest parts

1% components in equalization circuits to insure accurate compensation of recording characteristics. Long life electrolytic capacitors and other premium grade components for long trouble-free service.

★ High flexibility

Six inputs with option of extra phono, tape head, or mike input. Four AC outlets. Controls include tape AB monitor switch, loudness with disabling switch, full range feedback tone controls. Takes power from Dynakit, Heathkit, or any amplifier with octal power socket.

★ Outstanding appearance

Choice of bone white or charcoal brown decorator colors to blend with any decor. Finished in indestructible vinyl coating with solid brass escutcheon.

★ Best buy

Available from your Hi-Fi dealer at only \$34.95 net (slightly higher in the West), and yet the quality of performance and parts is unexcelled at any price.

Descriptive brochure available on request.

DYNA CO., 617 N. 41st St., Phila., Pa.
Pat. Pending

STATEMENT REQUIRED BY THE ACT OF MARCH 24, 1912, AS AMENDED BY THE ACTS OF AUGUST 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF RADIO-ELECTRONICS, published monthly at Mount Morris, Ill. for October 1, 1957.

1. The names and addresses of the publisher, editor, managing editor, and business managers are:
Publisher, Hugo Gernsback, 154 W. 14th St., New York 11, N. Y.; Editor, Hugo Gernsback, 154 W. 14th St., New York 11, N. Y.; Managing editor, Fred Shunaman, 154 W. 14th St., New York 11, N. Y.; Business manager, none.

2. The owner is: Gernsback Publications, Inc., 154 W. 14th St., New York 11, N. Y.; Hugo Gernsback, 154 W. 14th St., New York 11, N. Y.; M. Harvey Gernsback, 154 W. 14th St., New York 11, N. Y.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) none.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

5. The average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the 12 months preceding the date shown above was: (This information is required from daily, weekly, semiweekly, and triweekly newspapers only.)

M. Harvey Gernsback
Publisher and Editor

Sworn to and subscribed before me this 10th day of September, 1957.
[Seal] Viola H. Scherer
(My commission expires March 30, 1958)

ANNUAL INDEX

Vol XXVIII

RADIO-ELECTRONICS

KEY TO SYMBOLS AND ABBREVIATIONS


* Construction Articles
† Section of full-length article
ClinicTelevision Clinic
CorresCorrespondence
NBNews Briefs
PatPatents
QBQuestion Box
RECRadio-Electronic Circuits
TTOTry This One

Regular departments not indexed are Business, Technicians' News, New Devices, People, Technical Literature, Books.

A

Abbreviations and Symbols (Kimball)	Jan 150, Feb 100, Mar 123
Ac-Dc Power Supply* (Pearce)	Dec 46
Current Flow (Corres)	May 18
Transistor (Corres)	Jan 22
Add a Tuner Test to Your Field-Strength Meter (Centerville)	Dec 35
Adding a Tape Recorder to a Hi-Fi System (Crowhurst)	Feb 35
Afc Improves FM Tuners* (Montgomery)	Jan 123; (QB) Apr 123; Jul 53
A-I-R Generator, Transistorized* (Queen)	Aug 92
All-Transistor Tape-Head Preamp* (Gicca)	Oct 36
Amateur	
80-Meter Novice Converter for Broadcast Receivers (QB)	Feb 120
500-Million-Mc Transceiver* (Pallatz)	Oct 93
Headset Booster, Assemble This* (Louis)	Sep 38
10-Meter Transistor Rig Goes Vfo* (Reed)	Sep 58
30-Mc Transistor Superrégen* (Bohr)	May 57
Transistor Shortwave Receiver* (Braunbeck)	Aug 84
Transistorized Rig Works 10-Meter Dx* (Griffith)	May 60
Correspondence	Aug 22
Amplifiers—See Audio, Television, etc.	
Antennas	
Air (Pat)	Mar 139
FM (REC)	May 113
Loopstick, Rotatable (Pat)	May 113
Television—See Television	
Apple Tube, How It Works (Colgate)	Jan 40
Applying Variable Damping (Crowhurst)	Jul 30
Assemble This Headset Booster* (Louis)	Sep 38
AUDIO—HIGH FIDELITY	
Amplifiers	
Af, 3-tube†	Apr 48
Bookshelf Audio* (Montgomery)	Apr 32
Correction	Jun 119
Class-B	
Compensated, Transistor (Pat)	Aug 127
Hi-Fi (Pat)	Jul 114
Conversion (RCA 648PTK) (QB)	Apr 122
Copy-Cat* (Drenner)	Sep 42
Crossover	
Colbert 3-CFD†	Jun 30
Electronic (Crowhurst) Jan 137*	
(Augsburger) May 40;	
(Ravenswood)	Sep 35
Heathkit XO-1†	Jun 30
Magnavox AMP-150†	Jun 32
Multichannel Electronic* (Crowhurst)	Dec 52
White Beta-Tron†	Jun 32
Direct-Coupled (Pat)	Jun 124
4-Stage (What's New)	Jan 136
High-Quality (AEL 30W)* (Tang)	Jul 35
Correction	Sep 100
Mobile, for Tuner (QB)	Mar 128
—Modulator, 6-Transistor, Delivers 10 Watts* (Hamlin)	Aug 47
Multichannel Amplification (Scott)	Jun 30
Phono* (REC)	Jul 116
R-C-Coupled, Design Calculations for (Ravenswood)	Oct 49
Remote, Low-Cost* (Jordan)	May 34
60-Watt, Uses New KT88's* (Steckler)	Aug 43
Tube Data and Design (Ravenswood)	Nov 47; Dec 56
TV Tube for High Fidelity* (Becker)	Feb 39
Twin-Coupled, High Fidelity at Low Cost* (Crowhurst)	Nov 39
Correction	Dec 147
Wide-Band (Pat)	Dec 128
Transistor (Pat)	Aug 127
Williamson, More Gain for (TTO)	Sep 146
Baby Sitter, Deluxe Remote* (Kaufman)	Nov 50
Bias Supply (QB)	Jun 118
Cartridges	
Audax DL-6 and Hi-Q7†	Apr 38
Connoisseur Mark II†	Jun 35
Electro-Sonic†	Jun 34
Electro-Voice 84†	Jul 37

Fairchild 225-A†	Jun 34
Fen-Tone B&O 350A+† May 36; P-7000A†	May 37
G-E RPX-052†	Apr 37
Leak Dynamic†	Jun 34
Mirastwin MST-2†	May 37
Modern Phonograph (Hirsch)	
Part I—Types of Pickups; Variable-Reluctance Cartridges	Apr 37
Part II—More Variable-Reluctance Cartridges	May 36
Part III—Moving-Coil Magnetic Cartridges	Jun 34
Part IV—Amplitude-Responding Types	Jul 36
Pickering Fluxvalve†	May 36; Dec 51
Recoton-Goldring 500†	May 37
Shure Studio Dynetic†	Jul 37
Sonotone Series 3†	Jul 36
Tannoy Variolant†	May 37
Weathers FM†	Jul 38
Compressor (Pat)	Jun 124
Control Unit, Hi-Fi Master* (Marshall)	Oct 45
Crossover, 3-Way (Crowhurst) (See also Audio, Amplifiers, Crossover)	Jan 137
Damping, Variable, Applying (Crowhurst)	Jul 30
Dividing Networks, Electronic (Ravenswood)	Sep 35
Drivers and Inverters (Marshall)	Mar 55
Earphones, Phasing Jun 40; (REC)	Dec 120
Electronic Voice for Silent Chief (Goodwin)	Jul 34
Enclosures	
Corner Speaker, True	Jun 33
Flexibility Unlimited* (Colaguori)	Feb 32
Kits Aid Audio Builders (Leslie)	May 38
Correspondence	Aug 16
Feedback, Negative, Controls Selectivity	May 44
Filter, Phonograph (QB)	May 126
Flexibility Unlimited (Colaguori)	Feb 32
Harmonic Analysis Made Easy (Shulman)	Jun 88
Headset Booster, Assemble This* (Louis)	Sep 38
Hearing Aid	
Binaural (NB)	Aug 8
Class-B, Transistorized* (Queen)	Apr 35
Correction	Sep 100
TV* (Cozzo)	Dec 78
Inverter(s)	
Drivers and (Marshall)	Mar 55
Phase, Choosing the (Crowhurst)	
Part I—Split-Load Inverter	Aug 49
Part II—Paraphase, Floating Paraphase, Long-Tail	Sep 40
Last Link, Physiology of Hearing (Crowhurst)	May 43
Organ, Simplest Electronic* (Hubbard)	Jul 39, Aug 54
Needles, Electronic Diamond Grinding of (What's New)	Sep 45
Oscillator, 2-Tone, Transistor (Pat)	Aug 126
PA	
From Auto Radio (QB)	Aug 114
How to Lose Money With PA System (Howard)	Aug 40
Phono Shutoff, Automatic for LP's* (Becker)	Jun 39

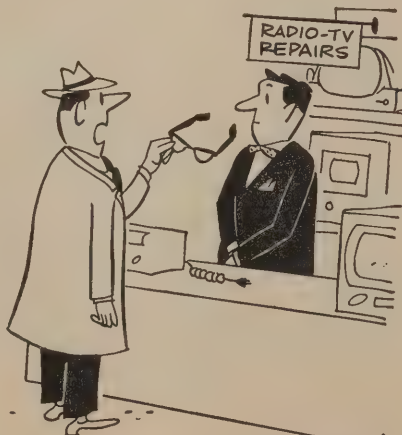

"The hearing aid works all right but the radio is noisy around 7 mc."

Pickup Arms	Dec 50
Audax KT-12/KT-16†	Dec 50
Fairchild 280A/281A†	Dec 49
G-E A1-500/A1-501†	Dec 51
Hi-Fi (Hirsch) (Part I)	Dec 49
Pickering 109D†	Dec 50
Shure Studio Dynetic†	Dec 51
Zenith Cobra (QB)	Jul 110
Power-Line Spikes and Buzz (Reed)	Sep 43
Preamp	
For Tape and Mike* (Horowitz)	Jul 33
Phono, Compensates for Cable Capacitance* (Montgomery)	Dec 47
6-8-Volt Battery Eliminator for (QB)	May 136
Tape-Head, All-Transistor* (Gicca)	Oct 36
Quiz, True or False, for Audiophiles (Burststein)	Nov 49
Radios, Improving Sound in AM (Stratmoen)	Mar 60
Record(s)	
8-Rpm (NB)	Dec 12
Hi-Fi Problem (Corres.)	Dec 18
New (Review) (Monitor) Jan 152, Feb 94, Mar 131, Apr 129, May 131, Jun 94, Jul 97, Aug 108, Sep 133, Oct 146, Nov 122, Dec 130	
Player Switching, Novel (TTO)	Oct 162
Stereo Disc (NB)	Dec 8
Tracking (Crowhurst)	Oct 40
Schematics	
Colbert 3-CFD 3-Channel Frequency Divider	Jun 31
Fairchild Electronic Phono Drive	Sep 44
Heathkit XO1 Electronic Crossover	Jun 31
Magnavox AMP-150 Twin-Channel Amplifier	Jun 32
White Beta-Tron Dual Amplifier	Jun 32
Selectivity	
Negative Feedback Controls	May 44
Variable	Sep 37
Servicing—See Also Technotes, Try This One	
Audio Specialists	Oct 43
Too Well Checked (Cohn)	May 42
Speakers	
Acoustic Fundamentals and (Klipsch)	Oct 44
Correspondence	
May 18, Jul 14, Aug 22, Sep 18	
Adding, to Shirt-Pocket Radio (Queen)	Jan 144
Bass	
Reproduction in (Villchur)	Oct 38
Response, Better (Augsburger)	Sep 32
Correspondence	Nov 16, Dec 18
Cheap, Can Be Improved? (George)	May 45
Corner, True	Jun 33
Corona Wind†	Nov 44
Distortion (Corres)	Dec 18
Future (Shirley)	Nov 44
Ionic (Pat)	Oct 159
Ionophone (DuKane)†	Nov 44
Ionovac (Electro-Voice) (What's New)	Apr 47; Nov 44
Isophase (Pickering)†	Nov 45
JansZent	Nov 45
Outside Cabinet (What's New)	Oct 52
Protecting (QB)	Jan 175
Second, Adds Realism (Crowhurst)	Mar 52
Spherical (What's New)	Apr 46
Correspondence	Aug 20
Tweeter, Electrostatic (QB)	Aug 116
2-Transistor Portable Operates* (Rhita)	Jan 134
Speech-Music Discriminator (Pat)	Jun 123
Correspondence	Jan 21, Feb 10
Stereo Disc (NB)	Dec 8
Stereophony Trend (NB)	Dec 6
Switching, Novel (TTO)	Oct 162
Syncope by Automation (Klein)	Jun 36
Correspondence	Sep 21
Tape(s)	
Stereo, Comes of Age (Burststein)	Mar 27
(Corres)	Mar 15
Triple-Track (NB)	Mar 15
Tape Recorder(s)	
Adding to a Hi-Fi System (Crowhurst)	Feb 35
Correspondence	May 26
Hum and Noise in Magnetic Recorders, Tracking (McRoberts)	Jun 41
Monitor (REC)	Apr 127
Preamp for* (Horowitz)	Jul 33
Takeup Tension (Tech)	Jun 120
Transistor (What's New)	Jan 136
Telephone Circuits (Pat)	Apr 108
Turntable	
Electronic Drive, Variable-Speed (Fairchild) (What's New)	Jul 56; Sep 44
Neutral Indicator (QB)	Jun 118
Vibrato, Phase-Swing; Easy to Build and Apply* (Dorf)	Mar 57
Auto Radios—See Radio, Receivers and Tuners	

SCHOOL DIRECTORY

TOP-FLIGHT ELECTRONICS

Train for technical representative, field engineer, electronic specialist on missiles, computers, radar, automation, radio, color-TV. Basic and advanced theory and laboratory. Mathematics. Major firms select our graduates. Dormitories-campus. 21 months' program. High school graduate or equivalent. G.I. approved. Start February and September.

Write for illustrated catalog today.
VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana



ENGINEERING DEGREES

UNDER AND POSTGRADUATE



E.E.
Option Electronics

Earned through
HOME STUDY
Residence Classes Also Available

PACIFIC INTERNATIONAL UNIVERSITY
(Operating as a College of Engineering only at present)
5719-M, Santa Monica Blvd., Hollywood 38, Calif.

ELECTRONICS ENGINEERING DEGREE IN 27 MONTHS

Prepare for unlimited opportunities in electronics! B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory and design. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech., Engineering. B.S. degree in 36 mo. in Math., Chem., Physics. Also prep courses, G.I. appr. 20 bldgs., dorms, gym. Enter Dec., March, June, Sept. Catalog. Keeping Pace With Progress.

INDIANA TECHNICAL COLLEGE
1512 E. Washington Blvd., Fort Wayne 2, Ind.

college grads get ahead faster!

... have higher incomes... advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. Approved for Vets.

Bach. Sc. degree in 27 months
Complete Radio Eng. courses (TV, UHF, FM, Electronics). Also Mech., Civil, Elec., Chem., Aero., Eng. 36-months in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.). Superior students faster. More professional class hours. Small classes. Enrollment limited to 1550. Beautiful campus. Well-equipped labs. Prep courses. Enter Jan., Mar., June, Sept. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to write Jean McCarthy, Dir. Adm., for Catalog and "Your Career in Engineering and Commerce."

TRI-STATE COLLEGE
24127 College Ave., Angola, Indiana

CODE SENDING SPEED
Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.
CANDLER SYSTEM CO.
Dept. 3-O, Box 928, Denver 1, Colo., U.S.A.

ELECTRONICS
PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION
TELEVISION SERVICING
BLACK & WHITE—COLOR
APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

ATTENTION...

SERVICE TECHNICIANS' ASSOCIATIONS
CLUB MEMBERS



STUDENT GROUPS

SPECIAL SUBSCRIPTION RATES TO RADIO-ELECTRONICS ARE AVAILABLE TO ASSOCIATIONS, CLUBS, SCHOOLS, EMPLOYEE GROUPS, ETC. FOR INFORMATION WRITE . . .

G. ALIQUO
Radio-Electronics

154 West 14th Street, New York 11, N.Y.

Interesting, Pictorial FREE BOOKLET

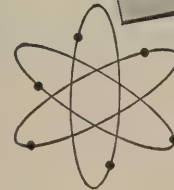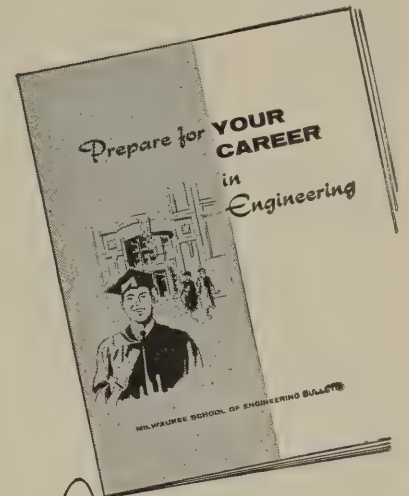

to help
you
decide on

YOUR CAREER IN ELECTRONICS RADIO-TV COMPUTERS

Here is a graphic story about dynamic careers for engineers and engineering technicians. Booklet covers such subjects as:

- Wide variety of job opportunities.
- The courses offered, degrees you can earn, and what you are qualified to do.
- Pictures of the Milwaukee School of Engineering, its facilities, plus Milwaukee scenes.
- Recreation, student organizations, fraternities.
- Scholarships, part-time work, admission requirements.

— and many other important and interesting facts to help you understand and decide on your career in engineering. Send for your free copy today — no obligation whatsoever.

Milwaukee School of Engineering
—dedicated to serving young men and industry

SEND COUPON

Milwaukee School of Engineering

Dept. RE-1257 1025 N. Milwaukee St.
Milwaukee, Wisconsin

Please send me free the new booklet
"Prepare for Your Career in Engineering"
I'm interested in _____

(name of course)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I'm eligible for veteran's education benefit

Yes ☐ No ☐ Discharge date _____


ANNUAL INDEX (Continued)

Automatic Phono Shutoff for LP's (Becker)	Jun	39	European Approach to (Martin)	Aug	52	FM Antenna (REC)	Nov	141
Automation and the Tube Tester (McKay)	Oct	53	Facsimile Speeded (NB)	Aug	14	Radiation (NB)	Jun	10
B			Flashlamp (Pat)	Apr	106	Radio, Pocket-Size (What's New)	May	47
Balancing Meter Pointers (Cohn)	Mar	91	Harmonic Analysis Made Easy (Shulman)	Jun	88	Tuner		
Bass Reproduction in Loudspeakers (Villichur)	Oct	38	Impedances, Why Should (They) Be Matched? (Manly)	Mar	40	Afc Improves (Heathkit FM-3)* (Montgomery)	Jan 123;	
Better Bass Response (Augsburger)	Sep	32	Industrial Service Call (Slaughter)	Jun	80	—AM, Modernize Your (DiElsi)	Apr 123;	Jul 53
Correspondence	Nov	16	Interference Endangers Defense Systems (NB)	Jun	6	Amplifier, Mobile for (QB)	Mar	105
Binary Photographic Timer* (Rymsha)	Dec	106	L'Electrostyl to Revolutionize Stenography? (Martin)	Mar	38	Boosting 152-162-Mc Signals (REC)	Dec	118
Black-and-White Adjustments in Color TV (Mandl)	Jan	43	Lenses of Solid, Opaque Metal (What's New)	Jul	56	Easy-to-Align* (Abbatecola)	Jul	54
Black-Box Oscillator* (Bohr)	Sep	49	Light Meter for Electronic Flash* (Slaughter)	May	62	Tuning Indicator (QB)	Jul	109
Bookshelf Audio Amplifier* (Montgomery)	Apr	32	Lumistron, Electronoptics' New Sensation (Fips) (Fiction)	Jul 20,	Apr 16	Free-Power Receivers* (Hollmann)	Apr	85
Correction	Jun	119	Correspondence	Dec	12	Signal-Powered (REC)	Oct	164
Broadcast-Set Front End Traps If Interference* (Ives)	Aug	60	Magnet, "Super" (NB)	Mar	22	G		
Build a Dynaflex Broadcast Receiver* (Tooker)	Feb	82	Magnifier, "Ultra" (NB)	Dec	12	Getting Acquainted With Color TV (Middleton)	Jan	74
Build a Versatile Probe Set* (Hansen)			Mail Sorting (NB)	Jun	6	H		
Part I—Direct, Alignment, Isolation and High-Frequency Probes	Jun	50	Medicine			HAM—See Amateur		
Part II—Low-Frequency Detector and Low-Capacitance Probes	Jul	47	Cancer Detection (NB)	Mar	22	Hearing Aid	Aug	8
Build This Amplifier-Rectifier Vtvm for Audio Testing (Hedge)	Oct	59	Computer Checks Human Brain (Zaander)	Aug	55	Binaural (NB)	Apr	35
Correction	Dec	147	Endoscope (Pat)	Jun 123	Jun 6	Class-B Transistor* (Queen)	Apr	100
C			Radio "Pill" Transmits From Inside You (Leslie)	Jun	45	Correction	Apr	47
Captive Service—See Servicing			Microminiaturization (NB)	Jun	6	Miniaturization (What's New)	Dec	78
CD Monitor* (Mendelson)	Sep	56	Microwave			TV* (Cozzo)	Oct	45
Co or TV—See Television			Amplifier (What's New)	Sep	45	Hi-Fi Master Control Unit* (Marshall)		
Commercial Killers			Danger (NB)	Sep	10	Hi-Fi Pickup Arms (Hirsch)		
Speech-Music Discriminator (Pat)	Jun 123	Jun 10	Navigational Device (SINS) (NB)	Feb	6	Part I—Types; Separated Vertical and Horizontal Pivots; Fairchild 280A/281A; Audax KT-12/KT-16; Pickering 190D; Shure Studio Dynetic; G-E AI-500/AI-501	Dec	49
Correspondence	Jan 21,	Feb 10	Neon Lamps, Using (Clawson)	Dec	112	High Fidelity—See Audio		
Squelch That Blurb* (Schulke)	Jun	78	Panelcrescent Display Lamp (NB)	Sep	6	High Fidelity at Low Cost With Twin-Coupled Amplifier* (Crowhurst)	Nov	39
Computer Checks Human Brain (Zaander)	Aug	55	Pedro, Layman (Slaughter)	Sep	87	High-Fidelity Drivers and Inverters (Marshall)	Mar	55
Construction—See individual subjects. Construction articles are indicated with an asterisk (*).			Perveance, High? (Corres)	Nov	18	Hints on TV Tube Troubles (Glickstein)	Jan	64
Contact Potential for Loadless Metering (Bartholomew)	Apr	41	Phase Shifter, High-Frequency (Pat)	Apr	106	Hot Chassis		
Copy-Cat* (Drenner)	Sep	42	Photographic Timer, Binary* (Rymsha)	Dec	106	Correspondence	Feb 12,	Apr 22
Customers We Could Do Without (Margolis)	May	98	Photo-Sound Unit* (Vogelgesang)	Oct	64	Death Rides the (Shunaman)	Oct	100
D			Power Factor, What It Means (Manly)	Jul	82	Don't Be a Shock Absorber (Glickstein)	Mar	46
Death Rides the Hot Chassis (Shunaman)	Oct	100	Quiz, Industrial Electronics (Bukstein)	Apr	58	Line Plug, Three-way (Corres)	Feb 12,	Apr 22
Defective Interlace (Clawson)	Aug	30	Radio			Shocking Sink (Welz)	Aug	38
Deluxe Remote Baby Sitter* (Kaufman)	Nov	50	Signals From Jupiter (NB)	Aug	8	How the Apple Tube Works (Colgate)	Jan	40
Design Calculations for R-C-Coupled Amplifiers (Ravenswood)	Oct	49	Telescopes (Ko)	Aug	57	How to Lose Money With a PA System (Howard)	Aug	40
Do You Do a Maximum or Minimum Job? (Margolis)	Dec	98	Giant (Jodrell) (What's New)	Oct	52	How's Your Setside Manner? (Margolis)	Jan	72
Dynaflex Broadcast Receiver, Build This* (Tooker)	Feb	82	Relay			I		
E			Averts Toyland Tragedy (McRoberts)	Dec	102	Ignition Analyzer Checks Car Trouble Electronically (Gernsback)	Sep	46
Easy-to-Align FM Tuner* (Abbatecola)	Jul	54	Impulse (REC)	Nov	142	Impact Noise Meter Uses 3 Transistors (Rhita)	Oct	58
EDITORIALS (by Hugo Gernsback unless otherwise noted)			Polarized, Inexpensive (Lasker)	Feb	63	Improved Transistor Tester (Bohr)	Mar	82
Electron Keytones, Past and Future	Sep	31	Sensitive, Saves Standby Power* (Driver)	Oct	84	Inexpensive Radio-TV Service Aids (Scott)	Aug	88
Electronic Experimentation	Feb	31	Sound-Operated, Has Adjustable Time Delay (REC)	Jan	172	K		
Electromechanics	Aug	29	Sync-Triggert	Apr	49	Enclosure, Aid Audio Builders (Leslie)	May	38
Elusive Electron	Mar	33	Remote Controls—See Remote Controls			Circuit, Modern Touch in (Leslie)	Feb	78
Fantastic Electronics	Apr	31	Semiconductors—See Semiconductors;			L		
High-Fidelity Sound	Oct	35	Transistors			Last Link (Crowhurst)	May	43
Medical Electronics	Jul	29	Surveillance Kit* (Garner)			L'Electrostyl to Revolutionize Stenography? (Martin)	Mar	38
Tactile Electronics	Nov	31	Part I—Amplifier, Rf and Induction Pickups	Sep	81	Licensing		
Television of the Future	Jan	39	Part II—More Pickups; Accessories	Oct	62	ARTS (Chicago) Opposes (Tech News)	Jul	103
Transistor Growth	Jun	29	Telemetering			California Bill (Tech News)	Jun	106
US Government Needs Inventions	May	33	Lifeline of Guided-Missile Research (Koukol)	Apr	56	Columbus (Ohio) Rejects (Tech News)	Jul	101
USA at Bay	Dec	31	Ship (What's New)	Sep	45	Correspondence on Apr 22, Sep 21,	Nov	21
Electronic Crossover Amplifier* (Augsburger)	May	40	Thermionic Generator (Pat)	Mar	140	Delayed (Tech News)	Sep	135
Electronic Dividing Networks (Ravenswood)	Sep	35	Traffic Signals, Electronics Times (Sands)	May	78	Detroit (Tech News)	Jun	105
Electronic Texas Towers Guard Our Coasts (Brooks)	May	54	Ultrasonic Light Modulator (NB)	Sep	10	Endorsed (Tech News)	Apr	121
Electronic Voice for Silent Chief (Goodwin)	Jul	34	Zipper (What's New)	Feb	41	Long Beach (N.Y.) (Tech News)	Jun	105
ELECTRONICS			Enclosure Kits Aid Audio Builders (Leslie)	May	34	Opposed (Tech News)	Jan 123,	Apr 120
Alarms			Experimenter's Power Supply* (Hughes)	Jul	50	Pasadena (Calif.) (Tech News)	Jan	165
Aircraft anti-collision Radar (NB)	Mar 15,	Nov 10	Extended-Range Audio Oscillator* (Hedge)	Dec	36	R-TV Guild (L.I., N.Y.) Backs (Tech News)	May	125
Anti-shoplifter Device (Pat)	Oct	160	Extra TV Service, How to Sell It (Mandl)	Jan	48	Sought in Norwalk (Conn.)	Feb	110
Amplification—See also Semiconductors			Facsimile Speeded (NB)	Aug	14	TESA-Chicagoand Backs (Tech News)	Jul	101
Technique, New (NB)	Apr	6	500-Million-Mc Transceiver* (Pallatz)	Oct	93	TSA (Washington) Favors (Tech News)	Sep	135
Two New Approaches to (Leslie)	Nov	32	Flat TV Tube (Leslie)	Mar	43	Troy (N.Y.) Studios (Tech News)	May	124
Audio Vision (What's New)	Feb	41	Flexibility Unlimited (Colaguri)	Feb	32	Light Meter for Electronic Flash* (Slaughter)	May	62
Battery (ies)			Flyback and Sweep Circuit Testers (Scott)	Jul	42	Locating Intermittents (Boller)	May	94
Electricity From Gases (NB)	Nov	6	F			Loudspeakers and Acoustic Fundamentals (Klipsch)	Oct	44
Nuclear (What's New)	Apr	47	BUY OF THE YEAR!			Correspondence May 18, Jul 14, Aug 22,	Sep	18
Radioactive, Long-Life (Pat)	May	113	35			Loudspeakers of the Future (Shirley)	Nov	44
Smaller and Better (What's New)	Apr	46	1951			Low-Cost Remote Amplifier* (Jordan)	May	34
Solar, Charger (Pat)	Nov	154	SERVICE DRIFT			Low-Noise TV Booster* (Lange)	Nov	52
Storage Cells, Miniature (What's New)	Feb	41	1951			M		
Sun, Multiple (Turner)	Nov	38	1951			Meters—See Test Instruments		
Bicycle Horn* (Gottlieb)	Apr	80	1951			Modern Flyback Circuits (Dines)	Oct	132
Camera, Radio-Triggered (What's New)	Sep	45	1951			Modern Phono Cartridges (Hirsch)		
Clock, Cordless (Pat)	Nov	153	1951			Part I—Types of Pickups, Variable-Reluctance Cartridges	Apr	37
Controls			1951			Part II—More Variable-Reluctance Cartridges	May	36
Electrochemical device (NB)	Aug	12	1951			Part III—Moving-Coil Magnetic Cartridges	Jun	34
Fuel (What's New)	Feb	41	1951			Part IV—Amplitude-Responding Types	Jul	36
Humidity (Bartholomew)	May	81	1951			Modern Touch in Circuit Kits (Leslie)	Feb	78
Moisture Meter, Portable* (Parks)	Apr	61	1951			Modernize Your AM-FM Receiver (DiElsi)	Mar	105
Correction	Sep	100	1951			Modulator-Amplifier, 6-Transistor, Delivers 10 Watts* (Hamlin)	Aug	47
Counter			1951			Monitoring Sputnik (Scott)	Dec	40
Photodiode (REC)	Jul	117	1951			More About Transistor Types (Penfield)		
Scintillation, Transistorized* (Kueker)	Mar	34	1951			Part I—How Drift, Unijunction Transistors Work; Manufacture of Alloy and Diffusion Types	Nov	35
Crevasse Detector (NB)	Jun	8	1951			Part II—Manufacturing Micro-alloy, Grown, Junction, Rate-Grown, Grown-Diffused, Meltback Types	Dec	108
Crossword Puzzle (Henry)	May	56	1951					
Crystal Oscillator, Transistor (Pat)	Apr	108	1951					
Diamond Grinding of Needles (What's New)	Sep	45	1951					
Dog-Training Device (Pat)	Dec	129	1951					
Electricity in Air Less (NB)	Nov	12	1951					
Electroluminescent Lamp (NB)	Mar. 15,	Sep 6	1951					




"You sure charge plenty! Smith's TV used to do my servicing for half your rates right up to the day it went bankrupt."

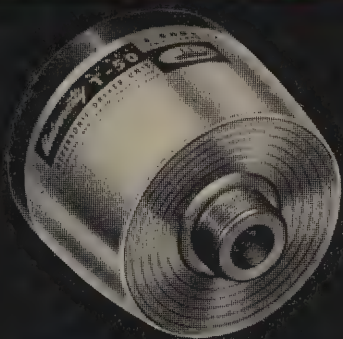NEWEST *University* achievements in High Frequency reproduction!



NEW HYPERSONIC T-50 DRIVER*

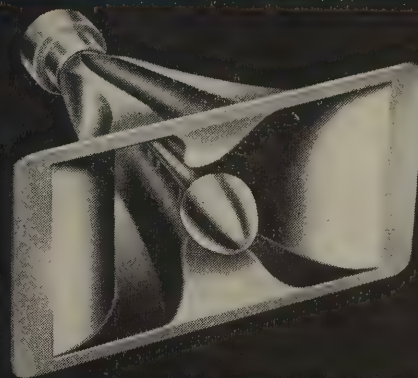
Smooth, distortion-free sound reproduction from 600 cps to inaudibility!



NEW RECIPROCATING-FLARE† H-600 HORN

Uniform, wide-angle dispersion of sound over the entire operating range!

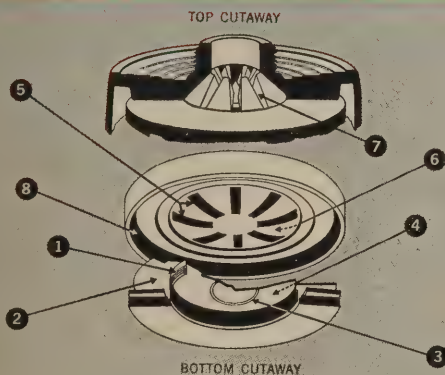NOW - add the T-50 Driver or H-600 Horn to improve your existing equipment . . . or, achieve the ultimate in high frequency performance by using the T-50 and H-600 together




Exclusive features of the T-50

① Individually-wound aluminum voice coil has maximum high frequency efficiency. ② Placed at the rear, enclosed side of diaphragm protects it against external damage and foreign matter. ③ Diaphragm is zonally re-enforced with concentric rib for maximum piston action, ④ and has convex radiating surface that achieves maximum uniformity of high frequency path lengths into mixing chamber. ⑤ Radial apertures in new phase-matching mixing chamber transmit all path lengths equally, ⑥ and reduce radial transmission impedance between diaphragm and mixing chamber surface, permitting tight spacing of diaphragm to mixing chamber surface for high frequency extension. ⑦ Constant cross-sectional area of die-cast mixing chamber apertures provides perfect acoustic match from diaphragm to throat of horn. ⑧ Diaphragm and mixing chamber are rim-centered on magnetic pot structure for optimum voice coil and gap alignment.

SPECIFICATIONS: Response: 600 cps to inaudibility; Recommended crossover: 700 cps; Power capacity: 50 watts, integrated program; Diameter: 4¼"; Depth: 4½"; Throat: 1½"—18 thread; \$49.50 net

* Patent pending

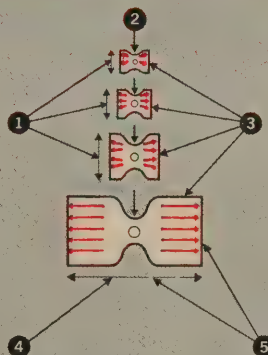


Exclusive features of the H-600

① Initial expansion of precision die-cast aluminum horn grows larger and larger in vertical direction ② while central contouring profiles get deeper and deeper ③ building up sound pressure more and more into the horizontal direction ④ and when contoured sound has been fully developed within horn, horn expansion in the horizontal direction takes over ⑤ until both ultimate expansion of horn and sound pressure are coordinated in the horizontal plane at the mouth ⑥ which is designed large enough to present a smooth radiation characteristic down to the lowest wave lengths ⑦ and where a radiating plane wave front equalizer ⑧ smoothens out the wave front to give an even, wide horizontal sound pattern.

SPECIFICATIONS: Air column: 7¾"; Horn Cut-off: 600 cps; Recommended crossover: 700 cps; Dispersion: 125° horiz. x 55° vert.; Bell mouth: 8¾" x 4¾" over-all; Depth (less driver): 7¾"; Throat: 1½"—18 thread; \$18.00 net

† U.S. patent #2,690,231

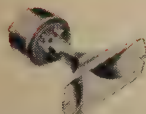More University tweeters, mid-range horns and drivers . . . for maximum versatility of application and flexibility of operation



MODEL HF-206



MODEL UXT-5



MODEL 4401



MODEL T-30



COBREFLEX

LISTEN

University sounds better



UNIVERSITY LOUSPEAKERS, INC., 80 SOUTH KENSICO AVE., WHITE PLAINS, N. Y.

DECEMBER, 1957

HF-206 Hypersonic Tweeter. Response to inaudibility. Crossover 5000 cps. Wide angle "reciprocating flare" die-cast aluminum horn. 8 ohms \$33.00 net.

UXT-5 Super Tweeter. Crossover 5000 cps up. Wide-angle response to 17,500 cps. 8 ohms. \$21.00 net.


4401 Tweeter. Crossover 2500 cps up. Wide-angle response to 15,000 cps. 8 ohms. \$18.00 net.

T-30 High Frequency Driver. As tweeter with H-600 in 2-way system; as mid-range with H-600 or Cobreflex in 3 or 4-way. Response: 200-15,000 cps. 8 ohms. \$30.00 net.

Cobreflex Horn. Crossover 350 cps up. Exclusive twin-flared 27" exponential air column. Dispersion: 120° x 60° Heavy precision aluminum die casting. \$23.00 net.

ANNUAL INDEX (Continued)

Multichannel Amplification (Scott)	Jun	30
Multichannel Electronic Crossovers* (Crowhurst)	Dec	52
Multiplexing and You (Lewis)	Oct	89
N		
Negative Feedback Controls Selectivity	May	44
Neon Lamps, Using (Clawson)	Dec	112
O		
Organizing a Profitable Home Servicing Business (Garrett)	Sep	94
Oscillators—See Test Instruments		
P		
Peaking in Color TV Bandpass Amplifiers (Centerville)	Jan	54
Pedro, Layman (Slaughter)	Sep	87
Phase-Shift Comparator Measures Frequency Ratios, Modulation* (Pugh)	Nov	118
Phase-Swing Vibrato Easy to Build and Apply* (Dorf)	Mar	57
Phone Cable to Hawaii (NB)	Dec	6
Phono Preamp Compensates for Cable Capacitance* (Montgomery)	Dec	47
Photographic Timer, Binary* (Rymsha)	Dec	106
Photo-Sound Unit* (Vogelgesang)	Oct	64
Portable Moisture Meter* (Parks)	Apr	61
Correction	Sep	100
Portable TV Pattern Generator* (Hansen)		
Part I—Crystal Control, Positive Lock-in	Jan	119
Part II—Construction Details	Feb	54
Part III—Adjustment, Operation	Mar	62
Power Factor, What It Means (Manly)	Jul	82
Power-Line Spikes and Buzz (Reed)	Sep	43
Practical Color TV Installation (Middleton)		
Part I—Fuzzball Needs a Little Help	Sep	107
Part II—Purity, Degaussing, Convergence	Oct	116
Part III—Horizontal Dynamic Convergence	Nov	61
Printed Circuits		
Resistor (Pat)	Jul	114
Television		
Antenna (What's New)	Apr	47
Circuitry (Clinic)	Jul	57
Connection Repair (Clinic)	May	109
Interaction (Clinic)	Aug	36
Parts Replacement (Clinic)	Aug	35
Proper Adjustments Keep Viewers Happy (Davis)	Jan	76
R		
Radar		
Anti-Collision (NB)	Mar 15,	Nov 10
Food Preservation (What's New)	Aug	54
Headphone (What's New)	Jan	136
Interference (QB)	Sep	143
Map of Flight Position (NB)	Oct	14
Signal Enhancement (NB)	Oct	10
Texas Towers Guard Our Coasts (Brooks)	May	54
Traffic Control (NB)	Feb	8
RADIO		
Alerting Device (Pat)	Oct	158
Amateur		
80-Meter Novice Converter for Broadcast Receivers (QB)	Feb	120
500-Million-Mc Transceiver* (Pallatz)	Oct	93
Headset Booster, Assemble This* (Louis)	Sep	38
10-Meter Transistor Rig Goes Vfo* (Reed)	Sep	58
30-Mc Transistor Superregen* (Bohr)	May	57
Transistor Shortwave Receiver* (Braunbeck)	Aug	84
Transistorized Rig Works 10-Meter Dx* (Griffith)	May	60
Correspondence	Aug	22
Antenna, FM (REC)	Nov	141
Battery Eliminator* (Rhita)	Mar 109; (REC)	Dec 118
Headset Booster, Assemble This* (Louis)	Sep	38
Kits, Modern Touch in Circuit (Leslie)	Feb	78
Low-Voltage Supply, Transistor* (Queen)	Oct	95
Modulation Control (Pat)	Nov	153
Multiplexing and You (Lewis)	Oct	89
Old Radios, Those	Sep	55
Oscillating Oscar (Von Zook)	Jan	133
Oscillator, Gated-Beam (Cohn)	Sep	59
"Pill" Transmits From Inside You (Leslie)	Jun	45
Power Supply, Experimenter's* (Hughes)	Jul	50
Quiz, Wrong (Gnessin)	Feb	81
Correspondence	Jun	14
Radiation, FM (NB)	Jun	10
Receivers, Tuners		
Ac, Straight for G-E 250 (QB)	Sep	143
Afc Improves FM (Heathkit FM-3)* (Montgomery)	Jan 123; (QB)	Apr 123; Jul 53
AM-FM Tuner, Modernize Your (DiElsi)	Mar	105
Amplifier, Mobile, for Tuner (QB)	Mar	128
Auto		
Heater Supply, Variable Dc, Uses Tuned Filters* (Sanford)	Mar	102
PA (QB)	Aug	114
13-Transistor (What's New)	Jun	49
Transistorized and Hybrid (Darr)		
Part I—New Tricks or "Look, Maw, No Vibrator!"	Nov	98
Part II—Printed-Circuit Boards; Some Special Circuitry	Dec	42
Bfo, Low-Noise (REC)	Aug	120
CD Monitor* (Mendelson)	Sep	56
Converter, 80-Meter Novice, for Broadcast (QB)	Feb	120
Discriminator, Stabilized (Pat)	Sep	142

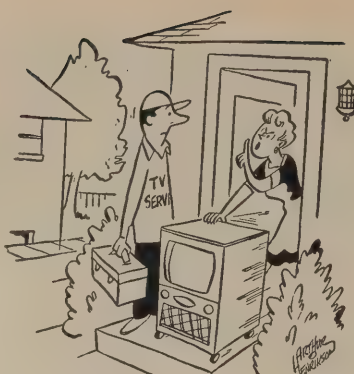

"The baby's asleep! Fix it out here!"

Dynaflex Broadcast Receiver, Build a* (Tooker)	Feb	82
Correspondence	Apr	16
FM		
AM, Modernize Your (DiElsi)	Mar	105
Amplifier, Mobile, for (QB)	Mar	128
Antenna (REC)	Nov	141
Boosting 152-162-Mc Signals (REC)	Dec	118
Easy-to-Align! (Abbatecola)	Jul	54
Radiation (NB)	Jun	10
Radio, Pocket-Size (What's New)	May	47
Afc Improves (Heathkit FM-3)* (Montgomery)	Jan 123; (QB)	Apr 123; Jul 53
Tuning Indicator (QB)	Jul	109
Free-Power* (Hollmann)	Apr	85
Frequency-Changer, 2-Tube†	Apr	49
If Transformers, Defective (Garrett)	Apr	97
Interference		
Broadcast-Set Front End Traps If* (Ives)	Aug	60
Radar (QB)	Sep	143
Power Supply		
Ac-Dc* (Pearce)	Dec	46
Hum Cancelling†	Apr	49
Regenerative, Uses New SB Transistor* (Bohr)	Apr	100
Satellites, Tracking US (McQuay)	Dec	44
Shortwave, Transistor* (Braunbeck)	Aug	84
Signal-Powered (REC)	Oct	164
Solar-Powered, Helmet (What's New)	Aug	54
Sound in AM, Improving (Stratmoen)	Mar	60
Sputnik, Monitoring (Scott)	Dec	40
Superregenerative (Pat)	Nov	153
TRANSISTOR		
Auto		
13-Transistor (What's New) and Hybrid (Darr)	Jun	49
Part I—New Tricks or "Look, Maw, No Vibrator!"	Nov	98
Part II—Printed-Circuit Boards; Some Special Circuitry	Dec	42
Free-Power* (Hollmann)	Apr	85
Has Rf Stage (Pugh) (Corres)	Apr	16
Pocket		
Adding a Speaker to (Queen)	Jan	144
Operates Speaker* (Queen)	Jun	42
7-Transistor* (Granoff)	Nov	84
2-Transistor* (D'Airo)	Mar	97
Portable, Operates Loudspeaker* (Rhita)	Jan	134
Servicing (D'Airo) Apr 92; (McRoberts)	Nov	103
Shortwave Regenerator* (Bohr)	Jan	21
(Corres)	Feb	129
Superregenerator (Pat)	May	57
30-Mc* (Bohr)	May	60
10-Meter Dx, Works* (Griffiths)	Aug	22
Correspondence	Sep	58
10-Meter Rig Goes Vfo* (Read)		



"Give me a .01 tubular, Joe, and plug this in, will you?"

Refrigerated (What's New)	Jan	136
Robot Broadcaster (What's New)	May	47
Schematic—Zenith 500 Royal	Apr	92
Servicing—See also Servicing; Technotes; Try This One		
Heater String, Misleading (Woychowski)	May	59
Old Timer's Hint (Corres)	Aug	20
Things Ain't Always What They Seem (Darr)	Aug	78
Transistor Radios (D'Airo) Apr 92; (McRoberts)	Nov	103
Tricks of the Trade (Layden)	Sep	60
Vtvm Measures Ac Amps (Lederer)	Aug	85
Signals, Reflected (NB)	Jul 6,	Aug 6
Stereophonic Broadcast (NB)	May	16
Sunspots and Disturbances (NB)	Jul	6
Transceiver, 500-Million-Mc* (Pallatz)	Oct	93
Transistor—See also Radio, Receivers		
L-C-R-Coupled Circuits (Pugh)	Jun	44
Tuners—See Radio, Receivers		
TV Sound Tuner* (Graham)	Jun	46
Correction	Oct	99
Typewriter Sends Morse Code†	Aug	53
Voltage Regulators, Selenium Diode* (Gnessin)	Jun	48
Volume-Control Circuit (Pat)	Sep	140

RADIO-ELECTRONIC CIRCUITS

Acc, Keyed British	Feb	126
Antenna, FM	Nov	141
Battery Eliminator	Dec	118
Bfo, Low-Noise	Aug	120
Biased, Dyna	Oct	165
Blinker, Neon Novelty	Sep	148
Boosting 152-162-Mc Signals	Dec	118
Continuity Tester for Series Tubes	Jan	171
Counter, Photo-diode	Jul	117
Doubler, Full-Wave	Jan	171
Frequency Indicators	Feb	127
Garage-Door Operator, Light Switch Controls	Nov	141
Low-Volter	Apr	127
Marker Pips, Polarized	Jun	102
Milvamp Revamped	Jun	99
Oscillator		
Audio, Stable	May	136
R-C	Mar	138
Phasing Earphones	Dec	120
Phono Amplifier, Transistor	Jul	116
Pulse		
Amplifier	May	135
Probe for Vtvm	Aug	120
Relay		
Frequency-Sensitive	Jul	116
Impulse	Nov	142
Quieting	Mar	137
Sound-Operated With Adjustable Time Delay	Jan	172
Resistance-Measurement Bridge	May	134
Selenium Rectifier Protection	Mar	136
Side-Tone Circuit	Jun	98
Signal-Powered Set	Oct	164
Tape-Recorder Monitor	Apr	127
Voltage-Step Indicator, Neon	Aug	121
Record Tracking (Crowhurst)	Oct	40
Records, etc—See Audio		
Relay		
Averts Toyland Tragedy* (McRoberts)	Dec	102
Frequency-Sensitive (REC)	Jul	116
Impulse (REC)	Nov	142
Polarized, Inexpensive (Lasker)	Feb	63
Ratchet (QB)	Sep	144
Sensitive, Saves Standby Power* (Driver)	Oct	84
Sound-Operated, Has Adjustable Time Delay (REC)	Jan	122
Sync-Triggert	Apr	49
Remote the TV Speaker (Sodaro)	Aug	39
Remote Controls		
Garage-Door Operator, Light Switch Controls (REC)	Nov	141
2 Channels? Easy* (Safford)	Oct	82
Touch-Plate Controller* (Sandretto)	Sep	61
Zauberschalter (What's New)	Jan	49
Rf Capacitance Meter* (Queen)	Mar	95
Rhomboids for TV Reception (Kline)	May	56

S

Satellites, Tracking US (McQuay)	Dec	44
Saturable Reactor Controls Sweep Generator (Scott)	Apr	39
Second Speaker Adds Realism (Crowhurst)	Mar	52
Selenium-Diode Voltage Regulators* (Gnessin)	Jun	48
Self-Calibrating Marker Generator* (Graham)	Jan	112
Semiconductors—See also specific subject; Transistors		
Amplification, 2 New Approaches to (Leslie)	Nov	32
and New Tubes Jan 166, Feb 116, Mar 126, Apr 118, May 121, Jun 115, Jul 99, Aug 104, Sep 137, Oct 155, Nov 137, Dec 122		
Chloroplasts as (NB)	May	12
Selenium Diode Voltage Regulators* (Gnessin)	Jun	48
Silicon-Carbide Low-Temperature Rectifier (NB)	Jul	6
Silicon Junction Diodes (Rhita)	Jun	85
Silicon, Ultra-Pure (Pat)	Jul	115
Spacistor (NB)	Sep 6; †Nov	32
Thermo-compression Attachment of Leads (NB)	Oct	10
Thyristor (NB)	Dec	6

A merely insert
card in slot

B flip power lever to
"power-on" position

C press calibrate
lever and adjust
calibration control


simple as **A-B-C**...

NEW RCA WT-110A AUTOMATIC TUBE-TESTER

means more service profits!

Dollar for dollar, feature for feature, you'll find RCA's WT-110A the fastest, most accurate automatic punched-card tester you can buy today. It's a virtually *obsolescence-proof design* ... from the exclusive RCA 700-card capacity magazine file that always keeps the pre-punched cards in type number sequence, to the fully automatic circuit setup (including *all* operating voltages) and the easy, do-it-yourself punch card accessories available to keep the tube-card file up-to-date!

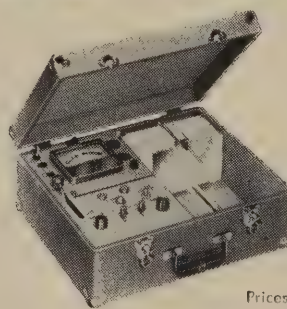See and test the WT-110A at your local RCA Distributor. Prove to yourself what a boost in business, prestige, profits the RCA-WT-110A can mean!



All this for
\$199.50

USER PRICE (Optional)
Prices higher in Hawaii and Alaska

- automatically sets up socket connections, and all operating voltages such as heater, signal, plate and screen voltages, and bias (both fixed and cathode).
- checks tubes for transconductance, gas, shorts, and leakage between elements.
- automatically selects correct conditions from 220 possible combinations of heater voltage (from 0.1 volt to 120 volts) at currents up to 4 amps., 10 bias voltages and 11 values of cathode resistors.
- tubes, such as rectifiers, tested under heavy load currents up to 140 ma per plate
- high-and-low sensitivity ranges for leakage tests.
- 12-volt plate and screen supply for testing new auto-radio tubes.
- meter protected against burnout.
- test card provided for checking instrument.
- 239 pre-punched cards supplied with instrument cover 95% of currently active TV tubes. Pre-punched accessory cards available.
- active card magazine capacity—350; storage capacity—350...a total capacity of 700 cards.



**TEST EQUIPMENT
RADIO CORPORATION OF AMERICA**
Electron Tube Division, Harrison, N. J.

ANNUAL INDEX (Continued)

Sensitive Relay Saves Standby Power* (Driver)	Oct 84
Servicing—See also specific subject	
Basement and Part-Time Technicians (Corres)	Jan. 22, Feb. 16, Apr 17, Jun 14, 16, 18, Sep 22, Oct 22
Do-It-Yourself (Corres)	Sep 18
Manufacturer's (Corres) Jan 21, Mar 24; (Tech News) Jan 164, Feb 107, 112, Apr 120, May 125	
Servicing Color TV Gating Circuits (Waner)	Jan 70
Servicing Gated-Beam Discriminators (McRoberts)	Aug 37
Servicing Modern Damper Circuits (Mandl)	Jul 59
Servicing Transistor Radios (D'Airo)	Apr 92;
(McRoberts)	Nov 103
Shortwave Transistor Regenerator* (Bohr)	
(Corres)	Jan 21
Simple Method Checks Coil Inductance (McCready)	Sep 54
Simple Power-Transistor Test (Caldwell)	Sep 51
Sine-Square-Wave Generator* (Queen)	Apr 42
60-Watt Amplifier Uses New KT88's* (Steckler)	Aug 43
Speech-Music Discriminator (Predmore)	
(Corres)	Jan 21, Feb 10
Sputnik, Monitoring (Scott)	Dec 40
Squelch That Blurb* (Schulke)	Jun 78
Sunspots	
Study (NB)	Jul 6
and TV (West)	Aug 33
TV Dx (Cooper) Jan 80, Mar 49, May 111, Jul 76, Sep 117, Nov 55	
Surveillance Kit, Electronic* (Garner)	
Part I—Amplifier, Rf and Inductance Pick ups	Sep 81
Part II—More Pickups; Accessories	Oct 62
Sweep Tube, TV's Workhouse (Hamlin)	Apr 50
Switch Probe for Rapid Measurement* (Frantz)	Sep 53
Symbols—See Abbreviations and Symbols	
Synchronized Color Subcarrier Signal Generator* (Novak)	Jun 53
Syncopation by Automation (Klein)	Jun 36

T

Tacan Data Link (NB)	May 8
Tall-Tower Techniques (Darr)	
Part I—Assembly; Guy Wires; Location	Jan 56
Part II—Assembly; Erection	Feb 48
Tape Recorders—See Audio	

TECHNOTES — See also specific subject, servicing. (Unless otherwise noted, references are to Technote Dept.)

Cabinet Finishes Marred (Magnavox Syntex)	Feb 124
---	---------

RADIO


Auto Antennas	Jun 121
Battery Operation (RCA 65BR)	Feb 125
Drift, Intermittent (Motorola 705 Auto)	Sep 151
FM Discriminator Sensitivity Loss	Feb 123
Shortwave Reception (RCA 7-BX-10 Portable)	Jun 122
Static Noise (Crosley R-104)	Jan 176
Tuning Capacitors Noisy	Apr 124
Volume Drop (Majestic 2C60P)	Apr 125
Wafer-Switch Repair	Aug 76

TAPE RECORDER

Fan Blades	May 130
Hum (RCA 7-TR-2, -3, TRC-1)	Jun 120
Takeup Tension (RCA 7-TR-2, -3-TRC-1)	Jun 120

TELEVISION

Adjacent-Channel Trap (Bendix T19)	Mar 135
Arc wandering (RCA CTC5N)	Nov 148
Antenna	
Gonset-Line Match (Clinic)	Oct 124
Line Check	Sep 152
Arcing	
Audio Socket (Trav-Lar 1710) (Clinic)	Apr 55
In Picture (Hoffman Colorcaster 706)	Jan 176
Intermittent (Sylvania 1-532) (Clinic)	Jan 68
Picture Tube Feb 123; (Motorola)	Apr 126
B Plus High (Olympic 766) (Clinic)	Oct 128
Beam Eliminator (Westinghouse V-2344) (Clinic)	Mar 51
Brightness	
Excessive (Admiral 22C2) (Clinic)	Jul 58
Lacking (Crosley 473) (Clinic) May 108, (Admiral 21F1)	Jun 76
Buzz (Crosley AT-10M)	Oct 150
Channel Switch (Westinghouse H-827T21)	Jun 122
Color	
Change (RCA CTC5)	Jul 111
Convergence (Motorola TS-902)	Jan 177
Fringing (Motorola TS-902)	Aug 122
Killer Adjustment (Stromberg-Carlson K-1) (Clinic)	Sep 106
Killer Control (Sylvania 15-inch)	Jul 111
Out (Raytheon)	Mar 134
Sync Poor (RCA 21-CT-663U)	Nov 149
Weak or None (RCA 21-CT-663U)	Nov 147
Compression (Truetone 2D1530B)	Oct 151
Convergence (Hoffman 703)	Sep 152
Crystal Bias in Uhf Tuner (Motorola WTT-81) (Clinic)	Apr 55
Drive Excessive (Sylvania 1-515) (Clinic)	Dec 94
Field Coil Resistance?	Dec 135
Fine Detail Poor (Magnavox CT-358BA) (Clinic)	Nov 56

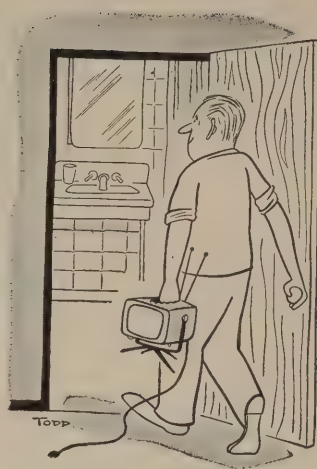

Front-End Fault (Sylvania 15-inch)	Oct 150
Global Resistor (G-E 17C125) (Clinic)	Jan 68
Ground Waves	Jun 76
Heater-String Modification (Clinic)	Feb 53
High Voltage	
Fuse (RCA KCS96)	Sep 151
Intermittent (Philco 50T1400) (Clinic)	Jan 69
Missing (RCA 21CT660 Color)	Jan 176
(Westinghouse H-626T16)	May 129
Rectifiers	Sep 152
Regulation (Du Mont RA-340/341, 342/343)	Apr 126
Regulator (TTO)	Sep 148
Transformer Replacement	May 149
Horizontal	
Curve (Philco 22D4162) (Clinic)	Nov 57
Drift (Crosley 431-1) (Clinic)	Jan 68
Drive	
Excessive (Sparton 15V215) (Clinic)	Sep 104
Line (Philco 7L40)	Dec 134
Range (Crosley 472) (Clinic)	Sep 106
Stabilization (Clinic)	Feb 53
Dynamic Convergence Lost (Motorola TS902-A)	Nov 148
Oscillators	Jun 120
Hunt (Emerson 120245DN) (Clinic)	Aug 36
Pull (Philco D-201) (Clinic)	Nov 56
Width (Stromberg-Carlson 421) (Clinic)	Jan 69
Interchangeability of 6BQ6, 6CU6, 6DQ6 (Clinic)	Aug 36
Interference on All Channels (RCA 21-CT-660U Color)	Apr 126
Intermittent Oscillation (Emerson)	Dec 133
Long-Range Reception (Clinic)	Oct 129
Parasitic Oscillations (Westinghouse V-2342) (Clinic)	Jul 58
Patch Cable (Sylvania 1-521, -533) Picture	May 130
Detector Failure	Apr 125
Everything Gone (G-E 805)	Nov 147
Flashes (Pacific Mercury 150) (Clinic)	Jun 61
Gone (DuMont RA-165)	Dec 135
Narrow, Brightness Down (Zenith Z-222C)	Nov 14
Not Centered (Philco 51T1601)	Apr 125
Pulling (Du Mont RA-340/341, 342/343)	Apr 126
Smear (Du Mont RA-370/371) (Clinic)	Aug 36; (Packard-Bell 88S1) (Clinic)
Streaks, Intermittent (Motorola 14T4)	Apr 124
Tube Off Center (Westinghouse V-2287)	Sep 150



"First high-fidelity hearing aid on the market!"


Popping Noise (Hoffman Colorcaster 706)	Jan 176
Power-Transformer Hum (Olympic DA) (Clinic)	Jul 58
Printed-Circuit	
Connection (Clinic)	May 109
Interaction (Clinic)	Aug 36
Raster Reduced (RCA 2T51) (Clinic)	Jan 69
Ringing (Pacific Mercury 150) (Clinic)	Dec 93
Sensitivity Increasing (Sylvania 1-520) (Clinic)	Sep 104
Snivets (Capehart CX-43) (Clinic)	May 110
Sync	
Buzz (Philco TV-300) (Clinic)	Jun 61
Improvement (Admiral 22C2) (Clinic)	Mar 51
Intermittent (G-E 14007) (Clinic)	Nov 57;
(Westinghouse V22431) (Clinic)	Nov 57
Poor (Bendix 21K3) (Clinic)	Nov 57
Tilt Control Shorted (Motorola TS-902)	Sep 150
Transistor Portable (RCA 7-BT-10K)	Oct 150
Tuner (Admiral)	Oct 151
Cascade (RCA T120) (Clinic)	Sep 100
Remote (G-E 901) (Clinic)	Sep 103
Turret	Jul 112
Vertical	
Buzz (Motorola TS-216) (Clinic)	Jan 69; (Admiral, Motorola) (Admiral, Motorola)
Instability (Crosley H-1TTOWH) (Clinic)	Feb 125
Jitter (Bendix FM27C)	Jan 68
Linearity (Crosley 483, 484)	Aug 122
Nonlinearity (Clinic)	Feb 124
Roll (Admiral 24E1) (Clinic) Nov 57; (G-E 21C200) (Clinic) Nov 57; (RCA 1956 Printed-Circuit Chassis)	Oct 129
Size Change (Du Mont RA-340/341, 342/343)	Jun 122
Sweep Loss, Reduced Raster (Crosley 466) (Clinic)	Apr 126
Sync	Apr 55
Instability (Philco TV-350) (Clinic)	Dec 94
Loss (RCA KCS83) (Clinic)	Feb 53
Video Detector Crystal (Du Mont 340/341, 342/343)	Mar 135
Voltage Vanishing (Du Mont RA109)	Sep 151
Volume	
Reduced, Excessive Hiss (RCA KCS47)	Apr 125
Weak With Smearing (Philco Rf 97)	Mar 134
Weak Signal and Oscillator Drift	Mar 134
Width	
Fluctuating and Monkey Chatter (Capehart CX-33)	Jul 111
Loss of (Setchell-Carlson 151) (Clinic)	Jan 69
Yoke Defective (RCA 7T104B) (Clinic)	Jan 69
TEST INSTRUMENTS	
Meter Response (Hickok 534)	Feb 124
Shorts, Excessive (Hickok 534)	Feb 123
Correspondence	Jul 14
Trace Dimming (Heath Scope OM-1)	Jun 121
Vtvm	
Erratic	Jul 113
Low Voltage Reading (EICO 221)	Aug 123
Telemetering, Lifeline of Guided-Missile Research (Brooks)	Apr 56
TELEVISION	
Agc from Sync Clippert	Jan 63
Amplifiers	
Bandpass, Peaking in Color (Center-ville)	Jan 54
Triode Sound If (Emerson)†	Jan 60
Video, Push-pull, Doubles Picture Signal (Libes)	Apr 53
Antenna	
Adding Stack (QB)	Mar 130
Helical, for Uhf (QB)	Jul 109
Printed Circuits in (What's New)	Apr 47
Rhomboids for TV Reception (Kline)	May 86
Correction	Jun 119
Stubs (Clinic)	May 106
Systems (Selling)†	Jan 49
Tall-Tower Techniques (Darr)	
Part I—Assembly; Guy Wires; Location	Jan 56
Part II—Assembly; Erection	Feb 48
Audio Quality (Selling)†	Jan 49
Auxiliary TV Circuits, Understanding (Garrett) (Part I)	Dec 80
Bilingual†	Aug 52
Bi-Trans, 2 Programs to Channel (NB)	Nov 6
Booster	
Dual Cascade (QB)	Jan 174
Low-Noise* (Lange)	Nov 52
Circuits, Most Useful 1957	Jan 84
Closed-Circuit, Penn Station (What's New)	May 47
Color	
Installation Problems (Middleton)	Dec 58
Peaking in Bandpass Amplifiers (Center-ville)	Jan 54
Practical Installation (Middleton)	
Part I—Fuzzball Needs a Little Help	Sep 107
Part II—Purity, Degaussing, Convergence	Oct 116
Part III—Horizontal Dynamic Convergence	Nov 61
Servicing—See Television, Servicing; Test Instruments	
Tape Recording (NB)	Jan 14
3-Dimensional (NB)	Oct 6

"HUNTERS & SPORTS HEATERS"

Kerosene or Gasoline Heater Reduced to \$4.95


Brand new, Evans blue flame heater. Output approx. 50,000 BTU. Ideal for garage or shack where not confined. Size: 10" dia. x 12" high. Cost Govt. many times our low price. Shipped in orig. packing; wt. 47 lbs. \$4.95

HRU-28A GENERATOR—\$79.50

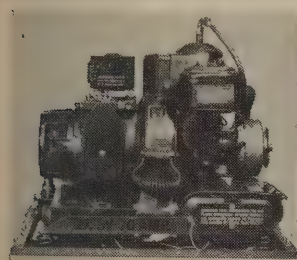

Homelite gasoline generator 28.5 V. DC at 2 KW. 3400 RPM motor speed. Electric or rope start. Use to power surplus aircraft radio equipment, cabin or marine power, aircraft starting, etc. These units rebuilt like new by the U.S. Air Force and have not been run since. Size 21 1/2" x 21 3/4" x 17 1/4". Original AF boxed. Guaranteed. Ship. wt. 210 lbs. Instruction book included.

RC-58-B FACSIMILE SET—\$59.50 ea.

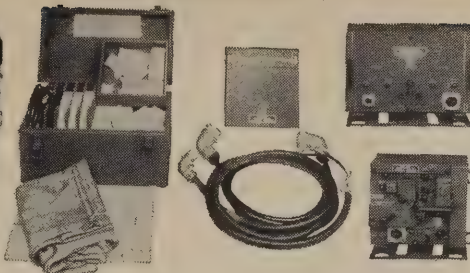


Brand new, complete, ready to operate by connecting to 12 V. DC source. Spare parts included with ample supply of ink and paper. Transmits and receives and prints, signatures and copy. Ideal for loan offices, banks or other businesses where signatures must be verified, etc. Use two sets together with 2 wires telephone line or radio carrier between. Cost Govt. approx. \$6000. Your price, in original packing, only \$59.50 ea. Ship. wt. approx 300 lbs.

TU-10B TUNING UNITS \$2.50 ea.




Brand New TU-10B tuning units for the BC-191 or 375 transmitter. The popular one for parts and case. Size 1 1/2" x 7 1/2". Ship. wt. 15 lbs.

LEEDS & NORTHRUP MICROMAX RECORDERS

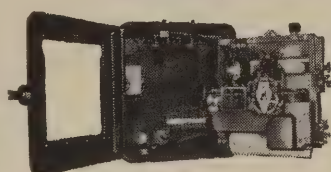

Strip type recorder used for controlling and recording wide variety of processes. Used originally for temp. range of 350-550° C. but may be changed for other applications. Operates on Wheatstone bridge principle using AC galvanometer movement. Original cost several times our low price. Removed from demilitarized equipment which in many cases was new. Sold as used but guaranteed, or money back if not satisfied. Ship. wt. approx. 165 lbs. \$179.50 ea.

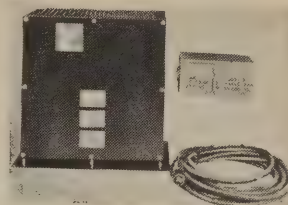30 AMP. BATTERY CHARGER WHILE SUPPLY LASTS—\$12.50 ea.



Cost Government \$300 ea. Our purchase of large quantity allows this bargain. Ward Leonard Mfgd. Type ED 33510. Charging rates up to 30 amps. on 12-30 volt battery combinations (6-15 cells). Operates from 110 V.D.C. Size 20" wide x 20" high x 10" deep. Shipped in original overseas pack with spares and cord. Wt. 65 lbs. Ship. wt. 145 lbs.

Receiver R-1/ARR-1—\$1.95


A two-stage RF superhet converter in range of 234-258 Mc. Ideal for conversion to various preselectors, ham 220 Mc. converter, or other uses. Uses 4-954 acorn tubes supplied. In compact aluminum case 10" x 3 1/2" x 3". Filaments operate from 12 or 24 V. by merely throwing switch contained in unit. Complete with conversion article as in Jan. 1949 "Radio-TV News." Brand new demilitarized units (input coil insulation broken—easily repaired). Used units that are not demilitarized also available—specify new or used. Ship wt. 4 lbs.

Price \$1.95 ea. 12 or 24 V. co-axial antenna relay for above or other mobile transmitter-receiver equip. New \$1.25 ea.

M-1 Odograph, over \$5,000 value—\$89.50

See Nov. 1944 Electronics for Full Description

This is a survey instrument for automatically drawing a map of the terrain over which the jeep or other vehicle to which it is attached traverses. These instruments were currently by Monroe Calculating Machine Co. and sold in excess of \$5,000. Our surplus purchase allows passing on these machines at this value. Order early, only 200 in stock. Units have been rebuilt by Corp of Engineers, U.S. Army and guaranteed good condition. Ideal for prospectors, oil companies, power line and farm use. Nothing else needed for operation except vehicle. Many are using the compass unit for automatic pilots on boats—many, many applications. A real machine. Ship. wt. approx. 300 lbs. Our Price \$89.50 ea.

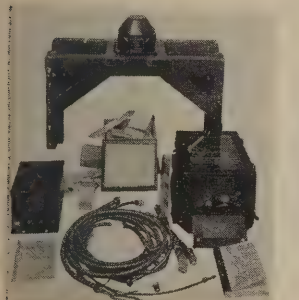


Freq. Crystals... Less Than 5¢ Ea.

Imagine crystals costing Govt. \$3.50 to \$12.50 ea. in this assortment. 100 brand new; various freqs.; plenty in ham bands. Practically all types of holders; all mounted; guaranteed to oscillate. Assortment of 100. Ship. wt. 4 lbs. \$4.95

Andover Power Plants \$185 ea.


This is the D2 plant that has been always in such great demand for use as portable welders and auxiliary power. Delivers 28.5 V. DC up to 200 amps. continuous. The lightweight aircraft type motor on these plants had a Govt. acquisition cost of \$2937.00 ea. Motor is 2 cylinder 4 cycle aircooled with hi-tension magneto type shielded ignition rated at 10 HP at 3200 RPM. Entire unit weighs approx. 125 lbs. Guaranteed good condition. Ship. wt. 300 lbs. Price \$185. Engines only from above plant for only \$125 ea. Ship. wt. 250 lbs.

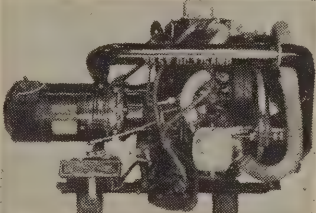

GOLF CAR MOTOR.....\$12.50
Brand New 6 v. 1/2" motor with separate terminals for armature & field to allow connection in series, shunt, or easy reversing. Approx. 5" dia. 10" length including 1 1/4" shaft extension. Shaft is 3/4" dia. Mounts by four 3/8" threaded studs 3/8" long on shaft end of motor.

Metal Locators—\$39.50

The famous SCR-625 mine detector which has been found to be unexcelled for locating hidden metallic objects such as pipes, treasure, etc. Hundreds in use by prospectors, mining companies, plumbers, veneer mills, etc. Comes complete in carrying case and checked ready for operation with addition of batteries below. Case size 28 1/4" x 16" x 8 1/4". Operating carrying wt. approx. 15 lbs. Ship. wt. 55 lbs. Price \$39.50 ea. Batteries for above SCR-625 \$4.25 set.

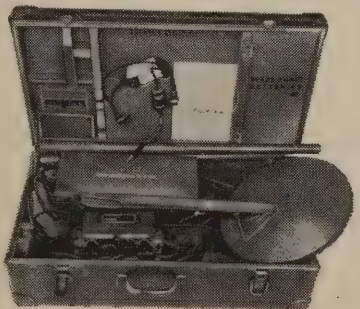


SYNCHRO MOTORS

\$2.95 ea.

110 V. 60 cycle

Purchase of a large quantity of these motors allows this special price. Navy type 5 synchros motors that cost the Govt. \$80 ea. Apply to many uses such as beam rotation and indication, weather vanes, etc. By merely hooking like wires of a pair of these together and applying 110 V. 60 cy. to the junction of the two Rotor wires, any movement applied to either shaft is repeated on the other unit which may be 100's of feet away. Units are used but guaranteed not burned out. Ship. wt. 7 1/2 lbs. ea. Order a pair for \$5.75.

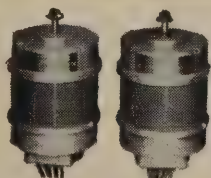

BC-604 Transmitter—\$9.95 ea.

30 watt crystal controlled on 10 preselected channels in range of 20-27.9 Mc. F3 emission. Operates from 12 V. or 24 V. DC (dynatron not supplied). Tubes and meter supplied worth the price of entire unit. Size 18" x 10" x 12". Excellent to new condition. Ship. wt. approx. 100 lbs. ea. Price \$9.95 each. Receiver and Transmitter combination \$25.00 set. Order a receiver and transmitter combination for mobile or fixed station or for wireless intercom.



Mobile Hams Attention!

6-12-24 V. VIBRATOR POWER SUPPLY \$9.95

PE-237 Non-synchronous vibrator type. Input: 6 V. 36 amp., 12 V. 17 amp., or 24 V. 9.5 amp. DC. Output: 525 V. DC, .095 amp., 1105 V. DC, 4.2 Ma., 6.5 V. DC 2 amp., 6 V. DC 1/4 amp., 1.35 V. DC, 450 Ma. Higher current drain may be obtained with no ill effect. This power supply has been successfully used for powering the BC 604 Xmt. below. Steel brown crackle case size 20 1/4" x 11" x 10". Ship. wt. 119 lbs. ea. Excellent to new condition. Price \$9.95 ea.



SURPLUS ENGINE—New—\$17.95

2.3 H.P. 2 cy. horizontal engine manufactured by or for Jacobsen. Ball bearing crankshaft. Weighs only 8 3/4 lbs. Attach your own coil and battery. Ideal for air-propelled boats, ice sleds, models, etc. \$17.95 Shipped as shown with propeller but less hub for attachment.

Storage Battery Pack—BB-208 \$3.50 ea.

Contains three 36 V. 18 cell lead acid batteries size 4 1/4" x 1-7/16" x 15/16". Wt. approx. 5 oz. ea. and one 6 v. 3 cell lead acid battery size 4-3/16" x 1 1/4" x 15/16" wt. 5 oz. All batteries dry charged and must be filled with 1.265 sp.g. sulphuric acid before use. (Acid not incl.) Ideal for models, vest packet transmitters and other compact service requirements. All new in vacuum sealed can. Ship. wt. of all 4 batteries 2 lbs.



TS-9 Handset—\$1.99

Ideal for your mobile rig. Contains 250 ohm rec. element and single button carbon mike transmitter unit. Will replace your T-17 hand mike or other SB mike. Excellent to new condition. Ship. wt. 5 lbs. Price \$1.99 ea.



ESSE RADIO CO. 42 WEST SOUTH ST. INDIANAPOLIS 25, IND.

DECEMBER, 1957

REMIT SHIPPING CHARGE AND INSTRUCTIONS WITH ALL ORDERS. OTHERWISE ORDER WILL BE SHIPPED EXPRESS COLLECT. ALL ITEMS GUARANTEED TO YOUR SATISFACTION OR MONEY REFUNDED IF RETURNED PREPAID WITHIN 10 DAYS OF RECEIPT

ANNUAL INDEX (Continued)

Commercial Killers		
Speech-Music Discriminator (Pat)	Jun	123
Correspondence	Jan 21, Feb	10
Squelch That Blurb* (Schulke)	Jun	78
Dx (Cooper)	Jan 80, Mar 49, May 111	Jul 76, Sep 117, Nov 55, Aug 53, Aug 33, Mar 124
And Fish		
Sunspots and TV (West)		
Target for Dx-ers		
Tips From a Dx-er's Notebook (Cooper)		
Transoceanic (Graf)	Nov	58
Educational (NB)	Jul	79
Electron-Gun Assembly, Low-Voltage (What's New)	Apr	46
Flyback Circuits, Modern (Dines)	Oct	132
Hearing Aid* (Cozzo)	Dec	78
Hot Chassis		
Death Rides the (Shunaman)	Oct	100
Don't Be a Shock Absorber (Glickstein)	Mar	46
Shocking Sink (Welz)	Aug	38
Kinescope		
Brightener (Pat)	Mar	139
Flat (Pat)	Jan	169
Medical Uses		
Cancer Defection (NB)	Mar	22
Endoscope (Pat)	Jun	123
Modular (NB)	Mar	15
Over-the-Horizon (NB)	Feb 8, May 8, Oct 6	Aug 54
Portable (What's New)		
Radiation (NB)	May 8: (QB)	Oct 127
Scare (NB)	Aug 6: (Corres)	Oct 16
X-Rays from TV Sets Corres	Dec.	16
Receivers, Trends in 1956-57 (Scott)	Jan	60
Remote Controls, 2 New (Maxwell)	Feb	42
Schematics		
Admiral 18Z41 (18Z4ESA, -FSA, -LSA, -PSA; runs 10-13) Jan 84;		
14YP38 B-Plus Arrangement	Jan	62
Du Mont RA-380/381 Agc and Sync Clipper	Jan	63
Emerson 120284-P, -85-T, -86-P, -87-T, -90-P	Jan	86
G-E ER-S-MM56 (17T025, -26)	Jan	88
Motorola Uhf Tuner	Jan	63
Muntz 600 Sound Section and Reflex Amplifier	Jan	62
Philco 7170, -71, -70-U, -71-U	Jan	90
RCA Portable KCS1108 (8-PT-7030, -I, -4)	Jan	61
RCA Victor KCS98A, -C, -E, -F (21-T, 7112, -13; 20-T-7117; 21-T-7152, -53, -57; 21-T-7355, -57)	Jan	92
Westinghouse V-2344, -54, -45, -55	Jan	94
Zenith 400 Remote Control 16Z20 (16Z25)	Feb 43;	Jan 96
Servicing—See also Technotes, Test Instruments, Try This One		
Antennas; Stubs (Clinic)	May	106
Bar Generator for Your Kit* (Bohr)	Oct	55
Brush With Death	Oct	113
Color		
Bar Generators (Clinic)	Nov	56
Black-and-White Adjustments (Mandl)	Jan	43
Gating Circuits (Waner)	Jan	70
Getting Acquainted With (Middleton)	Jan	74
Loss (Clinic)	Sep	100
Picture Analysis (Clinic)	Oct	124
Customers We Could Do Without (Margolis)	May	98
Damper Circuits, Modern (Mandl)	Jul	59
Dummy Tube	Oct	150
Extra TV Service... How to Sell It (Highstone)	Jan	48
Filter Implosion	Aug	123
Gated-Beam Discriminators (McRoberts)	Aug	37
Hints (McRoberts)	Sep	121
Home Servicing Business, Organizing a Profitable (Garrett)	Sep	94
Hot Coil	Nov	79
In 1966 (NB)	Dec	6
Interference (Clinic)	Mar	50
Adjacent-Channel (Clinic)	May	106
Interlace, Defective (Clawson)	Aug	30
Intermittents, Locating (Boller)	May	94
Keystoning†	Jul	78
Kit, Universal (Highstone)	Jan	22
(Corres)	Jun	60
Low-Voltage Power Supplies (Clinic)		
Maximum or Minimum Job.		
Do You Do (Margolis)	Dec	98
Picture Quality-Control Signals (What's New)	Jul	56
Positive Grid	Nov	82
Printed Circuits (Clinic)	May 108;	Aug 35
Proper Adjustments Keep Viewers Happy (Davis)	Jan	76
Scope, Saved by the (Middleton)	Jul	78
Sell (Extra Service), How to (Mandl)	Jan	48
Setside Manner, How's Your (Margolis)	Jan	72
Shop on Wheels (Highstone)	Jan	46
Signal Attenuation (Clinic)	Apr	54
Sunspots and TV (West)	Aug	33
Tale From Cuba (Fenton)	Nov	60
Thermal Cutout	Jun	77
Tubes Faulty in Color Section (Clinic)	Dec	84
Two-in-One Proposition (Miller)	Dec	82
Unusual Occurrences	June	76
Voice From the Future (Highstone)	Jan	78
(Fiction)		



"I'm afraid I'm going to have to take him into the shop."

Correspondence	Apr 16, 17
Vtvm for Your Multimeter* (Dewar)	Feb 57
Width (Clinic)	Jan 67, Feb 52
Shop on Wheels (Highstone)	Jan 46
Sound Tuner* (Graham)	Jun 46
Correction	Oct 99
Speaker, Remote the (Sodaro)	Aug 39
Station List (Correct to Dec. 1, 1956) (Schiller)	Jan 82
Latin American (Schiller)	Aug 34
Modifications	Jan 16, Feb 8, Mar 22, Apr 10, May 12, Jun 8, Jul 10, Aug 8, Sep 14, Oct 10, Nov 12, Dec 8
Tape Recording of Pictures (Pat)	Jan 170
Tax (NB)	Jun 10
Test Instruments—See Test Instruments	
Thirty Years of (Shunaman)	Jan 50
3-Dimensional (What's New)	Jun 49
Color (NB)	Oct 6
C-R Tube (Pat)	Aug 126
Toll (NB) Jul 8; (Corres)	Nov 21
Trends in 1956-57 Receivers (Scott)	Jan 60
Tubes—See Tube(s)	
Tuners	
Admiral Disc Typet	Jan 60
Motorola Uhf†	Jan 63
Sound* (Graham)	Jun 46
Correction	Oct 99
Tuning Indicator (Liddell)	Jun 57; Apr 48
Uhf-Vhf Deintermixture (NB)	May 16
Underwater Camera	Jun 59
Video Stage, Reflex (Pat)	Jul 114
Voice From the Future (Highstone)	
(Fiction)	Jan 78
Correspondence	Apr 16, 17
Wall Type Sets (NB)	Aug 14
World-Wide (NB)	Feb 8, May 8, Oct 6
10-Meter Transistor Rig Goes Vfo* (Read)	Sep 58
TEST INSTRUMENTS	
Absorption Analyzer (Kingston V54)†	May 48
Af Generator, Modifying (QB)	Apr 122
A-I-R Generator, Transistor* (Queen)	Aug 92
Antenna Lead-in Tester (Superior 76)†	Aug 88
Audio Oscillator, Extended-Range* (Hedge)	Dec 36
Bar Generator(s)	
Color (Clinic)	Nov 56
For Your Service Kit* (Bohr)	Oct 55
Battery Eliminator (QB) Feb 120; (REC)	Dec 118
Biased (Dyna) (REC)	Oct 165
C-R Bridge (Superior 76)†	Aug 88
Capacitance	
Bridge, Transistor* (D'Airo)	Feb 60
Meter, Rf (Queen)	Mar 95
Capacitor Checker (QB) Mar 28; *(Cozzo)	May 51




"Most severe case of coronio I ever saw. Turn the light back on."

Carrier, Tube and Tool (TTO)	Sep	145
Coil Inductance, Simple Method Checks (McCreedy)	Sep	54
Contact Potential for Loadless Metering (Bartholomew)	Apr	41
Continuity Tester		
For Series Tubes (REC)	Jan	171
Pocket (TTO)	Jul	119
Crystal-Controlled Generators†	Aug	53
Current Tester (Pearce)	Apr	43
Field-Strength Meter, Add Tuner Test to (Centerville)	Dec	35
Flyback		
And Sweep Circuit Testers (Scott)	Jul	42
Checker (Knightkit)†	Jul	44
Frequency-Marker Insert* (Graham)	Aug	96
Headset Booster, Assemble This* (Louis)	Sep	38
Horizontal Oscillator†	Aug	53
Ignition Analyzer Checks Car Trouble Electronically (Gernsback)	Sep	46
In-Circuit Horizontal System Tester (Simpson 382)†	Jul	43
Inconductor†	Apr	39
Kilovolt, Transistor* (Queen)	Feb	58
Line Plug, Three-way (Corres)	Feb 12, Apr	22
Marker Generator		
Bandwidth* (Graham)	Jul	45
Crystal (TTO)	Aug	114
Self-Calibrating* (Graham)	Jan	112
Time-Base* (Arnold)	Nov	110
Uhf (Pat)	Feb	128
Meter Pointers, Balancing (Cohn)	Mar	91
Moisture Meter, Portable* (Parks)	Apr	61
Correction	Sep	100
Multivibrator, Adjustable (Pat)	Dec	128
Noise Meter, Impact, Uses 3 Transistors (Rhita)	Oct	58
Oscillator		
Audio (REC)	Oct	166
Black-Box* (Bohr)	Sep	49
Pattern Generator		
Flying Spot (Dyna-Scan) (Scott)	Mar	65
Portable TV* (Hansen)		
Part I—Crystal Control; Positive Lock-in	Jan	119
Part II—Construction Details	Feb	54
Part III—Adjustment, Operation	Mar	62
Phase-Shift Comparator Measures Frequency Ratios, Modulation* (Pugh)	Nov	118
Picture-Tube Checker (Heathkit CC-1)†	Aug	88
Pickup, Crystal, Test (TTO)	Oct	162
Preamp for Vtvm's, Transistor* (McCreedy)	Apr	44
PicProbe (Radionic 300)†	May	49
Probes		
High-Frequency Peak-to-Peak (Middleton)	Aug	91
Versatile Set, Build a* (Hansen)		
Part I—Direct, Alignment, Isolation and High-Frequency	Jun	50
Part II—Low-Frequency Detector and Low-Capacitance	Jul	47
Substitution (TTO)	Mar	141
Switch for Rapid Measurement* (Frantz)	Sep	53
Vom Signal-Tracing (Middleton)	Feb	46
Resonance Indicator (Dynamic 60)†	Aug	90
Rf Signal Generator, More Af Output for (TTO)	Sep	149
Schematics		
B&K 1000 Picture and Pattern Generator	Mar	80
Dynamic 820 Sweep Analyzer	Jul	42
EICO 368 TV-FM Sweep Generator	Mar	40
Heathkit Ignition Analyzer IA-1	Sep	46
Kingston V54 Absorption Analyzer	May	49
Knight Flyback Checker	Jul	44
Simpson 382 In-Circuit Horizontal System Checker	Jul	44
Scope		
Amplifier (Philco 8300A)†	Aug	89
Calibrator, Transistor* (Bohr)	Jun	55
Sawtooth From (QB)	Sep	144
Switch* (Graham)	May	52
Sweep-Reversing (QB)	Aug	116
Service Aids, Inexpensive Radio-TV (Scott)	Aug	88
Signal Generator		
AM High-Speed (Hickok 290X)†	Aug	88
Synchronized Color Subcarrier Signal Generator* (Novak)	Jun	53
2-Transistor* (Chernof)	Nov	114
Sine-Square-Wave Generator* (Queen)	Apr	42
Substitution Box (Showers)	Jun	52
Capacitor (Dewar)	Sep	48
Resistor (TTO)	Sep	146
Sweep		
And Flyback Circuit Testers (Scott)	Jul	42
Circuit Analyzer (Win-Tronix 820 Dynamic)†	Jul	42
Generator (EICO 368), Saturable Reactor Controls (Scott)	Apr	39
Sync-Pulse Adapter (Win-Tronix 915/960)†	Jul	43
Three-Way Line Plug (Corres) Feb 12, Apr	Apr	22
Timer†	Apr	49
Transistor Test†	Feb	62
Improved* (Bohr)	Mar	82
Power Transistor, Simple (Caldwell)	Sep	51
Rotary Heater	Mar	37
Tube Tester(s)		
Automation and (McKay)	Oct	53
(Swontek) (Corres)	Mar	24

ANNUAL INDEX (Continued)

Tuner Test, Add to Field-Strength Meter (Centerville)	Dec 35
TV, 2 New (Scott)	May 48
Vtvm(s)	
Ac Amps, Vtvm Measures (Lederer)	Aug 85
Amplifier-Rectifier for Audio Testing* (Hedge)	Oct 59
Correction	Dec 147
Calibration Circuit for Peak-Reading (Pat)	Oct 158
Care and Repair (Samuel)	Dec 32
Milvamp Modified (REC)	Jun 99
Preamp, Transistor, for* (McCready)	Apr 44
Pulse Probe for (REC)	Aug 120
Voltages, Regulating Bias and Polarizing (Ives)	Oct 61
Thirty Years of Television (Shunaman)	Jan 50
Those Old Radios (Von Zook)	Sep 55
Three-Way Crossover Design (Crowhurst)	Jan 137
Things Ain't Always What They Seem (Darr)	Aug 78
Time-Base Marker Generator* (Arnold)	Nov 110
Tips From a TV Dixer's Notebook (Cooper)	Nov 58
Too Well Checked (Cohn)	May 42
Touch-Plate Controller* (Sandretto)	Sep 61
Tracking Hum and Noise in Magnetic Tape Recorders (McRoberts)	Jun 41
Tracking US Satellites (McQuay)	Dec 44
Traffic Control	
Electronics Times Signals (Sands)	May 78
Tacan Data Link (NB)	May 8
TRANSISTORIZED	
A-I-R Generator* (Queen)	Aug 92
Amplifier(s)	
Class-B, Compensated (Pat)	Aug 127
-Modulator, 6-Transistor, Delivers 10 Watts* (Hamlin)	Aug 47
Phono* (REC)	Jul 116
Wide-Band (Pat)	Aug 127
Bar Generator, TV, for Your Service Kit* (Bohr)	Oct 55
Capacitance	
Bridge* (D'Airol)	Feb 60
Meter, Rf* (Queen)	Mar 95
Clock, Cordless (Pat)	Nov 153
Counter	
Photodiode (REC)	Jul 117
Scintillation* (Kueker)	Mar 34
Headset Booster, Assemble This* (Louis)	Sep 38
Hearing Aid, Class-B* (Queen)	Apr 35
Kilovolt* (Queen)	Feb 58
Low-Voltage Supply* (Queen)	Oct 95
Noise Meter, Impact, Uses 3 Transistors (Rhita)	Oct 58
Oscillator	
Audio, 2-Tone (Pat)	Aug 126
Black-Box* (Bohr)	Sep 49
Crystal (Pat)	Apr 108
Preamp	
Tape-Head, All-Transistor* (Gicca)	Oct 36
For Vtvm's* (McCready)	Apr 44
Radios—See Radios, Receivers	
Scope Calibrator* (Bohr)	Jun 55
Signal Generator, 2-Transistor* (Chernof)	Nov 114
Sine-Square-Wave Generator* (Queen)	Apr 42
Solar-Battery Charger (Pat)	Nov 154
Tape Recorder (What's New)	Jan 136
Telephone Circuit (Pat)	Apr 108
Voltage Regulator (Pat)	Feb 128
TRANSISTOR(S)	
Ac Power Supply for (Battery Eliminator)* (Rhita)	Mar 109
Batteries for (TTO)	Nov 146
Circuit(s)	
Breakers for* (Taylor)	Nov 37
Design Kit (Transimulator) (What's New)	Jul 56
L-C-R-Coupled (Pugh)	Jun 44
Oscillator, Regulated (Pat)	May 114
Power From Local Radiation (Pat)	Sep 140
Rectifier (TTO)	Oct 161
Replacement (NB)	Jan 14
Symbols (Corres)	Jan 22
Test, Simple Power-Transistor (Caldwell)	Sep 51
Testert	Feb 62
Heater, Rotary	Mar 37
Improved* (Bohr)	Mar 82
Testing and Handling* (Hamlin)	Feb 61
Types, More About (Penfield)	
Part I—How Drift, Unijunction Transistors Work; Manufacture of Alloy and Diffusion Types	Nov 35
Part II—Manufacturing Micro-alloy, Grown, Junction, Rate, Grown, Grown-Diffused, Meltback Types	Dec 108
Unijunction, Using the (Garner)	Jul 91
Transoceanic TV DX (Graf)	Jul 79
Trends in 1956-57 TV Receivers (Scott)	Jan 60
Tricks of the Trade (Layden)	Sep 60
True or False Quiz for Audiophiles (Burstin)	Nov 49
TRY THIS ONE—See also Servicing; Technotes	
Amplifier, Williamson, More Gain for	Sep 146
Anchoring Amplifier Covers	Dec 116
Audio Switching, Novel	Oct 102
Batteries for Transistors	Nov 146
Battery Holders	Jun 104
Bfo Circuit	Jan 180
Carbon-Tef Fumes	Nov 146
Carrier, Tube and Tool	Sep 145
Chassis Drilling	Dec 116
Component Leads, Straighten	Jul 119
Containers From Syringes	Jun 104

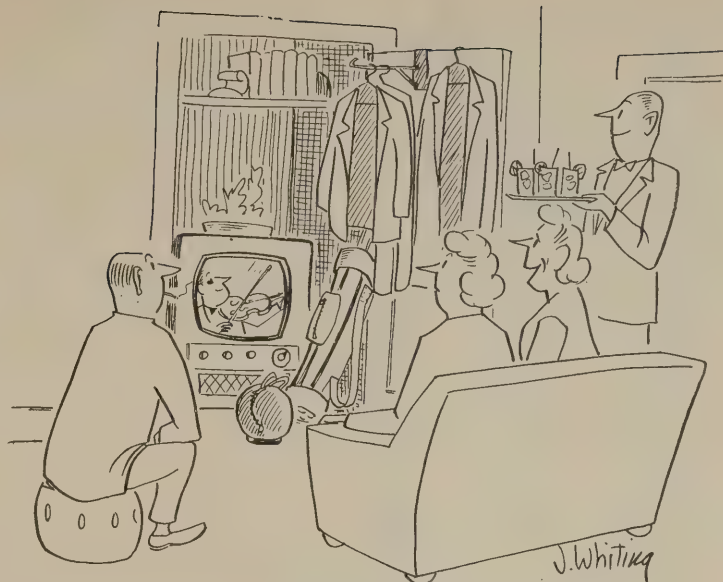

"We like the idea of having it built in but it leaves us a little short of closet space."

Continuity Tester, Pocket	Jul 119	Phone Tips	Dec 116
Control Shafts, Cut	Oct 161	Pad	Sep 146
Corona Feeler	Jan 178	Vise	Oct 162
Dial-Stringing Aid	Feb 181	Speaker	
Fuse Puller	Nov 145	Repairs	Jan 181
Ground, Low-Resistance	Feb 130	Switching	
Heat-Damage Prevention	Nov 146	Audio	Oct 102
High-Voltage		Autos	May 139
Filament Winding	Jan 178	Substitution Box (Resistor)	Sep 146
Regulator	Sep 148	Tapping, Breakless	May 137
High-Resistance Measurements	Aug 125	Terminal Marking	Nov 144
Induction Measurement	Nov 144	Transformer, Isolation	Mar 143
Intermittent		Tube	
Heating Kink	Jun 103	Sockets for Kits	May 138
Locator	Sep 148	Type Numbers	Apr 182
Jacks, Cooling Hot	Mar 143	Tuning-Slug Repair	May 139
Lead-in Protection	May 137	Turret-Spring Tool	Feb 131
Lightning Protection	Jul 118	Volume-Control Knob	Feb 131
Line-Voltage Regulator	Jul 118	Wire Eyes, Forming	Jul 118
Loading Device	Jan 180	TUBE(S)	
Marker Generator, Crystal*	Aug 124	Data and Amplifier Design (Ravenswood)	
Neon Flasher, Low-Voltage	Jun 103	Part I—R-C-Coupled Pentode Amplifiers	Nov 47
Oscillator, Audio	Oct 166	Part II—R-C-Coupled Triode Circuits; Swing to Drive Output Tubes	Dec 56
Phone-Tip Adapter	May 137	New and Semiconductors	
Panels		Jan 166, Feb 116, Mar 126, Apr 118, May 121, Jun 115, Jul 99, Aug 104, Sep 137, Oct 155, Nov 137, Dec 124	
Colorful	Aug 124	Obsolete, Replacement of (QB)	Feb 122
Etched	Oct 161	Television	
Pickup, Crystal, Test	Oct 162	Acceleration-Voltage Compensation (Pat)	Sep 142
Probe		Apple Tube, How It Works (Colgate)	Jan 40
Saver	Dec 116	Brightener, Kinescope (Pat)	Mar 139
Substitution	Mar 141	Flat (Leslie)	Mar 43
Vtvm Combination	Jun 103	High-Fidelity, TV Tube for* (Becker)	Feb 39
Record Player Slippage	Jun 104	110° (What's New)	Jun 49
Rectifiers		Phosphors, Transparent (NB)	Jul 6
From Salvaged Tubes	Dec 117	Semiconductor Camera (Pat)	Jan 169
Transistor	Oct 161	Spot Wobble (NB)	Jul 8
Resistance Measurement		Sweep, TB's Workhorse (Hamlin)	Apr 51
High	Aug 125	3-Dimensional C-R (Pat)	Aug 126
With Vtvm	Feb 132	Troubles, Hints on (Glickstein)	Jan 64
Resistor Repairs	Nov 145	Wamoscope (What's New)	Aug 54
Rf Signal Generator, More Af Output		Tester(s) (Swontek) (Corres)	Mar 24;
For	Sept 149	(Tech News)	Jun 107
Servicing Aid	Nov 144	Automation and (McKay)	Oct 53
Shoestring as Spaghetti	Nov 145	Vacuum Tube, End of (NB)	Mar 22
Slip-on Eraser Uses	Jul 119	Tuners—See specific subject	
Socket Contact Improvement	Apr 133	Twin-Coupled Amplifier, High Fidelity at Low Cost* (Crowhurst)	Nov 39
Soldering		Correction	Dec 147
—Gun Application	Feb 131	2 New Approaches to Amplification (Leslie)	Nov 32
		2 New TV Remote Controls (Maxwell)	Feb 42
		2 New TV Tube Testers (Scott)	May 48
		U	
		Understanding Auxiliary TV Circuits (Garrett) (Part I)	Dec 80
		Using Neon Lamps (Clawson)	Dec 112
		Using the Unijunction (Garner)	Jul 91
		Universal TV Service Kit (Corres)	Jan 22
		V	
		Variable Dc Heater Supply Uses Tuned Filters* (Sanford)	Mar 102
		Voice From the Future (Highstone) (Fiction)	Jan 78
		Vtvm for Your Multimeter* (Dewar)	Feb 57
		Vtvm—Its Care and Repair (Samuel)	Dec 32
		W	
		Wrong Quiz (Gnessin)	Feb 81
		Zauberschalter (What's New)	Jun 49
		Z	
		END	



"That's right... now grab the terminal marked 500 volts."

TUBES

● Individually boxed ● First quality only
 ● Brand New ● 90-DAY RETMA guarantee
 No rebrands ● No private brands ● No rejects

1B35	\$	3.35	371B		.75	5636	2.75
5B41		3.95	404A		.90	5642	1.00
CL-2		10.00	403B		2.90	5646	4.00
2C35		2.00	404A		1.00	5646	1.00
1019A		9.00	417A		30.00	5654	1.35
2C40		6.75	417A		2.25	5676	.65
2C51		2.75	417A/5842			5687	2.50
2E24		2.25	450-TL		45.00	5691	5.00
2K25		13.50	UG-610		3.50	5692	5.00
2K45		3.50	WL/655/658			5693	5.00
3B45		1.50			90.00	5703A	3.95
3K74		1.50	GL673		12.50	5718	1.75
3B24W		4.25	703A		1.75	5726	1.00
8B29		15.00	703A		7.00	5725	1.50
3C45		6.75	75TOL		30.00	5726	.65
3J30		25.00	803		1.50	5744	1.00
4-105A		3.50	807		4.00	5778	1.00
4-125A		30.25	807		1.10	5783	1.25
4-250A		35.00	807W/5933		1.50	5812	1.00
4-40A		4.00	814		2.50	5819	1.00
4B24-EL3C		4.50	814		2.50	5819	23.95
4PR6A		30.00	815		2.50	5840	3.50
5C52		24.00	816		1.75	5881	.45
5A15W		1.00	822A		2.00	5915	1.00
6C21/450TL		1.00	836		2.01	5915	.50
614		13.50	837		1.25	6111	4.50
15F		0.00	838		1.00	6112	.50
FG32		4.25	872A		1.60	6130/3C45	4.75
335TG		2.25	872A		90	6181	45.00
VK50/32V		1.00	815	(GE)	2.00	6201	1.50
RC-60/1641		8.00	918		1.10	6350	1.50
		1.15	927		95	6539	9.00
HY69		2.10	954		.10	6587	1.00
RR72 or 73.39		1.00	955		.30	8020	1.00
F123A		6.75	956		.30	8021	.70
1WXR130.		1.00	957		.30	9002	1.25
GL299		1.50	958A		.35	9004	1.25
304TL		12.50	901		.25	9006	.20
357A		14.00	CK1007		45	many others	
			5517		1.00	\$(Surplus)	

DUMONT 5" OSCILLOSCOPE, Model 274A. At less
 than 1/3 reg. price! Exc. cond. **\$59.95**
DYNAMOTOR, Vy compact. 12 VDC in, 420 VDC @
250 ma, int. out. (160 ma, cont.).....\$9.95
 Lots of 3, each..... **8.95**

Pris: 115 V. 60 Cy. . . Tapped at 105V. Secondary
1100 volts CT @ 250 Ma.—6.3 V. at 5 Amps. 5
volts @ 3 Amps. (125 volt bias winding). Ideal
for 6X4, 6X5, 6X6, 6X8, 6X9, 6X45, 6X50, 6X55, 6X60, 6X65,
6X70, 6X75, 6X80, 6X85, 6X90, 6X95, 6X100, 6X105, 6X110,
6X115, 6X120, 6X125, 6X130, 6X135, 6X140, 6X145, 6X150,
6X155, 6X160, 6X165, 6X170, 6X175, 6X180, 6X185, 6X190,
6X195, 6X200, 6X205, 6X210, 6X215, 6X220, 6X225, 6X230,
6X235, 6X240, 6X245, 6X250, 6X255, 6X260, 6X265, 6X270,
6X275, 6X280, 6X285, 6X290, 6X295, 6X300, 6X305, 6X310,
6X315, 6X320, 6X325, 6X330, 6X335, 6X340, 6X345, 6X350,
6X355, 6X360, 6X365, 6X370, 6X375, 6X380, 6X385, 6X390,
6X395, 6X400, 6X405, 6X410, 6X415, 6X420, 6X425, 6X430,
6X435, 6X440, 6X445, 6X450, 6X455, 6X460, 6X465, 6X470,
6X475, 6X480, 6X485, 6X490, 6X495, 6X500, 6X505, 6X510,
6X515, 6X520, 6X525, 6X530, 6X535, 6X540, 6X545, 6X550,
6X555, 6X560, 6X565, 6X570, 6X575, 6X580, 6X585, 6X590,
6X595, 6X600, 6X605, 6X610, 6X615, 6X620, 6X625, 6X630,
6X635, 6X640, 6X645, 6X650, 6X655, 6X660, 6X665, 6X670,
6X675, 6X680, 6X685, 6X690, 6X695, 6X700, 6X705, 6X710,
6X715, 6X720, 6X725, 6X730, 6X735, 6X740, 6X745, 6X750,
6X755, 6X760, 6X765, 6X770, 6X775, 6X780, 6X785, 6X790,
6X795, 6X800, 6X805, 6X810, 6X815, 6X820, 6X825, 6X830,
6X835, 6X840, 6X845, 6X850, 6X855, 6X860, 6X865, 6X870,
6X875, 6X880, 6X885, 6X890, 6X895, 6X900, 6X905, 6X910,
6X915, 6X920, 6X925, 6X930, 6X935, 6X940, 6X945, 6X950,
6X955, 6X960, 6X965, 6X970, 6X975, 6X980, 6X985, 6X990,
6X995, 6X1000, 6X1005, 6X1010, 6X1015, 6X1020, 6X1025,
6X1030, 6X1035, 6X1040, 6X1045, 6X1050, 6X1055, 6X1060,
6X1065, 6X1070, 6X1075, 6X1080, 6X1085, 6X1090, 6X1095,
6X1100, 6X1105, 6X1110, 6X1115, 6X1120, 6X1125, 6X1130,
6X1135, 6X1140, 6X1145, 6X1150, 6X1155, 6X1160, 6X1165,
6X1170, 6X1175, 6X1180, 6X1185, 6X1190, 6X1195, 6X1200,
6X1205, 6X1210, 6X1215, 6X1220, 6X1225, 6X1230, 6X1235,
6X1240, 6X1245, 6X1250, 6X1255, 6X1260, 6X1265, 6X1270,
6X1275, 6X1280, 6X1285, 6X1290, 6X1295, 6X1300, 6X1305,
6X1310, 6X1315, 6X1320, 6X1325, 6X1330, 6X1335, 6X1340,
6X1345, 6X1350, 6X1355, 6X1360, 6X1365, 6X1370, 6X1375,
6X1380, 6X1385, 6X1390, 6X1395, 6X1400, 6X1405, 6X1410,
6X1415, 6X1420, 6X1425, 6X1430, 6X1435, 6X1440, 6X1445,
6X1450, 6X1455, 6X1460, 6X1465, 6X1470, 6X1475, 6X1480,
6X1485, 6X1490, 6X1495, 6X1500, 6X1505, 6X1510, 6X1515,
6X1520, 6X1525, 6X1530, 6X1535, 6X1540, 6X1545, 6X1550,
6X1555, 6X1560, 6X1565, 6X1570, 6X1575, 6X1580, 6X1585,
6X1590, 6X1595, 6X1600, 6X1605, 6X1610, 6X1615, 6X1620,
6X1625, 6X1630, 6X1635, 6X1640, 6X1645, 6X1650, 6X1655,
6X1660, 6X1665, 6X1670, 6X1675, 6X1680, 6X1685, 6X1690,
6X1695, 6X1700, 6X1705, 6X1710, 6X1715, 6X1720, 6X1725,
6X1730, 6X1735, 6X1740, 6X1745, 6X1750, 6X1755, 6X1760,
6X1765, 6X1770, 6X1775, 6X1780, 6X1785, 6X1790, 6X1795,
6X1800, 6X1805, 6X1810, 6X1815, 6X1820, 6X1825, 6X1830,
6X1835, 6X1840, 6X1845, 6X1850, 6X1855, 6X1860, 6X1865,
6X1870, 6X1875, 6X1880, 6X1885, 6X1890, 6X1895, 6X1900,
6X1905, 6X1910, 6X1915, 6X1920, 6X1925, 6X1930, 6X1935,
6X1940, 6X1945, 6X1950, 6X1955, 6X1960, 6X1965, 6X1970,
6X1975, 6X1980, 6X1985, 6X1990, 6X1995, 6X2000, 6X2005,
6X2010, 6X2015, 6X2020, 6X2025, 6X2030, 6X2035, 6X2040,
6X2045, 6X2050, 6X2055, 6X2060, 6X2065, 6X2070, 6X2075,
6X2080, 6X2085, 6X2090, 6X2095, 6X2100, 6X2105, 6X2110,
6X2115, 6X2120, 6X2125, 6X2130, 6X2135, 6X2140, 6X2145,
6X2150, 6X2155, 6X2160, 6X2165, 6X2170, 6X2175, 6X2180,
6X2185, 6X2190, 6X2195, 6X2200, 6X2205, 6X2210, 6X2215,
6X2220, 6X2225, 6X2230, 6X2235, 6X2240, 6X2245, 6X2250,
6X2255, 6X2260, 6X2265, 6X2270, 6X2275, 6X2280, 6X2285,
6X2290, 6X2295, 6X2300, 6X2305, 6X2310, 6X2315, 6X2320,
6X2325, 6X2330, 6X2335, 6X2340, 6X2345, 6X2350, 6X2355,
6X2360, 6X2365, 6X2370, 6X2375, 6X2380, 6X2385, 6X2390,
6X2395, 6X2400, 6X2405, 6X2410, 6X2415, 6X2420, 6X2425,
6X2430, 6X2435, 6X2440, 6X2445, 6X2450, 6X2455, 6X2460,
6X2465, 6X2470, 6X2475, 6X2480, 6X2485, 6X2490, 6X2495,
6X2500, 6X2505, 6X2510, 6X2515, 6X2520, 6X2525, 6X2530,
6X2535, 6X2540, 6X2545, 6X2550, 6X2555, 6X2560, 6X2565,
6X2570, 6X2575, 6X2580, 6X2585, 6X2590, 6X2595, 6X2600,
6X2605, 6X2610, 6X2615, 6X26

The device that makes license free transmission a reality! 2 way voice or MCW can be transmitted over concentrated invisible infra-red rays. Information on how to construct a 2-way transmit-receive station available. See p. 93, Oct. 57.

Radio-Electronics

CL-2 LAMP, w/info (worth \$50).....\$10.00

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices. Packed 1000 to case.



SIZE	FOR TUBE	PER 100
Miniature.....	6AU6, etc.....	\$1.00
GT.....	6SN7, etc.....	1.25
Large GT.....	1B3, etc.....	1.50
Large G.....	5U4G, etc.....	2.00

WHITE GLOSSY BOXES
Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

White glossy only. Ministacker holds 10 Mini, tube cartons; "GT" stacker holds 10 "GT" cartons.

SIZE	PER EACH
Ministacker	11 ¹ / ₂ c
GT	02

\$12.50 Per Case of 1000 FOB NYC.

All cartons & stackers f. o. b. NYC

WRITE FOR "BARRY'S SEPT. '57 GREEN SHEET"

TERMS: 25% deposit with order, balance C.O.D.
All merchandise guaranteed for cost of merchandise
only. F.O.B. N.Y.C.
Subject to price variation and stock depletion
MINIMUM ORDER \$10.00

TRADES ACCEPTED—OPEN MON. TO SAT.

160

Mallory (P.R.) & Co., Inc.	126-127
Merit Coil & Transformer Corp.	161
Miller (Gustave)	160
Moss Electronic Distributing Co., Inc.	96-97

MAYBE YOU'RE THE MAN TO
WRITE THEM. ASK FOR AN
AUTHOR'S GUIDE.

**154 West 14th Street
New York 11, N.Y.**

Belgian manufacturers seek a suitable firm for exclusive sale or manufacture under their license. Write with bank and commercial references to ELIT, 40, rue de la Loi, Bruxelles, Belgium.

~~~~~

**MAKE \$50-\$100 EXTRA PER WEEK**  
Install Surgistors on all calls  
See your distributor or write:  
**WUERTH TUBE-SAVER CORP.**  
9125 Livernois Ave., Detroit 4, Mich.



**MERITAPE**  
Low Cost. High  
Quality Record-  
ing Tape—in  
boxes or cans





## Seeing Double?

SURE... THEY LOOK ALIKE  
BECAUSE

THEY ARE EXACTLY ALIKE

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH  
**MERIT**

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit is superior!



COMPARE IT WITH

**MERIT**

MERIT COIL & TRANSFORMER CORP.  
4427 N. CLARK ST., CHICAGO 40, ILLINOIS

## 2 WAY PORTABLE RADIO SET

**Sends—Receives up to 10 miles as shown**


or hundreds of miles with outside antenna! 80 and 40 meter amateur radio bands (novice) also Aircraft and overseas broadcasts (3 to 8 mc.) POWERED WITH SELF-CONTAINED PORTABLE RADIO BATTERIES. NO AC PLUG-INS NEEDED! Take it with you everywhere you go—Keep in contact with home, friends. Has 5 watt crystal controlled transmitter—Sensitive Regenerative Receiver. Send receive switch. Wt. only 3 lbs. Size, only 6"x4"x4" TESTED—PROVEN—SIMPLIFIED—PRACTICAL—Full information given on quick easy to get license.

**SEND ONLY \$3.00** (bill, ck, mo)

man \$11.95 COD postage on arrival or send \$14.95 for postpaid delivery. Complete kit includes all parts, tube, coils, plastoid cabinet, easy instructions. (Set of batteries—\$2.95; crystal \$1.25). COMPLETELY WIRED AND TESTED POSTPAID \$19.95. A regular \$49.95 value—Order now before price goes up. GUARANTEED—AVAILABLE ONLY FROM:  
WESTERN RADIO Dept. ENR-12 KEARNEY, NEBR.

## ENGINEERING

**B. S. DEGREE  
IN 27 MONTHS**

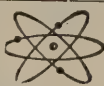

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter Dec., March, June, Sept. Catalog.

**INDIANA TECHNICAL COLLEGE**  
1712 E. Washington Blvd., Fort Wayne 2, Indiana  
Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

☐ Electronics ☐ Chemical ☐ Aeronautical  
☐ Civil ☐ Mechanical ☐ Electrical  
B.S. DEGREE IN 36 MO. in: ☐ Math. ☐ Chem. ☐ Physics

Name.....  
Address.....

|                                              |         |
|----------------------------------------------|---------|
| National Radio Institute.....                | 3       |
| National Schools.....                        | 5       |
| Newark Electric Co.....                      | 147     |
| Opportunity Adlets.....                      | 134-135 |
| ORRadio Industries Inc.....                  | 8       |
| Oxford Components, Inc.....                  | 134     |
| Pentron Corp.....                            | 120     |
| Phaostron Instrument &<br>Electronic Co..... | 129     |
| Pickering & Co., Inc.....                    | 124     |
| Progressive Edu-Kits, Inc.....               | 140     |
| Pyramid Electric Co.....                     | 139     |

|                                    |                   |
|------------------------------------|-------------------|
| Quality Electronics.....           | 148               |
| Radiart Corp.....                  | 10                |
| RCA Electron Tube<br>Division..... | Back Cover        |
| RCA Institutes.....                | 17                |
| RCA (Test Equipment).....          | 155               |
| Raytheon Manufacturing Co.....     | 26                |
| Rek-O-Kut Co., Inc.....            | 117               |
| Rinehart & Co., Inc.....           | 21, 132, 146, 149 |
| Rockbar Corp.....                  | 125               |

|                                                |         |
|------------------------------------------------|---------|
| Sams (Howard W.) & Co.,<br>Inc.....            | 25, 142 |
| Service Instrument Corp.....                   | 142     |
| Sherwood Electronic Labs., Inc.....            | 107     |
| Shure Brothers, Inc.....                       | 118     |
| Simpson Electric Co.....                       | 110-111 |
| Sonotone Corp.....                             | 122     |
| Sprague Products Co.....                       | 121     |
| Sprayberry Academy of<br>Radio Television..... | 23      |
| Stan-Burn Radio & Electronics.....             | 128     |
| Sunair Electronics, Inc.....                   | 137     |

|                                           |                    |
|-------------------------------------------|--------------------|
| Techmaster Corp.....                      | 131                |
| Thorens Co.....                           | 14                 |
| Tranvision Inc.....                       | 148                |
| Trio Manufacturing Co.....                | 79                 |
| Triplett Electrical Instrument<br>Co..... | Inside Front Cover |
| Tung-Sol Electric Co.....                 | 6                  |

|                                   |     |
|-----------------------------------|-----|
| Uncle Sam Recording.....          | 146 |
| University Loudspeakers, Inc..... | 153 |

|                       |     |
|-----------------------|-----|
| Vaco Products Co..... | 133 |
|-----------------------|-----|

|                               |     |
|-------------------------------|-----|
| Weller Electric Corp.....     | 138 |
| Wen Products, Inc.....        | 24  |
| Western Radio.....            | 161 |
| Winegard Co.....              | 94  |
| Winston Electronics, Inc..... | 22  |
| World Radio Labs.....         | 145 |
| Wuerth Tube-Saver Corp.....   | 160 |


### SCHOOL DIRECTORY PAGE 151

Baltimore Technical Institute  
Candler System Co.  
Indiana Technical College  
Milwaukee School of Engineering  
Pacific International University  
Tri-State College  
Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 1413 Howard St. Tel. ROgers Park 4-8000. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire. Tel. DUnkirk 7-2328. San Francisco: Ralph W. Harker and Associates, 444 Market St. Tel. GARfield 1-2481.

FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. Australia: McGill's Agency, Melbourne. France: Brenano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Trilectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency, Ltd., Johannesburg. Capetown, Durban, Natal; Universal Book Agency, Johannesburg. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3.
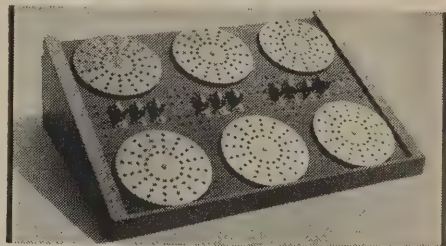
## Kits for Christmas! GENIAC COMPUTER KIT



Control Panel of GENIAC set up to do a problem

You can construct over 50 different circuits and 40 different machines that compute, reason, solve puzzles and demonstrate a wide variety of basic computer circuits with the GENIAC electric brain construction kit. Thousands of schools, colleges, industrial firms and private individuals have bought GENIACS since we first brought them on the market.

We have recently added a circuit for composing music, which gives us special pleasure because it was designed by a 16 year old boy who learned about computers from his GENIAC. Dozens of other youngsters have created their own designs for computing circuits, used GENIACS in their school projects and established a solid foundation of information on computers with GENIACS.

Each kit comes complete with Beginners Manual, Study Guide, instructions for building all the machines and circuits (exclusive with our GENIAC), parts tray, and our complete question answering service. When you buy a GENIAC you are buying a first course in computer operation.

Each kit comes with a one week money back guarantee if you are not satisfied.

Price of Kit complete with parts tray, rack, all components, manuals and texts \$19.95 (postpaid in U.S., add 80c west of Mississippi). \$2.00 outside United States.)

**OLIVER GARFIELD CO., INC.**

Dept. RE127B

126 LEXINGTON AVENUE  
NEW YORK 16, N.Y.

## Industrial Engineers and Maintenance Men

## An Opportunity

To make some extra money by writing down-to-earth articles on industrial electronic service for RADIO-ELECTRONICS. If you or your organization is doing that kind of work, and you have had experience or experiences that may be helpful to others starting or trying to start in the field, let us hear about it. You don't have to be a writer—we have a staff of editors to put your experiences into article form. For an Author's Guide, address:

Industrial Electronics Editor  
RADIO-ELECTRONICS  
154 West 14th St.  
New York 11, N. Y.



# FREE! LAFAYETTE CATALOG

A Must For  
Every Hi-Fi  
Enthusiast


*Lafayette*




## NEW 180 PAGE ELECTRONIC CATALOG FEATURING THE BEST BUYS IN THE BUSINESS

The newest and largest assortment of Electronic, Radio and TV parts, Hi-Fi and Public Address Components and systems, Test Equipment, tubes, Transistor Kits and miniaturized components for transistor circuitry, Ham Equipment, Builders Kits, Tools, Books, Microscopes, Binoculars, Telescopes, Cameras, and Drafting Equipment.—ALL AT LOWEST PRICES—Catering to the economy minded dealer, serviceman, engineer, technician, experimenter and hobbyist. CRAMMED FULL OF MONEY SAVING BUYS. SEND FOR YOUR FREE COPY TODAY.

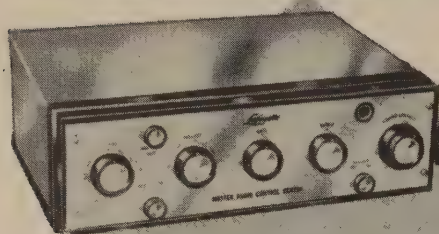
## Introduces Hi-Fi Gems ... at prices everyone can afford



KT-300  
IN KIT  
FORM  
39.50

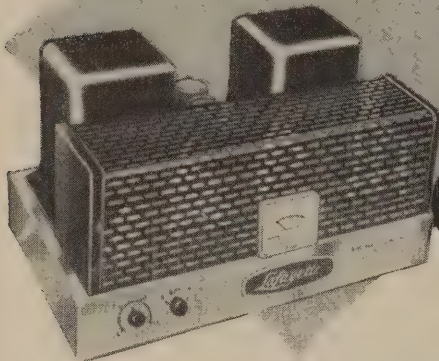


KT-400  
IN KIT  
FORM  
69.50

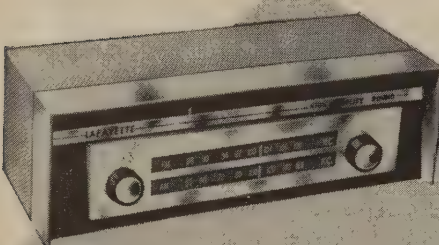

LT-40  
FM-AM  
"MUSIC  
MATE"  
TUNER  
64.50  
LESS  
CAGE

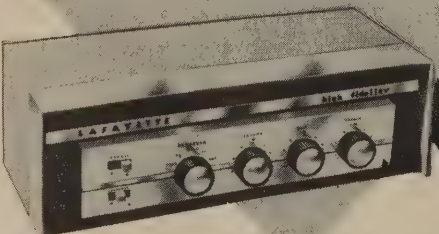NEW! "MUSIC MATES" TUNER AND AMPLIFIER  
COMPLETELY WIRED AND TESTED



LA-40  
15 WATT  
"MUSIC  
MATE"  
AMPLIFIER  
43.50  
LESS  
CAGE

### LAFAYETTE MASTER AUDIO CONTROL CENTER

with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.

Years Ahead of Every Other Control Unit ... Ahead in Sound ... Ahead in Styling  
Ahead in Design ... Ahead in Features ... Available in Kit and Wired Form

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (Stereophonic) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% IM distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phone, tuner or tape. Tasteful styling, brilliantly executed. Size 12 1/4" x 9 1/4" x 3 1/4". Shpg. wt., 10 1/2 lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions. Net 39.50

LT-30—Same as above completely wired and tested with cage and instruction manual. Net 59.50

### DELUXE 70 WATT BASIC AMPLIFIER

- Conservatively Rated At 70 Watts • Ultra-Stable • Variable Damping
- Metered Balance And Bias Adjust Controls • Available in Kit And Wired Form

Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wide range linear output transformer, variable damping control, meter for bias and balance and gold finished chassis. Frequency response 10-100,000 cps  $\pm$  1db. Hum and noise 90db below full output. IM distortion less than 1 1/2% at 70 watts, less than 0.3% below 30 watts. Harmonic distortion less than 2% at 70 watts from 20 to 20,000 cps  $\pm$  1db. Output impedance 4, 8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14 1/2" x 10" x 7 1/4" including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions. Net 69.50

LA-70—Same as above completely wired and tested with cage and instruction manual. Net 94.50

### Lafayette CUSTOM HI-FI "MUSIC MATES"

#### STYLE MATCHED TUNER AND AMPLIFIER

##### MODEL LT-40 "MUSIC MATE" DELUXE FM-AM TUNER

- ARMSTRONG CIRCUIT • AFC DEFEAT • FOSTER-SEELEY DISCRIMINATOR
- TEMPERATURE COMPENSATED OSCILLATOR • MEETS FCC RADIATION REQUIREMENTS

A sensitive, selective, stable FM-AM tuner. Temperature compensated oscillator and AFC assure drift-free performance and "locking-in" of stations once they are tuned. The Armstrong circuit with limiter and Foster-Seeley discriminator uses 6 tubes, a rectifier and 2 long-life matched germanium diodes. Superior frequency response, hum and distortion specifications assure excellent reception. Has built-in antennas for both AM and FM as well as provision for outdoor antenna. Finished in attractive dark maroon and gold. Size 13 1/2" W x 5 1/4" D x 4-3/16" H. Shpg. wt., 10 lbs. Available with cage for shelf use or without cage for custom mounting.

Lafayette LT-41—FM-AM Tuner (Less Cage) Net 64.50

Lafayette LT-40—FM-AM Tuner (With Cage) Net 67.50

##### MODEL LA-40 15 WATT "MUSIC MATE" AMPLIFIER

- 20-20,000 CPS  $\pm$  .5DB • TAPE HEAD AND RECORD EQUALIZATION
- LESS THAN 1% DISTORTION • PUSH-PULL EL84 OUTPUT TUBES
- RUMBLE FILTER • 5 INPUT CHANNELS • LOUDNESS CONTROL

Brilliantly engineered, beautifully styled and moderately priced, this deluxe amplifier matches the tuner in both decor and performance. Utilizes new premium quality EL84 tubes in push-pull. In addition to separate bass, treble and volume controls, has 3 position loudness switch to retain correct tonal balance. 5 inputs, fully equalized, for Crystal or Ceramic Phono, Magnetic Phono, Tape, Tuner and Aux. A hum adjustment control minimizes subsidiary hum. Rumble filter switch to eliminate motor vibration. Speaker and tape output. Output impedances 4, 8 and 16 ohms. Has all of the prerequisite features for a fine hi-fi system. Size 12 1/4" W x 8 3/4" D x 4 1/4" H. Shpg. wt., 12 lbs.

Lafayette LA-41—Amplifier (Less Cage) Net 43.50


Lafayette LA-40—Amplifier (With Cage) Net 46.50

### NEW "DYNA-SLIM" MICROPHONE

- HIGH IMPEDANCE — 50,000 OHMS
- ON-OFF SWITCH • "QUICK-SLIP" ADAPTER

New dynamic, high output microphone with all the features of "mikes" costing 3 times Lafayette's price! Output level —55db. Smooth response from 60 to 10,000 cycles. Omnidirectional head. External on-off switch. Slips on or off stand adapter in a wink. Standard 3/8" — 27 adapter permits tilting mike for multi-angle use. Satin black and chrome finish. Complete with detachable cable and connector. 8" long, 1 1/4" max. dia. tapered panel. Shpg. wt., 2 lbs.

PA-43 Net 6.95

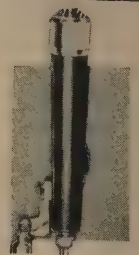

*Lafayette Radio*

DEPT  
JL

P. O. BOX 511  
JAMAICA 31, N. Y.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_  
STATE \_\_\_\_\_

SEND  
FREE  
CATALOG  
305

CUT OUT AND MAIL TODAY!



# Exclusive Lafayette Money-Saving Values



MODEL  
PK-225

## SPECIAL MONEY-SAVER COMBINATION

PK-225 Turntable, PK-90 12" Tone Arm, New GE VRII Series Triple-Play Cartridge Model 4G-052 with Genuine GE Diamond and Sapphire Styli. **SPECIAL! Net 81.50**

## PROFESSIONAL TURNTABLE WITH HYSTERESIS-SYNCHRONOUS MOTOR

The Lafayette Model PK-225 is a true hysteresis-synchronous motor and is free from speed variations due to fluctuations in line voltage, load and temperature. It is the smoothest type known, completely free from "cogging" (the minute variations of speed which show up as wow and flutter)

**ONLY LAFAYETTE'S HYSTERESIS-SYNCHRONOUS MOTOR**, in its price class, is made to extremely fine tolerances (on the order of .00001 inches)! Only Lafayette's motor has 16 cores; a high permeability rotor magnet, ball thrust bearings, oilite sleeve bearings plus felt oil reservoir, cooling fins as an integral part of the rotor and a hollow rotor core for maximum efficiency and minimum heat. Only Lafayette's motor can be oiled from above, without disassembly, through a unique oil feed system. Only Lafayette's motor has a self-aligning armature.


Here's THE turntable—the last word in professional high-fidelity performance! A fine precision instrument in every sense. Just look at some of these **OUTSTANDING FEATURES:-** **WOW AND FLUTTER:** Less than 0.2% • **TURN-TABLE:** Heavy, diecast aluminum. Lathe-turned for perfect balance and concentricity. 12" diameter—weighs approx. 4 lbs. and provides amazingly constant speed; the extra-heavy rim acts just like a flywheel to prevent speed variations • **TRUE-HYSTERESIS-SYNCHRONOUS MOTOR:** For smooth, low-noise, wow- and flutter-free operation • **RUM-BLE: AND NOISE:** 50db below average recorded level • **INTEGRATED SPEED CONTROL:** For all 3 speeds—78, 45 and 33½ rpm • **2 OVERSIZE, HEAVY DUTY IDLERS:** Precision-ground; provide positive constant-speed rim drive • **SINGLE BALL THRUST BEARING:** Turntable rides smoothly over ball bearing floating on thin film of oil • **FREE FLOATING, SHOCK-MOUNTED MOTOR** • **RUBBER CUSHION SHOCKMOUNTS** • **AUTOMATIC IDLER DISENGAGEMENT** • **CORK AND RUBBER MAT** • **STAINLESS STEEL PRECISION SPINDLE** • **POWER REQUIREMENTS:** For 105-130 volts, 60 cps AC; draws 16 V.A. • **ACCESSORIES SUPPLIED:** 45 RPM adaptor, Strobe disc • **SIZE:** 2½" above and 4" below motor board; 14¼" deep x 12¼" wide • **SHIPPING WEIGHT:** 16 lbs.

Deluxe Woodbase for PK-225 and 12" Tone Arm (Specify Finish). Shpg. wt., 13 lbs. Net 14.95

Deluxe Woodbase for PK-225 and 16" Tone Arm (Specify Finish). Shpg. wt., 15 lbs. Net 15.95

LAFAYETTE MODEL PK-225 Net 64.50

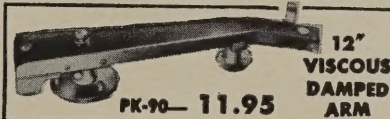
## VISCOUS DAMPED TRANSCRIPTION TONE ARMS



PK-90—11.95

12" VISCIOUS DAMPED ARM

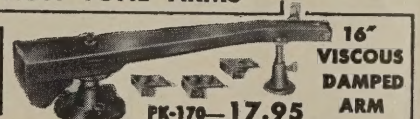LICENSED UNDER CBS U. S. PATENT NO. 2676806



PK-170—17.95

16" VISCIOUS DAMPED ARM

## LAFAYETTE MATCHED HIGH-FIDELITY PHONO SYSTEM

**NOBODY BUT LAFAYETTE** can bring you a phono system of this quality—and at this price. Indeed a Lafayette "best buy" system designed around the new Lafayette LA-69 20 watt amplifier. The performance of this phono system surpasses the most critical requirements of music lovers at a price below that of commercial phonographs. Twenty-four combinations of record equalization provide an almost endless variety of tone compensation to match varying recording characteristics. In addition to the LA-69 this system includes the famous Garrard RC-121 4-speed Record Changer featuring full automatic and manual positions and Simple-mix operation; the new improved VRII Variable Reluctance GE Triple Play Turnover Cartridge Model 4G-052 with genuine GE diamond and sapphire styli, and the celebrated Lafayette SK-58 12" Coaxial Hi-Fi Speaker. All units are supplied with plugs, jacks and prepared coded interconnecting cables for quick easy installation. For 110-125 volt, 60 cycle AC. Shpg. wt., 50 lbs.

HF-179—Complete Phono System Net 119.50




Reg. Value **SALE!**  
~~158.55~~ **119.50**

New GE VRII Diamond-Sapphire Styli

LA-69

SK-58

RC-121

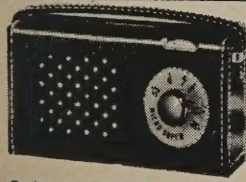

**6 TRANSISTOR SUPERHET RECEIVER KIT**

- 100% SUBMINIATURIZED
- SENSITIVE, SELECTIVE, STABLE
- PUSH-PULL OUTPUT
- PLENTY OF POWER
- AN INCOMPARABLE VALUE

The Lafayette KT-119 6 Transistor Superhet Transistor Kit provides superior commercial quality with maximum sensitivity, selectivity and stability. The circuit features 6 selected transistors and crystal diode, a specially matched set of 3 IF's, Oscillator coil, high Q loop, and audio transformer coupling. Has efficient 2½" speaker and earphone jack for private listening. Complete with all parts, transistors, pre-punched chassis and easy to follow step-by-step instructions. 6½" x 3½" x 1½". Shpg. wt., 3 lbs.

KT-119—Complete Kit—Less Case & Battery Net 29.95

BATTERY RCA VS300 Net 1.23 BURGESS P6 Net .77

MS-339—Sturdy, attractive brown leather case with carrying strap for KT-119. Shpg. wt., 1 lb. Net 2.95

MS-366—Sensitive matching earphone Net 1.29



**3 TRANSISTOR SUPERHET POCKET RADIO KIT**

- A TRUE POCKET SUPERHET RECEIVER
- NO EXTERNAL ANTENNA
- NO EXTERNAL GROUND

A remarkable sensitive, super-selective pocket superhet receiver with astonishing performance over the complete broadcast band. Uses 2 high-frequency and one audio transistor plus efficient diode detector and features 2 specially matched IF transformers for maximum power transfer. The components are housed in a professional looking beige plastic case. The receiver's appearance enhanced by attractive maroon and silver station dial. Sensitive built-in ferrite antenna eliminates need for external antenna. A designer's dream in a true pocket superhet receiver! Complete with all parts, transistors battery, case, dial and easy to follow step-by-step instructions. 4½" x 2½" x 1-1/16". Shpg. wt., 1 lb.

KT-116—Complete Kit, less earphone Net 16.95

MS-260—Super Power Dynamic Earphone Net 3.95

## NEW POCKET AC-DC VOM MULTITESTER

2,000 ohm per volt sensitivity on both DC and AC  
160 ua 3" METER 1% PRECISION RESISTORS  
SILVER CONTACT SELECTOR SWITCH  
FULL SCALE RANGES

D.C. Volts: 0-10; 0-50; 0-500; 0-1000 Volts—A.C. Volts: 0-10; 0-50; 0-500; 0-1000 volts—D.C. Current: 500 ua and 500 ma—Resistance: 0-10K; 0-1 Meg—Decibels: —20 to +22; +20 to 36 db (0 db—0.775 V)—Capacity: 250 mmd. to .2 mfd—.005 mfd to 1 mfd—Output Ranges: 0-10; 0-50; 0-500; 0-1000 volts.

Best Buy in America! A very accurate and sensitive VOM. This Multitester is a complete instrument (not a kit) with high quality and sensitive 160 microamp meter; 2000 ohm per volt on both AC and DC. Single selector switch, 1% precision resistors, 3" meter. Features extreme versatility, accuracy and ruggedness. In attractive plastic front panel, with metal bottom for ruggedness and shielding. First capacity range requires 50 volt AC source. Second capacity range requires 10 volt AC source. Size 4½" x 3½" x 1½". Complete with test leads and batteries. Shipping weight 4 lbs.

RW-27A Complete 8.95

**HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER**  
LOOK AT THESE FULL SCALE RANGES!

D.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200; 0-6000 Volts—A.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts—Resistance: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms—D.C. Current: 0.60 Microamp; 0-6; 0-60; 0-600 Milliamps—Decibels: —20 to +17 db (0db—0.774V)—Capacity: .0001-.01; .005-.15 mfd—Inductance: 20-2000 millihenry—Output Ranges: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts.

The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT ON D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contacts on selector switch, 35 ua 3" meter. Dependable, rugged and accurate. Even the test leads are heavy duty with high voltage insulation. Voltage source required for low capacity range is 120V for high range capacity and inductance scale is 6V A.C. Attractive plastic front with metal bottom. Size 6½" x 4½" x 2½". Complete with batteries and leads. Shipping weight 4½ lbs.

RW-30A Singly, Each 19.95

In lots of 3, Each 19.25

**Lafayette Radio**

165-08 Liberty Ave.  
JAMAICA 33; N. Y.

100 SIXTH AVE., NEW YORK, N. Y.

BOSTON, MASS., 110 Federal St. PLAINFIELD, N. J., 139 West 2nd St.  
NEWARK, N. J., 24 Central Ave. BRONX, N. Y., 542 E. Fordham Rd.



It's New! Send for this


# FREE

booklet today!

see  
what the  
rapidly  
expanding  
field of  
**ELECTRONICS**  
offers  
you

- BETTER JOB
- BETTER PAY
- PROMOTION
- GREATER SECURITY
- GREATER CONFIDENCE
- BETTER LIVING FOR YOU AND YOUR FAMILY

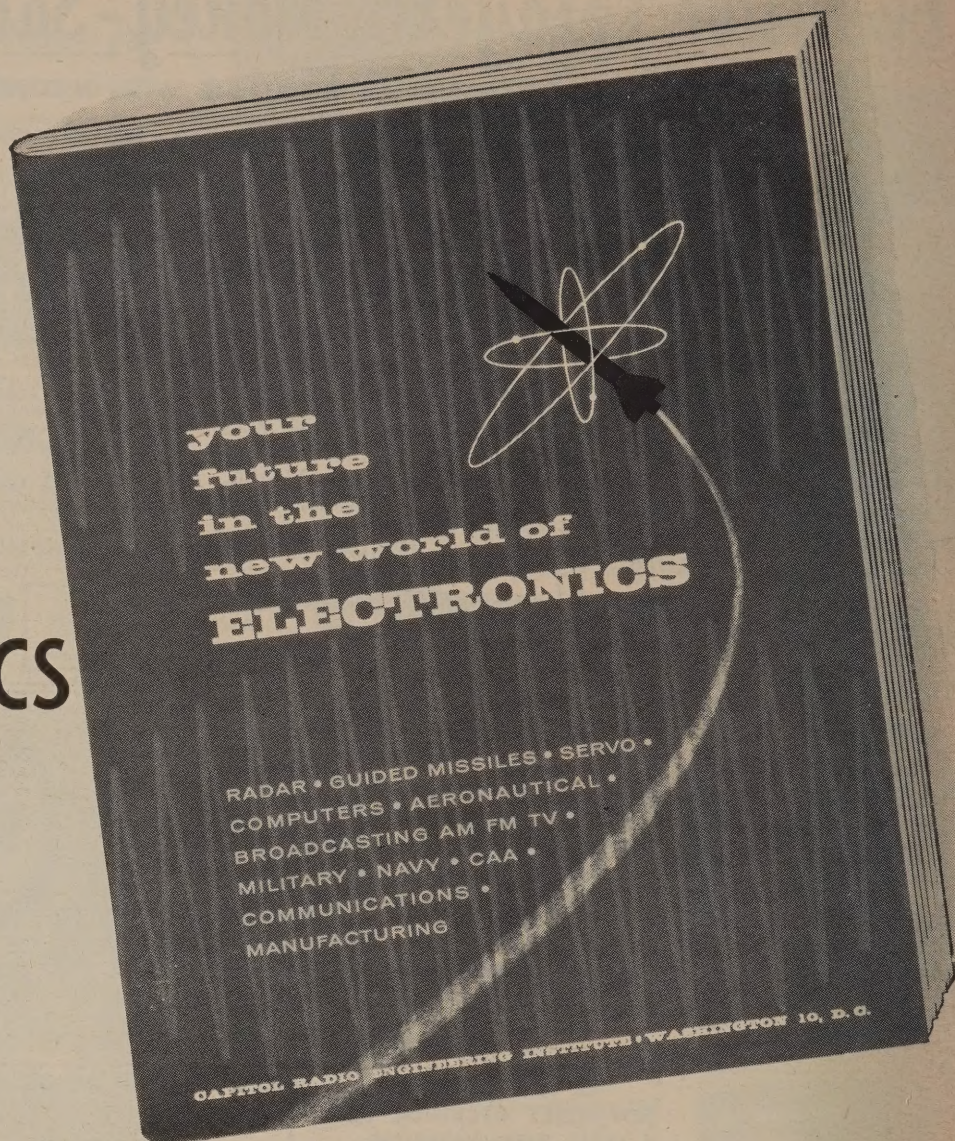All these benefits can be yours if you act now! Take that first big step this minute—No obligation whatsoever!



**TAKE A MINUTE TO MAIL THIS COUPON FOR FREE BOOKLET !**

### CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula—Founded 1927  
Dept. 1412-W, 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE Illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

CHECK FIELD OF GREATEST INTEREST

|                          |                                                  |
|--------------------------|--------------------------------------------------|
| <input type="checkbox"/> | Radar, Servo and Computer Engineering Technology |
| <input type="checkbox"/> | Electronic Engineering Technology                |
| <input type="checkbox"/> | Broadcast (AM, FM, TV) Engineering Technology    |
| <input type="checkbox"/> | Television Engineering Technology                |
| <input type="checkbox"/> | Aeronautical Electronic Engineering Technology   |

Name..... Age.....

Street .....

City..... Zone..... State.....

CHECK: ☐ Home Study ☐ Residence School ☐ Korean Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED BY.....

TYPE OF PRESENT WORK.....



EDUCATION:  
YEARS HIGH SCHOOL.....  
YEARS COLLEGE.....

ELECTRONICS EXPERIENCE.....

IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED?



# Electro-Voice®

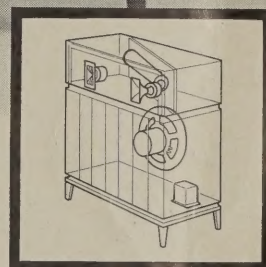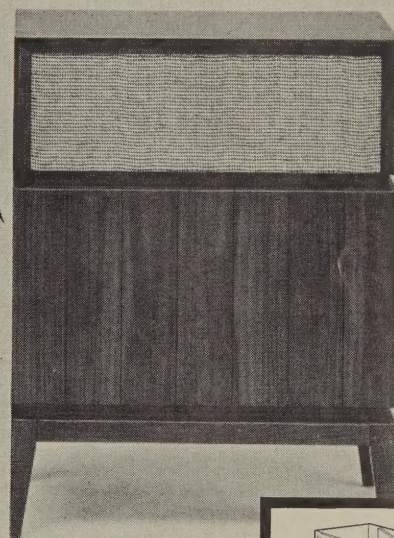

## Here is Why Electro-Voice Phase Loading Improves Along-the-Wall High-Fidelity Reproduction

**Phase Loading**—a great Electro-Voice development—gives you performance from along-the-wall speaker enclosures that approaches the performance of a corner horn! Specifically designed for use along-the-wall, phase-loaded cabinets give you almost a full added octave of smooth, augmented bass. The bass driver unit is placed low and close to the rear reflecting wall so that the direct sound from the cone and the reflected sound reach the listener's ears from very nearly the same source. This prevents phase cancellations, gives smooth, augmented bass range.

**Phase Loading** also permits a sealed cavity behind the driver cone of precise volume. The compliance of this cavity is made to react with the mass of the cone and the outside air throughout the second octave, adding this range to the response not otherwise attainable. This is *why* Phase Loading is demonstrably superior. Hear it today!

### NEW ELECTRO-VOICE PHASE LOADED ENCLOSURES

**The Carlton IV.** Smart, handsome low-boy design using acoustically correct "Tapatex" grille cloth for accent. It harmonizes gracefully with modern furnishings. Employs a complete *phase loaded* system affording extended bass response range with smooth, resonance-free characteristics. Includes Model 105E deluxe 15-inch, 4-way components completely wired and installed. Size: 33½" high, 26¼" wide, 19½" deep. Mahogany Complete—Net each.....\$359.00

**The Sheraton.** Complements the Carlton phase loaded speaker enclosure, affording extensive facilities for amplifier, tuner, turntable or record changer, tape deck plus record and tape storage. Compartment dimensions: Record Player, 18" long x 17¼" wide x 9½" overall depth (adjustable mounting board raises for manual player); Amplifier-tuner, 18" long x 17¼" deep; Storage, 13" high x 19" wide x 17¼" deep. Overall size: 33½" high x 37½" wide x 19½" deep. Mahogany Cabinet Only—Net each.....\$173.00

### THERE'S AN ELECTRO-VOICE PHASE LOADED ENCLOSURE FOR EVERY APPLICATION

**The Suzerain IV.** With phase loaded Model 105E 15-inch deluxe speaker system, wired and installed. Size: 36½" high x 26" wide x 19¼" deep. Mahogany Complete—Net each.....\$395.00

**The Suzerain IVA.** Model 117B 15-inch standard speaker system, wired and installed. Same size as Suzerain IV. Mahogany Complete—Net each.....\$301.00

**The Carlton IVA.** Similar to Carlton IV but with economy Model 117B 15-inch standard speaker system, wired and installed. Mahogany Complete—Net each.....\$265.00

**The Duchess IV.** Model 105E 15-inch deluxe speaker system, wired and installed. Size: 29¾" high x 25" wide x

19" deep. Mahogany Complete—Net each.....\$356.00

**The Duchess IVA.** Model 117B 15-inch standard speaker system, wired and installed. Same size as Duchess IV. Mahogany Complete—Net each.....\$262.00

**The Empire IV.** Model 105E deluxe 15-inch 4-way components wired and installed. Size: 29¾" high x 32" wide x 16" deep. Mahogany Complete—Net each.....\$359.00

**The Empire IVA.** Model 117B 15-inch standard speaker system, wired and installed. Same size as Empire IV. Mahogany Complete—Net each.....\$265.00

All Electro-Voice furniture is available in Blonde Lined Oak or Circassian Walnut at slightly higher price. Enclosures may be purchased separately, without speaker systems.


Electro-Voice offers you this wide selection of phase loaded speaker systems and enclosures, each carefully made by dedicated craftsmen, designed by the industry's best engineers and stylists to integrate with either modern, traditional or contemporary furnishings.

NO FINER CHOICE THAN







# Electro-Voice


ELECTRO-VOICE, INC.

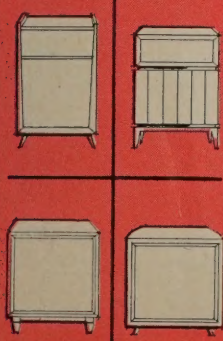BUCHANAN, MICHIGAN



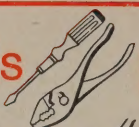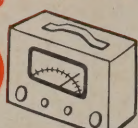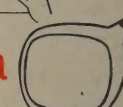

Here's how to make picture tube profits: First, you  
 need your everyday tools  plus good test equipment  
 (RCA) , plus your skill  and knowledge  Then,  
 you need top-quality, dependable RCA Silverama   
 Picture Tubes that rejuvenate nearly any make of set,  
 and make friends of your customers. And, finally,  
 you need the sales "tools", too. And these RCA makes  
 available to you in abundance. See your Authorized RCA  
 Tube distributor for the most powerful merchandising  
 aids available, including these two brand new headliners:

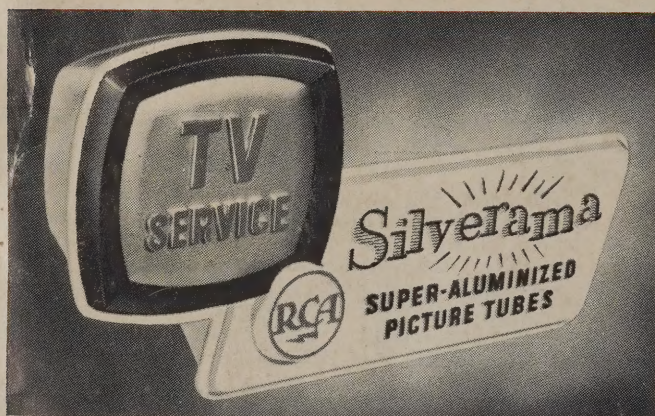

**ILLUMINATED SERVICE SIGN.** This new, compact, TV Service Sign with flasher, tells 'em you handle the best TV tubes on the market, the brand they know best—RCA Silverama.



**SAFE-TV MAT.** This "how-did-I-ever-do-without-it-before" heavy rubber protective mat prevents face plate damage to out-of-chassis picture tubes.

Put these and a world of other new, fresh RCA promotion aids to work for you. With all these aids to help you sell the top picture tube brand in the industry, plus RCA newspaper and magazine ads, TV commercials, booklets, folders, ad mats, seals, and other hard-hitting promotional items, you can't miss making those big ticket, big mark-up, easy-to-make picture tube dollars.



**PICTURE TUBES**  
**RADIO CORPORATION OF AMERICA**

Electron Tube Division, Harrison, N. J.